73

11 New Projects To Build!

Simple One-Tube Receiver
Page 64

Improved K2OAW IDer
Page 51

Unbelievable Dropped Array
Page 10

$9 Signal Generator
Page 116

Detailed 1982 Index
Page 156

0 74470 65946 12

December 1982 $2.49½
Issue #267

Amateur Radio's Technical Journal

A Wayne Green Publication

The Hangman's 2-Meter Collinear
Make your tower do double duty. Drop this array from the top and get 6-dB gain W1GV/4 10

Deep-Six Squelch Tails
Kerchunks take a dive with the addition of this audio delay. WA2NYE 14

Build Yourself A Paralyzed Beam
Go from east to west in less than a second with this 2-meter array. And put your rotator out to pasture. WB2WIK 24

Taming the 2-Meter Linear
It lives in the forest of spurious oscillations and answers to the call of the correct bias. Catch one for yourself. VE3LMP 28

The Frugal Floppy Bazooka
This 2-meter antenna coils up into a small package, but it shoots a straight signal. N7BGZ 32

Taking It Higher
Raising a repeater's antenna is the way to wider coverage, right? Wrong. W4MLE 36

Dial-A-Frequency
Let your fingers do the walking with this remote control. All you need is a spare telephone. K1WGN 44

Improving God's IDer
Put more flexibility in the K2OAW circuit—and save the advantages of the original K9XI 51

The Bunesti Caper
The two British agents needed a power amp—fast. Could the American ham build one? W9PJF 56

The Tube Returns
Move over, ICs. This receiver is easy to build, cheap, and works like a dream W1BG 64

The Program That Knows It All
Repeater info, third-party agreements, you name it—this TRS-80 BASIC program knows it. W8XW 72

Berserk Direction-Finding
Zero in on transmitters in seconds with this TRS-80 program. It will tell you how to get there, too. WD8CBE 76

Shack from Scratch
Building a ham shack in a new home can be a breeze. Just plan ahead. W2XQ 84

Winning the Coax War
The electrical length of feedline depends on its velocity factor. Don't get caught short W9PJF 90

Red-Hot and Ready to Go
Anyone who has ever soldered knows that the cord gets in the way. Find freedom with this homebrew cordless iron. W7RXV 101

Cutting Current to Size
Measuring large ac currents can be difficult unless you know a trick or two. W7CRY explains how. W7CRY 108

Construct This All-American Audio Signal Generator
The perfect project for starting a test bench or rounding one out. WA2SUT 116

Maximum Modulation for CB Conversions
Many CB rigs lack the gain for full modulation. This preamp will help AJ0P 122

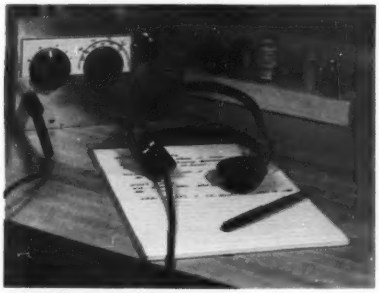

One-Tube Receiver—64

Never Say Die—6
Reader Service—130
Circuits—132, 139, 153
Ham Help—133, 134, 144, 160, 170, 171, 186
Social Events—133
RTTY Loop—134
Fun!—135
Letters—136
New Products—140
Corrections—144
Review—148
Contests—150
1982 Index—156
Awards—166
DX—170
Satellites—171
Propagation—193
Dealer Directory—193

IC-R70

NEW!

The Commercial Grade Communications Receiver that everyone has been asking for........at a price you can afford!

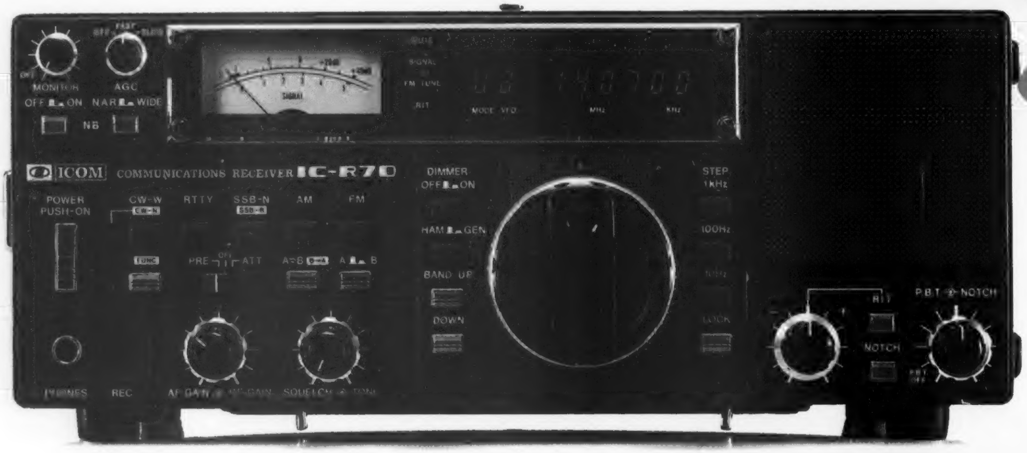

GENERAL COVERAGE RECEPTION AT ITS BEST

Listen to the world of HF with the R70, a 100KHz to 30MHz commercial grade receiver designed by ICOM Incorporated, the leader in advanced receiver design. Built from knowledge gained by designing receivers for commercial, marine, and amateur use, the R70 surpasses other receivers on the market...even receivers costing more than twice as much.

Utilizing ICOM's DFM (Direct Feed Mixer), the R70 is a receiver which in normal usage is virtually immune to intermodulation distortion or cross modulation, yet still maintains superior sensitivity. Whether you are a SWL (short wave listener), Ham (amateur radio operator), maritime operator or commercial user, the R70 provides the features you need.

DESIGN

The R70 incorporates an UP conversion system, utilizing a direct feed mixer proven to be the best design for minimizing interference from strong adjacent signals. A preamp is provided for making the weakest of signals readable. High grade filters in conjunction with the built-in PBT (pass band tuning) system and notch filter, provide the ultimate in interference rejection. Selectable AGC (fast/slow/off), noise blanker (wide or narrow), and tone control improve readability under the worst conditions. An AGC derived squelch, operative in all modes, adds to operating ease.

Dual VFO's with three tuning rates provide quick QSY (frequency change), memory for an important station, or by equalizing the VFO's (A=B), a digital RIT. 13.8 VDC operation is provided as an option, 117 VAC is standard.

HAM'ING

The R70 is an ideal general coverage receiver to complement any ham shack. Use it with your existing transmitter or transceiver to provide dual receiver capability.

The R70's built-in monitor system lets you listen to your own transmitted audio and a mute input automatically protects the R70's receiver from your signal.

An option for FM allows listening to the 10 meter FM activity.

As an additional plus to ICOM IC-720A owners, the R70 has an optional interface that will allow the R70 to control the transmit frequency of the 720A for the ultimate in hamming versatility.

SWL'ING

For the short wave listener, the readout section of the R70 gives all the information for logging a station to be returned to at a later time. Frequency, mode, VFO, signal strength are all displayed. A dial lock prevents accidental loss of a signal.

A front mounted speaker provides 3 watts of crisp clear audio. A record jack allows easy attachment of a tape recorder.

ICOM SYSTEM

Like all ICOM HF products, the R70 fits into the ICOM system concept of accessories allowing you to use previously purchased accessories such as the HP1 headphone, SP3 external speaker, and AH1 auto bandswitching antenna.

PRICE

Check with your local ICOM dealer for pricing on the R70. You will be amazed.

ICOM
The World System

ICOM America, Inc., 2112-116th Ave NE, Bellevue, WA 98004 **(206)454-8155**/3331 Towerwood Drive, Suite 307, Dallas, TX 75234 **(214)620-2780.**

All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions.

5-STORE BUYING POWER *in action!*

NEVER BEFORE... NEVER AGAIN!

ICOM

IC-730

SALE!

REGULAR $829

$649.95

LIMITED TIME ONLY...
LIMITED QUANTITY
ACT!

KENWOOD

CALL NOW FOR SPECIAL PRICES

TS-930S

TR-2500

NEW

TR-7950
2 METERS, 45 WATTS,
21 CHANNEL MEMORY

TS-830S

KLM/Tri Ex

KT-34A
4 ELEMENT TRIBANDER
REGULAR $389.95

SALE! $309

KT-34XA
6 ELEMENT TRIBANDER
REGULAR $569.95

SALE! $459

CALL FOR OTHER KLM PRICES.

TRI EX W51 TOWER w/KLM KT-34A *$1099*

TRI EX W51 TOWER w/KLM KT-34XA *$1239*

TRI EX W51, 51' TOWER
REGULAR $999.95 **$829.95**

PRICES ARE FOB CALIF. EXCEPT FOR CERTAIN COMBINATIONS. PLEASE INQUIRE.

ETO ALPHA

ALL ALPHA AMPLIFIERS IN STOCK FOR FAST DELIVERY
CALL FOR SPECIAL PRICES

EXAMPLE
76PA
REGULAR $2395

SALE! $1799

MIRAGE AMPLIFIERS

AVAILABLE AT LOW PRICES

2 METER AMPLIFIER

B-3016	**B-1016**
30W in, 160W out.	10W in, 160W out.
REG. $239.95	REG. $279.95
SALE! $199.95	**SALE! $249.95**

YAESU HANDHELDS

2 METER
FT-208R

70CM
FT-708R

SALE!
$289.95

FREE SHIPMENT *(U.P.S. Brown)* *CONTINENTAL U.S.A.*

EXCEPT FOR SOME ALPHA, TRI EX and KLM ITEMS.

SERVING HAMS BETTER.
North...south...east...west.

Bob Ferrero, W6RJ/K6AHV, Jim Rafferty, N6RJ
other well known hams give you courteous, personalized service.

FREE PHONE 800 854-6046

9:30AM to 5:30PM PACIFIC TIME.

OVER-THE-COUNTER, 10AM to 5:30PM.
MONDAY THROUGH SATURDAY
CALIFORNIA CUSTOMERS PLEASE PHONE OR VISIT LISTED STORES.

HAM RADIO OUTLET

ANAHEIM, CA 92801
2620 W. La Palma,
(714) 761-3033 (213) 860-2040
Between Disneyland & Knott's Berry Farm

BURLINGAME, CA 94010
999 Howard Ave., (415) 342-5757
5 miles south on 101 from S.F. Airport.

master charge

VISA

OAKLAND, CA 94609
2811 Telegraph Ave., (415) 451-5757
Hwy 24 Downtown. Left 27th off-ramp.

SAN DIEGO, CA 92123
5375 Kearny Villa Road (619) 560-4900
Hwy 163 & Clairemont Mesa Blvd.

VAN NUYS, CA 91401
6265 Sepulveda Blvd., (213) 988-2212
San Diego Fwy at Victory Blvd.

AEA • ALLIANCE • ALPHA • AMECO • AMPHENOL • ARRL • ASTRON • AVANTI • BENCHER • BERK-TEK • BIRD • B&W • CALLBOOK • CDE • COLLINS • CUBIC • CURTIS • CUSHCRAFT • DAIWA • DATONG • DENTRON • DRAKE • DX ENGINEERING • EIMAC • HUSTLER • HY-GAIN • ICOM • J.W.MILLER • KENWOOD • KLM • LARSEN • LUNAR • METZ • MFJ • MICRO-LOG • MINI-PRODUCTS • MIRAGE • NYE • PALOMAR • ROBOT • ROHN • SHURE • SWAN • TELEX • TELREX • TEMPO • TEN-TEC • TRISTAO • YAESU and many more!

Prices, specifications, descriptions subject to change without notice. Calif. residents please add sales tax.

SWR & Power Meter

10
3
1.5
1.2
1.1
1.0
SWR
200
125
70
30
10
0
POWER
OFF
2000
200
20
Palomar Engineers
M-827

- The most advanced automatic computing RF measuring instrument in amateur radio.
- Logarithmic SWR scale.
- Power ranges 20/200/2000 watts.
- Frequency range 1-30 MHz.

Automatic. No "set" or "sensitivity" control. Computer sets full scale so SWR reading is always right. Complete hands-off operation.

Light bar display. Gives instant response so you can see SSB power peaks. Much faster than old-fashioned panel meters. Baton switch selects three power ranges.

Logarithmic SWR display. Computer expands the display where you need it so it's easier to see, easy to use.

Computer operated. Now an analog computing circuit and digital comparator automatically compute SWR regardless of power level. Frees you from checking zero, setting a "sensitivity" knob and from squinting at old-fashioned cross pointer mechanical meters. With this new meter computing is done electronically and displayed with moving light bars. Individual bars for SWR and power.

Model M-827 Automatic SWR & Power Meter $119.95 in the U.S. and Canada. Add $3 shipping/handling. California residents add sales tax.

MasterCard VISA

ORDER YOURS NOW!

Send for FREE catalog describing the SWR & Power Meter and our complete line of Noise Bridges, Preamplifiers, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

Palomar Engineers

1924-F West Mission Rd.
Escondido, CA 92025
Phone: (619) 747-3343

Ducks are getting smaller! and...

better!

Because you and the leading radio manufacturers want the best-performing, the best looking antenna, Centurion has grown to be the Duck leader. We've developed many smaller antennas to make the hand-held radio perform better, and now the newest duck...the Tuf Duck "mini". It's shorter (about 3") yet it's a full 1/4 wave radiator on VHF.

Actual Size

CENTURION
TUF DUCK™
ANTENNAS

CENTURION
Phone 402/467-4491
Telex 48-4377 CENTURION LCN
P.O. Box 82846 Lincoln, NE 68501 2846

INFO

Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the *73* editorial offices. "How to Write for 73" guidelines are available upon request.

Editorial Offices:

Pine Street
Peterborough NH 03458
Phone: 603-924-9471

Advertising Offices:

Elm Street
Peterborough NH 03458
Phone: 603-924-7138

Circulation Offices:

Elm Street
Peterborough NH 03458
Phone: 603-924-9471

Subscription Rates

In the United States and Possessions:
One Year (12 issues) $25.00
Two Years (24 issues) $38.00
Three Years (36 issues) $53.00

Elsewhere:

Canada and Mexico—$27.97/1 year only, U.S. funds. Foreign surface mail—$44.97/1 year only, U.S. funds drawn on U.S. bank. Foreign air mail—please inquire.

To subscribe, renew or change an address:

Write to *73*, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent issue of *73*. For gift subscriptions, include your name and address as well as those of gift recipients.

Subscription problem or question:

Write to *73*, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73: Amateur Radio's Technical Journal (ISSN 0745-080X) is published monthly by 73, Inc., a subsidiary of Wayne Green, Inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Entire contents copyright © 1982, Wayne Green, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition—University Microfilm, Ann Arbor MI 48106. Postmaster: Send address changes to *73*, Subscription Services, PO Box 931, Farmingdale NY 11737.

1942-1982
Celebrating our 40th
Anniversary in business
SPECIAL ANNIVERSARY PRICE
$799.95 Amateur Net

TR5 Transceiver

A NEW DIMENSION IN PERFORMANCE

• U.S. Made • Competitive Price • All Solid State • 12V DC • SWR Protected •
• Broadband • No Tune Up • Full Break-in CW • 150 Watts PEP, SSB or CW Input •
• High Dynamic Range • Excellent Sensitivity/Selectivity • Digital Readout •
• 160-10 Meters Plus WARC Bands and MARS Coverage*•

Front panel switching allows independent MODE and optional crystal filter selection.

A passive double balanced mixer is employed in the receiver front end. This stage is preceeded by a low noise high dynamic range bipolar rf amplifier to provide good, strong signal performance and weak signal sensitivity.

Accurate digital readout of operating carrier frequency is displayed to 100 Hz.

A rugged, solid-state PA provides continuous duty in SSB and CW modes. A cooling fan (FA7) is available for more demanding duty cycles, such as SSTV or RTTY. The PA also features very low harmonic and spurious output.

VOX GAIN, VOX DELAY, VOX disable, QSK, selectable AGC time constants, RIT and noise blanker selection are front panel controlled for ease of operation.

The TR5 is designed with modular construction techniques for easy accessibility and service.

GENERAL

Frequency Coverage: 1.8-2.0*, 3.5-4.0, 7.0-7.5, 10.0-10.5, 14.0-14.5, 18.0-18.5*, 21.0-21.5, 24.5-25.0*, 28.0-28.5*, 28.5-29.0, 29.0-29.7* MHz. (*With accessory range crystal).

Modes of Operation: Usb, Lsb, Cw.

Frequency Stability: Less than 1 kHz drift first hour. Less than 150 Hz per hour drift after first hour. Less than 100 Hz change for a ± 10% line voltage change.

Readout Accuracy: ± 10 ppm ± 100 Hz.

Power Requirements: 13.6 V-dc regulated, 2 A. 12 to 16 V-dc unregulated, 0.8 V rms maximum ripple, 15 A.

Dimensions:
Depth: 12.5 in (31.75 cm), excluding knobs and connectors.
Width: 13.6 in. (34.6 cm).
Height: 4.6 in. (11.7 cm) excluding feet.

Weight: 14 lb. (6.35 kg)

TRANSMITTER

Power Input (Nominal): 150 Watts, PEP or Cw.

Load Impedance: 50 ohms.

Spurious and Harmonic Output: Greater than 40 dB down.

Intermodulation Distortion: Greater than 30 dB below PEP.

Carrier Suppression: Greater than 50 dB.

Undesired Sideband Suppression: Greater than 60 dB at 1 kHz.

Duty Cycle:
Ssb, Cw: 100%.
Lock Key (w/o FA7 Fan): 30%, 5 minutes maximum transmit.
Lock Key (w/FA7 Fan): 100%.

Microphone Input: High Impedance.

Cw Keying: Instantaneous full break-in, adjustable delay.

RECEIVER

Sensitivity: Less than 0.5 uV for 10 dB S+N/N except less than 1.0 uV, 1.8-2.0 MHz.

Selectivity: 2.3 kHz minimum at −6 dB. 4.1 kHz maximum at −60 dB (1.8:1 shape factor).

Ultimate Selectivity: Greater than −95 dB.

Agc: Less than 5 dB output variation for 100 dB input signal change, referenced to agc threshold.

Intermodulation: (20 kHz or greater spacing) *Intercept Point:* Greater than 0 dBm. *Two-Tone Dynamic Range:* Greater than 85 dB.

I-f Frequency: 5.645 MHz.

I-f Rejection: 50 dB, minimum.

Image Rejection: 60 dB, minimum below 14 MHz. 50 dB, minimum above 14 MHz.

Audio Output: 2 watts, minimum @ less than 10% THD (4 ohm load).

Spurious Response: Greater than 60 dB down.

ACCESSORIES AVAILABLE

Model 7021 SL300 CW Filter
Model 7022 SL500 CW Filter
Model 7027 SL1000 RTTY Filter
Model 7023 SL1800 RTTY Filter
Model 7026 SL4000 AM Filter
Model 7024 SL6000 AM Filter
Model 1570 PS75 AC Power Supply
Model 1545 RV75 Synthesized Remote VFO
Model 1531 MS7 Speaker
Model 1507 CW75 Keyer
Model 1558 NB5 Noise Blanker
Model 7077 Microphone

R. L. DRAKE COMPANY DRAKE

540 Richard St., Miamisburg, Ohio 45342. USA
Phone: (513) 866-2421 • Telex: 288-017

W2NSD/1
NEVER SAY DIE

editorial by Wayne Green

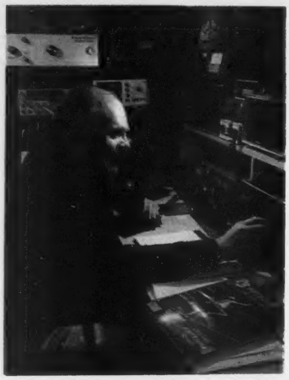

SHOULD DXCC BE PROHIBITED?

The blatant arrogance of the PY0SB DXpedition shook the amateur bands, bringing on wild attacks of jamming in retaliation. Frankly, after trying to use the twenty-meter band for an hour, I didn't blame the jammers much. Not since Don Miller have I heard such a total disregard for the hobby.

This was, in my estimation, amateur radio at its worst. Those refugees from CB set up on one of the most rare spots in the world and then, transmitting outside of the American phone band, asked US hams to call them anywhere from 14,200 to 14,300. This went on, totally killing the band for any other use as thousands of stations called steadily, hour after hour. There was no possible way to make a normal contact anywhere in that entire band while this was going on.

This is totally unnecessary, as anyone with even a small amount of DXing experience knows. It is arrogant. It is a shameless flaunting of the power of one group to bring the whole band to a halt. It isn't even a fast way of making contacts. There is not even a remote excuse for such a display.

I've operated from some fairly remote spots and have faced as big pileups as anyone. I got started in seriously working DX in late 1945, the day our first DX band opened after the war. When I moved to New Hampshire, I started all over again, working 100 countries in the first week on twenty phone, 200 in the first month, and 300 in the first year. So I know the receiving end of the stick.

In 1958, I went on my first serious DXpedition...KC4AF, Navassa Island. Since then, I've operated from a bunch of places...come to mind 5Z4, ZS6, 3D6, 7P8, OD5, YK1, YA1, VU, 9N1, HL6, VR2, 5W1, KS6, FO8, HH, JY, OH0, KH2, KW6, and a bunch of non-rare countries. I've tried every way known to ham to get the most contacts per hour on the air from these rare places, so I have a good idea of what works and what does not work. Hmmm, I forgot to mention VP5, J6, and a revisit to Navassa in 1972.

The results of all this? Well, unless your signal is particularly weak, the fastest operation is when you operate on a fixed channel, thus containing the band mayhem to one single pileup. I've found that out by making regular announcements to this effect: "I will be listening for about ten seconds on this channel for the last letter of your call. Please do not all jump in immediately, but wait so your calls will be spaced a bit. I will make a note of the last letter of your call and call you with it after writing down as many as I can hear. Do not...I repeat...do *not* call more than a couple of times. If I hear anyone pushing and shoving on channel I will work you, but there will be no QSL. Neither of us wants that."

The result is a relatively orderly sorting out of the problem, which is to get the call letters of those on channel as quickly as possible. The rest of the contact is a matter of a couple of seconds. The long, hard part is getting the calls through.

By asking for the last letter, I am able to quickly get things down to two or three, at most, responding when I break. It makes everyone shut up and listen. I can then confirm the call, exchange signals, and be on to the next. With this system, I can double or triple the throughput of any system which calls for tuning a band of frequencies, looking for calls in the open.

The calling stations, perceiving that I am able to cope with the chaos and that they will have a fair chance of getting through, respond very positively and line up, doing as I ask. Megawatts of power are saved. The entire band, except for about 6 kHz which I am using, is open for everyone...and at least twice as many operators are made happy with a new one. And think of the agonizing frustration saved for the thousands of ops, calling hour after hour, hoping to get through.

Another solution to the whole problem would be, of course, to get the League to cancel their Honor Roll and DXCC certificates so we wouldn't have this enormous pressure to make a radio contact with some stupid island somewhere. That would spoil a lot of fun for thousands of us DXers, but it would at least stop such carnage as the Peter and Paul jokers dumped on us.

This whole DX thing, while it may be fun for amateurs in most of the ordinary countries, is a royal pain in the...er...ear for the ham who lives in a rare spot.

HAM BILL SIGNED

It began as S.929, turned into H.R.5008, and came out of the Washington mill as H.R.3239, but the effect is the same: sweeping changes in amateur radio.

The bill, which has been signed by President Reagan, will give hams more control over licensing and policing and may also expand the 5-year ticket into a license renewable every 10 years.

With this moneysaving measure, FCC-approved hams and ham organizations will be both writing and administering exams. However, the exams may be written only by a ham with at least the class license that the exam is for, and tests can be given only by hams with a higher-class license. Extras, of course, will be allowed to test Extras.

Amateur radio's traditional self-policing policies have also been given a shot in the arm by the bill. The FCC can now use hams to track down illegal transmissions and accept reports on illegal activities which have been filed by hams. This bill gives the FCC permission to "recruit and train" hams for this purpose, and these amateurs will also be allowed to send warning notices to offenders. However, the amendment does not give hams authority to officially charge violators.

The self-regulatory aspect of the bill is the brainchild of Sen. Barry Goldwater K7UGA, who drafted the initial version as S.929. But to get it enacted, the concepts of S.929 were incorporated into a larger house bill, H.R.5008, which addresses a wide variety of changes in the Communications Act of 1934.

Hams plagued by RFI will find some respite under this bill, which will "establish minimum performance standards for home electronic equipment and systems to reduce their susceptibility to interference from radio frequency energy." However, the bill does not affect equipment already manufactured.

Other changes in the Communications Act eliminate licenses for CBers and radio control operators. Though CB operators will still be expected to comply with regulations, the change allows the Commission to officially wash its hands of the 27-MHz band.—WB8JLG.

"Comm-packed."

BIG performance... small size... smaller price!!!

TR-2500

The TR-2500 is a compact 2 meter FM handheld transceiver featuring an LCD readout, 10 channel memory, lithium battery memory back-up, memory scan, programmable automatic band-scan, Hi/Lo power switch and built-in sub-tone encoder.

TR-2500 FEATURES:

- **Extremely compact size and light weight**
  Measures 66 (2-5/8) W x 168 (6-5/8) H x 40 (1-5/8) D, mm (inches). Weighs 540 grams (1.2 lbs) with Ni-Cd pack.
- **LCD digital frequency readout**
  Shows frequencies and memory channels, four "Arrow" indicators.
- **Ten channel memory**
  Nine memories for simplex or ±600 kHz offset. "M0" memory for non-standard split frequency repeaters.
- **Lithium battery memory back-up**
  (Estimated 5 year life.) Maintains memory when Ni-Cd pack is fully discharged or removed.

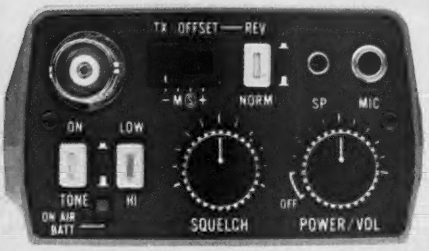

- **HI/LOW power selection**
  2.5 watts or 300 mw.
- **Memory scan**
  Scans only channels in which frequency data is stored.
- **Programmable automatic band scan**
  Upper and lower frequency limits and scan steps of 5-kHz and larger.
- **UP/DOWN manual scan**
- **Built-in tuneable sub-tone encoder**
  Tuneable (variable resistor) to desired CTCSS tone.
- **Built-in 16-key autopatch encoder**
- **"SLIDE-LOC" battery pack**
- **Repeater reverse switch**
- **Keyboard frequency selection**
- **Extended frequency coverage**
  Covers 143.900 to 148.995 MHz in 5-kHz steps.
- **Optional power source**
  Using optional MS-1 mobile or ST-2 AC charger/power supply, radio may be operated while charging. (Automatic drop-in connections.)

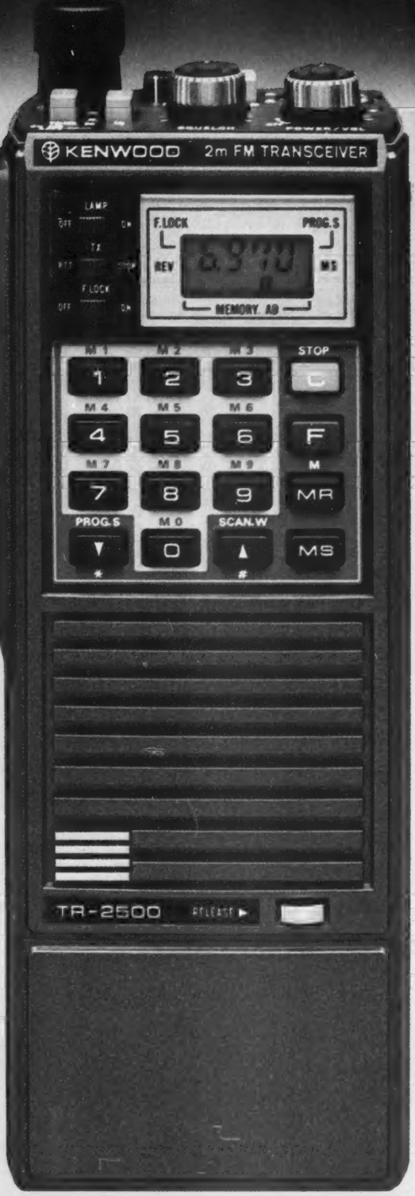

Actual size

- **High impact plastic case**
- **Battery status indicator**
- **Two lock switches**
  Prevent accidental frequency change and accidental transmission.

Standard accessories include:

- Flexible antenna with BNC connector
- 400 mAH Ni-Cd battery pack
- AC charger

Optional accessories:

- ST-2 Base station power supply/charger (approx. 1 hr.)
- MS-1 13.8 VDC mobile stand/charger/power supply

TR-3500

70 CM FM Handheld

- 440-449.995 MHz in 5-kHz steps
- TX OFFSET switch keyboard programmable ±5 kHz to ±9.995 MHz
- 1.5 W/300 mW HI/LOW power switch
- Auto. squelch position on squelch control
- Tone switch for TU-35B optional programmable CTCSS encoder
- Other features include 10 memories, lithium battery memory back-up, programmable automatic band scan, memory scan, UP/DOWN manual scan, repeater reverse, 16-key autopatch, keyboard frequency selection, slide-lock battery.

- VB-2530 2-M 25 W RF power amp., w/cables, mtg. brkt. (TR-2500 only)
- TU-1 Programmable CTCSS encoder (TR-2500 only)
- TU-35B Programmable CTCSS encoder (mounts inside TR-3500 only)
- PB-25 Extra 400 mAH Ni-Cd battery
- PB-25H Heavy-duty 490 mAH Ni-Cd battery
- DC-25 13.8 VDC adapter.
- BT-1 Battery case for manganese/alkaline AA cells
- SMC-25 Speaker-microphone
- LH-2 Deluxe leather case
- BH-2A Belt hook
- RA-3 m 3/8λ telescoping antenna (for TR-2500).
- WS-1 Wrist strap
- EP-1 Earphone

More information on the TR-2500 and TR-3500 is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.

KENWOOD
...pacesetter in amateur radio

Specifications and prices are subject to change without notice or obligation.

STAFF

PUBLISHER/EDITOR
Wayne Green W2NSD/1

EXECUTIVE VICE PRESIDENT
Sherry Smythe

ASSISTANT PUBLISHER/EDITOR
Jeff DeTray WB8BTH

MANAGING EDITOR
John Burnett

ASST. MANAGING EDITOR
Susan Philbrick

EDITORIAL ASSISTANTS
Nancy Noyd
Richard Phenix
Steve Jewett

TECHNICAL EDITOR
Avery L. Jenkins WB8JLG

ASSISTANT TO THE PRESIDENT
Matthew Smith KA1IEI

ASSOCIATES
Robert Baker WB2GFE
John Edwards KI2U
Bill Gosney KE7C
Sanger Green
Chod Harris VP2ML
Dr. Marc Leavey WA3AJR
J. H. Nelson
Bill Pasternak WA6ITF
Peter Stark K2OAW

PRODUCTION MANAGER/ PUBLICATIONS
Nancy Salmon

ASST. PRODUCTION MANAGER/PUBLICATIONS
Michael Murphy

ADVERTISING GRAPHICS MANAGERS
Steve Baldwin
Fiona Davies
Bruce Hedin
Jane Preston

PRODUCTION
Frances Benton
Linda Drew
Denzel Dyer
Phil Geraci
Donna Hartwell
Louis Marini
Scott Philbrick
Dianne K. Ritson
Anne Rocchio
Mary Seaver
Deborah Stone
Theresa Verville
Judi Wimberly
David Wozmak

PHOTOGRAPHY
Sandra Dukette
Laurie Jennison
Irene Vail
Robert M. Villeneuve
Thomas Villeneuve

TYPESETTING
Sara Bedell
Melody Bedell
Marie Barker
Michele DesRochers
Jennifer Fay
Lynn Haines
Linda Locke
Nancy Wilson-Newman
Debbie Nutting
Karen Stewart

GENERAL MANAGER
Debra Wetherbee

CONTROLLER
Roger J. Murphy

ACCOUNTING MANAGER
Knud Keller KV4GG/1

CIRCULATION MANAGER
Patricia Ferrante
603-924-9471

BULK SALES MANAGER
Ginnie Boudrieau
1-(800)-343-0728

ADVERTISING
603-924-7138
Jim Gray W1XU, Mgr.
Nancy Ciampa, Asst. Mgr.
Ross Kenyon KA1GAV
Cornelia Taylor

You wouldn't believe how soon the thrill of working stations for ten-second contacts palls. You might not find it as difficult to believe what a nuisance being expected to fill out and mail thousands of QSL cards is. Imagine, if you will, the excitement with which a ham in Tonga receives his 780th QSL from a WB2 station. It just goes into the nearest leftover washing machine carton.

Even with a QSL manager to take on the brunt of the card chore, the responsibility for keeping the log, getting a copy to the manager, and forever making instant contacts, with growing resentment whenever you stop to try to make friends with anyone forcing you to shut down...it's driven most hams in rare spots off the air.

With so many things of value which people can accomplish in this world, I am saddened when I see some ham who has gotten swept up in the DX Honor Roll excitement. What a frivolous waste of life it is to devote it to trying to make this silly list...and stay there...often at almost any expense.

Continued on page 172

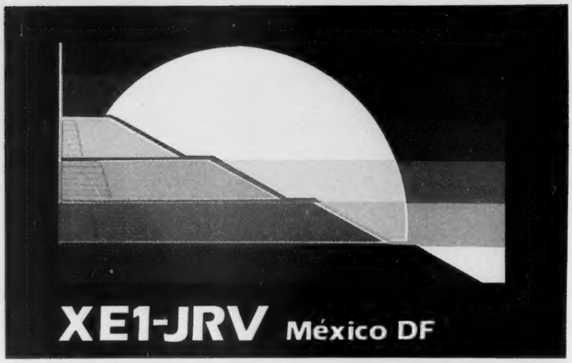

QSL OF THE MONTH: XE1JRV

This month's QSL Contest winner is Jesus Retana XE1JRV. This modern rendition of an ancient temple is highlighted by the bright yellow sun, adding warmth and contrast to an otherwise stark scene.

To enter *73*'s QSL of the Month Contest, put your QSL card in an envelope with your choice of a book from *73*'s Radio Bookshop, and send it to *73*, Pine Street, Peterborough NH 03458, Attn: QSL of the Month. Entries without an envelope or book choice will not be considered.

Well...I Can Dream, Can't I?

by Bandel Linn K4PP

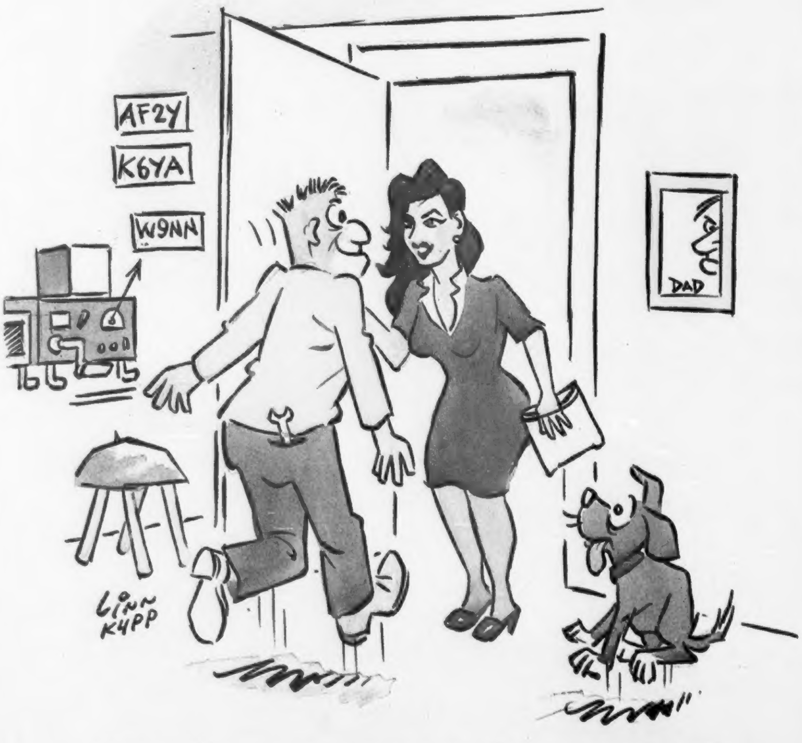

"Are you the handsome one who advertised for 'Ham Help'?"

THE RTTY ANSWER

iRL FSK-500
TUNING
THRESHOLD
BW
SHIFT
NORM
REV
WIDE
NAR
OFF
ON
M
S
iRL FSK-1000
TUNING
MARK
SPACE
M
S
LIMIT
INPUT LEVEL
THRESHOLD
OUT
IN
NORM
REV
SHIFT
850
425
170
WIDE
NAR
AUTOSTART
FSK
MARK
FAST
SLOW
OFF
ON
LINE
LOCAL
MARK
SPACE
FSK
ON
OFF

iRL™

Now...300 Baud & Super-RATT

for either iRL terminal unit

☐ All circuits on small module inside TU
☐ No changes to our outstanding filters
☐ Just add one switch and the module
☐ Factory installed or you can do it

the most powerful RTTY program
for your Apple computer

☐ 65 pages of excellent documentation
☐ Features galore
☐ Available with or without custom cable

and still the finest in RTTY

the FSK-1000 Terminal Unit

☐ Unparalleled selectivity achieved with sophisticated true limiterless design
☐ Ultra sharp active filters
☐ Tuneable shift (80-1000 Hz.)
☐ Selectable bandwidths (100/55 Hz.)
☐ Three mode autostart
☐ Positive dynamic range indicator
☐ Extruded aluminum enclosure
☐ Adjustable "mark hold"
☐ Keyboard activated transmit
☐ Optional AFSK keyer
☐ Internal loop supply, RS232, & TTL

the FSK-500 Terminal Unit

☐ Superior selectivity
☐ Selectable bandwidths
☐ All standard shifts
☐ 3 shift AFSK keyer included
☐ Narrow shift I.D. included
☐ Preselector included for QRM supression
☐ Economically priced
☐ Fully wired and tested
☐ Compact size
☐ RS232 or TTL
☐ Optional loop supply

from iRL 700 Taylor Road Columbus, Ohio 43230 (614) 864-2464
Visa or Master Card accepted.

If you write RTTY computer programs, call us. We are looking for new ideas in software.

Stan Gibilisco W1GV/4
533 Coral Way, Apt. 14
Coral Gables FL 33134

The Hangman's 2-Meter Collinear

Make your tower do double duty. Drop this array from the top and get 6-dB gain.

Here is a 2-meter FM base-station antenna that's inexpensive, easy to build, and has about 6 dB omnidirectional gain. It can be mounted on the side of a tower or put on a mast of its own. No special tuning equipment is required. All you need is an swr meter.

Design

The antenna described here is a 6-element vertical collinear array. It consists of six half-wave radiators placed end-to-end and fed in phase. The resulting directional pattern is theoretically a circle in the horizontal plane, with a gain of about 6 dB over a dipole. Results of testing at W1GV/4 indicate substantial improvement, both for transmitting and receiving, over a 5/8-wave antenna with ground plane at 25 feet.

Fig. 1 shows the configuration of the collinear antenna. Each element is 38 inches long. The end-to-end spacing between elements is negligible, about 1 inch. Allowing for a foot or two at the top and bottom, the entire antenna requires a vertical space of about 22 feet. Of course, the higher the system is placed, the better the performance will be.

Proper phasing is obtained by quarter-wave stubs between the elements. For all practical purposes, these stubs do not radiate, provided they are cut to the correct length. At 146.5 MHz, 18 inches with 2-inch spacing gives a reasonant, ultra-low-loss matching section. Fig. 2 illustrates the construction details for each stub.

The antenna can, as previously mentioned, be mounted on the side of a tower or alongside a TV mast; it can even be hung from a tree branch! If the antenna is mounted on the side of a tower, the directional pattern will be modified slightly. The gain will be reduced in the direction of the tower and increased in the direction away from the tower. Therefore, you should position the antenna to provide the most gain in whatever direction you desire the best coverage (Fig. 3).

If the antenna is suspended next to a TV mast or hung from a tree limb, the pattern will be omnidirectional.

Construction

To put this antenna on a tower, you will need the following hardware, in addition to the usual tools and soldering apparatus:

- 6 42-inch lengths No. 12 solid uninsulated copper wire

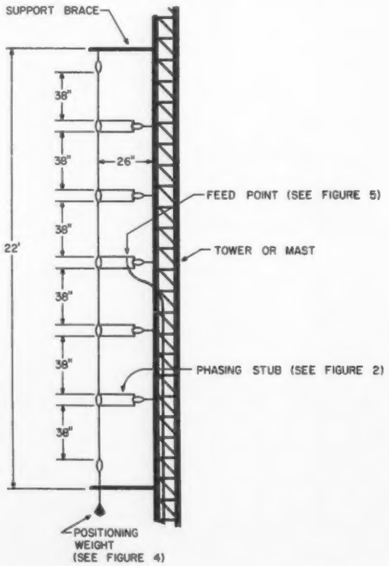
SUPPORT BRACE
38"
38"
26"
38"
22'
38"
38"
38"
FEED POINT (SEE FIGURE 5)
TOWER OR MAST
PHASING STUB (SEE FIGURE 2)
POSITIONING WEIGHT (SEE FIGURE 4)

Fig. 1. Configuration of the 6-element, 2-meter wire collinear antenna. The overall height is 22 feet. The array is fed at the physical center.

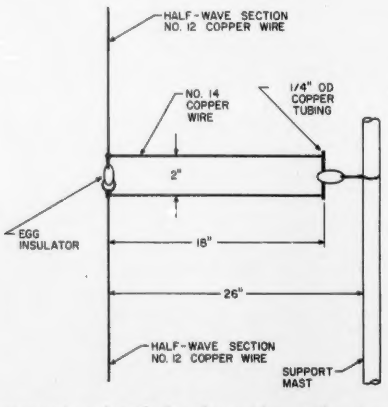
HALF-WAVE SECTION NO. 12 COPPER WIRE
NO. 14 COPPER WIRE
1/4" OD COPPER TUBING
2"
EGG INSULATOR
18"
26"
HALF-WAVE SECTION NO. 12 COPPER WIRE
SUPPORT MAST

Fig. 2. Construction details for the tuning stubs. A spacing of 2 inches provides minimum loss while allowing essentially no radiation. When the stub is pulled tight, the wires will stay in place because of their stiffness.

- 10 20-inch lengths No. 14 solid uninsulated copper wire
- 1 20-foot (approx.) roll No. 12 solid wire
- 5 2-inch lengths 1/4-inch o.d. copper tubing
- 5 porcelain insulators (non-egg type)
- 7 small egg insulators
- 2 3-foot, 2-inch o.d. wooden dowel rods
- 2 screw-in-type TV standoff insulators
- 1 15- to 20-pound weight
- 1 roll of electrical tape
- 1 strong set of legs

First, screw the TV standoffs into one end of each dowel. Then, attach the rods sideways to the tower braces, 22 feet apart. (If the tower braces do not exactly line up to 22 feet, use the next brace that will allow a spacing greater than 22 feet.) Of course, the higher the overall position, the better! The dowels should extend 26 inches out from the tower. Use No. 12 wire to secure the dowels to the tower braces.

To assemble the antenna, attach the seven egg insulators at the ends of the six antenna elements, making a long chain. Wrap and solder each wire end to the egg insulators. To minimize interelement capacitance, it's best to loop the wires through the egg insulators as shown in Fig. 2, in such a way that if the insulator should break, the wires will come apart. The elements should each measure exactly 38 inches from loop tip to loop tip. Attach an 18-inch length of No. 12 wire to one end of the array and a 48-inch length to the other end.

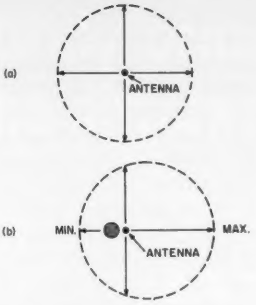

Fig. 3. Radiation patterns for a vertical array in free space (a) and near an obstruction such as a tower (b). The viewing position is directly overhead. The obstruction tends to reduce the gain in some directions while increasing it in others.

To construct the phasing stubs, solder two 20-inch lengths of No. 14 wire to each element end (see Fig. 1). Wrap 1 inch of wire around each element end. Space the wires 2 inches apart. Put a 2-inch piece of copper tubing through one end of a standard porcelain or glass insulator and twist a short piece of stiff wire around the tubing if necessary to keep it from slipping up and down in the hole. Wrap 1 inch of the free ends of the stub wires around the ends of the tubing and solder them in place. When you are done, you should be able to pull the stub tight and have both wires evenly spaced, straight, and 18 inches long (Fig. 2). You will have to construct five of these stubs, in locations shown by Fig. 1.

Now you're ready to hang this contraption. Grab the top end—the one with the 18-inch piece of wire attached—climb the tower (don't forget your safety belt!), and affix the wire to the TV standoff insulator at the end of the upper dowel. Then, climb back down to the lower dowel and run the 48-inch end wire through the standoff insulator there. Rotate the plastic inside the standoff so the wire can't pop out, and crimp the insulator ring to keep it in place. Cut the lower wire so that roughly 8 inches remains below the standoff. Then attach the weight to the end of the wire (Fig. 4). This weight keeps the array taut as the wires expand and contract with changes in temperature. An alternative arrangement to the weight is to use an elastic band in place of the lower section of wire; however, the array may have a tendency to "oscillate" in the wind if this scheme is used.

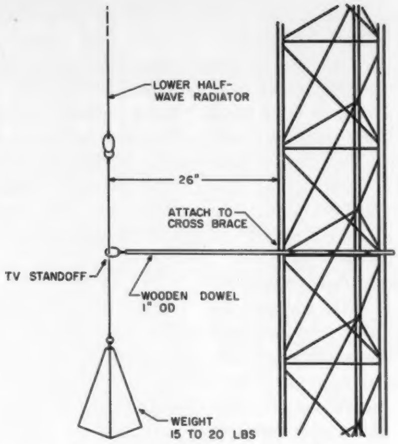

Fig. 4. Arrangement for keeping the array taut. The distance between the weight and the TV standoff should be great enough to allow for contraction with cold weather, but small enough to prevent excessive swinging of the weight.

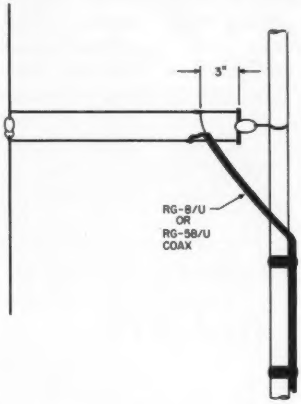

Fig. 5. Feedpoint diagram. The array should be fed at the center stub. A good starting point is 3 inches from the shorted end; however, some adjustment will probably be necessary to get a perfect match. Here, the center conductor of the transmission line is connected to the top part of the antenna and the shield to the bottom part. However, they could just as well be reversed.

To position the stubs, you'll need five pieces of wire about two feet long. Run one end through the insulator at the end of the stub, twist the wire onto the insulator, and pull the stub reasonably tight. Twist the other end of the wire around the tower support nearest the array (Fig. 2).

The Feedpoint

You can rest a bit now. As you're sipping a cool drink, admire the new appendage to your antenna farm. But don't get carried away; you still don't have it hooked up. And the final tuning procedure may require three or four more excursions up the tower.

Fig. 5 shows the matching section for the 6-element wire collinear. The transmission line is connected to the center stub. A good starting point is 3 inches from the shorted end, as shown. However, you'd better not solder the wires there right away. The size of your tower will have some effect on the exact final position. Larger towers will lower the impedance for any given tap point, as compared to smaller towers.

The feedpoint should be moved slightly toward or away from the shortened end of the stub until the swr is minimum at 146.5 MHz. It should be possible to get a nearly perfect match (at W1GV/4, a 1.3 swr was obtained). Always keep the coax shield and center-conductor taps at the same distance from the end of the stub; don't try to get fancy by putting them in different places.

The final tap position will be about 15 percent of the way from the shorted end of the stub to the antenna end. When the ideal position has been found, solder the wires in place and wrap the connections with electrical tape. Or, better, use silicone rubber cement. Tape the feedline cable to the inside of the tower to minimize possible induced currents on the coax from antenna coupling.

Closing Remarks

This antenna is a pleasure to use and requires essentially no maintenance. Since it is made from materials usually available at flea markets, the cost can be very low. I had much of the necessary hardware already in my junk box.

A gain of 6 dB over a dipole represents a quadrupling of the effective radiated power. But you get this gain on receive, too! With my Azden PCS-3000 at 25 Watts, I'm running 100 Watts effective radiated power, neglecting line losses. My installation, being attached to a TV mast with the bottom almost at ground level, is essentially omnidirectional. It is generally possible, in this pancake-flat South Florida area, to communicate with mobile stations via simplex out to 50 or 60 miles. Before, with the 5/8-wave antenna at 25 feet, the reliable range was only 30 to 40 miles. Of course, repeater operation is a breeze. I'm full-Q into all of the local repeaters.

There isn't any reason why more elements cannot be added to this array, except for height limitations and certain engineering requirements. An 8-element array would require about 28 feet of vertical space and would produce about 7.5 dB gain over a dipole; a 10-element array would give around 8.5 dB gain.

As the number of elements is further increased, tuning of the stubs and elements becomes more and more critical, and special equipment will be required to ensure correct phasing for optimum performance. (Even with a 1-inch error on each element, the total discrepancy would be 5 inches at the top and bottom of a 10-element array; this is 23 degrees at 146.5 MHz! Such an imprecision would surely degrade the performance of the antenna.) Furthermore, as the number of elements increases, the bandwidth of the array gets narrower because the error adds up for each element off resonance. There is a point of diminishing returns.

A 6-element array can provide good communication without the headaches of painstaking adjustment and narrow bandwidth, and so it represents a good compromise. This antenna is ideal for the 2-meter FM operator who wants omnidirectional operation, but is presently using only a ground plane.■

2300 MHz VARIABLE DOWNCONVERTER

ANTENNA KIT
$1695

32 WASHERS
31 SPACERS
MOUNTING BRACKET
6" RG 174 COAX
'F' CONNECTOR
• 35" ROD
6½" x 4" P.V.C. PIPE
2 DRILLED END CAPS
• HARDWARE

POWER SUPPLY KIT
$1695

POWER TRANSFORMER
COURSE TUNE POT.
FINE TUNE POT.
3 'F' CONNECTORS
RESISTORS & CAPS
LED WITH HOLDER
TERMINAL STRIP
P.C. BOARD
RF CHOKE
KNOB
WIRE
2 SWITCHES
4 DIODES
LM 317 REG.

WOOD GRAIN CABINET WITH SILK SCREENED front and back $10.95 Extra
BUILT POWER SUPPLY....................$34.95

Complete Down Converter System
INCLUDES
ANTENNA KIT
POWER SUPPLY KIT
CONVERTER KIT
SPECIAL $49.95

QUANTITY DISCOUNTS
Any Price in Adv.

10 pcs.	12% off
25 pcs.	18% off
50 pcs.	25% off
100 pcs.	30% off
1000 pcs.	35% off

No Mixing for Quantity Discount

PARTS

Converter P.C. Board Plated through holes for stability	$4.95
Power Supply P.C. Board	2.95
MRF 901	2.00
NEO2135	4.95
2835 Diodes	.95
.001 Chip Caps.	10/3.95
Choke Set of 4	1.95
LM 317 Regulator	1.25
'F' Connectors Chassis	.50
Wall Transformer 12 VAC 700 MA	4.95
'U' Bolt	.95
BALUN 75 to 300 ohm	1.95
BALUN for rabbit ears	2.95

*RG 59/U COAX WITH CONNECTORS FACTORY MADE

100 Ft.	$17.50
50 Ft.	9.50
25 Ft.	5.75
3 Ft.	2.50

CONVERTER KIT
$1695

P.C. BOARD PRE-DRILLED SOLDER PLATED WITH PLATED THROUGH HOLES FOR A MORE STABLE PICTURE.

NEW !!
.... 2137 HOT TRANS...

3	~~MRF 901 TRANSISTOR~~
2	HP 2835 Diodes
6	.001 Chip Caps.
9	Resistors
4	Prewound chokes
1	Electrolytic Cap.
1	Pre Made Probe

◉◉◉◉◉◉◉◉◉◉

★ WIRED P.C. BOARD TESTED, READY TO CONNECT TO CAN WITH PROBE & CABLE CONNECTOR ATTACHED.
$24.95

We will tune converter board for $12.50
trouble shoot add 7.50
trouble shoot power supply..$12.50
plus any parts needed.

We will accept telephone orders for Visa & Mastercard
No C.O.D. Orders
TO ORDER CALL 317-291-7262
800-428-3500
Complete kit weighs 10 lbs. Please add sufficient postage
6254 LaPas Trail
Indianapolis, Indiana 46268

ELECTRONIC RAINBOW INC

✓146

JRC
NRD-515
ALL WAVE RECEIVER

Entirely professional level!
You'll find the difference the more you use it.

ULTIMATE QUALITY, NRD-515

Receiver, NRD-515

SPECIFICATIONS

Receiving frequency range:	100kHz to 30MHz continuous (30 bands)	
Receiving modes:	USB/LSB/CW/RTTY/AM	
Receiving system:	Up conversion type Double superheterodyne First IF: 70.455MHz	
Sensitivity (S/N 10dB):	CW/SSB	AM
1.6 to 30MHz	0.5μV	2μV
100 to 1600kHz	2μV	6μV
Selectivity:	6kHz/2.4kHz/0.6kHz/0.3kHz (*Option) * *	
Stability:	Within 50Hz/one hour	
Power requirements:	AC 100/117/220/240V,50/60Hz, 50VA	
Dimensions and Weight:	340mm(W)×140mm(H)×300mm(D); Approx. 7.5kg	
Preset memory (Option):	24ch.	
Frequency stability:	Less than 50Hz per hour after warming up.	
Image rejection ratio:	70dB or more	
IF rejection ratio:	70dB or more	
Input impedance:	50 to 75 ohms, unbalanced	
AF outputs;		
Speaker output:	1W or more (4 ohms)	
Record/line output:	1mW or more (600 ohms)	

Highest grade all-wave receiver

NRD-515

Best for 59

Transmitter, NSD-515

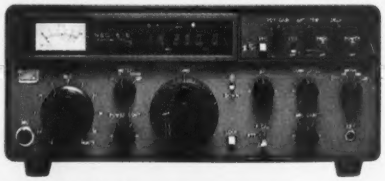

SPECIFICATIONS

Rated output power:	100W NSD-515 (50W 28MHz band)
Frequency range:	1.8MHz-2.0MHz/3.5MHz-4.0MHz/7.0MHz-7.3MHz/14.0MHz-14.35MHz/21.0MHz-21.45MHz/28.0MHz-29.0MHz/29.0MHz-29.7MHz/Optional new bands approved by WARC '79 10.1MHz-10.15MHz/18.068MHz-18.168MHz/24.89MHz-24.99MHz/
Mode of emission:	A3J (USB/LSB) A1 (CW) F1 (RTTY)

- For more information please contact to;

JRC
Since 1915

Japan Radio Co., Ltd.

MAIN OFFICE: Mori Building Fifth, 17-1, Toranomon 1-chome, Minato-ku,
Tokyo 105, Japan Cable Address: "JAPANRADIO TOKYO"
Phone: (03) 591-3451 Telex: 0222-3068
U.S.A. BRANCH OFFICE: T. Hayashi,
120 East 56th Street, New York, New York 10022
Phone: 212-355-1180 Telex: 230-645636 JAPANRADIO NYK

AUSTRALIA: N.S.W.—EMONA ELECTRONICS PTY LTD. Phone: 398-6378
Victoria—VICOM IMPORTS PTY LTD. Phone: (03) 62 6931
FINLAND: Kotka—VISI RADIO OY Telex: 53260 VISI SF
FRANCE: Paris—SOCIETE G.E.S. (GENERAL ELECTRONIC SERVICES) Phone: (1) 345 35 92
CANADA: Vancouver—GLENWOOD TRADING CO., LTD. Phone: 604 984 0404
GERMANY: Hannover—RICHTER & CO. Phone: (0511) 352 1111
ITALY: Milanese—TECHNOVENT, ITALIA, SRL Phone: 02 32 83 089

SWITZERLAND: SEICOM AG Phone. 064 515566
U.K.: Derbyshire—LOWE ELECTRONICS, LTD. Phone: 0629-2430
U.S.A.: N.J.—GILFER ASSOCIATES, INC. Phone: 201 391 7887
Ohio—UNIVERSAL ELECTRONICS, INC. Phone: (614) 866-4605
NEW ZEALAND: Dunedin MALVICOM INTERNATIONAL, LTD. Phone: 697-625

Robin Becker KA3W
2912 N. Calvert St.
Baltimore MD 21218

Deep-Six Squelch Tails

Kerchunks take a dive with the addition of this audio delay.

Squelch tails are ugly. Few things are more annoying to repeater users than a long squelch tail every time someone drops his carrier. At WR3AFM, a Baltimore Amateur Radio Club (BARC) multiple-receive-site repeater,[1] this problem is compounded by a second squelch tail, that of the link receiver. The resulting overall squelch tail is approximately 110 milliseconds in duration. However, thanks to the circuit described below, it is no longer audible.

A squelch tail is the noise heard at a receiver's audio output after the transmitting station has dropped its carrier but before the receiver's squelch circuit can mute the audio output. This is what you hear whenever the repeater carrier drops off the air, for example. The duration of the squelch tail is a function of your particular receiver.

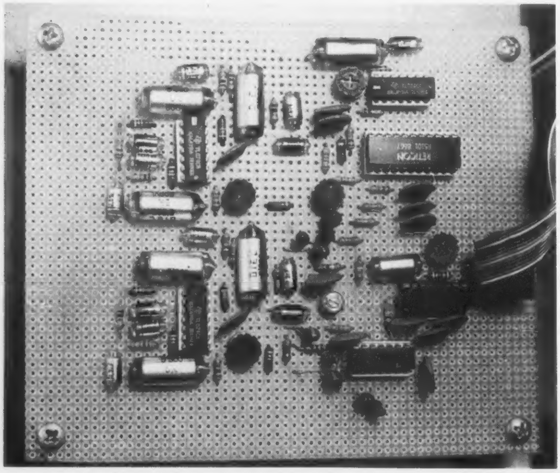

Photo A. The completed board installed at WR3AFM. The delay line is in the upper right. The I/O connector is in the far right. (Photo by N3IC)

Another source of squelch tails is a repeater receiver. Consider first a conventional single-site machine. Whenever the transmitting station drops its carrier, the repeater receiver's output follows with a burst of squelch noise. Since the repeater transmitter is still on the air at this point, this squelch tail is heard by all stations monitoring the machine.

Next, consider a split-site repeater (or a multiple-site repeater like WR3AFM) as shown in Fig. 1. In this type of setup, the repeater receiver (or each satellite receiver in a multiple-site scheme) is coupled to the repeater transmitter via a link, often on 450 MHz. The repeater receiver operates as before, appending a squelch tail to each transmission. The receiver output is sent by the link transmitter to the repeater transmit site, where it is received by the link receiver. When the link transmitter carrier drops, shortly after the repeater receiver squelch tail ends, the link receiver will append a squelch tail of its own to the audio output. Since the link receiver feeds the repeater transmitter (or voter, in the multiple-site case, which, in turn, feeds the transmitter), this (link) squelch tail also is heard by all monitoring stations.

In order to eliminate the squelch tail nuisance, a delay line was inserted into the audio-signal path. To see how this will allow the squelch tail to be silenced,

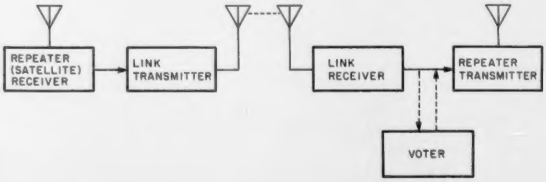

Fig. 1. Split-site (or multiple-site) diagram.

introducing a new dimension...

COMPUTERIZED ANTENNA CONTROL FROM PRO-SEARCH™

or Contesters, X'ers, Handicapped perators and General urpose Ham perators:

he Most Advanced ntenna Control vailable...

- The Only Computerized Unit
- The Only Talking Unit
- The Only Scanning Unit
- The Only Programmable Unit
- The Only Automatic Braking Unit

ontesters:

ro-Search seeks out a re-programmed heading, plus tores various common head-ngs and automatically scans or those rare multipliers, iving the operator hands-free peration and more time for ontesting.

X'ers:

ro-Search loads in short path nd long path headings and vith the touch of a button, the ystem works between both eadings. Plus you have all of he other features of the Pro-earch to aid you in catching hat rare DX station.

andicapped Operators:

ro-Search offers ease of peration...control the entire ystem with just one touch. A alk loop...vocally calls out the eadings, allowing blind opera-ors to accurately program and ear their headings.

eneral Purpose Operators:

ro-Search **has numerous ses.**

re-set beam headings for CEDS, VHR WORK, and many thers. Current headings can e read, by displaying the resent directions with LEDS. ro-Search also displays and tores the last station worked, vhich can be recalled by the uto-Locate system with the ouch of a button.

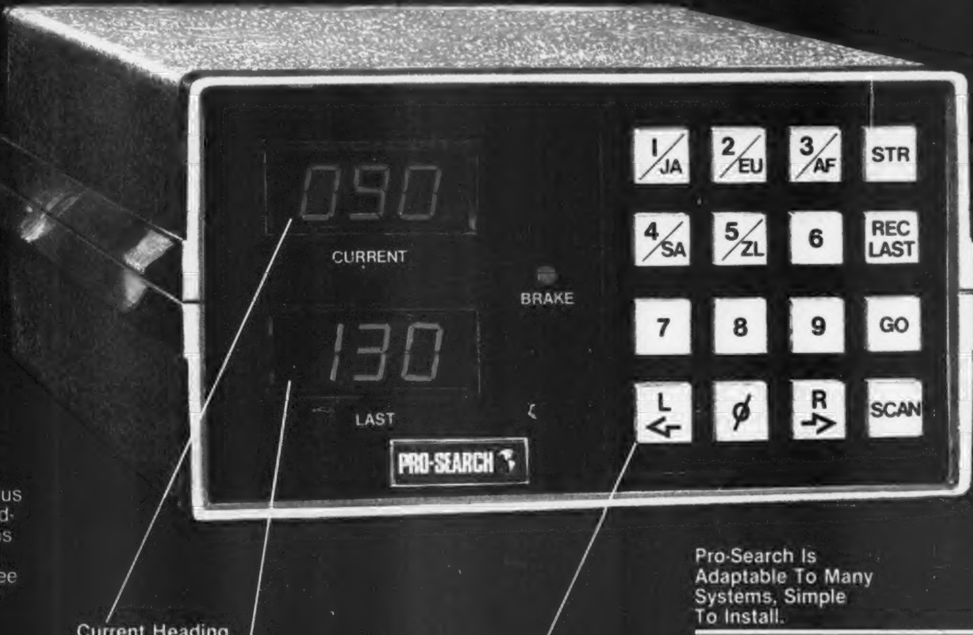

Current Heading Display

Last Heading Display and Visual Confirmation of Computer Instructions

Programmable Keyboard and Memory Functions

Pro-Search Is Adaptable To Many Systems, Simple To Install.

*Pro-Search is NOW available for most popular rotors. CDE, HY-GAIN, TELREX, WILSON, ALLIANCE, and PROP-PITCH.

Disconnect your present antenna control system and connect ours.

Some modifications are necessary, depending on type of rotor.

To Order:

1-800-325-4016
1-314-994-7872 (Missouri)

Or write:

Pro-Search Electronics
A Division of Wurdack and Associates, Inc.
10411 Clayton Road
Suite 305
St. Louis, Missouri 63131

*Patent Pending

PRO-SEARCH
Reaching The World

refer to Fig. 2. Note that although the figure specifically illustrates the multiple-site (or split-site) system, by ignoring the link (second) squelch tail it is valid also for a single-site system.

Fig. 2(a) shows the audio output of a satellite receiver and its associated squelch tail. This signal is sent via a link transmitter to a link receiver, and from there to the voter, with the added link receiver squelch tail. The audio output of the voter, shown in Fig. 2(b), contains the satellite receiver squelch tail and the link receiver squelch tail. The carrier-operated switch (COS) depicted in Fig. 2(c), with logic high equivalent to on and logic low equivalent to off, changes state after both squelch tails are completed. Since the COS is usually employed to gate (switch on or off) the repeater transmitter audio (or the transmitter itself), both squelch tails are transmitted by the repeater.

Fig. 2(d) shows the voter audio output delayed in time. It can be seen that the squelch tails in Fig. 2(d) occur after the COS goes low. Using the COS signal to gate the audio in Fig. 2(d) gives Fig. 2(e). This audio contains no squelch tail at all.

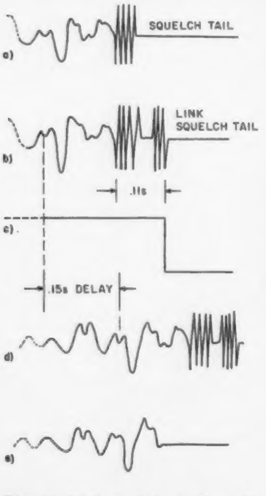

Fig. 2. Using delayed audio to eliminate squelch tails. (a) Repeater (satellite) receiver audio output. (b) Link receiver audio output. (c) COS. (d) Delayed link receiver (voter) audio output. (e) Gated repeater transmitter audio.

The length of the satellite-receiver squelch tail is somewhat dependent on the received signal. Since the link transmitters and receivers are fixed, the link squelch tail is always the same length. To take this variability into consideration, the length of the delay was chosen to be longer than the worst squelch tail usually encountered. This ensures absolutely no transmitted squelch tail, but also chops off a small amount of audio in some cases. At worst, however, if the carrier is dropped immediately following a word, one syllable might be lost. This turns out to be insignificant in practice. Of the almost 500 members of BARC, only one seems ever to have problems with lost syllables, and then only on one-word transmissions! Overall performance has been great, and the total parts cost of approximately $70 puts the project within reach of most everyone.

General Theory

A block diagram of the overall system is shown in Fig. 3. Starting with the delay itself, the various blocks will be examined.

The heart of the circuit is a Reticon R5101 Charge-Coupled Device (CCD) which performs the delay. The CCD acts as an analog shift register. It stores time samples of the analog input signal as packets of charge. The amount of charge in each packet is proportional to the amplitude of the analog input at the time of sampling. The packets of charge are shifted through 2000 stages before they reach the output of the CCD. Thus, the chip has 2000 samples of the input stored at any given time, each separated in time by T seconds, where T is the time between samples. The CCD uses two clock cycles per shift, and hence the overall delay time (Td) is given by Td = 2000 × (2/Fc), where Fc is the clock frequency supplied by the oscillator block and is equal to 2/T.

Instead of using a CCD, other schemes could be used to achieve the desired delay. These include tape loops and digital sampling, which are discussed briefly below.

The tape-loop scheme involves continuously recording and simultaneously playing back the received audio on a tape recorder. Since there is a physical gap between the record head and the playback head, a time-delay is introduced (Td = G/V, where G = gap length in inches and V = tape speed in inches per second). A Td of up to one second is typical at slow tape speeds with this approach. This scheme is the simplest to implement, but was not used because of the problems of reliability of such factors as the tape transport mechanism, tape breakage, and dirt on the tape heads.

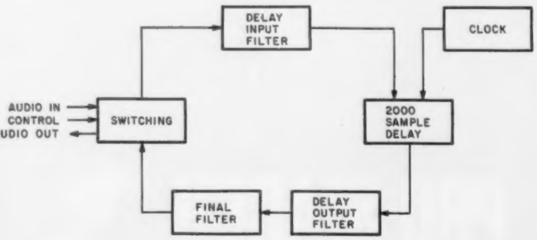

Fig. 3. System block diagram.

The digital-sampling scheme is similar to the CCD technique except that the audio signal is first digitized by an analog-to-digital converter, then stored in a digital shift register, and finally converted back to analog form by a digital-to-analog converter. This approach has the advantage of being able to achieve any desired delay by adding more shift registers. To get a reasonable signal-to-noise ratio and still preserve the dynamic range of speech, we would need either many bits (12 or more) in the digital words or we would have

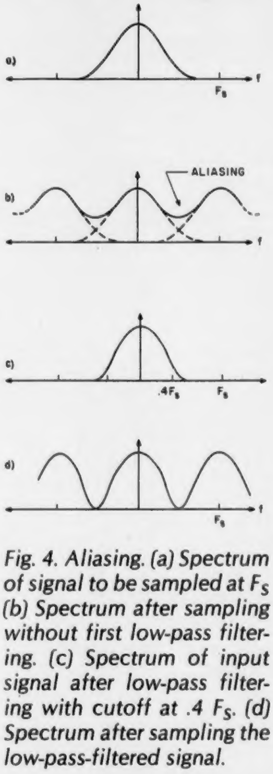

Fig. 4. Aliasing. (a) Spectrum of signal to be sampled at F_S (b) Spectrum after sampling without first low-pass filtering. (c) Spectrum of input signal after low-pass filtering with cutoff at .4 F_S. (d) Spectrum after sampling the low-pass-filtered signal.

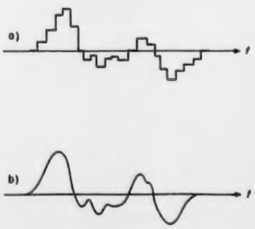

Fig. 5. CCD output filtering. (a) Before filtering. (b) After filtering.

CT2100

HAL Puts MORE Behind The Buttons

45-1200 Baud RTTY
1-100 WPM Morse

Code

2 Page Display

72 or 36 Character Lines

Status Indicator on Screen

Black or White Characters

Unshift on Space (For Baudot)

Half or Full Duplex

Synchronous Idle ("Diddle")

Auto TX/RX Control

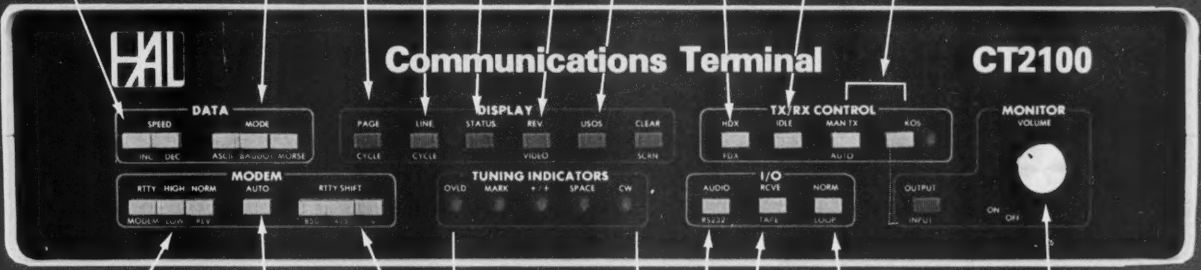
HAL
Communications Terminal
CT2100
DATA
SPEED
MODE
INC DEC
ASCII BAUDOT MORSE
DISPLAY
PAGE LINE STATUS REV USOS CLEAR
CYCLE CYCLE VIDEO SCRN
TX/RX CONTROL
HDX IDLE MAN TX KOS
FDX AUTO
MONITOR
VOLUME
MODEM
RTTY HIGH NORM AUTO RTTY SHIFT
MODEM LOW REV
TUNING INDICATORS
OVLD MARK +/+ SPACE CW
I/O
AUDIO RCVE NORM
RS232 TAPE LOOP
OUTPUT
INPUT
ON OFF

Four Internal RTTY Demodulators
- High Tones (U.S. Standard)
- Low Tones (IARU Standard)
- 103 Modem (1070/1270 HZ)
- 202 Modem (1200/2200 HZ)

Auto Mark-Hold

All 3 RTTY Shifts (High or Low Tones)

LED Tuning Indicators
-Plus-
On-Screen Tuning Bar
-Plus-
Ext. Scope Connections

Audio or RS232 Data

Input Audio From Receiver or Tape

Transmit and Receive With RTTY Loop Devices

Audio Monitor For Either Input or Output Signals
Internal Speaker
Plus External Output

CT2100 System:

- CT2100 Communications Terminal
- KB2100 Keyboard
- Video Monitor
- Printer (300Bd Serial ASCII-MPI-88G)
- RM2100 Rack Adapter
- MSG2100 2000 Character "Brag Tape" ROM

- 24 Line Display
- 2 Pages of 72 Character Lines
  -or-
  4 Pages of 36 Character Lines
- Split Screen (with KB2100)

HAL
Communications Terminal
CT2100
KB2100

CT2100

9" TV Monitor

KB2100

345

HAL COMMUNICATIONS CORP.
Box 365
Urbana, Illinois 61801
217-367-7373

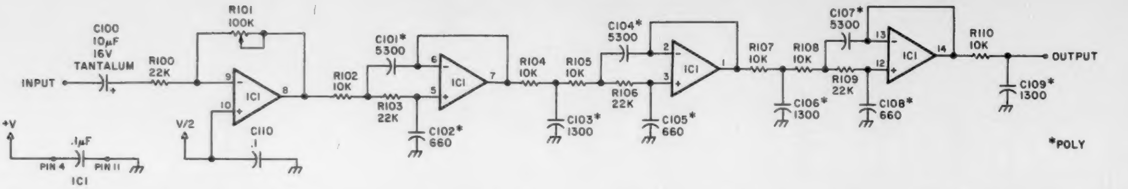
R101
100K
C100
10μF
16V
TANTALUM
R100
22K
INPUT
9
10
IC1
8
+V
.1μF
PIN 4
PIN 11
IC1
V/2
C110
.1
C101*
5300
R102
10K
R103
22K
6
5
IC1
7
C102*
660
R104
10K
R105
10K
C103*
1300
C104*
5300
R106
22K
2
3
IC1
1
C105*
660
R107
10K
R108
10K
C106*
1300
C107*
5300
R109
22K
13
12
IC1
14
C108*
660
R110
10K
OUTPUT
C109*
1300
*POLY

Fig. 7. Delay input and delay output filtering. Note: IC1 and IC2 are TL074Cs. IC1—100 series; IC2—200 series.

Frequency (Hz)	Gain (dB) (I/O 2 to I/O 6)
12	−3
20	−1.32
50	−.21
100	0
1k	.53
2k	1.59
2.2k	1.63
2.37k	1.59
3k	0
3.43k	−3
4k	−10
5k	−30
6k	−51

Fig. 6. Measured overall response. Conditions: 1) Delay = 150 ms (F_{clock} = 26.67 kHz); 2) two-pole adjustable low-pass filter set for 0 dB at 3 kHz.

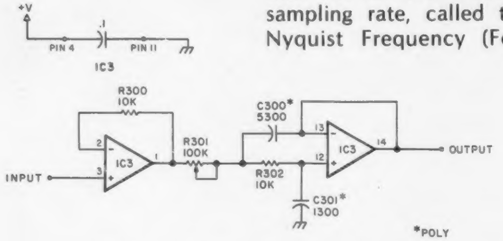
+V
.1
PIN 4
PIN 11
IC3
R300
10K
2
3
IC3
1
INPUT
R301
100K
C300*
5300
13
12
IC3
14
R302
10K
C301*
1300
OUTPUT
*POLY

Fig. 8. Final filter. IC3 is a TL074C.

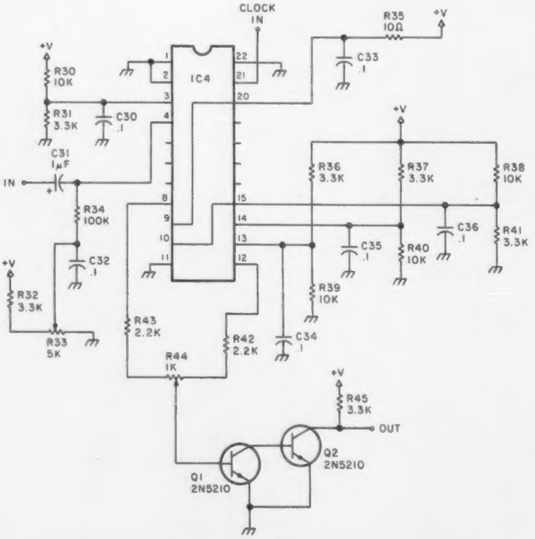
CLOCK
IN
R35
10Ω
+V
C33
.1
IC4
1
2
3
4
8
9
10
11
22
21
20
15
14
13
12
+V
R30
10K
R31
3.3K
C30
.1
C31
1μF
IN
R34
100K
C32
.1
+V
R32
3.3K
R33
5K
+V
R36
3.3K
R37
3.3K
R38
10K
C35
.1
R40
10K
C36
.1
R41
3.3K
R39
10K
C34
.1
R43
2.2K
R42
2.2K
R44
1K
+V
R45
3.3K
OUT
Q1
2N5210
Q2
2N5210

Fig. 9. 2000-sample delay. IC4 is a Reticon R5101.

to use a compression-expansion (companding) technique. Either way, due to the high cost of analog-to-digital converters and digital memory (the shift registers) and because of its higher total package count, these approaches were undesirable.

As in any time-domain sampling system, the input must be a band-limited process. In a low-pass application, such as with speech, any input components whose frequency is greater than one-half the effective sampling rate, called the Nyquist Frequency (Fc/4 here), must be removed prior to sampling to prevent a form of distortion called "aliasing." If not removed by filtering, these components will appear at the output as lower frequency (alias) signals (see Fig. 4).[2] Once aliasing occurs, it cannot be removed by filtering, since the aliased components are indistinguishable from the original components. The necessary filtering is performed here by a 3-section, 9-pole low-pass filter.

Since the CCD is a discrete time system (that is, its output changes only at specific times, resembling a staircase), the output also contains high-frequency terms which must be removed by filtering (see Fig. 5). This filtering is again performed by a 3-section, 9-pole low-pass filter.

Since the frequency response of the CCD is somewhat dependent on the clock frequency selected, a tunable low-pass filter is provided. By tweaking this filter, the overall response may be optimized for a particular clock rate. The response for the board at WR3AFM is given in Fig. 6. The tunable filter was set so that the response at 3 kHz was equal to that at 100 Hz (0 dB). Notice the excellent flatness over the speech bandwidth (−0 dB, +1.6 dB). The steep roll-off past 3 kHz also serves to attenuate wideband noise from other sources preceding the delay line.

Variable-gain input and output buffers are provided. The input buffer is set to limit the input to the CCD to less than 1 volt peak to prevent overloading the device, and the output buffer is set to achieve unity overall gain (0 dB) at 100 Hz. Thus, the whole board is transparent to the rest of the repeater.

The switching stage allows the delay to be bypassed (if desired) and permits the audio to be gated with the COS signal. This eliminates the need for any external audio switching.

Circuit Design

Filters

The circuit was designed in a fairly straightforward manner. Quad bi-FET op amps were chosen because their high input impedance makes designing with them simple. Specifically, the TL074 is a low-noise version of the popular TL084, which could be substituted, as could many other audio op amps.

Since the frequency response of the CCD starts to roll off at about 1.5 kHz when set for a 150-millisecond delay, some form of equalization was required to extend the usable bandwidth of the system. High-frequency pre-emphasis (that is, boosting the high-frequency components ahead of the CCD, as opposed to post-emphasis) has the advantage that the input signal is kept large with respect to the noise at all times. However, since the CCD overloads at about 1-volt peak input, any boost in the spectrum ahead of the CCD must be accompanied by an overall cut in the input level (relative to that permissible with no pre-em-

AZDEN ★ NEW! ★ AZDEN ★ NEW! ★ AZDEN ★ NEW! ★ AZDEN

THE GIANT **AZDEN**® COMPANY

REVOLUTIONIZES THE STATE OF THE ART

AWE AND **AZDEN**® INTRODUCE THE BRILLIANT NEW **PCS-2800**

MICROCOMPUTER CONTROLLED

SUPERIOR COMMERCIAL GRADE

10 METER

FM TRANSCEIVER

SPECIAL

$229.00

AZDEN
10M FM TRANSCEIVER
PCS-2800
S/RF
UL
MAIN
MM
MEMORY ADDRESS
9.00
MHz
100K UP
10K UP
MHz UP
100K DOWN
10K DOWN
AUTO SCAN
MAIN
M ADRS
M SCAN
M1 CALL
M CALL
M WRITE
SCAN MODE
SLOW
NORMAL
MIC/CONT
POWER/VOL
PUSH
RF ATT/SQL
PULL
HIGH/LOW
VOL&SQL
INT/EXT

COMPARE THESE FEATURES
WITH ANY UNIT AT ANY PRICE

- **FREQUENCY RANGE:** Receive and transmit: 28.000 to 29.995 MHz, 10KHz steps with built-in – 100 KHz repeater offset.
- **ALL SOLID STATE-CMOS PL DIGITAL SYNTHESIZED.**
- **SIZE:** UNBELIEVABLE! **ONLY** 6 3/4" x 2 3/8" x 9 3/4". **COMPARE!**
- **MICROCOMPUTER CONTROLLED:** All scanning and frequency-control functions are performed by microcomputer.
- **DETACHABLE HEAD:** The control head may be separated from the radio for use in limited spaces and for security purposes.
- **SIX-CHANNEL MEMORY:** Each memory is re-programmable. Memory is retained even when the unit is turned off.
- **MEMORY SCAN:** The six channels may be scanned in either the "busy" or "vacant" modes for quick, easy location of an occupied or unoccupied frequency. AUTO RESUME. **COMPARE!**
- **FULL-BAND SCAN:** All channels may be scanned in either "busy" or "vacant" mode. This is especially useful for locating repeater frequencies in an unfamiliar area. AUTO RESUME. **COMPARE!**
- **INSTANT MEMORY-1 RECALL:** By pressing a button on the microphone **or** front panel, memory channel 1 may be recalled for immediate use.
- **MIC-CONTROLLED VOLUME AND SQUELCH:** Volume and squelch can be adjusted from the microphone for convenience in mobile operation.
- **DIRECT FREQUENCY READOUT:** LED display shows operating frequency, **NOT** channel number. **COMPARE!**
- **TEN (10) WATTS OUTPUT:** Also 1 watt low power for shorter distance communications. LED readout displays power selection when transmitting.
- **DIGITAL S/RF METER:** LEDs indicate signal strength and power output. No more mechanical meter movements to fall apart!
- **LARGE ½-INCH LED DISPLAY:** Easy-to-read frequency display minimizes "eyes-off-the-road" time.
- **PUSHBUTTON FREQUENCY CONTROL FROM MIC OR FRONT PANEL:** Any frequency may be selected by pressing a microphone or front-panel switch.
- **SUPERIOR RECEIVER SENSITIVITY:** 0.28 uV for 20-dB quieting. The squelch sensitivity is superb, requiring less than 0.1 uV to open. The receiver audio circuits are designed and built to exacting specifications, resulting in unsurpassed received-signal intelligibility.
- **TRUE FM, NOT PHASE MODULATION:** Transmitted audio quality is optimized by the same high standard of design and construction as is found in the receiver. The microphone amplifier and compression circuits offer intelligibility second to none.
- **OTHER FEATURES:** Dynamic Microphone, built in speaker, mobile mounting bracket, external remote speaker jack (head and radio) and much, much more. All cords, plugs, fuses, microphone hanger, etc. included. Weight 6 lbs.
- **ACCESSORIES:** 15' REMOTE CABLE....$29.95. FMPS-4R A/C POWER SUPPLY....$39.95. TOUCHTONE MIC. KIT....$39.95. EXTERNAL SPEAKER....$18.00.

AMATEUR-WHOLESALE ELECTRONICS ORDER NOW TOLL FREE

8817 S.W. 129th Terrace, Miami, Florida 33176
Telephone (305) 233-3631 ● Telex: 80-3356

U.S. DISTRIBUTOR DEALER
INQUIRIES INVITED

1-800-327-3102

CREDIT CARD HOLDERS MAY USE OUR TOLL FREE ORDERING NUMBER.

phasis). Post-emphasis completely avoids this problem, but it also boosts any noise added by the CCD circuitry. As a compromise, equal amounts of pre- and post-emphasis were employed.

The low-pass filters were designed to provide the needed boosting as well as to attenuate the high-frequency components. In order to achieve a 150-millisecond delay, Fc = 26.67 kHz from the equation, above. Thus, the Nyquist Frequency (Fc/4 here) is 6.67 kHz. The low-pass filters must attenuate at and above this frequency. The 9-pole filters shown in Fig. 7 have a peak (boost) of approximately 6 dB before rolling off at −54 dB/octave. The overall response is shown in Fig. 6.

The final output filter, a buffer and 2-pole low-pass filter combination, is shown in Fig. 8.

CCD/Clock

Fig. 9 shows the circuitry surrounding the CCD that was suggested by the manufacturer, which was found to work well. The clock signal is produced from a simple two-inverter oscillator and is shown in Fig. 10.

Switching

Since WR3AFM is controlled by an 8080 microprocessor, all control signals are supplied by TTL open-collector outputs. Thus CMOS 4066 analog switches were a natural choice to handle the audio gating. The switching circuits are shown in Fig. 11.

Construction Notes

The board was built using point-to-point techniques. The actual layout, shown in Fig. 12, was carefully planned to ensure neat wiring and no ground loops. Any popular construction technique should work. Whatever method is used, however, the ground leads should be heavy enough to keep op-amp noise reasonable.

All op-amp Vcc inputs were bypassed to ground with a .1-uF disc capacitor right at the chip, on the underside of the board. Polystyrene capacitors were used in the filters to achieve close tolerance and good temperature stability. Sockets were used for all chips, with the one for the CCD being a must.

The input and output audio, switching, and power-supply connections can conveniently be made using ribbon cable and a 14-pin DIP socket. A suggested pin configuration is shown in Fig. 13. Unused lines should be grounded at the board end only, to reduce noise and prevent ground loops. The ground lead from the DIP socket should be connected to the ground bus on the board at the spot that results in the smallest amount of noise on the audio-output line. In the layout shown in Fig. 12, the best spot was found to be near the inverter chip.

Finally, as shown in Fig. 14, a 10-uF filter capacitor was placed from Vcc to ground and from Vcc/2 to ground. Tantalum capacitors were used because of their small size and low leakage, but any type capacitor will do.

Parts

The CCD is available for $50 from Reticon Corporation, 910 Benicia Avenue, Sunnyvale CA 94086, and their distributors (write to them for info). For most other parts, a good supply house is Digi-Key Corporation, PO Box 677, Thief River Falls MN 56701.

Adjustment

To set the clock frequency, adjust R21 while observing pin 15, IC5, on a scope or frequency counter. The desired frequency may be found from the equation, above. For a 150-millisecond delay, Fc = 26.67 kHz.

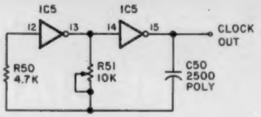
IC5
IC5
12
13
14
15
CLOCK OUT
R50 4.7K
R51 10K
C50 2500 POLY

Fig. 10. Clock. IC5 is a CD4049AE.

R101 is adjusted to prevent overloading the CCD. Since the maximum pre-emphasis is 6 dB, the maximum signal at pin 8, IC1, must not exceed .5 volts peak for any input signal. However, to achieve the best signal-to-noise ratio, it is desirable to keep the signal as large as possible. Therefore, apply a sine wave at the maximum level to be encountered in operation (such as the level that gives 5-kHz deviation on the repeater) to the input (I/O pin 2) and adjust R101 until the level at pin 8, IC1, is .5 volts peak.

To adjust the bias and symmetry of the CCD, apply an audio-frequency sine wave to the input (I/O pin 2). Adjust the amplitude of the sine wave until distortion is just evident at pin 14, IC2. Next, set R33 and R44

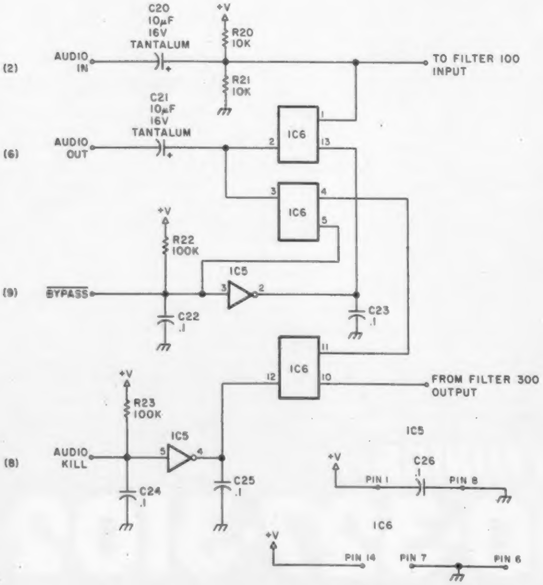
C20 10μF 16V TANTALUM
+V
R20 10K
R21 10K
(2)
AUDIO IN
TO FILTER 100 INPUT
C21 10μF 16V TANTALUM
(6)
AUDIO OUT
IC6
IC6
IC6
1
2
13
3
4
5
+V
R22 100K
IC5
(9)
BYPASS
C22 .1
C23 .1
11
12
10
FROM FILTER 300 OUTPUT
+V
R23 100K
IC5
(8)
AUDIO KILL
C24 .1
C25 .1
IC5
+V
C26 .1
PIN 1
PIN 8
IC6
+V
PIN 14
PIN 7
PIN 6

Fig. 11. Switching. IC6 is a CD4066.

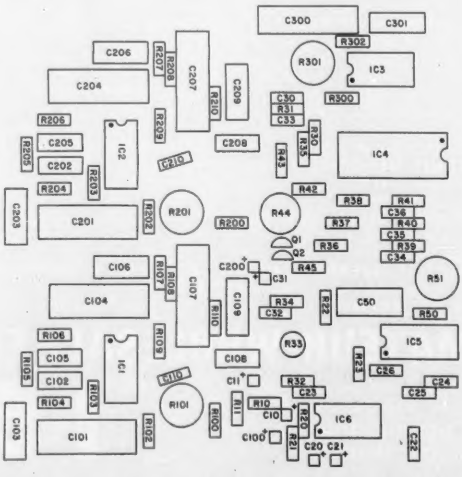
C300
C301
R302
C206
R207
R208
C207
R301
IC3
C204
C209
R210
C30
R31
C33
R300
R206
R209
C205
IC2
C208
R30
R35
IC4
R205
C202
C210
R43
R203
R204
R42
R44
R38
R41
C36
R40
C35
R39
C34
C203
C201
R202
R201
R200
R37
R36
Q1
Q2
C106
R107
R108
C107
C200
C31
R45
R51
C104
R110
C109
R34
C32
R22
C50
R50
R106
R109
R33
IC5
C105
R105
IC1
C108
R23
C26
C102
R103
C110
C11
R32
C23
C24
C25
R104
R101
R11
R10
C10
R20
IC6
C103
C101
R102
R100
C100
R21
C20
C21
C22

Fig. 12. Parts layout.

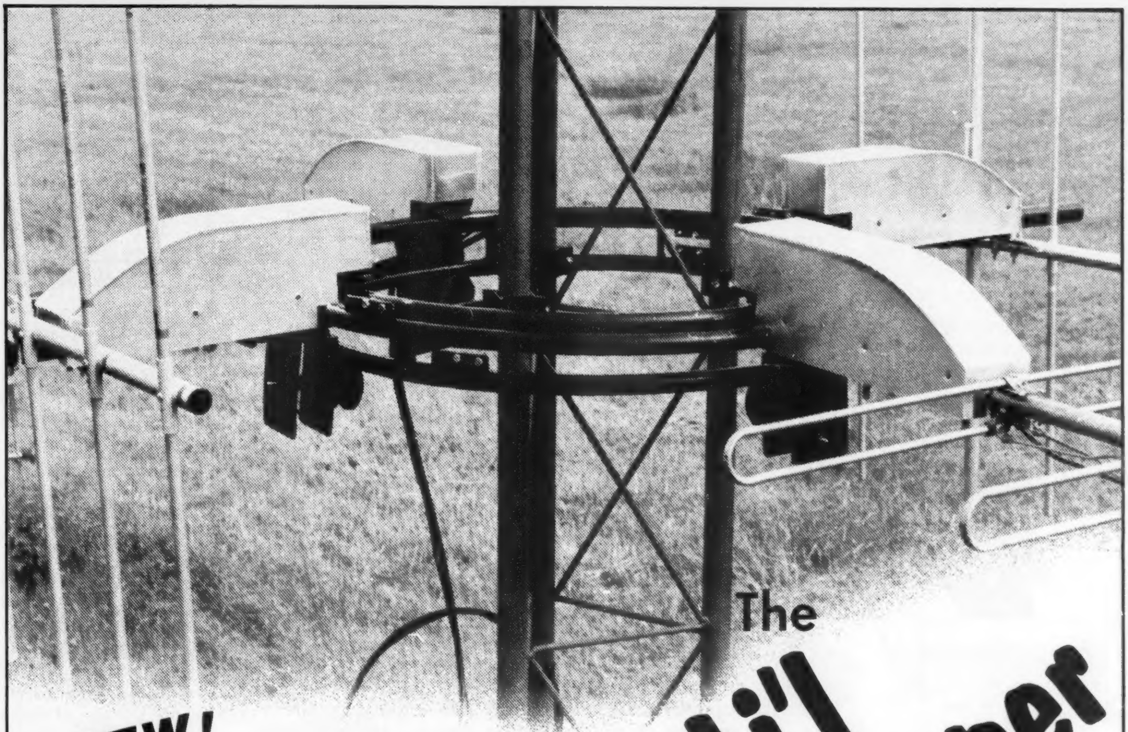

The Li'l Slipper

NEW!

POLAR RESEARCH'S

Multi-Directional, Motor Driven Antenna Mounting Systems For Discriminating Radio Operators!

(ANTENNAS NOT INCLUDED)

Never before has an antenna mounting system been available to radio operators with the advantages and features of Polar Research's Li'l Slipper. The tremendous versatility and widespread applications of the Li'l Slipper system eliminate any cumbersome, awkward, inefficient and inaccessible antenna configurations due to the old normal single mast, vertical antenna stacking. Greatly reducing tower interference to the radiation pattern of the antenna, the Li'l Slipper's design effectively distributes wind-load evenly on the tower's structure while maintaining all antennas in a true perpendicular position, tangent at any point to the rotor's arc.

Exclusive Li'l Slipper features include a high torque geared drive motor; all electric, end-of-rotation circuitry; acceptance of masts up to 2" O.D. on all four housings; and limitless applications with VHF, Split-Boom, H.F. Beams, Quads, TV/FM antennas, and even UHF Dishes and Corner Reflectors.

POLAR RESEARCH, INC.
THIEF RIVER FALLS, MINNESOTA, U.S.A.

✓176

Call Toll Free 1-800-328-2041

U.S. AND FOREIGN PATENTS PENDING

Polar Research, Inc.
P.O. Box 781
Thief River Falls, MN 56701; Phone (218) 681-7413

DEALER INQUIRIES INVITED

✓See List of Advertisers on page 130

to minimize the distortion, and then increase the input until the distortion is again visible. Continue this process until no further reduction in distortion is observed.

Adjust R301 so that the overall gain is equal (I/O pin 2 to I/O pin 6) at 100 Hz and 3 kHz. This gives a desirable response for a voice channel.

Finally, adjust R201 so that the overall gain (I/O pin 2 to I/O pin 6) is unity (0 dB) at 100 Hz (or 3 kHz).

Pin 2—Audio input
Pin 6—Audio output
Pin 7—Ground
Pin 8—Audio kill
Pin 9—$\overline{\text{Bypass}}$
Pin 14— + 12 volts

Fig. 13. I/O connector wiring.

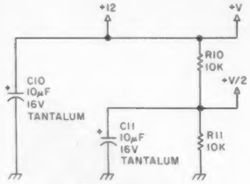

Fig. 14. Power supply filtering.

Echoes, Etc.

Since the unit introduces delay in the audio path, a rather interesting echo effect can be observed. Referring to Fig. 15, notice that due to the delay some audio output continues from the repeater after the transmitting station's carrier drops. The length of this audio is equal to the length of the combined squelch tails. Depending on the speed of the station's T-R switching, the operator will hear the end of his transmission coming back.

The only drawback of the device also is visible in Fig. 15. The final portion of audio is chopped by the circuit. The amount of audio lost is equal to the difference between the length of the delay and the length of the combined squelch tails. Since the usual squelch tail lasts for 110 milliseconds (at WR3AFM), if a short squelch tail was acceptable, the delay could be shortened to 110 milliseconds. In practice, almost everyone holds their PTT for a short amount of time after they stop speaking, so this is really a moot point.

The delay also causes a strange phenomenon if an operator is monitoring the repeater on a secondary receiver. It is virtually impossible to talk while listening to your own voice delayed by 150 milliseconds. This effect has encouraged the more fun-loving walkie owners to engage in the friendly game of sneaking up behind an unsuspecting repeater user while he is transmitting and then turning up the volume on the walkie. This fun alone justifies the work involved in building the delay line.■

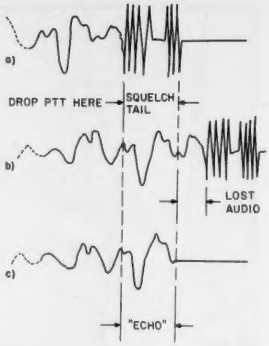

Fig. 15. Echo. (a) Transmitted audio plus squelch tails. (b) Delayed audio. (c) Repeater output.

References

1. Glaser, R., "An 8080 Repeater Control System," *73 Magazine*, February, 1979.

2. For a more complete discussion of sampling and signal processing in general, see, for instance, Schwartz, M., *Information Transmission, Modulation, and Noise*, McGraw-Hill, 1970 (second edition), or Rabiner, L. and Schafer, R., *Digital Processing of Speech Signals, Prentice-Hall, 1978.*

SPEEDCALL'S NEW #312 TOUCH-TONE DECODER ENDS RADIO BACKGROUND "CHATTER" FOREVER.

Output: Single open collector output. 200mA
Input Signal Range: 20 mV to 6 V (flat input).
Code Capacity: 3 to 8 digits address plus select any of the 16 touch-tone digits as desired.
Battery Voltage: 13.8 VDC Nom. (9 to 16 VDC) @ 30 mA nominal on standby.
Assembled Dimensions: 3/4" high, 2-1/8" wide and 3-3/4" long.

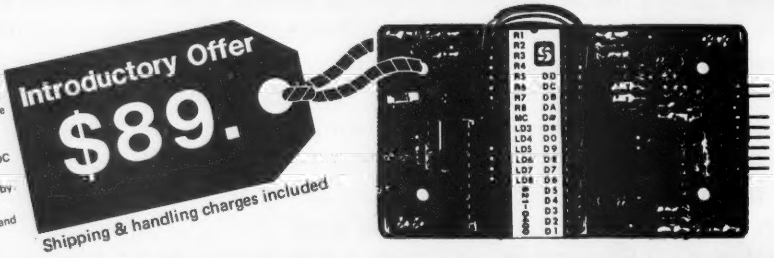

- LOW COST COMMERCIAL GRADE KIT!
- EASY TO ASSEMBLE COMPACT UNIT!
- STATE-OF-THE-ART FLEXIBILITY!

Speedcall Corporation, with 20 years of reliability and know-how in the Mobile Radio Industry, now offers the Model 312K; a unique, low-cost DTMF selective call Touch-Tone® Decoder. It's specially designed in kit form for radio buffs, with all of the quality and performance that made Speedcall #1 in signaling!

No more annoying background chatter, no more missed calls. At last it's possible for individuals and repeater groups to have their own personal and emergency touch-tone DTMF network! And you may use all 16 touch-tone digits to expand your selection of formats and permit special control applications.

To order, send check or money order to:

DEPARTMENT "K"
SPEEDCALL
CORPORATION
2020 National Avenue • Hayward, California 94545
415-783-5611
↙198
(California Residents add 6% Sales Tax)

VISA
master charge

SWD-1 VIDEO CONVERTER

FOR CABLE TV

VIDEO CONVERTER KIT

The SWD-1 Video Converter is utilized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms. 117VAC.

SWD-1 Video Converter Kit **$69.95**

VTR ACCESSORIES

SIMPLE SIMON VIDEO STABILIZER

Simple Simon Video Stabilizer, Model VS-125, eliminates the vertical roll and jitter from "copy guard" video tapes when playing through large screen projectors or on another VTR. Simple to use, just adjust the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments. Includes 12V power supply.

VS-125 Video Stabilizer, wired **$54.95**

SIMPLE SIMON VIDEO SWITCHING BOX

SIMPLE SIMON

The Affordable Video Control Center

Excellent in isolation and no loss routing system. Simple Simons VSB-300 Video Switching Box enables you to bring a variety of video components together for easy viewing/dubbing. Also you gain the ability to record one channel while viewing another. Unit includes two F-type quick connector ended cables.

VSB-300 Video Switching Box, wired **$19.95**

UHF ANTENNAS and ACCESSORIES

MDS-AMATEUR-ETV 32 ELEMENT YAGI ANTENNA

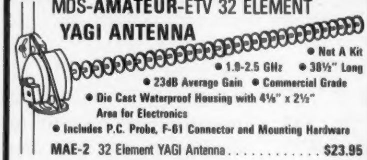

- **Not A Kit**
- **1.9-2.5 GHz**
- **38½" Long**
- **23dB Average Gain**
- **Commercial Grade**
- **Die Cast Waterproof Housing with 4⅛" x 2½" Area for Electronics**
- **Includes P.C. Probe, F-61 Connector and Mounting Hardware**

MAE-2 32 Element YAGI Antenna **$23.95**

Kato Sons' Down Converter Kit ★1.9 - 2.5GHz★

Designed for Simple Simon by former Japanese CQ Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antenna housing. Requires 1 hour assembly. IC and capacitors pre-soldered.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit **$34.95**

Kato Sons' Regulated Varible DC Power Supply

For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.

Model KSPS-1A Assembled Power Supply **$23.95**

SPECIAL INTRODUCTORY SAVINGS

ORDER ALL THREE ITEMS

MAE-2, KSDC-KIT and KSPS-1A for Only. **$74⁹⁵**

Regular price if ordered separately $82.85

— CO-AX CABLES ARE NOT INCLUDED —

ZYZZX VHF-UHF Wideband Antenna Amplifier

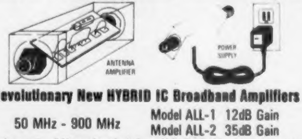

Revolutionary New HYBRID IC Broadband Amplifiers

50 MHz - 900 MHz

Model ALL-1 12dB Gain
Model ALL-2 35dB Gain

These units are not available anywhere else in the world. Each unit will serve many purposes and is available in Kit or Assembled form. Ideal for outdoor or indoor use. I/O impedance is 75 ohms. Amplifiers include separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors to tune or adjust.

ALL-1 Complete kit w/power supply	$24.95	**ALL-1** Wired/Tested w/pwr supply	$34.95
ALL-2 Complete kit w/power supply	34.95	**ALL-2** Wired/Tested w/pwr supply	44.95

Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA

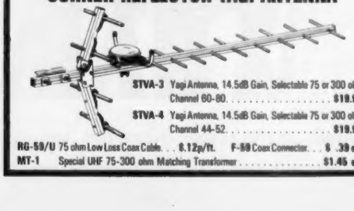

STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80. . . . . **$19.95**

STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52. . . . . **$19.95**

RG-59/U 75 ohm Low Loss Coax Cable. . . **$.12p/ft.** **F-59** Coax Connector. . . **$ .39 ea.**

MT-1 Special UHF 75-300 ohm Matching Transformer . . . . **$1.45 ea.**

Switch to Bambi™!

Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.

The Bambi Electronic Video Switch is an electronic switching network which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ...not being able to use more than one function at a time.

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Wired **$129⁹⁵**

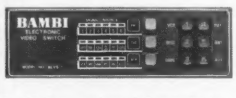

Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/outout selection without refering to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.

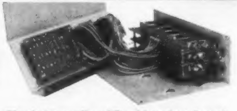

Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually sheilded for 65dB min. isolation).

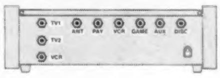

Bambi's Specifications:

● Input/Output Impedance	75 ohm
● Signal Loss	3dB ±1dB
● Noise	4dB ±1dB
● Input Return Loss	12dB min.
● Isolation	65dB min.
● Power Req.	117VAC 60 Hz, 2W
● Dimensions	10¼ W x 6⅜ D x 3⅛ H
● Weight	4½ lbs

7+11 SWD PARTS KITS

MITSUMI VARACTOR UHF TUNER

Model UES-A56F

$24.95

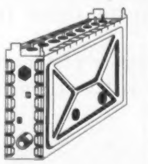

Freq. Range UHF470 - 889MHz
Antenna Input 75 ohms
Channels 14-83 Output Channel 3

KIT NO	PART NO	DESCRIPTION	PRICE
1	VT1-SW	Varactor UHF Tuner, Model UES-A56F	$24.95
2	CB1-SW	Printed Circuit Board, Pre-Drilled	18.95
3	TP7-SW	P.C.B. Potentiometers, 1-20K, 1-1K, and 5-10K ohms, 7-pieces	5.95
4	FR35-SW	Resistor Kit, ¼ Watt, 5% Carbon Film, 32-pieces. . .	4.95
5	PT1-SW	Power Transformer, PRI-117VAC, SEC-24VAC, 250ma	6.95
6	PP2-SW	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT w/Switch	5.95
7	SS14-SW	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Heat Sink 1-piece	29.95
8	CE9-SW	Electrolytic Capacitor Kit, 9-pieces.	5.95
9	CC33-SW	Ceramic Disk Capacitor Kit, 50 W.V., 33-pieces	7.95
10	CT-SW	Varible Ceramic Trimmer Capacitor Kit, 5-65pfd, 6-pieces	6.95
11	L4-SW	Coil Kit, 18mhs 2-pieces, .22µhs 1-piece (prewound inductors) and 1 T37-12 Ferrite Torroid Core with 3 ft. of #26 wire.	5.00
12	ICS-SW	I.C. Sockets, Tin inlay, 8-pin 5-pieces and 14-pin 2-pieces	1.95
13	SR-SW	Speaker, 4x6″ Oval and Prepunched Wood Enclosure	14.95
14	MISC-SW	Misc. Parts Kit Includes Hardware, (6/32, 8/32 Nuts, & Bolts), Hookup Wire, Ant. Terms, DPDT Ant. Switch, Fuse, Fussholder, etc.	9.95
When Ordering All Items, (1 thru 14), Total Price			139.95

7+11 PWD PARTS KITS

INTRODUCING OUR 7+11 PWD PARTS KITS

NEW

Kit No	PART NO	DESCRIPTION	PRICE
1	1VT1-PWD	Varactor UHF Tuner, Model UES-A56F	$24.95
2	2CB1-PWD	Printed Circuit Board, Pre-drilled	18.95
3	3TP11-PWD	PCB Potentiometers 4-20K, 1-.5K, 2-10K, 2-5K, 1-1K, and 1-50k. (11 pieces)	8.95
4	4FR-31-PWD	Resistor Kit, ¼W, 5% 29-pcs, ½ W 2-pcs	4.95
5	5PT1-PWD	Power Transformer, PRI-117VAC, SEC-24VAC at 500ma.	9.95
6	6PP2-PWD	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT with switch	5.95
7	7SS17-PWD	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Transistors 2-pcs, Heat Sinks 2-pcs	29.95
8	8CE14-PWD	Electrolytic Capacitor Kit, 14-pieces.	6.95
9	9CC20-PWD	Ceramic Disk Capacitor Kit, 50 WV, 20-pcs.	7.95
10	10CT5-PWD	Varible Ceramic Trimmer Capacitor, 5-65pfd, 5-pieces	4.95
11	11L5-PWD	Coil Kit, 18mhs 3-pcs, .22µhs 1-piece (prewound inductors) and 2 T37-12 Ferrite Toroid cores with 6 ft. #26 wire.	6.00
12	12ICS-PWD	IC Sockets, Tin inlay, 8 pin 4-pcs, 14 pin 1-pc and 16 pin 2-pcs.	2.95
13	13SR-PWD	Enclosure with PM Speaker and Pre-drilled Backpanel for mounting PCB and Ant. Terms	14.95
14	14MISC-PWD	Misc. Parts Kit, Includes Hardware, (6/32, 8/32 Nuts & Bolts), Hookup Wire, Solder, Ant. Terms DPDT Ant. Switch, Fuse, Fuseholder, etc.	9.95
15	15MC16-PWD	Mylar Capacitors, 14-pcs and Silver Mica Capacitors 2-pieces	7.95
When Ordering All Items, (1-15), Total Price.			159.95

SIMPLE SIMON ELECTRONIC KITS,™ Inc.

3871 S. Valley View, Suite 12, Dept. 7, Las Vegas, NV 89103

NEED 6 OR MORE OF AN ITEM?
WRITE FOR QUANTITY DISCOUNTS

In Nevada Call: **702-871-2892**
Outside Nevada Call: **1-800-782-3716**

Available by Mail Order Only
Send Check* or Money Order. Minimum Order: $16.95. Add 10% Shipping and Handling on orders under $40.00. For orders over $40.00, add 5%. Minimum Shipping and Handling $2.00. **Cat. $1.00**
— VISA and Mastercard Acceptable —

*Check orders will be held 30 days before shipping.

Steven D. Katz WB2WIK
24 Louis Drive
Budd Lake NJ 07828

Build Yourself A Paralyzed Beam

Go from east to west in less than a second with this 2-meter array. And put your rotator out to pasture.

"Five-nine here in Northern New Jersey, OM. 73 and thanks for the point. Anyone else calling?" Bzzz, whoosh . . . "three" . . . sputter, bzzz, whrrr. "Oh, gosh . . . the W3 calling, you're in the noise here, but you're off the back of the beam; I'll start turning in your direction . . ." Click, click, click . . . 30 seconds later . . . click, click, click. "OK, now: the W3 who was calling, are you still there? Try again now."

What a waste of time to be constantly turning beams during a VHF contest. Especially on FM, where a good operator in the metropolitan area can run 60 or more contacts per hour on 146.52 MHz or other popular simplex channel, if only he doesn't have to spend half his time turning a beam. But in a densely-populated area (and there are many such regions in the US) one simply cannot use an omnidirectional

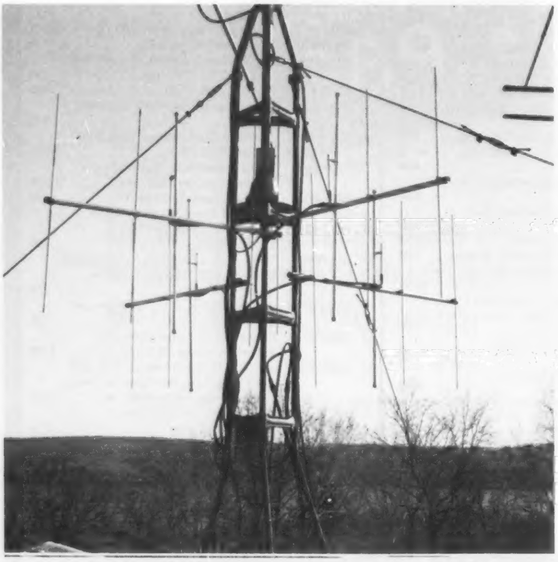

The four A147-4 beams installed on the tower.

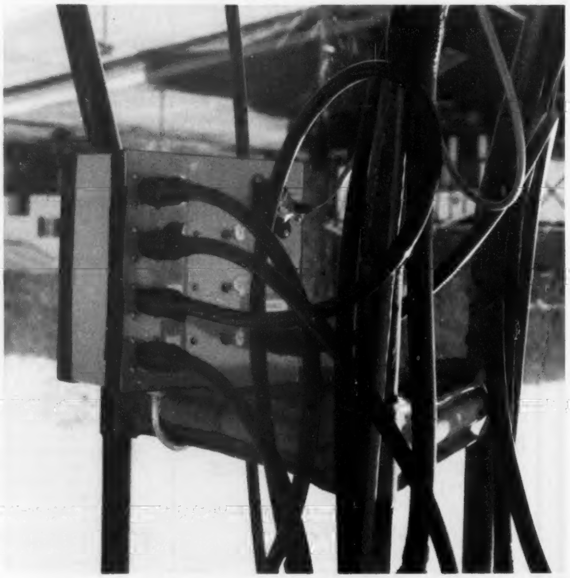

The relay box mounted on the tower. Note the well-taped PL-259s.

gain array, due to high QRM levels. What to do? Thought you'd never ask.

How about four vertical yagis, aimed at compass points or areas of known activity, side-mounted on your tower or mast, with remote switching from a single feedline? Too expensive? Not really. Cumbersome? Not as much as a rotator. Tricky? Not at all. Simple, in fact, and requiring little time or homebrewing expertise. And the benefits are attractive, not only to the VHF contester, but to any active FMer; of course, the principle described lends itself to a variety of other interesting applications, such as diversity reception experiments or phasing of HF steerable arrays.

Personally, I used four Cushcraft A147-4 short-boom 4-element 146-MHz yagis, for their ease of matching to an unknown line impedance, light weight, and low cost. If all the control box parts listed in the parts list are purchased new at list prices per the 1980 Allied Electronic catalog and added to the *73* advertisers' prices for the coax and antennas listed, the total cost of this entire project is $159.88. The only additional expense would be the feedline (hardline sells for 49¢ per foot from several *73* advertisers), the hardline connectors (brand new for $8.00 each from Phelps-Dodge, or available for much less at flea markets), and the 4-conductor control cable (the Belden cable listed sells for $12.00 per 100′ list price).

Sound like a lot of dough? I agree; that's why I bought most of the stuff (except for the antennas) at local surplus stores, which brought the cost of this project down to less than sixty bucks (minus antennas). The Cushcraft antennas specified sell for $21.00 each, but could be replaced with home-brew antennas—either yagis or quagis—for a fraction of that.

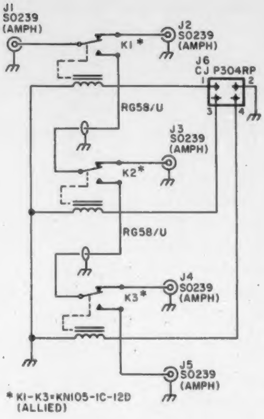

Fig. 1. Relay box.

The A147-4s were selected here because they are small and light, they are end-mount types ideal for direct tower mounting, and they develop slightly over 6 dB gain, which is a tad more than my omnidirectional Phelps-Dodge Stationmaster. The Stationmaster, a well-respected, 20-foot-long fiberglass monster, sells for about $240.00; my 4-beam system works as well, and offers the advantage of selectable directivity for QRM reduction . . . and it costs far less.

See Fig. 1 for the circuit of the relay box and Fig. 2 for the control box. Real Novice stuff. Mount K$_1$, K$_2$, and K$_3$ in a line on one flat, removable panel of the Bud AU-1029 cabinet. Mount the four output SO239 connectors in a line parallel to and about an inch away from the relays. Mount the SO239 "common" or "input" connector an inch from K$_1$, on the opposite side of the relay from the four output connectors. Mount the Cinch Jones P304RP connector in whatever space is left on the same panel. Now all components and all wiring are on just one flat aluminum panel. The rest of the utility cabinet is only a weatherproof box for the relays.

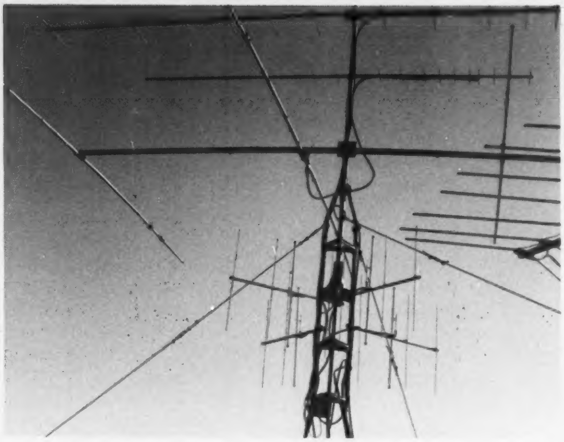

Here you can see the company the four A147-4s have: 4 el on 20, 15, and 10 meters; 19 el on 70 cm; 16 el on 2 meters. Guys are broken up with ceramic insulators.

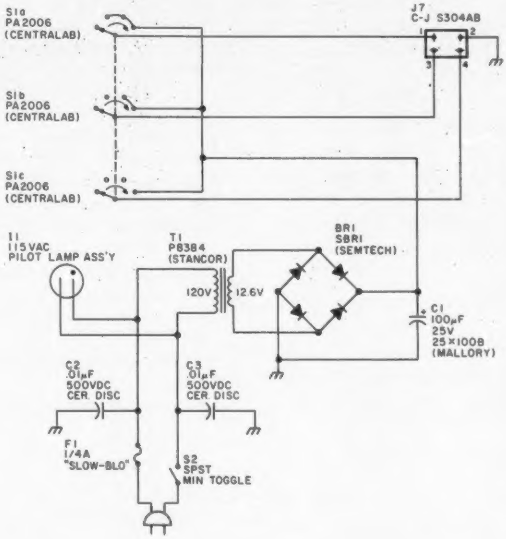

Fig. 2. Control box.

Use the flattened braid from RG-58/U for the connections from each UHF receptacle to each corresponding relay terminal, per the schematic in Fig. 1. Keep these braid jumpers as short as possible—mine are about one inch long each. If this box is intended for use at 146 MHz, this is important. Use short lengths of RG-58/U to make the K$_1$-to-K$_2$ and K$_2$-to-K$_3$ jumpers (see Fig. 1), keeping all exposed leads short. Solder the RG-58/U braid to ground lugs installed near each relay for this purpose.

The three relay coils must operate independently but they can have a common ground: thus, the wiring shown and the four-pin connectors.

After all the wiring in both the relay and control boxes is completed and double-checked, make up a short 4-conductor cable with the appropriate Cinch Jones connector at each end, and bench-test the two units together. The dc output from the bridge rectifier should measure slightly over 17 volts with the rotary switch in position 1 (no load). This will drop to less than 17 volts with the switch in position 2, and then to about 16 volts in positions 3 and 4. The 12-volt relays specified seem to handle the slight overvoltage (and resultant overcurrent) just fine—their coils do not get hot even after hours of applied voltage. The maximum power dissipated in each relay coil is about 1.8 Watts.

Parts List

4	lengths of RG-8/U foam coax (Belden 8214), cut 64″ long each
1	length of RG-58/U, about 36" long
1	suitable length of RG-331/U (½″ alumifoam "hardline") feedline
8	PL-259 UHF plugs, silver-plated (Amphenol 83-1SP)
1	Phelps-Dodge #66-654 UHF hardline connector
1	Phelps-Dodge #66-656 UHF hardline connector
5	SO239 UHF receptacles (Amphenol 83-1R)
1	Cinch Jones P304CCT, 4-conductor cable plug
1	Cinch Jones S304CCT, 4-conductor cable receptacle
1	Cinch Jones P304RP, 4-conductor recessed panel plug
1	Cinch Jones S304AB, 4-conductor flush panel receptacle
1	Bud AU-1029 utility cabinet
1	Bud SC-2133 cowl minibox
3	Allied KN105-1C-12D relays (SPDT, 12 V dc/150-Ohm coil, 10-A contact rating)
1	Stancor P8384 transformer (12.6 V c-t, 1 A)
1	Semtech SBR1 bridge rectifier (100 piv/leg, 1.5 A dc)
1	Centralab PA2006 rotary switch (3 pole, 4 position)
1	Allied #652-0503 SPST miniature toggle switch
1	Mallory 25X100B electrolytic capacitor (100 μF, 25 W V dc)

Miscellaneous: #4-40 and #6-32 hardware and solder lugs; knob for rotary switch; pilot lamp assembly, 120 V ac; zip-cord/ac line plug assembly; GE silicone bathtub caulk, waterproof; terminal strips; grommet for ac line cord; hookup wire.

Note: None of the parts listed is particularly critical, and each may be substituted for as desired. However, I strongly recommend the following:

- Use only Amphenol rf connectors. Cheap substitutes may work at low frequencies, but at 146 MHz, PL-259s are marginal performers unless they're good ones and assembled properly.
- Use Cinch Jones 4-conductor plugs and sockets. They're easier to work with and are far more durable than cheap substitutes.
- Use Belden 8214, Times FM-8, or other high-quality, foam-dielectric cable for antenna/relay-box interconnects. Avoid CB-grade coax.
- If you cannot find truly high-quality foam coax, use Belden 8237 or any brand MIL-Spec RG-8/U cable (be sure the cable says "MIL" or "MIL-C-17" right on it) and change the length from 64″ each to 53″ each.
- *Do* use hardline as transmission line if your run to the shack is more than 50 feet. The difference in loss at 146 MHz is well worth the slightly higher cost. Why use a gain antenna system if that gain is thrown away in the feedline?
- The relays listed are somewhat critical. Avoid miniature and encapsulated relays; also avoid the plug-in type. Usually, the built-in interconnect leads are far too long for rf work, especially at VHF.

Before the final installation of the relay box, drill two holes through one side of the box for a suitable U-bolt to clamp the box to your tower leg or mast. Then assemble the box on the tower or mast and caulk all corners and joints with the specified silicone caulking compound. I also wrapped the corners with Scotch 33 vinyl electrical tape.

The relay box provides a nice low vswr through about 50 MHz, but at 146 MHz it does not. Using my Bird model 43 wattmeter, a range 25C slug, a Dielectric Communications model 4050 50-Ohm, 50-Watt microwave dummy load, and a 146-MHz, 25-Watt transmitter, I measured the vswr looking into the box (with each output terminated in the 50-Ohm load) and found it to be less than 1.5:1 in position 1, but over 2:1 in the other three positions. However, there was no actual *loss* through the relays, just an impedance mismatch. What to do? Simple; tune the antennas to match the box!

Here's what to do to make it all work well at 146 MHz:

- Connect each antenna, once mounted in its permanent position, to its respective port on the box, using the 64″ RG-8/U foam cables and PL259 connectors. The 64″ is a nice length because it reaches, and also because it is one wavelength (in foam cable) at 146 MHz, thus making the box think the antenna is coupled directly to it.
- Connect the control box to the relay box with a length of 4-conductor cable. Locate the control box on your roof or tower for this temporary arrangement.
- Connect a 10-to-25-Watt two-meter exciter through 50-Ohm cable (any length) to a 50-Ohm coupler (I used a Bird 43) which is connected directly (like with a double-male UHF adapter) to the "common" port of the relay box.
- Apply power to the rig and the control box. With the control box switch in position 1, transmit and measure vswr. If it's low, great. If not, adjust the gamma match on antenna 1 to bring reflected power to a minimum.
- Perform the same gamma-match adjustments on antennas 2 through 4, switching to each in turn by using the control box. It should be possible to bring the vswr of each antenna down to reasonable proportions with the gamma match provided on each A147-4.

Now the system is adjusted. Remove the wattmeter, etc. Locate the control box in the shack, run the feedline and control cables down into the shack, and you're on the air.

Voila! A really high-class antenna system in just an afternoon's work. My whole installation (pictured) took about four hours, including wrestling with the hardline. The two boxes took just one evening to assemble. It was worth it. As you can see in the picture, I do own a Stationmaster for 146-MHz FM work, and although it is an excellent antenna, it is 20′ long, weighs over 25 lbs., catches a lot of wind (and ice), and cost over $200.00. The four beams are more versatile, occupy less space, work at least as well, and were far less expensive.

Now, when I hear a weak station calling, I can "turn the beam" in less than one second to pull him in. What a difference! ■

ege, inc.

HOLIDAY SPECIALS

Call for Quotes
Dealer Inquiries Invited

Information and Virginia Orders: (703) 643-1063
13646 Jefferson Davis Highway, Woodbridge, Virginia 22191
Store Hours: M-W-F 12 noon—8 p.m.; T-Th-S 10 a.m.—4 p.m.

ICOM

THE PERFECT GIFTS FOR CHRISTMAS

HF TRANCEIVERS
720-A— The Top of the Line
730— A Great Mobile Rig
740—The Newest Model

HANDHELDS
IC 2A/2AT— 2m
IC 3AT— 220 MHz
IC 4AT—440 MHz

MOBILE RIGS
25A for 2m
35A 220 MHz
45A 440 MHz

New for SWL Listening—
The R70

A Complete Line of Accessories
In Stock—CALL for Quotes

MORSE/RTTY SYSTEMS FOR CHRISTMAS

A Complete Ham Computer System
VIC-20 + Kantronics Interface
+ Hamsoft for the VIC-20

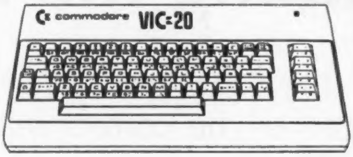

A $537 Value
for under $450
—Call for
a Quote—

SANTEC

144up 2m Synthesized Hand-held	295.00
440up MHz Synthesized Hand-held	CALL

AMPLIFIERS—TOKYO HY-POWER

HL32V 2m Amplifier, 2 in, 30 out	75.00
HL82V 2m Receive Preamp, 2 in, 80 out	149.95
HL160V 2m Receive Preamp, 2/10 in, 160 out	299.95
HL20U 440-450 MHz Amplifier, 2 in, 20 out	98.95
HL90U 430-440 MHz Amplifier, 10 in, 90 out	320.00

TUNERS—TOKYO HY-POWER

HC150 200-watt SWR/Watt Meter	83.95
HC2000 2000-watt with Meters and Switch	289.95

COMPLETE LINE OF FILTERS AND ACCESSORIES IN STOCK
—CALL FOR QUOTES—
—Shipping not included in prices—

MICROLOG

THE COMPLETE
RTTY/MORSE
SYSTEM
—CALL FOR
OUR LOW PRICE—

MONITORS —Call for Quotes—
9" and 10" Green or Amber Screens In Stock

THANKSGIVING SALE

2 DAYS ONLY—NOVEMBER 26-27

Special "Hamfest Pricing" *Limited to Stock Items*

ASTRON POWER SUPPLIES (13.8 VDC)

RS-7A 5 amps continuous, 7 amp ICS	48.60
RS-12A 9 amps continuous, 12 amps ICS	68.35
RS-20A 16 amps continuous, 20 amps ICS	87.20
RS-20M same as RS-20A + meters	105.50
RS-35A 25 amps continuous, 35 amps ICS	131.95
RS-35M same as RS-35A + meters	151.95
VS-35M 25 amp continuous, adjust volt & amp	171.00
VS-20M 16 amp continuous, adjust volt & amp	124.00

MFJ PRODUCTS (Call for other MFJ items)

989 New 3-kW Antenna Tuner	285.95
962 1.5-kW Tuner switch/meter	185.95
949B 300-watt Deluxe Tuner	119.95
941C 300-watt Tuner switch/meter	78.95
940 300-watt Tuner switch/meter	67.95
102 24-hour Clock	29.95
202 Noise Bridge	48.95
401 Econo Keyer	41.95
406 Deluxe Keyer	60.97
408 Deluxe Keyer with Meter	69.95
412 Pacemaker Keyer with Bencher	87.95
496 Keyboard II	285.95
752B Dual Tunable SSB/CW Filter	78.95

BENCHER PADDLES Black/Chrome	34.95/42.95
AEA KEYERS, READERS, ANTENNAS	CALL

MM-2, CK-2, KT-2, MBA/RO, MBA/RC, Isopoles
—CALL FOR OUR LOW PRICES—

BENJAMIN MICHAEL CLOCKS

173B 24-hour Crystal Clock	29.95
173C 24-hour Crystal Clock	20.95
173DM Dual 12/24-hour Clock	56.95
973A Analog 24-hour 14-inch Clock	36.95

DAIWA/MCM/J.W. MILLER

CN-520 SWR/Watt Meter	59.95
CN-540 SWR/Watt Meter	69.95
CN-620B 2-kW HF Watt Meter	106.95
CN-630 VHF-UHF Watt Meter	126.00
CN-720B 2-kW HF Watt Meter	149.95
CNW-418 Antenna Tuner	169.95
CNW-518 Antenna Tuner	279.95
CNA-2002 Auto 25-kW Antenna Tuner	399.95

SUPER SPECIALS

ROTORS

ALLIANCE HD73	89.95
CDE Ham IV	195.95
AZDEN PCS 300 Hand-held	279.95
NEW! PCS 4000 2m XCVR	283.95
KDK FM 2030 25-watt FM XCVR	278.95

BIG DISCOUNTS

KENWOOD, ICOM, YAESU
AMERITRON HF AMPLIFIERS
— Call for quotes —

TEN-TEC SPECIALS

515 Argonaut HF XCVR	399.95
525 Argosy HF XCVR	499.95
546 Omni-C HF XCVR	1069.00

Complete Line of Filters and Accessories in Stock
— CALL FOR QUOTE —

MIRAGE VHF/UHF AMPLIFIERS/METERS

B23 2m Amplifier, 2 in, 30 out	CALL
B108 2m Amplifier, 10 in, 80 out	CALL
B1016 2m Amplifier, 10 in, 160 out	CALL

VOCOM ANTENNAS/2m AMPLIFIERS

5/8 wave 2m Hand-held Antenna	14.95
2 watts in, 25 watts out 2m Amplifier	66.95
200 mW in, 25 watts out 2m Amplifier	78.95
2 watts in, 50 watts out 2m Amplifier	99.95
2 watts in, 100 watts out 2m Amplifier	157.95
Power Pocket for ICOM 2A/2AT	179.95

CABLE BY SAXTON

RG213 Mil Spec	26¢/ft
RG8/U Foam 95% Shield	24¢/ft
8-wire Rotor 2 #18, 6 #22	16¢/ft
Mini-8	12¢/ft

TELEX HEADSETS/HEADPHONES

C1210/C1320 Headphones	28.95/40.95
PRO COM 200 Headset/Dual Imp Mic	78.95
PRO COM 300 lt/wt Headset/Dual Imp Mic	71.95

ANTENNAS

AVANTI AP 151.3G 2m On-glass Antenna	28.95
LARSEN LM-150 5/8 Mag Mount	36.00
MOSLEY HF ANTENNAS	CALL
MINIQUAD HQ-1	127.95
SUPER STICK II 5/8 2m Antenna	15.95
BUTTERNUT HF6V 10-80m Vertical	109.95

HY-GAIN ANTENNAS	CALL FOR QUOTES
TH3MK3S 10-15-20m Tribander	215.95
TH5MK2S New Model Tribander	307.00
TH7DX 10-15-20m Tribander	375.95
V2S 2m Vertical	37.50
14AVQ 10-40m Vertical	51.95
18AVQ 10-80m vertical	99.50
HY-GAIN ANTENNA/TOWER PACKAGES	CALL

CUSHCRAFT (Other antennas in stock)

A4 New Triband Beam 10-15-20m	224.95
A3 New Triband Beam 10-15-20m	172.95
AV3 New 10-15-20m Vertical	44.50
ARX-2B New Ringo Ranger 2m	34.50
A32-19 2m "Boomer" DX Beam	81.95
220B 220 MHz "Boomer"	74.95
214B "Jr. Boomer" 144-146 MHz, SSB	68.20
214FB "Jr. Boomer" 144.5-148 MHz, FM	68.20
A147-11 11-element 2m	37.95

KLM ANTENNAS (Other antennas in stock)

KT34A 4-element Triband Beam	309.95
KT34XA 6-element Triband Beam	459.95
144-148-13LB 2m 13-element with Balun	77.95
144-148-16C 2m 16-element for Oscar	93.55
420-450-14 420-450 MHz 14-element Beam	37.54
420-450-18C 420-450 MHz 18-element for Oscar	58.70
432-16LB 16-element 430-434 MHz Beam/Balun	60.70

HUSTLER

5-BTV 10-80m Vertical	99.95
4-BTV 10-40m Vertical	79.95
3-TBA New 10-15-20m Beam	188.95

HF MOBILE RESONATORS	Standard	Super
10 and 15 meter	8.25	14.00
20 meters	11.25	16.25
40 meters	13.00	19.00
75 meters	14.00	29.75

ORDER TOLL FREE 1-800-336-4799

(Orders Only, Please)

Order Hours: M-F 11 a.m. to 7 p.m.; Saturday 10 a.m. to 4 p.m.
Bonus: 2% Discount for Prepaid Mail Orders (Cashiers Check or Money Order)

✓453

Send stamp for a flyer. Terms: Prices do not include shipping. VISA and Master Charge accepted. 2% discount for prepaid orders (cashier's check or money order). COD fee $2.00 per order. Prices subject to change without notice or obligation. No personal checks accepted. Returns subject to 10% restocking fee.

Calvin McCarthy VE3LMP
98 Windsor Street
Thunder Bay, Ontario
Canada P7B 1T7

Taming the 2-Meter Linear

It lives in the forests of spurious oscillations and answers to the call of the correct bias. Catch one for yourself.

Class C amplifiers for the two-meter band are a "dime a dozen," with commercial models, kits, and schematics available from a good number of suppliers. Linear amplifiers are another story. Their design and construction is all black magic, and manufacturers are the only wizards in on the mystery. With a little sleuthing, I found that Motorola would sponsor my initiation into this exclusive cult, allowing me to build an amplifier to boost the output of my 2-meter OSCAR station from 2.5 Watts to 20 Watts.

In order to linearize a solid-state rf power amplifier, you must solve two problems. First, you must bias the transistor into the linear region while supplying a substantial amount of varying base current. Secondly, you must tame any spurious oscillations generated by the high-gain transistor used.

First, the biasing problem will be faced. A small-signal transistor amplifier is usually biased with a voltage-dividing network such as that shown in Fig. 1(a). The current flowing through the network resistors is set to be about ten times the current needed by the base. With our amplifier needing from 10 mA to 100 mA of base current at any time, this circuit would not be practical. As well, the bias voltage must be held at a constant stiff value for all values of base current, which is not possible with a resistive voltage-divider network.

An alternate solution to this biasing problem, which satisfies the need for a constant bias voltage while supplying varying currents, is the solid-state voltage regulator. Either the shunt regulator of Fig. 1(b), where the total bias supply current is greater than the maximum base current and the surplus current is shunted to ground by the reference diode, or the series pass regulator of Fig. 1(c) can be used. The series regulator reduces the current which must flow through the reference diode by i_{base}/hfe, and the total bias current used becomes virtually the base current needed at each instant. The bias voltage is set by the forward voltage drop of the diode reference which is approximately 0.6 volts. The series regulator bias is set by two forward-biased diodes in series, the second diode voltage drop compensating for the base-emitter junction drop of the series pass transistor so that the bias supply voltage output will equal only one PN junction voltage drop.

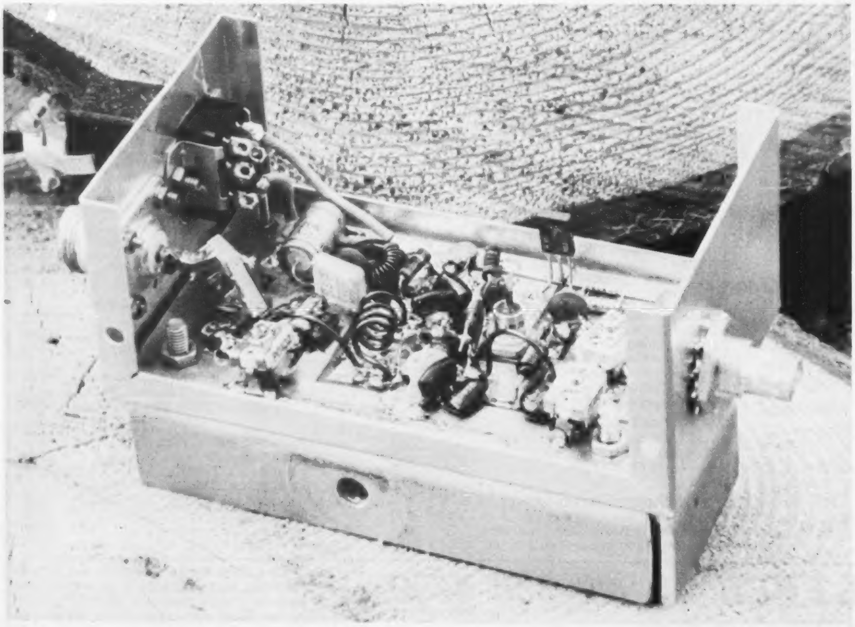
MRF 2-meter linear amplifier.

Now for a very important point! As a transistor warms, its base will draw more current, which increases collector current, which warms the transistor more, and this will continue until the component self-destructs. To offset this, the base bias voltage must be reduced as the transistor warms. By mounting D_{ref} as

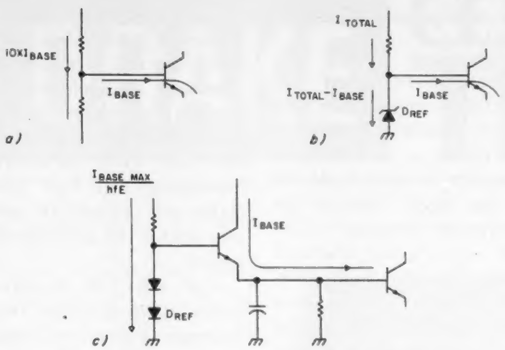

Fig. 1. Bias possibilities. (a) Voltage divider arrangement. (b) Zener diode stabilized. (c) Pass transistor circuit.

close to the rf transistor as possible to provide thermal contact, the diode junction voltage will *decrease* as the diode warms, neutralizing the base-emitter junction change of the rf transistor and thus keeping the base current under control. Remember! Attach the reference diode so that it will be warmed by the rf power transistor. Either physically attach it to the transistor body or to the heat sink as close to the transistor as possible. *Do not* expect the reference diode to thermally track if the thermal path is broken by air.

Low-frequency oscillations also are a problem. My amplifier first oscillated in the HF band because at these frequencies the transistor has very high gain. Bypassing the collector current feed did not tame these troublsome responses, so I took the brute-force method and fed back the collector signals to the base through a feedback network. The rf choke is a virtual short for the oscillations but an open circuit for the desired VHF response. The capacitor is a virtual short for the undesired oscillation but an open circuit for the collector supply. This network was placed between the collector and base with very short leads and the unwanted oscillations were completely suppressed.

The amplifier which I built (Fig. 2) is a modified version of the class C amplifier described by W4MNW in the November, 1977, issue of *73 Magazine*. I lifted RFC1 from ground, added bypass capacitors to the lifted end so the rf input would continue to see a ground, then connected the base bias supply to RFC1. The low-frequency feedback network was added to stabilize the amplifier and the linear amplifier was a reality. It would appear to be quite possible to linearize many of the class C amplifiers now in FM and CW use in the same way.

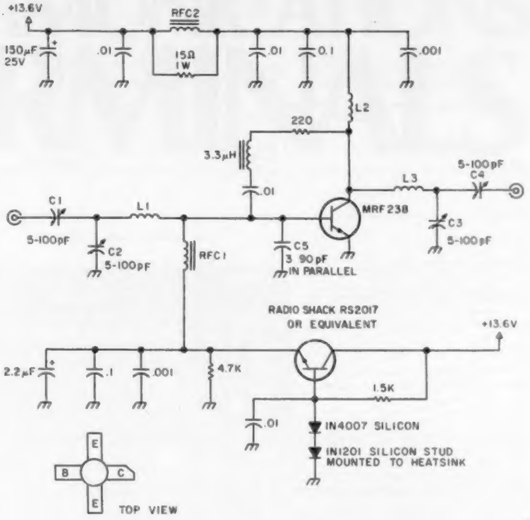

Fig. 2. Amplifier schematic.

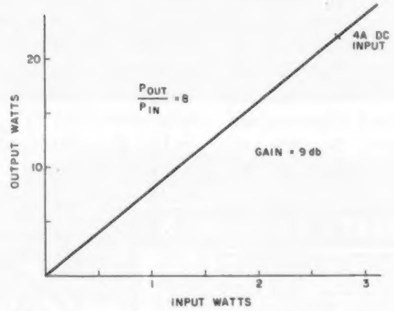

Fig. 3. Amplifier linearity.

The testing of this amplifier was done with a regulated and current-limited power supply. This saved the transistor from destruction before I had tamed the low-frequency oscillations. The transistor is rated for a collector current of four Amperes, but I set the supply to limit current to a maximum of one Ampere until I was satisfied that the amplifier would not hurt itself.

Low-frequency oscillations manifest themselves by a sudden jump in collector current and corresponding drop in supply voltage. The first time this happened I thought I had destroyed the transistor, but the power supply protection had saved it. I was able to continue my study of the problem and a wideband oscilloscope revealed a pulse-type response on the collector output. This was suppressed by the feedback network shown in the schematic.

I made an interesting observation about amplifier efficiency while tuning the amplifier. There is a particular collector current needed to give a particular output power—not so collector voltage. Thus 0.5 Watts input will become 4 Watts output at 2 Amperes collector current whether the collector voltage is 5 or 12 volts. Under the same conditions, the dc input power changes from 10 Watts to 24 Watts. For maximum efficiency, it seems that the amplifier should be operated at the maximum linear power output possible for the applied collector voltage, or if it is desired to operate the amplifier at reduced power, the collector voltage should be re-

Coil Construction Details

RFC1	10 turns #22 on 270-Ohm, ½-Watt resistor
RFC2	13 turns #22 on T50-6 toroidal core
L1	½ turn #16, approx. 1½"
L2	4 turns #16, 1/4" i.d.
L3	Curved wire, #16, 1-1/4" long

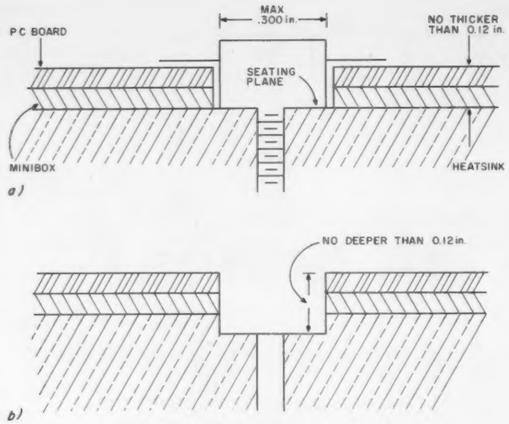

Fig. 4. MRF238 mounting details.

duced. Linear operation at 4-Ampere dc input is shown in Fig. 3.

The amplifier was built in a 5¼″ × 3″ × 2½″ minibox on double-sided epoxy glass PC board. The circuit lands were etched, but islands of PC board epoxied to the ground plane would serve as well. Be very certain that the capacitors that make up C5 are soldered with *short* leads as close to the transistor body as possible. Connect the ground plane on both sides of the board with eyelets or wire running through the board and solder on each side. A heat sink is necessary. My heat sink has 35 square inches of radiating area and it seems to be just satisfactory. A larger one is recommended.

The mounting of the MRF238 is very critical (see Fig. 4). Careless technique will result in a destroyed transistor if stress is placed on the leads. Mount the transistor seating plane with very good thermal contact to the heat sink. The thickness of the case metal and the PC board must not be greater than .120 inch. If it is, the transistor leads will be forced up, putting a strain on the transistor cap. On heating, the bonding material will fail and you will be out buying a new expensive transistor. If the PC board and case thickness together is much less than .120 inch, you may want to mill out the heat sink as in Fig. 4(b) so the transistor leads will not be bent down when soldered to the PC board. *Do not* solder the leads before tightening the stud mounting nut. *Do not* hold the transistor leads while tightening the nut. *Do* hold the transistor securely by the wrench flat on the end of the stud while tightening the nut. Only after the mounting nut has been tightened carefully may you solder the leads to the board.

The MRF238 Motorola transistor is available from Ramsey Electronics and Semiconductor Surplus, both *73* advertisers.■

References

1. Charles F. Clark AF8Z, "Solid-State Linear Amplifiers," *Ham Radio*, January, 1980, p. 48.
2. D.J. Lynch W4MNW, "Build a 2-Meter Power Amp," *73 Magazine*, November, 1977, p. 96.
3. Motorola Semiconductor Products, Inc., Box 20912, Phoenix AZ 85036:
AN546—Solid-state linear amplifier design.
AN555—Mounting stripline-opposed emitter (SOE) transistors.
AN791—A simplified approach to VHF power amplifier design.

QUALITY SPECIALS

SOPHISTICATED I.C.'S

DATA SHEETS AND APPROPRIATE APPLICATION NOTES ARE PROVIDED FREE WITH ALL INTEGRATED CIRCUITS LISTED BELOW

PART # & MANUF.	DESCRIPTION	PRICE(ea.)
RDD104 (LSI COMP. SYS.)	CMOS DIVIDER I.C. HAS TRUTH-TABLE SELECTABLE INPUT TO YIELD DIVIDE BY 10, 100, 1000, or 10000 OUTPUTS.	$ 3.50
LS7031 (LSI COMP. SYS.)	D.C. TO 5MHZ SIX DECADE MOS UP COUNTER WITH 8 DECADE LATCH AND MULTIPLEXED BCD OUTPUTS AND DIGIT STROBES. ACCESS TO LSD LATCHES ALLOWS ATTACHMENT OF PRESCALERS FOR COUNTING TO 500MHZ	$13.75
LS7220 (LSI COMP. SYS.)	14 PIN DIP AUTOMOTIVE/MARINE ANTI—THEFT DIGITAL LOCK CIRCUIT HAS 5,040 4-DIGIT COMBINATIONS WITH 25 MICROAMP STANDBY. "SAVE" MODE FOR VALET PARKING	$ 3.50
ZN450E (FERRANTI)	3½ DIGIT, DIGITAL MULTIMETER I.C., WITH LCD DRIVE. ON CHIP CLOCK AND REFERENCE. A COMPLETE DMM CIRCUIT CAN BE MADE WITH 8 PASSIVE EXTERNAL COMPONENTS.	$14.25
FEO201D (AND CORP.)	3½ DIGIT LCD DISPLAY	$12.00
TSC7126 (TELEDYNE)	3½ DIGIT A/D CONVERTER. LCD DRIVER DESIGNED FOR LOW POWER APPLICATIONS (ImW) WITH A 9V BATTERY (EQUIVALENT TO INTERSIL 7126)	$16.95

CAPACITORS

DIPPED TANTALUMS

	1-99(ea.)	100+(ea.)
1 mfd/35V	$.30	$.20
33mfd/35V	.30	.20
1 mfd/35V	.30	.20
1.5 mfd/20V	.30	.20
2.2 mfd/15V	.30	.20
6.8 mfd/25V	.60	.35
68 mfd/10V	.60	.40

COMPUTER GRADE

mfd	WVDC	Price (each)
2,250	100	$3.95
4,000	80	3.95
12,000	50	5.00
21,000	40	3.95
27,000	30	4.95
53,000	25	5.95
160,000	20	8.95

AXIAL ELECTROLYTICS

	1-99(ea.)	100+(ea.)
1 mfd/40V	$.15	$.12
1.5mfd/25V	.15	.12
4.7mfd/15V	.15	.12
10 mfd/63V	.17	.14
47 mfd/25V	.17	.14
150 mfd/10V	.17	.14
220 mfd/10V	.27	.20
470 mfd/25V	.50	.40
1000 mfd/25V	.70	.60
2200 mfd/10V	.70	.60
2200 mfd/40V	.85	.65

RADIAL ELECTROLYTICS

	1-99(ea.)	100+(ea.)
2.2mfd/25V	$.15	$.12
4.7mfd/35V	.15	.12
33 mfd/25V	.15	.12
47 mfd/16V	.15	.12
220 mfd/25V	.15	.12
330 mfd/35V	.20	.15
470 mfd/25V	.35	.27
580 mfd/20V	.35	.27
1000 mfd/25V	.70	.50
2200 mfd/10V	.70	.60
3300 mfd/10V	.70	.60

MISCELLANEOUS

DESCRIPTION	PRICE (ea.)
20 PIN S.T. LOW PROFILE I.C. SOCKETS (TIN PLATED)	$ .40
40 PIN S.T. LOW PROFILE I.C. SOCKETS (TIN PLATED)	$ .85
1K or 25K SLIDE POTENTIOMETERS	$ .75
250 OHM HORIZONTAL TRIM POT	$ .30
1 MEG OHM HORIZONTAL TRIM POT	$ .30
220 KILOOHM HORIZONTAL TRIM POT	$ .30
POWER-LINE FILTER (SURPLUS) 5 AMP, 230VAC, 50/60Hz	$5.00
POWER-LINE FILTER (SURPLUS) 10 AMP, 115/250V, 50-400Hz	$8.50

GOLDSMITH
SCIENTIFIC
CORPORATION
P.O. BOX 318, COMMACK, NY 11725
PHONE ORDERS WELCOME—(516) 979-7944
MINIMUM ORDER $10.00—U.S. FUNDS ONLY
NEW YORK STATE RESIDENTS ADD SALES TAX
POSTAGE—ADD 5% PLUS $1.50 INSURANCE, C.O.D. $2.00 EXTRA
AVAILABILITY OF CERTAIN ITEMS MAY BE LIMITED.

✓195

POWER
VIDEO
AUDIO
EXTERNAL POWER
MODEL 7600A SATELLITE RECEIVER

Gillaspie

The Model 7600A

The Model 7600A Satellite Receiver is the new look from Gillaspie. State of the art technology. Distinctively styled. The successful integration of the most sought after high performance characteristics and ease of operation capabilities. Attractively packaged. Affordably priced.
A classic in its own time. From Gillaspie, of course.

- FULL FREQUENCY tunable audio
- Reception 3700 to 4200 MHz
- Built-in video modulator
- Simplified channel tuning
- Improved video sensitivity
- All wood cabinet

The Model 7600A Satellite Receiver System Package comes with its antenna mounted Image Reject Mixer (Down Converter), built-in video modulator, 100′ of RG59-U cable and 100′ of Belden DC cable with connectors installed.

Gillaspie & Associates
365 San Aleso Avenue, Sunnyvale, CA 94086 (408) 730-2500
Get The Last Word *First!*

✓37

DRAKE COMMUNICATIONS TERMINALS

DRAKE Θ-9000E

Microprocessor Controlled

DRAKE Theta 9000E

The ultimate in communications versatility, the **Drake Theta 9000E** provides complete transceive capability of CW (Morse Code), RTTY (Baudot), and ASCII. A full computer RS232 interface, cassette tape storage port, selective calling feature with answer-back, light pen graphics, printer interface and word processing software are all standard.

Seven large 256 character memories are backed up with battery power so there is no need to reload information with each use. Memories may also be partitioned providing up to 29 separate storage locations. A type-ahead buffer of 3120 characters makes it easy to compose your response while still receiving. Operator controlled scrolling permits review of up to 10,720 previously received characters. Line length is selectable at 40 or 80 characters, your choice, and all mode and speed indicators are displayed on the screen for instant status recognition. The 9000E has 3 tone groups and 3 shifts which are all keyboard selected.

You won't buy any other communications terminal once you have studied all the advanced operating convenience built into the **Drake Theta 9000E**. It's complete.

Θ-550
COMMUNICATIONS TERMINAL

DRAKE Theta 550

The **Drake Theta 550** is a compact receive-only communications terminal and is designed to demodulate and display the three most popular over-the-air modes of data communications: CW (Morse Code), RTTY (Baudot), and ASCII. Any standard TV monitor can be used.

A full-featured microprocessor controlled unit, the Drake Theta 550 has selective calling, battery backed-up memory, audio monitor, and informative L.E.D. tuning indicators. There is also interfacing to permit the addition of a dot matrix printer for "hard" copy and a keyer paddle input to permit CW transmission with full iambic operation.

CW automatically tracks over a speed range of 5 to 50 words per minute and RTTY modes offer nine selectable standard speeds of transmission. 12 volts DC is required.

This unit is ideal for shortwave listeners and hams who have been missing the increasing volume of data communications over the air.

LA7 Line Amplifier

Line output, input levels as low as 15 mV rms (47 kilohm) will result in an output of 1 mW nominal into a 600 ohm balanced line. Output level adjustable by internal preset level control. Interfaces low level audio to RTTY terminal unit or phone line that requires a 600 ohm balanced/unbalanced input. One 36″ phono to phono cable supplied.

R. L. DRAKE COMPANY DRAKE®

540 Richard St., Miamisburg, Ohio 45342. USA
Phone: (513) 866-2421 • Telex: 288-017

Larry Franks N7BGZ
24001 SE 103rd Street
Issaquah WA 98027

The Frugal Floppy Bazooka

This 2-meter antenna coils up into a small package, but it shoots a straight signal.

Another 2-meter antenna for your handie-talkie? You bet! When you combine low cost, portability, and reasonable gain as this antenna does, it is well worth covering the subject again. The design of this gain vertical was inspired by the excellent article by W1IS in the May, 1981, issue of *73 Magazine*. One of the current-distribution charts reminded me of the "bazooka" coax-to-dipole decoupling scheme which uses a grounded sleeve in place of radials, and the "floppy bazooka" was born.

Construction

My prototype antenna was assembled from RG-58A/U (with the stranded center conductor), which is (a) very flexible and (b) what I had on hand. I started with about 20 feet of the cable and terminated one end with a BNC male to match the connector on my HT. The next step is to remove approximately 34 inches of the outer cover and braid from the loose end of the coax, leaving about ¼ inch of braid exposed and the center conductor intact.

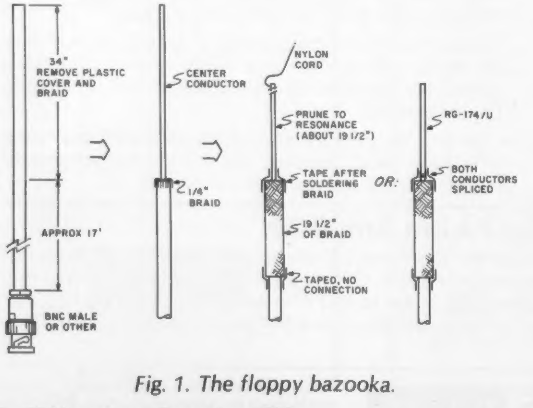

Fig. 1. The floppy bazooka.

Why 34 inches if a quarter wave at 146 MHz is about 19 inches? Because I had to compress the braid slightly, increasing its diameter and decreasing its length, to slide it over the feedline. After doing so, I *carefully* soldered the ¼ inch of exposed braid on the feedline to the braid sleeve, taking care to not melt the center conductor dielectric. I provided as much coverage as possible with the braid splice.

I covered the splice with heat-shrink tubing, although electrician's tape will do fine. Pull the braid down snug on the feedline and *now* measure the 19½ inches you expected, from the splice just covered to the lower end of the sleeve. I found this dimension to be very noncritical, but the shortening with compression varied from sample to sample of coax, which is why I started with 34 inches! After cutting the sleeve to length, I secured the end to the feedline in the same way I covered the splice.

Testing

The *first* test I made was with an ohmmeter: checking at the BNC end for a potential short. Don't trust the ability to receive a full-quieting signal as proof of proper wiring—I live less than a mile from a local repeater, which breaks the squelch on my HT fine without any antenna plugged in at all!

After avoiding the "smoke test," it was time to prune that 34-inch center conductor to resonance. My first cut was to 20½ inches, and out came the swr bridge. One quarter of an inch at a time, I marched up the band—on low power and avoiding repeater inputs, of course. I found that the antenna would give better than a 2:1 swr over about a 1.5-MHz range, with 19¼ inches hitting 146 MHz on the nose.

I wasn't thrilled with that bandwidth, so I opted for a simple modification: a "thicker" radiator. I started with a 20-inch piece of RG-174/U, with the center conductor and braid shorted together where they are spliced to the center conductor of the RG-58A/U and shrink tubing again covering the evidence. After the same pruning procedure, this came much closer to my expectations, covering the entire 144–148-MHz band with a worst-case swr of 1.8:1.

Use

I attached some 1/8-inch nylon cord to the top of the center conductor with two small wire ties, and the installation problem of a non-self-supporting antenna was solved. The antenna can now be suspended almost anywhere. Bear in mind that it has a very low angle of radiation and must be kept quite vertical to take advantage of its gain characteristics. I chose the 17-foot length of feedline as a reasonable trade-off between losses and the ability to put the antenna in better (higher) places. The antenna and nylon "mount" bundle neatly into a tiny package hardly larger than my HT, making it an ideal traveler's antenna.

My comparison of the floppy bazooka's performance to other antennas was not rigorous, but very satisfying. It significantly outperformed my ¼-wave ground plane in fixed-station use and incredibly outperformed the rubber ducky.

The floppy bazooka is cheap, easy to build, and works very well. It also lends itself well to modification and experimentation. Try it! ■

15 Meter Mobile CW & USB

START YOUR DAY ON A GOOD KEY!!!
WORK OTHER HAMS LIKE: XE2BGM, ZL1PQ, KL7JFV, EA7EU, NN3SI, DJ8RR, DL0BBC, US6AK, JA3JMP, PY2-CPQ, FO8GW, KM6FF, VK2BD OE8MOK OA4ARB G3BRW VE7DYX CE1BLL W1AW

High 10W (PEP) low 2W (PEP): VFO tuning: noise blanker: fine-tuned SB, KHz ± CW off-set; digital frequency counter; 13.8V dc @ 3A, negative ground; L 9.5" × W 9" × H 2.5"; weight (2.3 kg) 5.7 lbs.; mobile mounting bracket.

N.C.G. CO.
NCG
JUST SLIGHTLY AHEAD

SOON — NEW
10-160 METERS

DLR. INFO. & ORDER, CALL
1275 N. GROVE ST.
ANAHEIM, CALIF. 92806 (714) 630-4541

NOTE: Price, specifications subject to change without notice and obligation.

318

COMMUNICATIONS DIVISION

(We Speak Your Language.)

Backed by over 54 years of experience, Harvey continues to offer the broadest selection and finest service available for the amateur radio community. This experience has taught us that the ham needs special treatment and that is why Harvey has established a special division dedicated to the needs of the U.S. and foreign ham alike.

One thing is for certain. A ham will never get the run around from Harvey. If we don't have something in stock, we say so and will order it for you—or—tell you where to get it. However, we are sincerely dedicated to the ham community and, as a result, our expansive inventory means that, more than likely, we will have what you are looking for *in stock*.

FT-ONE
MIC GAIN
RF POWER
ICOM HF ALL BAND TRANSCEIVER

ICOM IC-720A

Yaesu FT-One

AEA
Alliance
Antenna Specialists
ARRL
Astatic
Bearcat
Bencher
B&W
C.P.E.S.
Centurion
C.D.E.
Cushcraft
Daiwa
Digimax
R.L. Drake
Gotham Antennas
Grundig
H.M. Electronics
Icom
Kantronics
K.D.K.
Larsen
McKay Dymek
M.F.J.
Midland
J.W. Miller
Mirage
Wm. M. Nye
Regency
Santec
System One
Telex Hygain
Tempo
The Tuned Antenna
Trilectric
VoCom
W.S. Engineering
Yaesu

CALL TOLL FREE:
1-800-223-2642
Ask for Dou "Joe" Chin—KB2MU

HARVEY
129
25 W. 45th St., N.Y., N.Y. 10036 (212) 921-5920

DO ANTENNAS WORRY YOU?

(NOT TO SCALE)

We feel a novice student has enough to learn without immediately diving into antenna construction. Our new novice antenna is fully assembled and covers **all** the novice bands and beyond. One of its better features is the price. *(At last glance the competition wanted $123.50 for their fully assembled antenna with coax fitting that covers the four novice/tech bands.)*

MODEL ND-4
only $69.95

FEATURES:
- 118 feet long
- Heavy Copperweld® construction
- 100 feet of 450# test Nylon rope included
- Waterproof center connector with female coax fitting
- No antenna tuner needed
- 2 KW PEP input rated (750 W on 21 mHz)
- Retunable when you upgrade
- Installs as low as 25 feet

Average Bandwidths for 2:1 VSWR:
- 80 meters = 200 KHz plus
- 40 meters = 125 KHz
- 15 meters = 600 KHz plus
- 10 meters = 700 KHz plus

ALL PRICES ARE UPS PAID CONTINENTAL USA

Available at your favorite dealer or order direct from:

Van Gorden Engineering
P.O. Box 21305 • South Euclid, Ohio 44121
Dealer Inquiries Invited

TU-300

Flesher Corporation
TU-300

NEW **The TU-170A** with improved circuitry

the TU-300 is the only 300 baud terminal unit offered in kit or wired

- 300 baud communications rate
- crystal controlled AFSK with downshift CW ID
- autostart motor control with AC outlet
- remote operation

- high quality commercial construction
- modular design with steel case for RF shielding
- indicator type push-button switches
- separate send and receive "reverse shift" controls

- bar graph tuning and LED function indicators
- mark-hold and selective fading compensation
- 3 shifts (170Hz standard - other shifts extra)
- oscilloscope tuning outputs

- easy to tune multipole active filters
- TTL and RS 232-C compatible I/O's
- optional 20 and 60ma optically isolated loop supply
- simple kit construction - no instruments needed for alignment with AFSK installed

Send for our 1983 Catalog

Flesher Corporation
507 Jackson • P.O. Box 976 • Topeka, Kansas 66601
913-234-0198 • Telex 437125
✓23

new *In Repeaters*

Some people want the finest, Others want the lowest price.... Now you can have Both!

Introducing the *New Low Cost* Spectrum SCR 77 Repeaters—*2M, 220 & 440 MHz!*

SPECTRUM COMMUNICATIONS
SCR 77 FM REPEATER
13.8VDC
COR
TRANSMIT
VOLUME
SQUELCH
MODE
TRANSMIT KEY
REPEAT
COR DISABLE
AC LINE
AC POWER
LOCAL MIC

15 or 30 Wt. Xmtrs.

Includes:
- **0.3 µV Rcvr. 8 Pole IF Filter**
- **Crystals—high stability .0005%**
- **Local Mic**
- **Your Call programmed into IDer**
- **Provision for Auto-Switchover to Btry. Pwr.**
- **Built-in 115/230V AC Supply; basic Panel Controls, Spkr., LED Indicators**

If you're looking for a new Repeater, but you really don't need (or can't afford) all the features and options on our world famous, 'Super Deluxe' SCR1000/4000, then our new economy line of SCR77 Repeaters is ideal for you!

These new Repeaters maintain the quality of design, components and construction which made Spectrum gear famous. However, all of the "bells & whistles" which you may not need or want have been eliminated—*at a large cost savings to you!* The SCR77 is a real "workhorse" basic machine designed for those who want excellent, super-reliable performance year after year—*but no frills!* ('PL', 12 Pole IF Filter, Front End Preselector, and a 30Wt. Transmitter are the only "built-in" options available; but Autopatch, Remote Control, and other equipment can be connected via the rear panel jack.)

A complete line of duplexers, antennas, cabinets, cable, etc., is also available.

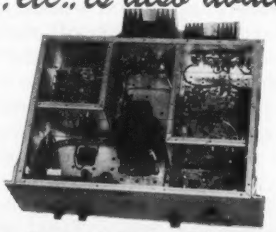

Of course, if you do want a full featured/super deluxe repeater, with higher power and a full list of available 'built-in' options, then you want our SCR1000 or 4000 "Dream Machine". These units will continue to be available for those who want 'The Ultimate in Repeaters'.

SCR77 Pricing (15Wt.): 2M or 220MHz, $995.00 Amateur Net. 440MHz, $1150.00. For no 'plug-in' ID board (Export), deduct $40.00. *Call or write today for a data sheet, or to place your order!* Sold Factory Direct or through Export Sales Reps only.

Now located in our new, larger plant! Thanks for your 8 + years of support!

SC ✓68 **SPECTRUM COMMUNICATIONS**

1055 W. Germantown Pk, S12 • Norristown, PA 19401 • (215) 631-1710 • Telex: 846-211

George L. Thurston III W4MLE
2116 Gibbs Drive
Tallahassee FL 32303

Taking It Higher

Raising a repeater's antenna is the way to wider coverage, right? Wrong.

When it comes to repeaters, higher is better! Right?

Not necessarily. It depends on what you want to accomplish.

Sooner or later, every repeater organization in the country gets the urge to move the repeater antenna up to twice as high as it already is, to improve coverage. Most of the time, it does improve. Every once in a while, though, some unexpected glitches result.

The Tallahassee Amateur Radio Society went through the process of moving from a downtown site with an antenna elevation of about 350 feet to a new commercial tower near the edge of town with an elevation of 800 feet above mean sea level (MSL). Sure enough, coverage was considerably extended. But sure enough, there were several surprising developments. What happened, and why, makes an interesting case study.

We knew from experience that the downtown site gave us an effective coverage range of about thirty miles in all directions over fairly mild terrain. South of the city, the coastal plain stretches away to the Gulf of Mexico, flat as a pizza, with an elevation of about 50 feet above MSL. But right in the middle of the city the terrain rises abruptly at the limestone scarp which, a few million years ago, was the coastline when sea levels were higher than now. These hills rise to elevations of 150 to 230 feet, with an average elevation of perhaps 175 to 200 feet above MSL on any bearing in the northern semicircle centered on Tallahassee.

What would happen when we moved from 350 feet to 800 feet? Would we be able to work 75 miles? 100 miles, as some members predicted?

The visual line-of-sight distance from an antenna to the horizon is expressed by the formula $R=\sqrt{2H}$, where R is the range (or radius) in miles and H is the height in feet of the antenna above average terrain. It is the basis, in commercial antenna engineering, for computer calculations of the antenna's performance, cranking in corrections for such things as absorption of radio energy by foliage and buildings, shadowing by hills, and the fact that radio signals can nearly always be heard beyond the visual horizon.

Without benefit of a computer, I modified the formula based on empirical observations of repeater performance in actual operation. The formula is intended to be an approximation, not a precise prediction. I cranked in a number of assumptions about ham radio which do not apply to commercial and public safety services.

For example, most amateurs are willing to settle for less than 100% reliability over a given path. And most of us are willing to accept a noisy signal if it is still readable. The modified formula turned out to be: $R=\sqrt{2.5H}$.

Applied to our downtown antenna site, it predicted a contour which agreed well with our experience with the repeater. Here it must be said that a number of other assumptions also must be made. For example, we assume that most mobiles will use about 15 Watts output to a quarter-wave whip, that they will be in motion, that they will have little or no ignition interference, that they have receivers with a sensitivity of half a microvolt or less for 20 dB of quieting, and that the ambient acoustical noise in the mobile will be fairly high.

The critical parameter was defined as the point at which "practical communication" through the repeater becomes possible between a mobile at the fringe of the coverage and a mobile or fixed station located within the full-quieting contour of the repeater. In effect, this boils down to: "Can I use the repeater to get useful information on road directions or weather conditions?"

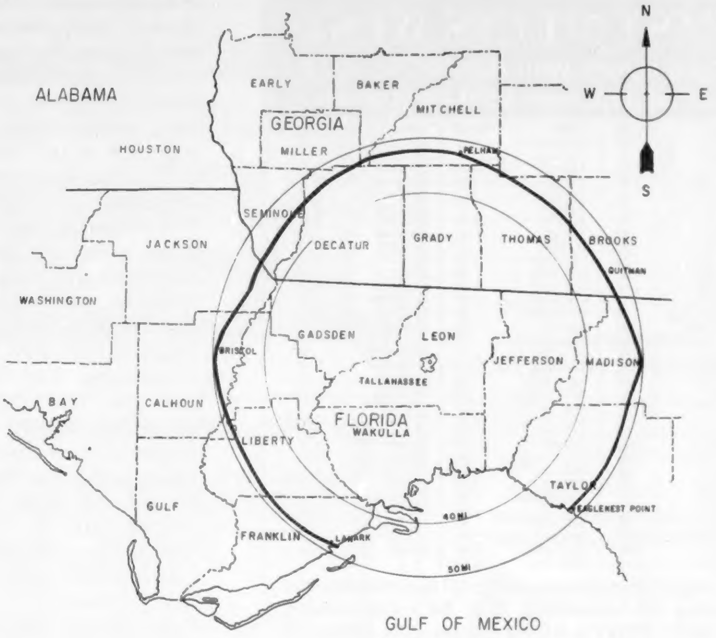

Fig. 1.

Once the repeater was installed in the new location, I began collecting data by the simple expedient of working mobiles as they passed through the area and noting their positions when effective practical communication became impossible. Each such observation was noted on a large scale map (half an inch per mile) as a big red dot. Eventually, each of the roads into town became plastered with dots which sometimes covered several miles of road. These "smeared" observation points resulted from the variations between observations. One mobile might be using 25 Watts to a 5/8-wave whip. The next might be running only 10 Watts to a quarter wave. Another might suffer severe ignition noise on reception or his receiver might be "hot" or slightly "deaf." Propagation conditions might exert some influence from day to day. The final point on the road was chosen at about the middle of the "smear."

The results of the tests were plotted on a map, with the observation points on the highways being connected by a smoothed line. Circles, also centered on the repeater site, showed the 40- and 50-mile radii. The formula predicted an effective working range of 44 miles, disregarding terrain effects.

The interesting distortions of the working contour are almost entirely the result of terrain. A peculiar flattening in the northwest quadrant results from a ridge of hills along the eastern bank of the Apalachicola River. Mobile signals almost "wink out" when they drop over the crest of the hill into the river flood plain. The southern semicircle bulges outward because the terrain in that sector is substantially lower than Tallahassee and is dead flat coastal plain. The Gulf coast itself cuts off the bottom of what would be a rough circle. No observations were taken from boats in the Gulf. I suspect that the contour would bulge outward in that sector because of the high conductivity of the salt-water ground.

One unexpected side effect is that the repeater signal in the city of Tallahassee is not strong enough to quiet fully most mobile receivers. A possible reason is that the antenna is designed to provide some gain and it does this by taking energy away from the upper and lower hemispheres of the radiation pattern and concentrating it around the "equator." The antenna is so high that most of the city lies in the deprived cone directly below it. The favored lobe of radiation widens gradually as it goes away from the tower, and at 10 miles or so the signal at ground level is quite strong.

Another unexpected problem arose in early work at the new site. We tried to use the top antenna at 800 feet for receiving and a side-mounted antenna at 485 feet for transmitting. Reflections and other effects resulting from the tower, guy cables, and other factors produced a radiation pattern which was pulled in strongly to the west and had a powerful lobe to the northeast with an effective range of nearly one hundred miles in the favored direction. We solved the problem by using the top omni antenna for both transmit and receive.

The repeater is on 146.31/.91 MHz, and in this area we have very little, if any, co-channel interference unless there's a strong band opening. For a few days, we experimented with a 146.16/.76 machine on that tower. The results illustrate one of the problems which go along with great height. Mobiles trying to bring up the Valdosta, Georgia, repeater on .16/.76 eighty miles away also brought up the Tallahasee repeater. And because of the strong northeast lobe, our signal was nearly as strong in Valdosta as the Valdosta signal was!

In urban areas, it is entirely possible to cover so large a ham population that the traffic load on a repeater becomes unacceptably high unless access is restricted in some way. When contemplating a repeater on a tower at 2,000 or 3,000 feet above average terrain, it may be desirable to choose a site considerably distant from any expected concentration of ham stations. Otherwise, the area deprived of signal by the antenna gain effect may become a real problem. The effect is greater on UHF than on VHF.

The Stone Mountain repeater near Atlanta, for example, covers Atlanta and most of the surrounding country like a blanket, but it is located about twenty miles east of the city itself. Repeaters located in the Great Smoky Mountains of Kentucky, Tennessee, and northern Georgia cover enormous ranges in their favored directions (where

EAST MEETS WEST
Ceco is now your number 1 source
for all Japanese semi conductors

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
AN214	.77	STK439	3.41	2SC1675L	.10
AN241	.71	TA7130	.47	2SC1678	.48
AN313	1.54	TA7193	2.64	2SC1946	8.93
AN7150	1.09	TA7203	1.06	2SC1946A	10.10
BA301	.37	TA7204	.77	2SC1947	3.25
BA311	.37	TA7205	.77	2SC1966	6.05
BA511A	.61	TA7210	1.70	2SC1968	9.49
BA536	.92	TA7222	.68	2SC1969	.91
BA1320	.67	UPC566	.24	2SC1970	.97
BA1330	.74	UPC1025	1.84	2SC1971	2.25
HA1322	1.00	UPC1156	.79	2SC1972	5.45
HA1339	1.10	UPC1181	.56	2SC2026	.24
HA1342	1.15	UPC1185	1.30	2SC2075K	.42
HA1361	.88	UPC1350	.68	2SC2131	2.32
HA1366W	1.05	2SA564	.09	2SC2237	3.72
HA1366WR	1.05	2SA684	.19	2SC2407K	.36
HA1367	.89	2SA733P	.10	2SC2458BL	.08
HA1377A	1.30	2SA950Y	.13	2SC2458Y	.08
HA1388	1.82	2SA1048Y	.08	2SC2459	.11
HA1397	1.63	2SA1048LY	.15	2SC2549	.11
HA1398	1.42	2SB172	.15	2SC2668-0	.09
LA1111	.41	2SC730	2.00	2SC2695	11.69
LA4030	.90	2SC940	.88	2SC3019	1.39
LA4031	.90	2SC945	.08	2SC3021	8.35
LA4032	.95	2SC945AQ	.08	2SC3022	12.49
LA4050	.86	2SC1096	.25	2SD388	1.09
LA4101	.86	2SC1165	3.45	2SD588	.91
LA4400	1.07	2SC1172B	1.99	2SK102GR	.40
LA4420	.70	2SC1177	7.25	2SK117GR	.19
M51513L	.80	2SC1306	.65	2SK168E	.16
STK013	4.30	2SC1307	1.60	2SK241Y	.22
STK435	2.95	2SC1308K	2.66	3SK39	.55
STK437	3.07	2SC1314	14.68		

Ceco is also your largest source for semi conductors including RF transistors, RCA SK replacements, RCA MRO, ECG's & GE. Take advantage of CeCo's money saving prices and off the shelf service.

Remember Ceco For All Your Tube, Video and CCTV Requirements
Catalog on Request

✓92

CeCo®
Call Toll Free: 800-221-0860 Elsewhere: 212-646-6300
Telex: TWX 235125 Cable Address: Ceco Tubes
2115 AVENUE X • BROOKLYN, N.Y. 11235

mountainous terrain doesn't block the signals) and they serve a largely rural population without the dense concentration of stations which might cause problems in, say, New York City, Chicago, or Los Angeles.

It should be kept in mind, when trying to apply our rule-of-thumb range formula to other locations, that terrain is often a much bigger factor than it is in Tallahassee. The formula will give reasonably accurate results only when it is applied to one particular radius using the "average terrain elevation" along that particular line. A repeater in Iowa may well have an almost circular pattern. A repeater located in California or West Virginia is likely to be a totally different matter. The formula is not applicable directly to repeaters on bands other than two meters because terrain losses will not be the same. However, on any band, range will vary in direct proportion to the square root of the height of the antenna, and it should not be difficult to work out a new H multiplier which would give reasonably accurate results on, say, 50, 220, or 450 MHz.

Clubs which put up repeaters with wide coverage areas should be prepared to welcome and to serve many itinerant mobiles travelling through the area who may frequently be more interested in working each other than in working locals. Repeater groups that want to communicate among themselves for rag-chew, emergency, or other purely local communications purposes should give serious consideration to using a lower antenna site or a closed repeater operation using some form of restricted access. ■

CHRISTMAS SPECIALS!

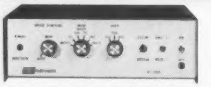

RT-1100 Receive Terminal
SPECIAL $399^00

- 60,66,75,100 WPM Baudot, 110 baud ASCII and 6-60 WPM Morse
- Active filter demodulator with scope tuning outputs. 170,425,850 Hz shifts
- Two page video display with 16 lines of 32 characters per page
- Parallel ASCII printer output

LIST $499^00

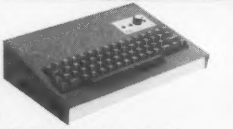

MKB-2000 (Morse Only)
SPECIAL $259^00

- Complete set of alphanumeric, punctuation, and special function keys
- 500 character text buffer with BREAK feature
- 10 reprogrammable 40 character message memories
- 1-199 WPM, keyboard selectable
- Random code, Intercharacter spacing, Weight control, Cassette interface

LIST $319^00

MVD-1000 (Morse Only)
SPECIAL $299^00

- Automatic speed tracking with self calibration, 6-60 WPM
- Active filters and digital sampling for increased noise rejection
- Operates with any TV set
- Two page display with 16 lines of 32 characters per page

LIST $369^00

Special prices effective thru December 31, 1982

Send For Free Information

Add $5.00 per unit for shipping U.S.A.

DGM ELECTRONICS, INC.
787 Briar Lane, Beloit, Wis. 53511
(608) 362-0410

AT LAST!

This service will be available nationally. Lab tested & time proven modifications professionally installed in your amateur Handy-Talkie 2M, 220, 440, MH2 transceiver by Henry Radios warranty technicians (KNOWN AS "A&W PRODUCTIONS")

HAVE ALL PL TONES AVAILABLE AT YOUR FINGER TIPS

Outboard the dip switch! Have it neatly inlayed into the back cover of your Handy-Talkie making all 32 PL Tones Selectable at a moment's notice.

$25 Got your own PL? Send it to us with your Handy-Talkie unit and we do the professional installation for you.

$55 We will install a new PL and inlay the dip switch into the back cover of your Handy-Talkie ready to operate.

Send us your Handy-Talkie unit and a check or money order plus $3.50 for shipping and handling payable to **A&W PRODUCTIONS, INC.**

For **TEMPO** units the dip switch is inlayed into the Push-to-Talk bar. The **TEMPO S-15** will have the dip switch inlayed into the back cover.

$45 We will install a **NEW BATTERY BEATER** in your **TEMPO S-1, S-2, S-4, S-5 READY** to operate. Your New Battery Beater will use the same jack as the charger with no new holes and regulation circuits built into unit. Comes with Cigar Lighter Adapter with internal fuse.

CONTACT A&W PRODUCTIONS FOR SPECIAL MODIFICATIONS YOU MAY WANT TO HAVE DONE. WE SPECIALIZE IN THE TEMPO HANDY-TALKIES.

WE ARE AN OFFICIAL "TEMPO" REPAIR STATION
ALL WORK GUARANTEED FOR 30 DAYS. SEND YOUR HANDY-TALKIE AND A CHECK OR MONEY ORDER TO:

AW PRODUCTIONS ✓164
3305 Pico Blvd., Santa Monica
California 90405 (213) 828-9310

ALL YOUR GEAR AT YOUR FINGERTIPS IN A CONVENIENT CONSOLE DESK

Requires only 60″ corner space
Formica desk top and shelves
Shelf height adjustable
Solid maple legs
***$495.00* check or M.O.**
Shipped freight collect
Allow 30–45 days delivery

Send for detailed brochure

CQ PRODUCTS
8280 Janes Ave.
Suite 137–1700
Woodridge, IL. 60517

✓152

(Chair and equipment not included)
Weight of table is 250 lbs.

Put Your Computer "On-The-Air"

Kantronics The Interface
RTTY-CW-uP Terminal Unit
CW
RTTY
Off
On
Tune

The Interface™

Sugg. Price $189.95

Your personal computer becomes a complete CW/RTTY/ASCII send and receive terminal with The Interface linking it to your transceiver.

If you own an Apple II or Apple II Plus, Atari 400 or 800, TRS-80 Color Computer, or VIC-20, The Interface will put your computer "On-The-Air".

Software for each system features split screen display, buffered keyboard, status display, and message ports. Attach any Centronics compatible printer for hard copy. Software is available, on diskette for the Apple and program boards for the others, at an additional cost.

Apple diskette	Atari board	VIC-20 board	TRS-80C board
$29.95	$49.95	$49.95	$59.95

See The Interface at your authorized Kantronics dealer, or contact:

Kantronics

(913) 842-7745 | 1202 E. 23rd | Lawrence, Kansas 66044

HI·Q BALUN

- For dipoles, yagis, inverted vees & doublets
- Replaces center insulator
- Puts power in antenna
- Broadbanded 3-40 MHz
- Small, lightweight and weatherproof
- 1:1 impedance ratio
- For full legal power and more
- Helps eliminate TVI
- With SO 239 connector

only $12.95

HI-Q ANTENNA CENTER INSULATOR

Small, rugged, lightweight, weatherproof

Replaces center insulator

Handles full legal power and more

With SO 239 connector

$6.95

HI·Q ANTENNA END INSULATORS

Rugged, lightweight, injection molded of top quality material, with high dielectric qualities and excellent weatherability. End insulators are constructed in a spiral unending fashion to permit winding of loading coils or partial winding for tuned traps.

May be used for
- Guy wire strain insulators
- End or center insulators for antennas
- Construction of antenna loading coils or multiband traps

Patent No
4 091 350

$4.95

DIPOLES

MODEL	BANDS	LENGTH	PRICE WITH HI-Q BALUN	WITH HI-Q CENTER INSULATOR
Dipoles				
D-80	80,75	130	$31.95	$27.95
D-40	40,15	66	28.95	24.95
D-20	20	33	27.95	23.95
D-15	15	22	26.95	22.95
D-10	10	16	25.95	21.95
Shortened dipoles				
SD-80	80,75	90	35.95	31.95
SD-40	40	45	32.95	28.95
Parallel dipoles				
PD-8010	80,40,20,10,15	130	43.95	39.95
PD-4010	40,20,10,15	66	37.95	33.95
PD-8040	80,40,15	130	39.95	35.95
PD-4020	40,20,15	66	33.95	29.95
Dipole shorteners - only, same as included in SD models				
S-80	80,75		$11.95 pr	
S-40	40		$10.95 pr	

All antennas are complete with a HI-Q Balun or HI-Q Antenna Center insulator, No. 14 antenna wire, ceramic insulators, 100 nylon antenna support rope (SD models only 50) rated for full legal power. Antennas may be used as an inverted V and may also be used by MARS or SWLs.

Antenna accessories—available with antenna orders	
Nylon guy rope 450# test 100 feet	$4.49
Ceramic (Dogbone Type) antenna insulators	$1.50 pr
SO-239 coax connectors	.55

All prices are postpaid USA 48
Available at your favorite dealer or order direct from

Dealer Inquiries Invited

Van Gorden Engineering

BOX 21305 B, SOUTH EUCLID, OHIO 44121

OVER 70 BRANDS IN STOCK

LAND-MOBILE RADIO

BIRD

DRAKE

HYGAIN • ARRL

AMATEUR RADIO

SHORTWAVE

SCANNERS

ICOM

TEN-TEC

B&W • CDE

BEARCAT • MORGAIN • MANY MORE...

Full Service Shop • Spectrum Analysis • Antennas
New and Used Equipment • CW-SSB-FM, Etc. • Towers
FCC Study Guides • Code Tapes • Books • Accessories

SPECTRONICS

Specialists in Amateur Radio, Short-Wave Listening And Contemporary Electronic Gear.

HOURS
MON, TUES, WED.: 9:30-6:00 PM
THURS, FRI.: 9:30-8:00 PM
SAT.: 9:30-3:00 PM

CLOSED SUNDAYS, HOLIDAYS

SPECTRONICS, INC.
1009 GARFIELD ST. OAK PARK, IL. 60304
(312) 848-6777

TALK FARTHER

VoCom Power Amplifiers

Drive Level	Output Power	Model Number
150-200 mW	25W	2C025-200 mW
1.5 W	20-25W	2C025-2W
1.5W	45-50W	2C050-2W
1.5W	80-90W	2C100-2/25
2W-5W	>30W	2C025-2W
2W-5W	>50W	2C050-2W
2W-5W	>100W	2C100-2/25
10W	100W	2C100-10/25
25W	100W	2C100-2/25
25W	100W	2C100-10/25

5/8 wave
4"
1/4 wave
2C025
2C050
2C100
Power Pocket

. . . with range-extending products from VoCom

25, 50, or 100 Watts Power — Whatever your present output level — from 200 mW handheld on "battery saver" mode to 25W mobile or base — you can use that to drive a compact, 12V power amp from VoCom for much more talk-out power (see chart). Each model has a front panel switch to let you go "barefoot" for short hauls, plus an L.E.D. indicator to show the mode you're in. Full 10 MHz bandwidth gives you virtually unchanged power across the entire 2-meter band. High efficiency design holds down generated heat, low input VSWR saves battery drain by your radio's final amp. Use the chart to see which VoCom Power Amplifier gives you the power out you'd like from the power that you now have.

Power Pocket™ Mobile Amplifier/Charger — Simply plug in your Icom IC-2A(T) and you have a 25W synthesized mobile rig — take it out again, all charged and ready, when you want hand-held operation. Accepts any IC-2A version. Delivers 25W RF output, 2½W audio with 4" speaker to overcome road noise. Charge pocket accepts all Icom battery packs, has independent charging switch, indicator. Mic preamp makes Power Pocket compatible with any mobile microphone and with Icom speaker/mic.

5/8 HT Gain Antenna boosts reception while giving your hand-held full quieting out of spots you're nearly dead in with a rubber duck; provides excellent improvement. Only 8" telescoped, 47" extended. Better than 1.5:1 VSWR. BNC connector.

Spring-loaded 1/4 wave antenna and 4" stubby duck also available. See your favorite amateur radio dealer.

VoCom
PRODUCTS CORPORATION
65 East Palatine Road
Prospect Heights, IL 60070
(312) 459-3680

✓90

Icom and IC-2A are trademarks of Icom-America Inc. Power Pocket and VoCom are trademarks of VoCom Products Corp. © 1982 by VoCom Products Corp.

Announcing

NEW AUTOPATCH

PRIVATE PATCH

Introducing **Private Patch.** A giant step forward in non-sampling Autopatch/Interconnect technology, capability and standard features. Our revolutionary new techniques of audio and digital signal processing offer several advantages over conventional sampling/scanning type Autopatches: 1. The annoyance of continuous squelch tails is *totally* eliminated. Makes conversation much more natural and enjoyable. 2. In addition to superb simplex capability, operation through repeaters is made possible. 3. The only connections made to your base transceiver are to microphone and speaker jacks. NO INTERNAL CONNECTIONS OR MODIFICATIONS NECESSARY! Use **Private Patch** simplex for local operation, through a repeater for extended range. CW ID makes your Autopatch legal, and alerts you to incoming calls when ringback is turned on. Channel monitor logic precludes ringback transmission if channel is in prior use. Eliminates accidental interference. Five digit owner programmable access code and operator/long distance inhibit switch assure security and protect your phone bill. Positive control is assured by **Private Patch** logic functions. A fully digital timing approach eliminates all Timing adjustments. Three/six minute timer shuts down **Private Patch** if you drive out of range. Resettable with reset code for additional talk time as required. Self contained AC supply. Modular phone jack and modular phone cord provided. All electronics contained on one high quality glass circuit card. **Private Patch** contains 42 integrated circuits and 16 transistors. Send for additional information. Compare our features. (State callsign when ordering.)

Special Factory Direct Introductory Price

1 YEAR WARRANTY

$489
Postage Paid

PHONE: (213) 540-1053

AUTOCONNECT
P.O. BOX 4155
TORRANCE, CA 90510

DEALERSHIPS INVITED ✓130

BARKER & WILLIAMSON

VERTICAL ANTENNAS

MODEL 370-31
Slim Line Vertical designed for 10, 15, 20 and 40 meters. All traps pretuned. Overall height 21 feet. Can be used with or without ground radials. Model 370-33 — 75 meter add on kit. 75 and 80 meter operation optional with model 370-33 add on kit. Power rating 1 KW-2 KW P.E.P.

MODEL 370-30
Economy model vertical for 10, 15, 20 and 40 meter operation. High Q factory tuned traps. Overall height 21 feet. Can be used with or without ground radials. Model 370-32 — 75 meter add on kit. 75 and 80 meter operation optional with model 370-32 add on kit. Power rating 1 KW-2 KW P.E.P.

MODEL 370-34
Radial Kit. Radial Kit for Models 370-30 and 370-31 Vertical antennas. All necessary wire and hardware for two ground plane radials. Write for more details and other antenna products.

B&W

Barker & Williamson, Inc.
10 Canal St.,
Bristol, Pa. 19007
215-788-5581

✓11

RTTY - 50

Basic Terminal Unit

- 60 mA Loop Keying
- PLL Demod w/2 pole filter
- AFSK Generator

$79⁰⁰

Call or write for FREE catalog with over 65 P.C. Boards & Kits.

RTTY - 100

Expanded Version of the Popular RTTY - 50

- AFSK
- 850/170
- TTL & RS232
- 60 mA Loop
- Loop Supply
- Auto Start
- 4 Pole Filters
- AGC (80db)

$189⁰⁰

COMMUNICATIONS DESIGN INC.
1105 Lehr St. — West Memphis, Arkansas 72301
(501) 735-4568

Surge protection plus master control for all your equipment

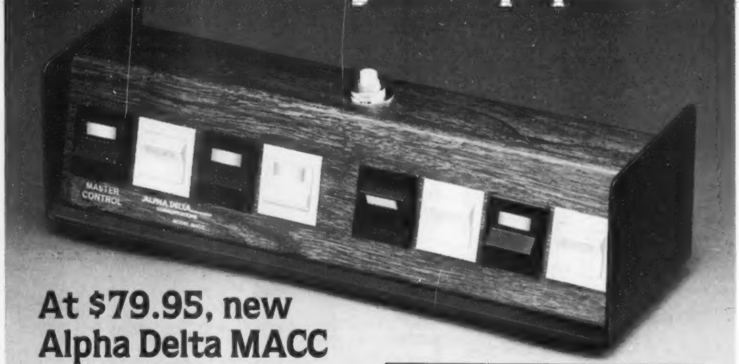

At $79.95, new Alpha Delta MACC is very low cost "insurance" on your total investment

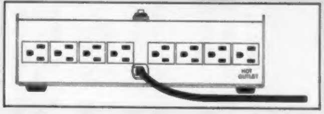

Modern solid-state circuitry is even more vulnerable to that old bugaboo, lightning. Strikes miles away can cause damage. So can transient currents from such common things as electric motors and fluorescent lights.

But Alpha Delta Master AC Control Console's 3-stage automatic restorable circuitry clips off the power surges and spikes to provide clean AC power. Its resettable circuit breaker adds further protection.

MACC gives you control convenience, too. It provides 8 plug-in "U" ground outlets for your components—including one "hot" for a continuously powered application such as your clock. Seven "on/off" rocker switches let you control individual components. And you can turn your entire system on or off with a single master rocker switch.

All switches light up when "on" to confirm system condition.

MACC is tested to IEEE pulse standards and rated at 15A, 125VAC, 60 Hz, 1875 watts continuous-duty total for console. See label for surge protection limitations.

Get MACC protection. Whatever the price, it can be the most important buy you make.

ALPHA DELTA Model MACC Master AC Control Console $79.95 (U.S.)

✓193

At your Alpha Delta dealer. Or in U.S., order direct, adding $4 for postage/handling to check or money order. (Ask for quotes on overseas postage and 240VAC MACC-E with VDE-approved sockets.) MasterCard and VISA accepted. Ohio residents add Sales Tax. Sorry, no C.O.D.'s

ALPHA DELTA COMMUNICATIONS
P.O. Box 571, Centerville, Ohio 45459 • (513) 435-4772

✓See List of Advertisers on page 130

Season's Greetings

Radio World

THE NORTHEAST'S LARGEST FULL LINE AMATEUR DEALER

AEA MM-2
KENWOOD TS830S
ICOM IC-720
YAESU FT707
TEN-TEC Omni
ROBOT 800
COLLINS KWM-380
DRAKE TR7-DR7

ORDER TOLL FREE 1-800-448-9338

FEATURING: Kenwood, Yaesu, Icom, Drake, Ten-Tec, Cubic, Dentron, Alpha, Robot, AEA, Telrex, Astron, Avanti, Belden, CES, Daiwa, J.W. Miller, Panasonic, B&W, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure, Tempo, VoCom, KLM, Hy-Gain, Larsen, Cushcraft, Hustler, Mini-Products, Bird, CDE, Rohn, Alliance, MFJ, Bearcat, Telex, Nye, Palomar Eng., Kantronics, Hayden, Ameco, Collins. Saxton

We provide factory authorized warranty service for most major lines of equipment, and after-warranty service on all other brands. Write or call for a quote. **You Won't Be Disappointed.**

We are just a few minutes off the NYS Thruway (I-90) Exit 32

VISA master charge

ONEIDA COUNTY AIRPORT TERMINAL BUILDING
ORISKANY, NEW YORK 13424
N Y Res Call (315) 736-0184

Warren - K2IXN
Bob - WA2MSH
Al - WA2MSI

✓397

hy-gain

ANTENNA ROTATORS

for your peace of mind.

Determine the total wind-load area of your antenna(s), plus any antenna additions or upgrading you expect to do. Now, select the matching rotator model from the capacity chart below. If in doubt, choose the model with the next higher capacity. You'll not only buy a rotator, you'll buy peace of mind.

	ANTENNA WIND-LOAD CAPACITY	
ROTATOR MODEL	MOUNTED INSIDE TOWER	WITH STANDARD LOWER MAST ADAPTER
AR22XL or AR40	3.0 sq. ft. (.28 sq. m)	1.5 sq. ft. (.14 sq. m)
CD45 II	8.5 sq. ft. (.79 sq. m)	5.0 sq. ft. (4.6 sq. m)
HAM IV	15.0 sq. ft. (1.4 sq. m)	N/A
T^2X	20.0 sq. ft. (1.9 sq. m)	N/A
HDR300	25.0 sq. ft. (2.3 sq. m)	N/A

For HF antennas with booms over 26' (8 m) use HDR300 or our industrial R3501.

✓316

Full details at better Amateur dealers or write:

TELEX hy-gain

TELEX COMMUNICATIONS, INC.

9600 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A.
Europe: Le Bonaparte—Office 711, Centre Affaires Paris-Nord, 93153 Le Blanc-Mesnil, France

hy-gain®

HF BROADBAND VERTICALS WORK THE WORLD

Hy-Gain broadband vertical antennas load the new auto-tune solid state rigs, require minimal space and provide low angle radiation without the expense or the problems of support structures.

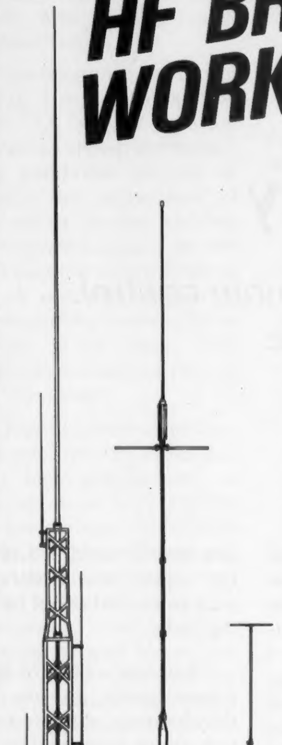

18AVT/WBS (80-10 meters) The most successful vertical antenna of all and for good reasons. Broadband performance covers the 40, 20, 15 and 10 meter bands in their entirety. Automatic 5 band switching is accomplished by mechanically superior, highly efficient factory tuned Hy-Q traps with large coils for consistent performance at 2:1 or lower VSWR on 40-10 meter band edges; bandwidth on 80 meters is approximately 40 kHz with VSWR below 2:1. A factory tuned matching network for 50 ohms impedance is dc grounded for lightning protection and reduced precipitation static. The mechanical integrity of this antenna is so stable that performance does not change with the weather. The 18AVT withstands winds to 80 mph (128 km/h) without guying. All stainless steel hardware is included.

14AVQ/WBS (40-10 meters) Offers very similar construction and the same excellent broadband performance as 18AVT over the entire 40, 20, 15 and 10 meter bands; automatic band switching with mechanically superior large-coil Hy-Q traps and very low angle radiation pattern. The smaller, low visibility size also makes the 14AVQ very suitable for roof mounting. The optional 14RMQ roof mounting kit includes base plate, mast and radial/guy wires. All antenna hardware is stainless steel.

18 HTS (80-10 meters. 160 meters with optional loading coil) The superb reliability of the 18 HTS is manifest in installations now over 20 years old. And, with the improvements we made over the years, the 18HTS is now better than ever. Automatic band selection is achieved through a unique stub decoupling system which effectively isolates various sections of the antenna so that an electrical ¼ wavelength (or odd multiple ¼ wavelength) exists on all bands. For example, outstanding broadband performance on 20, 15 and 10 meters is achieved with an extended ¾ wave collinear. On 80 meters bandwidth is approximately 250 kHz at 2:1 VSWR. With the optional base loading coil exceptional performance is also provided at 160 meters. The galvanized tower requires no guying and withstands winds to 100 mph (160 km/h). A special hinged base allows complete assembly at ground level and permits easy raising and lowering. Includes stainless steel hardware. WARC kits to be available.

Other Hy-Gain vertical multiband antennas are available though not shown here. The 12AVQS (20, 15, 10 meter) is similar to 18AVT above but with VSWR of 1.5:1 or less on all bands. The 18VS (80-10 meter) comes with a base loading coil and may be installed on a short mast driven into the ground. All include stainless steel hardware.

PHASE FOR GAIN

Any two identical Hy-Gain verticals can be phased for excellent gain and directivity. A great system for beam performance on 40, 80 and 160 meters or for 10, 15 and 20 meters where space is limited. Send for our free technical report "Phased Verticals".

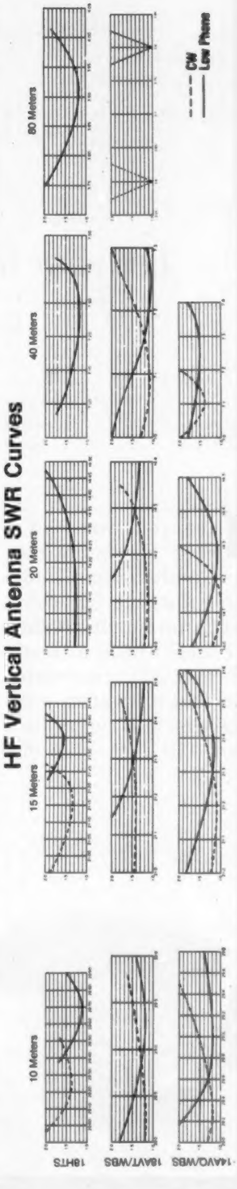

Hy-Gain Verticals that work the world at better Amateur Dealers.

TELEX® hy-gain®

316

TELEX COMMUNICATIONS, INC.

9600 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A.
Europe: Le Bonaparte–Office 711, Centre Affaires Paris-Nord, 93153 Le Blanc-Mesnil, France.

Steven W. Siter K1WGN
488 Marshall St.
Paxton MA 01612

Dial-A-Frequency

Let your fingers do the walking with this remote control. All you need is a spare telephone.

Have you ever had a need to remote control a multi-channel radio over a distance but didn't want to run a multi-conductor cable? I have a Heathkit® HW-202 two-meter radio that is located in my shop which is in a barn about 150 feet from the house. I wanted to be able to use the radio in both the barn and the house without moving it. One solution to this problem is described here.

The system I developed allows me to dial up any one of four channels in my two-meter radio. This is done using a standard dial telephone with a minor modification for push-to-talk operation. The telephone is connected to a controller via a single pair of wires that can be several hundred feet long. Several phones may be connected to the line, although only one may be used at a time. Of course, the telephone may be moved about by using jacks.

Photo A. Overall view of the remote two-meter dial-up system. The telephone can be located several hundred feet away from the radio and its controller.

I'll review a little of telephone basics, go into the development of the system, talk about construction details and adjustments, and offer some afterthoughts that you may want to include in your version. Successful duplication of the ideas presented depends on how resourceful you are, as some of the relays and transformers may be difficult to find.

Basic Terminology

We all use the telephone every day. It seems to be a simple enough device, and on close inspection, it is. Fig. 1 shows the basic circuit from the telephone to the central office. The two wires that connect these two locations are a twisted, balanced pair with a typical characteristic impedance of 600 Ohms. Longitudinal balance describes how closely each conductor matches the other along the

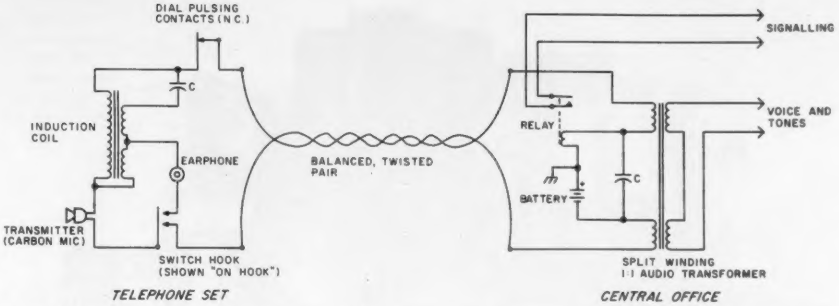
DIAL PULSING CONTACTS (N.C.)
C
INDUCTION COIL
EARPHONE
TRANSMITTER (CARBON MIC)
SWITCH HOOK (SHOWN "ON HOOK")
TELEPHONE SET
BALANCED, TWISTED PAIR
SIGNALLING
VOICE AND TONES
RELAY
BATTERY
C
SPLIT WINDING 1:1 AUDIO TRANSFORMER
CENTRAL OFFICE

Fig. 1. Basic telephone circuit. Note that dc current flows from the central office battery through the carbon microphone—but only when the switch is "off hook."

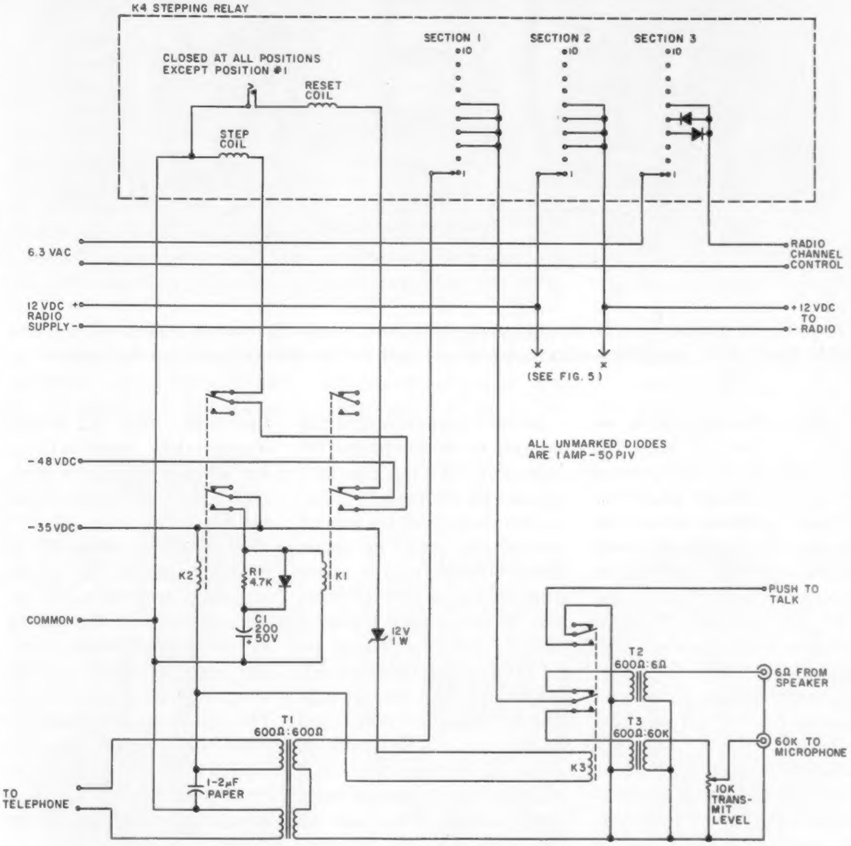
K4 STEPPING RELAY
CLOSED AT ALL POSITIONS EXCEPT POSITION #1
RESET COIL
STEP COIL
SECTION 1
SECTION 2
SECTION 3
10
1
6.3 VAC
RADIO CHANNEL CONTROL
12 VDC + RADIO SUPPLY −
+12 VDC TO − RADIO
(SEE FIG. 5)
ALL UNMARKED DIODES ARE 1 AMP - 50 PIV
−48 VDC
−35 VDC
K2
R1 4.7K
K1
C1 200 50V
COMMON
12V 1W
PUSH TO TALK
T2 600Ω:6Ω
6Ω FROM SPEAKER
T1 600Ω:600Ω
T3 600Ω:60K
60K TO MICROPHONE
K3
1-2μF PAPER
TO TELEPHONE
10K TRANSMIT LEVEL

Fig. 2. Schematic diagram of the dial-up two-meter remote controller.

route. This becomes increasingly important the longer the circuit becomes. The better the longitudinal balance, the less interference occurs from outside sources such as other telephone circuits in the same cable and parallel power conductors.

The telephone set shown in Fig. 1 is a simplified circuit. An actual type-500 phone as shown in Photo C has additional circuits to match the impedance of the set to the line and has additional contacts on the dial and the switch hook to short out the earphone when dialing or when the receiver is on hook. This eliminates annoying pops in the earphone.

Direct current continuity is a requirement of the circuit for signaling and to provide a dc bias current for the carbon microphone in the telephone. When you lift the telephone "off hook," the dc circuit is completed with current flowing through the microphone. When you turn the dial clockwise to the stop, a spring is wound up in the dial. When the dial is released, the spring returns the dial and a set of contacts opens and closes once for each digit dialed at a rate of 10 pulses per second. Many modern central offices can respond to 20 pulses per second, so some phones are so equipped. A tone-dial phone still requires a dc continuous circuit to tell the central office when it is off hook and to have dc bias for the carbon microphone and tone generating circuits.

At the central end of the circuit, note the one-to-one ratio transformer with a split winding on one side. This transformer allows the insertion of dc current and the picking off of the control signals while maintaining the circuit balance to ground. At the same time, voice and tone signaling (if applicable) are coupled through to the other side of the transformer. The capacitor shunting the power supply and relay coil on the line side of the transformer bypasses audio frequencies.

The circuit shown in Fig. 1 is the basis of my two-meter dial-up remote controller. I won't go further into the operation of the central office, but if anyone is interested in further study in this area, *Basic Telephone Switching Systems* by David Talley (Hayden Book Company, New York NY) makes good reading.

Development of the Dial-Up Remote

There are three control functions that must be provided in the two-meter dial-up system: the off-hook condition, dial pulses, and push-to-talk function. These three functions are provided by relays K1, K2, and K3, respectively, in Fig. 2. The telephone set itself must be modified to provide push-to-talk operation. More about this later.

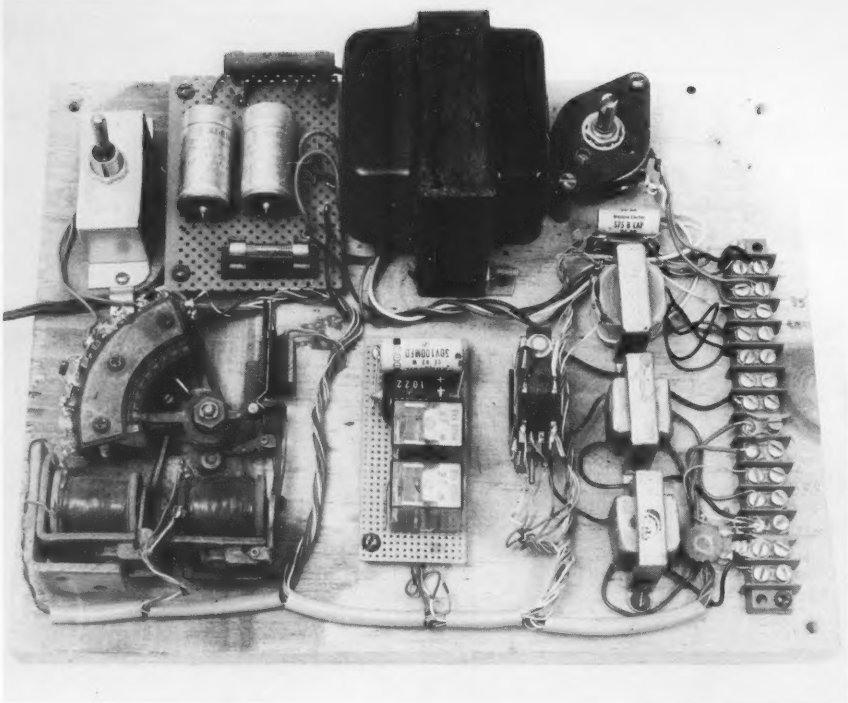

Photo B. The controller with power supply at the rear, stepping relay at the left, K1, K2, and K3 in the middle, and the audio transformers next to the terminal strip on the right.

When the telephone receiver is lifted off hook, the dc circuit is completed from the 35-volt source to K2 and to the series combination of the 12-volt zener diode and K3. Contacts on K2 apply 35 volts to K1 and charge C1 through R1. R1 is necessary to prevent contact arcing on K2. Now that K1 is picked up, the 48-volt source is removed from the reset coil on the stepping relay and applied to contacts on K2 which are connected to the stepping coil. A separate 48-volt source was necessary because of the particular stepping relay that I had available.

What happens now if the dc loop to the telephone set is broken for a fraction of a second by dialing a "1"? Relay K2 drops out for a brief period and picks up again when the dc loop is again completed. This removes the 35-volt source from K1 briefly, but the charge on C1 holds K1 closed through the diode. The 48-volt supply is therefore maintained to the contacts on K2 which close for the brief time that K2 drops out. This applies a single pulse of 48 volts to the stepping coil, advancing the switches one step to position two.

If you were to hang up at this time, relay K2 would immediately drop out. Relay K1 would remain energized for about one-half second because of the charge on C1. When K1 finally drops out, the 48-volt supply is applied to the reset coil. Because the switches are not in position one, the reset contacts on the stepping relay are closed. The reset coil will therefore reset the switches to position one, at which point the reset contacts on the stepping relay again would be open.

If we now lift the receiver and dial, for example, a three, the switches will advance to position four and stay there until we hang up again. Note that the stepping and reset coils never have voltage applied for any length of time. They usually are rated for intermittent duty only. Note also that dialing 12 or 21 has the same effect as dialing a three.

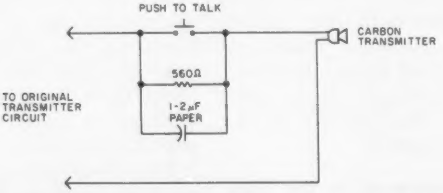

Fig. 3. Telephone set modification for push-to-talk operation.

Fig. 3 shows the modification for push-to-tak operation. The parallel combination of the pushbutton, resistor, and capacitor is inserted in series with the carbon microphone or at any point in the current loop, such as the line coming into the telephone. When the push-to-talk button in the handset is pressed, the 560-Ohm resistor is shorted, resulting in a higher voltage across K2 and the series combination of K3 and the zener diode. A zener diode was used in series with K3 rather than a resistor so all of the voltage difference brought about by pushing the push-to-talk button would appear across the relay. The capacitor shunts the resistor for voice frequencies.

Relay K3 must be selected carefully. It must have a drop-out voltage not much less than its pick-up voltage. The unit I used has a 12-volt coil and is a plug-in type from an old IBM keypunch machine. Most 12-volt relays will pick up at about 10 volts but many will not drop out once picked up until the voltage is less than three or four volts. The variable resistor in the power supply (Fig. 5) is adjusted for proper push-to-talk operation. You may want to experiment with electronic circuits to sense the push-to-talk voltage change and which would, in turn, drive the push-to-talk relay. Another alternative would be to run a separate pair of wires for the push-to-talk button.

The push-to-talk relay, K3, grounds the push-to-talk line to the radio and switches the 600-Ohm audio from the split-winding transformer, T1, between the radio microphone input and speaker output. Impedance matching is required on both of these circuits. I used some small, 120-to-12-volt (10:1 ratio) filament

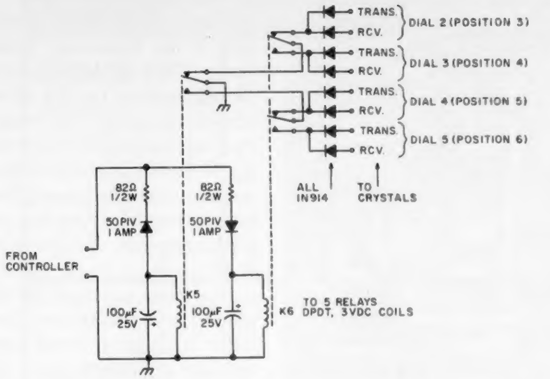
TRANS.
RCV.
DIAL 2 (POSITION 3)
TRANS.
RCV.
DIAL 3 (POSITION 4)
TRANS.
RCV.
DIAL 4 (POSITION 5)
TRANS.
RCV.
DIAL 5 (POSITION 6)
ALL 1N914
TO CRYSTALS
82Ω 1/2W
82Ω 1/2W
50PIV 1 AMP
50PIV 1 AMP
FROM CONTROLLER
K5
100µF 25V
100µF 25V
K6
TO 5 RELAYS DPDT, 3VDC COILS

Fig. 4. Channel-change circuit located in the radio.

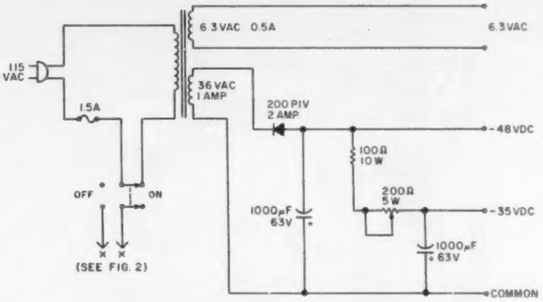
6.3VAC 0.5A
6.3VAC
115 VAC
36VAC 1 AMP
1.5A
200PIV 2 AMP
-48VDC
100Ω 10W
200Ω 5W
-35VDC
1000µF 63V
1000µF 63V
OFF
ON
(SEE FIG. 2)
COMMON

Fig. 5. Power supply schematic diagram.

transformers from my junk box.

The stepping relay that I used has three switch sections. It is a C. P. Clare model A321033 that was salvaged from an electrical circuit recloser. One section is used to connect the telephone circuit to the radio. This allows me to dial up other devices on other positions of the stepping relay, such as a weather receiver. The second section turns on the power to the two-meter transceiver. The third section changes channels in the radio. Stepping relays are available from time to time from surplus outlets such as Fair Radio Sales, 1016 East Eureka Street, PO Box 1105, Lima OH 45802.

Fig. 4 shows the channel-change circuit. Two miniature relays are used to select the appropriate crystals in the Heath HW-202. The resistors in series with the relays are necessary because the relays I had available have 3-volt coils. Note that when the stepping relay is in position three, neither relay is energized. When in position four, K6 is picked up, when in position five, K5 is picked up, and when in position six, both relays are picked up.

In each case, a different pair of crystal switching diodes is grounded. I disconnected the radio switch grounds from the chassis ground and reconnected them to be grounded when neither relay is energized, position three. This allows me to select with the radio switches which channel will be selected when dialing a two. It also allows the radio channel switches to function normally when not connected to the controller or when the controller is switched off. The other three positions are connected to the crystals of the most commonly used channels.

The power supply, Fig. 5, is straightforward. A small amount of 6.3-volt ac power is required for the channel-changing circuit. The 36-volt secondary on the transformer gives about 48 to 50 volts dc for the stepping relay. It must be capable of supplying the intermittent current requirements of the stepping relay, about 1 Ampere in my case.

Dropping resistors are used to supply a lower voltage for operation of K1, K2, and K3. This voltage should be relatively hum free as it is also used to bias the carbon microphone. The dropping resistor is made variable to allow setting the push-to-talk operating point. Positive grounds are used as this is telephone system convention but it certainly isn't necessary. If negative grounds are desired, it is only necessary to reverse the polarity of C1, the diodes associated with K1 and K3, and, of course, the power supply capaci-

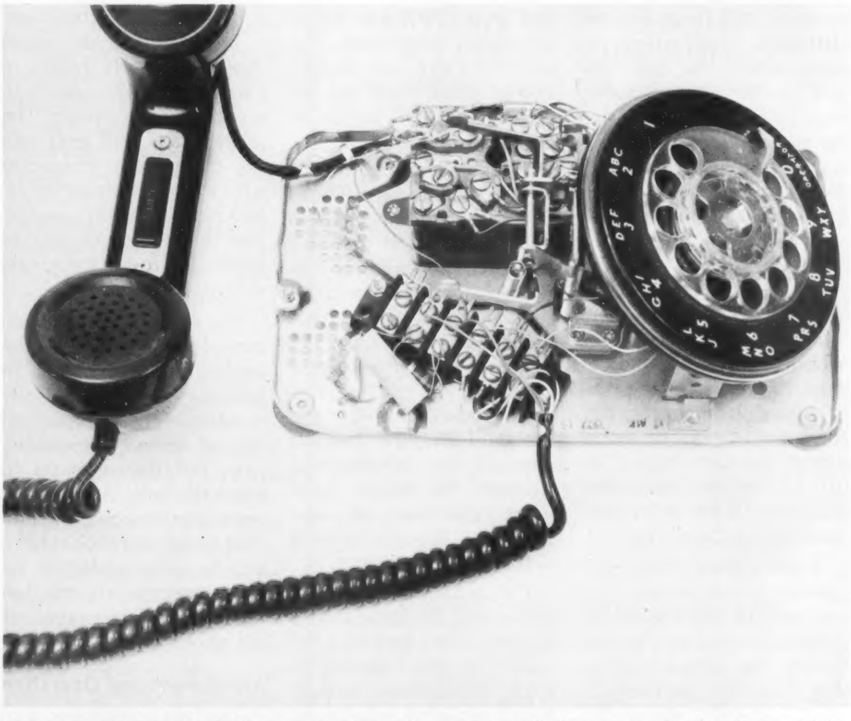

Photo C. Modified telephone set. Note the push-to-talk button in the handset and the resistor-capacitor combination mounted on the added terminal strip.

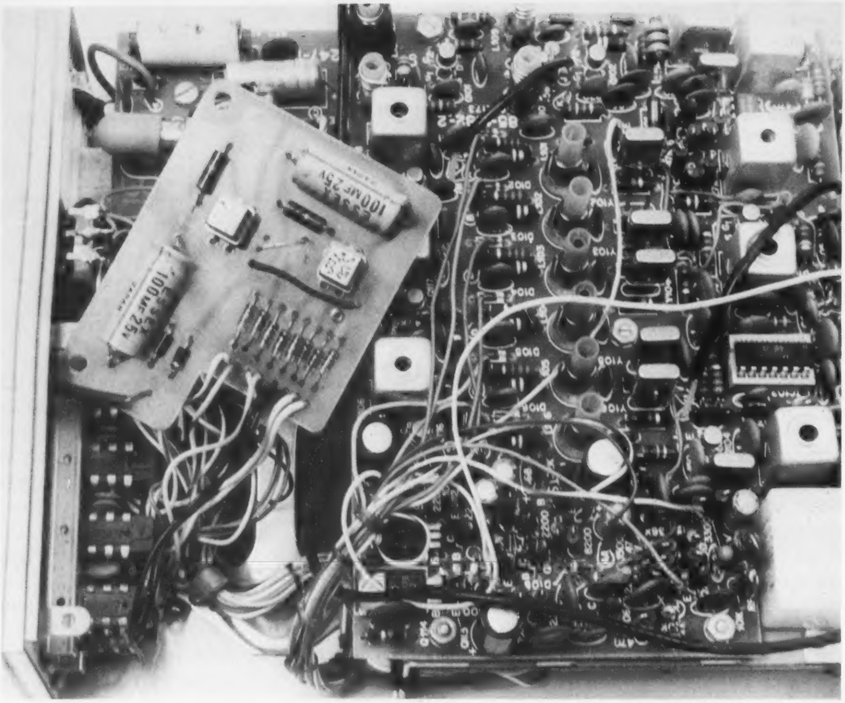

Photo D. Channel-change relay circuit board. The ungrounded side of the circuit pokes through the plastic filler where the burst encoder push-buttons would be located.

tors and diodes. Power supply requirements for other versions will probably be different depending on what relays the junk box and local surplus outlet may yield. Switch S1 turns on the power to the radio when switching the controller off so that the radio can be used in a normal fashion.

Construction

As can be seen by the photos, I mounted all components on a piece of wood. While this method of construction is simple and effective, it is not terribly attractive. I plan to reconstruct the unit in a 3″×10″×17″ chassis mounted on a 3½″×19″ relay rack panel. Layout is not critical.

Modification of the telephone consists of removing the bells to make room for a terminal strip on which to mount the added resistor and capacitor. See Photo C. The handset must be changed to a push-to-talk type (available from Graybar Supply, 345 Harrison Avenue, Boston MA 02118, and from Fair Radio Sales, previously mentioned). The resistor-capacitor-switch combination can be inserted anywhere in the dc current loop.

The channel-change relay circuit board (Photo D) was etched using a Radio Shack etch resist pen and etchant. The board is simple enough that no fancy techniques are required. Foil layout will vary depending on your radio and the relays you can find. The ungrounded side of the channel-change circuit clips to the wire poking through the plastic filler where the burst encoder would go. This can be seen in Photo A.

Cables between the controller and the radio should be only a few feet long because of the high-impedance microphone circuit. Run a separate return lead for the channel-change circuit. Otherwise, the return current will flow on the microphone cable sheath resulting in transmitted hum.

The 12-volt dc leads should be fairly heavy to carry the 2.5 Amperes or so required on transmit. The push-to-talk lead goes into the microphone connector with the microphone cable. Make the speaker connection to the remote speaker outlet and throw the speaker switch on the radio.

The connection between the telephone and the controller is a single pair of telephone wires, typically number 19. I use about 150 feet of ordinary telephone wire, but distances up to one-half mile or possibly more should work. The limiting factor will probably be getting the push-to-talk relay to operate properly due to additional resistance of the phone line.

Adjustments and Operation

The first adjustment is to set the variable resistor in the 35-volt portion of the power supply. Start by setting it for maximum resistance. Then with the push-to-talk button on the telephone pressed, decrease the resistance until K3 picks up. Note the position of the resistor shaft. Releasing the button should cause the relay to drop out. If it doesn't, the push-to-talk relay you've selected must be replaced with a different type with a higher drop-out voltage. Assuming your relay did drop out, continue decreasing the resistance while pressing and releasing the button. Note the point where the relay will no longer drop out. Set the variable resistor midway between this point and the point where the relay first picked up.

Setting the transmit level can be done several ways. The ideal way would be to use a deviation meter. Barring that, connect a VTVM set for ac to the microphone connector terminals at the radio. Note the level range for normal speech while using the radio's microphone. Now disconnect the microphone and connect the controller. Adjust the transmit level on the controller for a similar range while speaking normally into the telephone microphone. A third possibility would be to use on-the-air reports.

Once you've gotten everything working, operation is very simple. Lift the telephone receiver and dial a two for the channel selected on the radio switches, a three, a four, or a five for the specific channels you've chosen. You'll need to set the volume for a comfortable level in the telephone receiver. By switching the power supply to the off position, reconnecting the microphone, and switching back to the internal speaker, the radio is restored to normal operation including the channel selector switches.

We accept VISA, MC,
C.O.D., CHECK or M.O.

FIRST QUALITY COMPONENTS – NOT MAIL ORDER "SECONDS"

Min. order $10.00 - add
5% Shpg and $1.00 Ins

ARIES ZERO INSERTION FORCE SOCKETS -

cam actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets, including wire wrap.

Stock No.	No Pins	1-24	25	50
11055	24	$ 4.35	$ 3.90	$ 3.60
11056	28	4.50	4.05	3.75
11057	40	5.95	5.35	4.95
11058	64	10.50	9.45	8.70

RESISTOR ASSORTMENT 82508 - 700 pcs. (1 each below assort'd.) $22.50

Stock No. 82501 10 ea. of 10-12-15-18-22-27-33-39-47-56 OHM
Stock No. 83502 10 ea. of 68-82-100-120-150-180-220-270-330-390 OHM
Stock No. 82503 10 ea. of 470-560-680-820-1K-1.2K-1.5K-1.8K-2.2K-2.7 OHM
Stock No. 82504 10 ea. of 3.3K-3.9K-4.7K-5.6K-6.8K-8.2K-10K-12K-15K-18K OHM
Stock No. 82505 10 ea. of 22K-27K-33K-39K-47K-56K-68K-82K-100K-120K OHM
Stock No. 82506 10 ea. of 150K-180K-220K-270K-330K-390K-470K-560K-680K-820K-OHM
Stock No. 82507 10 ea. of IM-1.2M-1.5M-1.8M-2.2M-2.7M-3.3M-3.9M-4.7M-5.6M-OHM

$3.95 each for any assortment

WILD ROVER

Touch switch capsule.
Operating motion is .005" without the use of a levered arm. Extremely fast on and off with low noise. Normally open - rated 115 VAC, 1.6 amp-30 milliohm resistance - .615 radius by .160 thick.

Stock No.	1-9	10	25
12098	$ 1.28	$ 1.12	$ .95

60/40 ROSIN CORE SOLDER

Stock No	Dia	Length (feet)	Weight (oz.)	Price
50075	062	9	1.5	$1.16
50076	062	25	4	2.39
50077	062	50	8	4.25
50078	032	33	1.5	1.31
50079	032	88.5	4	2.47
50080	032	175	8	4.57

TI WIRE WRAP SOCKETS

Tin plated phosphor bronze contact - 3 wrap

Stock No.	No Pins	1-24	25	100
11301	8	$ .45	$ .40	$ .36
11302	14	.66	.59	.54
11303	16	.72	.64	.58
11304	18	.82	.73	.66
11305	20	1.11	.99	.90
11306	22	1.26	1.12	1.02
11307	24	1.41	1.25	1.14
11308	28	1.71	1.52	1.38
11309	40	2.31	2.05	1.86

TI LOW PROFILE SOCKETS

Tin plated phosphor bronze contact pins with gas tight seal

Stock No.	No Pins	1-24	25	100
11201	8	$.15	$.13	$.12
11202	14	.18	.15	.14
11203	16	.21	.18	.16
11204	18	.24	.21	.19
11205	20	.27	.24	.21
11206	22	.30	.28	.23
11207	24	.33	.30	.25
11208	28	.38	.34	.29
11209	40	.53	.45	.40

ELPAC POWER SUPPLIES - DC/DC CONVERTERS

SINTEC Stock No 300 MW Type	ELPAC No	Input Voltage (VDC)	Output Voltage (VDC)	Output Current (MA)	Dimensions (HxWxD) in Inches	Price
13825	CB3801	3.0-7.0	12±0.6	0-25	48x.51x3.05	$ 7.95
13826	CB3811	3.0-7.0	12±0.6	0-25	48x.51x3.05	7.95
13827	CB3802	3.0-7.0	15±0.7	0-20	48x.51x3.05	7.95
13828	CB3812	3.0-7.0	15±0.7	0-20	48x.51x3.05	7.95
13829	CB3804	3.0-7.0	28±0.7	0-10	48x.51x3.05	7.95
13830	CB3814	3.0-7.0	28±0.7	0-10	48x.51x3.05	7.95
1.5 W TYPE:						
13831	CL3801	4.0-7.0	12±0.6	125	651x1.2x1.77	$24.95
13832	CL3811	4.0-7.0	12±0.6	125	651x1.2x1.77	24.95
13833	CL3802	4.0-7.0	15±0.7	100	651x1.2x1.77	24.95
13834	CL3812	4.0-7.0	15±0.7	100	651x1.2x1.77	24.95
13835	CL3804	4.0-7.0	28±1.4	50	651x1.2x1.77	24.95
13836	CL3814	4.0-7.0	28±1.4	50	651x1.2x1.77	24.95
13825-1 DATA SHEET FOR DC/DC CONVERTERS						.25

Stock No. 13801- "Floppy Disc" Power Supply For Winchester Drives $109.00

13801-1 Data Sheet for 13801 $ .25

Special of the Month!

MEMORY SALE!

4116-3	200NS 16K Dynamic Ram Stock No. 47650	$2.10 ea.	8/$15.52
2114-L-3	300NS 4K Static Ram Stock No. 47640	$2.45 ea.	8/$17.84
2716	450NS 16K Eprom Stock No. 47632	$3.90 ea.	Any Quantity!

MODUTEC

Miniclamp AC Volt-Ammeter
allows singling one conductor out of many without disarrangement.

SET of THREE $99.00

Stock No.	AC Amperes	Price
13730	0-25A	$39.50
13731	0-50A	39.50
13732	0-100A	39.50

ACCESSORY LINE SPLITTER
allows fast readings of AC power consumption of plug in equipment without separation of leads.
Stock No. 13727 $9.95

POCKET SIZED BATTERY TESTER
for all types of small batteries from 1.35v to 4.5v
Stock No. 13733 $13.95

VOLT-I-CATOR
automotive diagnostic meter plugs into lighter socket and indicates battery condition and charging rates.
Stock No. 13736 $15.95

AC VOLTAGE TESTER
plugs into any 110v service receptable to check time voltage over 50-150 VAC
Stock No. 13735 $14.95

VOM-MULTITESTER
versatile Volt-Ohm-Milliammeter in small package
Stock No. 13729 $13.95

ELPAC POWER SUPPLIES - SOLV SERIES FULLY REGULATED

SINTEC Stock No.	ELPAC Part No.	Output Voltage	Output Current Rating	Dimensions (HxWxD) in Inches	OVP	Price
13802	SOLV15-5	5	3.0A	4-7/16x4x2	Fixed included	$39.95
13803	SOLV15-12	12	1.5A	4-7/16x4x2	Fixed included	39.95
13804	SOLV15-15	15	1.2A	4-7/16x4x2	Fixed included	39.95
13806	SOLV15-24	24	0.75A	4-7/16x4x2	Fixed included	39.95
13808	SOLV30-5	5	6.0A	5-5/8x4-7/8x3-3/16	OVP-4	59.95
13809	SOLV30-12	12	4.0A	5-5/8x4-7/8x3-3/16	OVP-4	59.95
13810	SOLV30-15	15	3.3A	5-5/8x4-7/8x3-3/16	OVP-4	59.95
13812	SOLV30-24	24	2.0A	5-5/8x4-7/8x3-3/16	OVP-4	59.95
13802-1	Data Sheet for SOLV Series					.25

PIN FORMING TOOL

puts IC's on their true row to row spacing. One side is for .300 centers. Flip tool over for devices on .600 centers. Put device in tool and squeeze.

ONE TOOL DOES 8 Thru 40 PINS!
Stock No. 11059 $12.95

OK MACHINE AND TOOL

IC INSERTION/ EXTRACTION KIT
Includes DIP IC extractors and inserters to accommodate all ICs from 14 to 40 pins. Tools that engage conductive surfaces are CMOS safe and include grounding lugs. Stock No. 13309 $37.74

SOCKET WRAP ID
DIP socket-sized plastic panels with numbered holes in pin locations. Slip onto socket before wire wrapping to identify pins. Also write on them for location, IC part number, function, etc. Simplifies initial wire wrapping, troubleshooting and repair

13295 - 14 pin
13296 - 16 pin
13297 - 18 pin
13298 - 20 pin
13299 - 22 pin
13300 - 24 pin
13301 - 28 pin
13302 - 40 pin
13303 - 96 pin

$1.82 per pack of 10

IC EXTRACTOR
One-piece, spring steel construction. Will extract all LSI, MSI and SSL devices with 8 to 24 pins. Stock No. 13313 $2.10

SINTEC CO.
Drawer Q Milford
NJ 08848-9990

VISA MasterCard

TOLL 800-526-5960
FREE in NJ (201) 996-4093

✓112
Send for Free Catalog - over 1100 parts.

Afterthoughts

If you don't mind running extra conductors between the controller and the radio, it would be simpler to run separate conductors for each channel rather than to use the relay switching scheme. The 6.3-volt winding wouldn't be required on the power transformer and there would be no concern about transmitting hum from the channel-change circuit. Also, more channels could be dialed.

Some stepping relays available from surplus outlets have more than 20 positions. All positions could be used by dialing digits that add up to the desired position minus one. For instance, to step to position 19 you would dial "99", "80", or "08".

The output of a dial-tone generator could be connected to position one of section one of the stepping relay.

You might leave power connected to the radio at all times and have a tone-dial decoder on the audio output ring a bell. Fellow hams can then reach you by using their tone-dial pads without you having to monitor the channel. Position one of section three of the stepping relay would select the appropriate channel.

Conclusions

I've described a system that will dial up channels remotely in a two-meter FM radio using a standard dial telephone. With it you can place as many remotes as you want at considerable distance from the radio on a single pair of wires. It has been in everyday operation. I've also offered some ideas for expansion to include other services. With this system as a basis, use your imagination and you can develop a great system to suit your own needs.■

WHEN YOU NEED JUST
A LITTLE MORE AUDIO

The FASTRAK® model 2003 audio amplifier module produces 250 mW of low THD audio. This transformerless design has a low parts count and does not require a heatsink.

The model 2003 features a dc-operated volume control. Output level is selected by changing a dc voltage with an on-board pot, remote pot or micro-computer D/A interface.

▶ Low-Z, ac-coupled output drives speaker or headphones.
▶ Dc-type volume control assures hum-free operation without using shielded cable to the volume control.
▶ No interstage transformers or heatsinks.
▶ Compatible with other FASTRAK® modules, such as the model 2002 sound synthesizer.
▶ One evening assembly using 3.6 by 1.0 inch pc board and instructions supplied.
▶ Price: $9.45

Price includes: glass-epoxy, etched, plated, drilled pc board; instruction manual; postage in U.S.A. (Ohio residents add 5% sales tax).

Send $1.00 for illustrated FASTRAK® product catalog and refund coupon.

P E I
PROHAM ELECTRONICS INCORPORATED
34620 LAKELAND BLVD EASTLAKE OH 44094
(216) 951-2110
✓199

SANTEC
ST-144/µP
M1
M2
M3
SCAN
M4
M5
M6
M7
M8
M9
SET
M0
MW
M
LOCK
OFF ON
SPX DPX
FREQ CLK
LAMP
OFF ON
+ M1 −
M-SET
OFF ON

You've got to get a Santec to get it right!

Compare Santec to anything you like, and you'll see — you've got to get a Santec to get: ■ memory channels which store standard repeater offsets for instant recall ■ less than 10 ma drain in receive to conserve power while you're monitoring ■ extremely wide power options of 0.1 W, 1.0 W or even 3.5 W for varying conditions ■ an accurate 24 hour clock for instant reference ■ and a full two year extended service plan which no one else will match.

When you get a Santec, you also get: ■ the widest frequency range of any handheld ■ odd offsets other than ± 600 kHz ■ variable step sizes in bandscan ■ a 500 ma battery with charger ■ a full six digit back-lighted LCD display for full frequency readout plus the memory channel number ■ the easiest keyboard entry of any handheld ■ eight modes of scan, search, manual control and open scan ■ the ability to change batteries without losing memory data ■ easily programmable bandscan ■ a frequency lock switch on the keyboard ■ an automatic low battery indicator ■ and much more.

FEATURE	SANTEC ST-144	YAESU FT-208	KENWOOD TR-2500
Size (mm)	68 x 170 x 47	61 x 168 x 49	66 x 168 x 40
Weight with Batt.	600 gm	720 gm	540 gm
Readout	LCD (full 6 digits)	LCD (4 digits)	LCD (4 digits)
Memory Channels	10	10.	10
Memory of Offsets	YES	NO	NO
Memory Backup	YES, Capacitance	Yes, Lithium Batt.	Yes, Lithium Batt.
Search Mode	YES	NO	NO
Step Size	5-100 kHz	5 or 10 kHz only	5-30 kHz
Battery	Quick Change Pack 500 ma-hr, 9.6 V	Quick Change Pack 450 ma-hr, 10.8 V	Slide-on Pack 400 ma-hr, 8.4 V
Frequency Coverage	142-148.995 Tx (149.995 optional) 142-149.995 Rx	143.5-148.495 Tx Rx	143.9-148.995 Tx Rx
Power (max)	3.5 W High 1.0 W. Med. 0.1 W Low	2.5 W High 0.2 W Low	2.5 W High
Priority	YES (in Mem Scan)	Yes (Priority Ch.)	NO
Clock	YES	NO	NO
Computer Current Saver	YES (10 ma)	NO (20 ma)	NO (27 ma)
Display	6 Digits + Mem. #	4 Digits + Mem. #	4 Digits

New! Affordable Price! See your Authorized Santec Dealer for details.

Competitors' specifications were obtained from published specifications sheets, and they are subject to change without notification to Santec or Encomm, Inc.

Shown with optional SM-3 speaker microphone.

Accessories for SANTEC Handheld Radios
clockwise from upper left
Leather Case (ST-LC)
Base Charger & Power Supply (ST-5BC)
Remote Speaker (MS-50S)
Mobile Charger (ST-MC)
Speaker Microphone (SM-3)

The ST-144/µP is approved under FCC Part 15

SANTEC™

© 1982, Encomm, Inc.
2000 Avenue G, Suite 800, Plano, Texas 75074
Phone (214) 423-0024 • TLX 79-4783 ENCOMM DAL
Repairs, Parts & Service Available

Export orders invited.

All stated specifications are subject to change without notice or obligation.

Encomm, Inc.
2000 Avenue G
Suite 800
Plano TX 75074

Please send me more information about:
☐ The ST-144/µP
☐ Authorized SANTEC Dealers

NAME ____________ CALL ______
ADDRESS ____________
CITY ____________ STATE ____ ZIP ____

YOU MAY SEND A DUPLICATE OF THIS FORM.

YES! I'd like to give 73 Magazine for the holidays. (12 issues—$19.97).

☐ Check enclosed

☐ MC ☐ VISA ☐ AE ☐ Bill me

Card# ____________________ Exp. date ____________________

Signature ____________________ Interbank # ____________________

Name ____________________

Address ____________________

City ____________________ State __________ Zip __________

Please enter a one year gift subscription to:

Name ____________________

Address ____________________

City ____________________ State __________ Zip __________

Canada & Mexico $22.97, 1 year only, U.S. Funds
Foreign $39.97, 1 year only, U.S. Funds Drawn on U.S. Bank

62DR6B

All Gift Subscriptions Begin with Jan. 1983 Issue.
73 Magazine•Box 931•Farmingdale, NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 73 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 Magazine
Box 931
Farmingdale, NY 11737

A. B. Reis K9XI
21 N. Caroline Street
Crystal Lake IL 60014

Improving God's IDer

Put more flexibility in the K2OAW circuit—and save the advantages of the original.

I have been a fan of Peter Stark's K2OAW IDer ever since the original design first graced these pages back in 1973. The simplicity of programming the thing, the low parts count requirement, and the lack of those hated Kernaugh maps made this, for me, the ideal IDer circuit. In the years since its first appearance, I have built maybe half a dozen of these circuits for my various repeaters and those of a few of my friends.[1]

With the advent of the FCC's decision to drop "R" calls for repeaters, regular

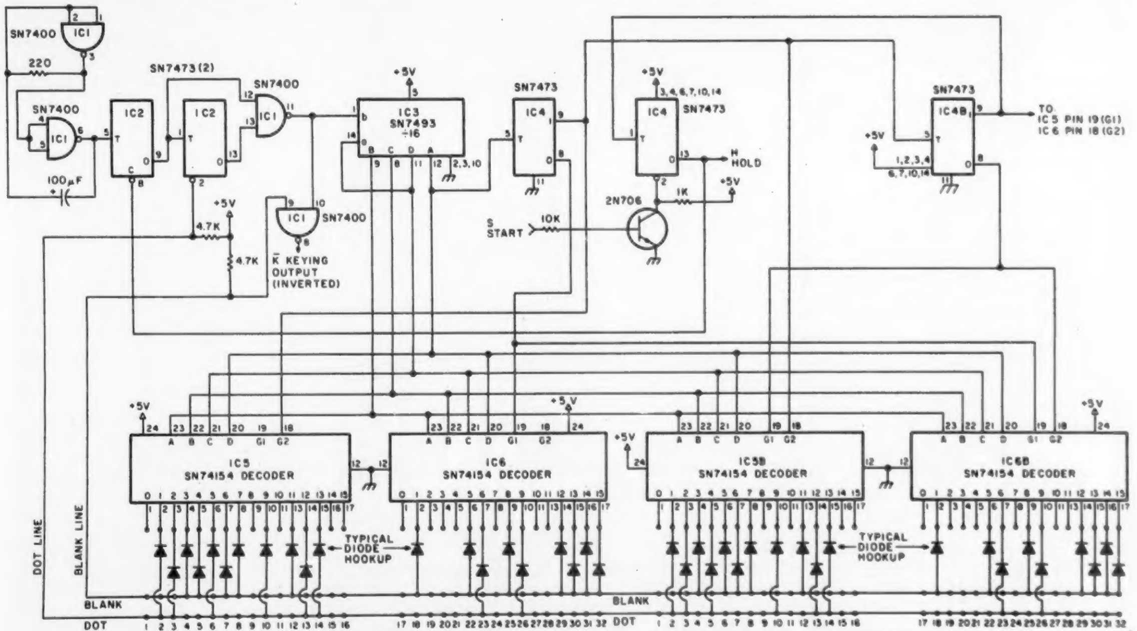
SN7400
IC1
220
SN7400
IC1
100μF
SN7473(2)
IC2
IC2
SN7400
IC1
+5V
IC3
SN7493
÷16
SN7473
IC4
+5V
IC4
SN7473
3,4,6,7,10,14
H HOLD
1K
+5V
2N706
S START
10K
SN7473
IC4B
+5V
1,2,3,4
6,7,10,14
TO
IC5 PIN 19 (G1)
IC6 PIN 18 (G2)
+5V
4.7K
4.7K
IC1
SN7400
K̄ KEYING OUTPUT (INVERTED)
+5V
IC5
SN74154 DECODER
+5V
IC6
SN74154 DECODER
+5V
IC5B
SN74154 DECODER
+5V
IC6B
SN74154 DECODER
TYPICAL DIODE HOOKUP
TYPICAL DIODE HOOKUP
DOT LINE
BLANK LINE
BLANK
DOT
BLANK
DOT
ORIGINAL CW ID'ER
ADDED CW ID'ER

Fig. 1. K2OAW ID circuit update as it appeared in 73 in June, 1979.

amateur callsigns, followed by "RPT" or "/R", have generally necessitated more character space than the old K2OAW circuit could provide. So, a couple of years ago, Peter obliged the troops with an update of that original design which doubled, from 32 to 64 characters, the amount of information available for use in the IDer.[2]

However, though a lot of us need more than 32 characters for our ID, we don't always need *all* 64 of 'em, particularly those of us who believe that a repeater ID should say its legal piece and shut up. So, for those who wish to keep the ID process from continuing long after the CW is gone and to save a lot of diodes for the blank line, I hereby propose the "K2OAW IDer Update Update." As you will see, the improvements cover a lot more than what I've talked about so far.

Fig. 1 is the K2OAW ID circuit update as it appeared in the June, 1979, *73*. Peter added just 3 ICs, a 7473 (IC4B), and two 74154s (IC5B and IC6B) to accomplish the doubling of capacity. I changed the "ID hold" half of the original 7473 IC4B to a 74C76 (C? Yeah. Read on.), now called Z11A, and added one more IC, Z8, a 74CO2 quad NOR gate. A 4001 would work just as well. To top things off, IC1A and IC1B, which comprised the clock oscillator in the original K2OAW circuit and its update, were scrubbed in favor of one half of an NE556 timer chip, running in the astable mode, with the other half being used for the ID audio oscillator. More on this later.

Fig. 2 shows how the two IC changes were implemented in the circuit. At the point in the ID where a stop bit is desired, two diodes are run to the appropriate pin on the 74C154 matrix, with one diode further connected to the dot line and the other attached to the blank line. The inputs of one gate of the 74CO2 (Z8B) are connected to the dot and blank lines. This gate actually functions as a negative logic AND gate. When this aforementioned stop pin pulls both lines low together, the output of Z8B goes high.

This output is sent to two places, the "zero set" pins of Z3, which heretofore were grounded, and an inverter made from Z8A. Bringing the zero set pins on Z3 high sets all of its BCD outputs low. Grounding them allows the IC to operate normally.

The output of inverter Z8A feeds the "set" input on one half of the 74C76, Z11. A momentary low on this pin drives the $\overline{Q}$ output (also known as the ID hold line) low, halting the ID process in its tracks.

Z7A, half of the NE556, replaced IC1A and IC1B in the old circuit because the 556 is a much more reliable circuit, in my experience. The other half of the 556 is used in the astable mode as the ID tone generator.

IC1A and IC1B are not wasted, however. IC1B, now Z1B, is used to replace Q1, a 2N706 from the original ID circuit. It is connected as an inverter between the start line and the clear input of the 74C76. IC1A, now Z1A, is also used as an inverter, the input

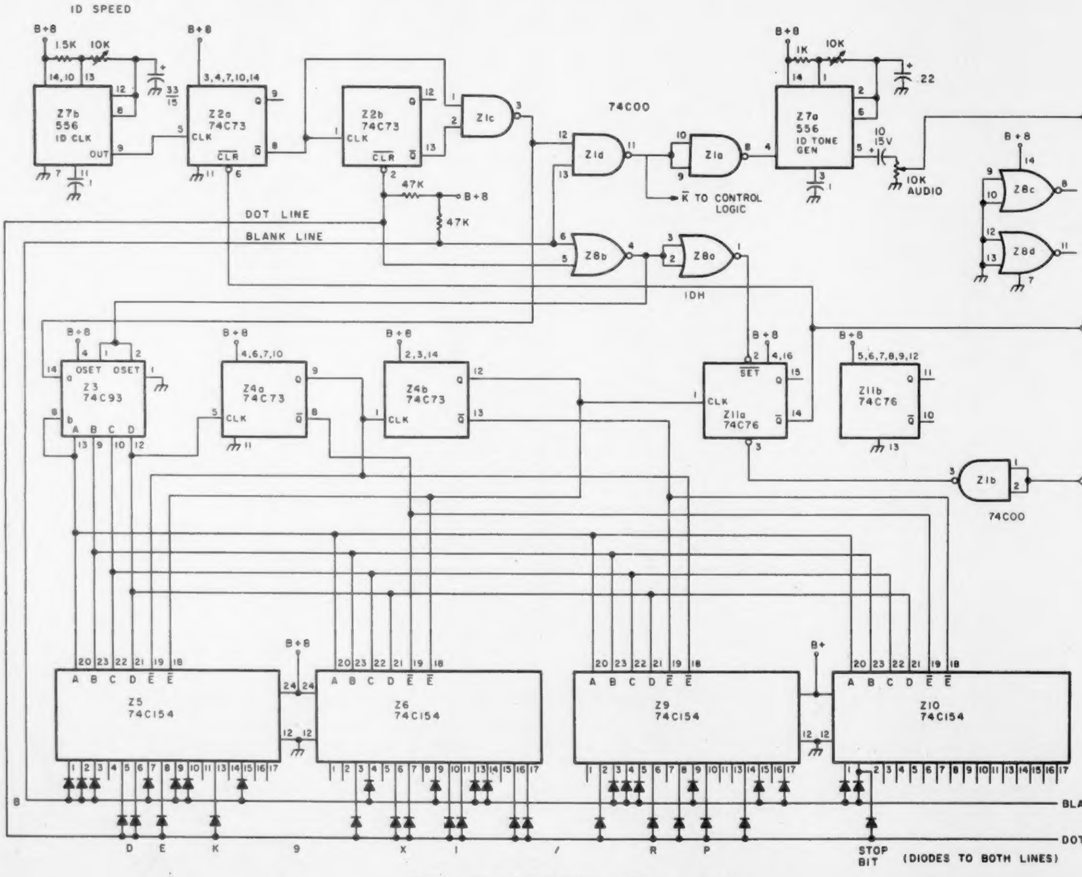
ID SPEED
B+8
1.5K
10K
33/15
Z7b 556 ID CLK
Z2a 74C73
Z2b 74C73
Z1c
74C00
Z1d
Z1a
K̄ TO CONTROL LOGIC
Z7a 556 ID TONE GEN
22
10 15V
10K AUDIO
AUDIO OUT
Z8c
Z8d
47K
DOT LINE
BLANK LINE
Z8b
Z8a
IDH
ID HOLD
Z3 74C93
0SET
Z4a 74C73
Z4b 74C73
Z11a 74C76
Z11b 74C76
Z1b
S ID START
74C00
Z5 74C154
Z6 74C154
Z9 74C154
Z10 74C154
B+
D
E
K
9
X
I
/
R
P
STOP BIT
(DIODES TO BOTH LINES)
BLANK LINE
DOT LINE

Fig. 2. The K2OAW update update.

TERMINALL

apple* + TRS-80*

APPLE REVIEW WINDOW

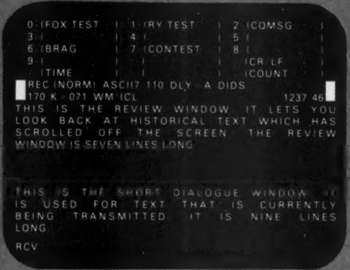

```
0 (FOX TEST    | 1 (RY TEST    | 2 (COMSG     )
3 (            | 4 (           | 5 (          )
6 (BRAG        | 7 (CONTEST    | 8 (          )
9 (            | (             |   (CR LF     )
/ (TIME        | (             |   (COUNT     )
REC (NORM) ASCII7 110 DLY  A DIDS
170 K - 071 WM ICL                       1237 46
THIS IS THE REVIEW WINDOW IT LETS YOU
LOOK BACK AT HISTORICAL TEXT WHICH HAS
SCROLLED OFF THE SCREEN THE REVIEW
WINDOW IS SEVEN LINES LONG

THIS IS THE SHORT DIALOGUE WINDOW IT
IS USED FOR TEXT THAT IS CURRENTLY
BEING TRANSMITTED IT IS NINE LINES
LONG
RCV
```

TERMINALL is a hardware and software system that converts your personal computer into a state of the art communications terminal. Terminall features simple connections to your computer and radio plus sophisticated and reliable software.

Simplicity

TERMINALL was designed from the outset to be easy to connect to your radio and easy to use. Plug into your receiver headphone jack and copy Morse Code or radioteletype (RTTY). Plug into your CW key jack and send Morse Code. Attach a microphone connector and send Baudot or ASCII RTTY using audio tones (AFSK). That's all there is to hooking it up.

The software is loaded into your computer from disk or cassette. Enter your callsign and the time and you will start receiving immediately. No settings or adjustments are necessary to receive Morse Code, it's fully automatic -and it works! You may type your message while receiving or transmitting.

You will be on the air, receiving and transmitting in any mode, in minutes. As we said, TERMINALL is simple.

More for your money.

- TERMINALL has the RTTY terminal unit - demod and AFSK - built in. This results in a lower total cost.
- **Fantastic Morse reception.** Six stage active filter demodulator copies the weak ones. Auto adaptive Morse algorithm copies the sloppy ones. Received code speed displayed on status line.
- **Outstanding documentation.** Professionally written, 90 page user manual contains step-by-step instructions.
- **Built in, separate, multi-stage, active filter RTTY and CW demodulators.** No phase lock loops. RTTY demodulator has 170 and either 425 or 850 Hz shift-keyboard selectable - and uses either the panel meter or scope outputs for easy tuning. Copy the weak ones. Copy the noisy ones. Copy the fading ones.
- **Built in crystal controlled AFSK.** Rock stable for even the most demanding VHF or HF applications. A must on many VHF RTTY repeaters.
- **Built in 110 or 220** volt AC power supply.
- **Built in parallel printer driver software.** Simply attach a parallel ASCII printer (e.g. the EPSON MX-80) to your printer port to obtain hardcopy in all modes.
- **Multi level displays** - allows examining and editing of historical text.
- **Word wrapping,** word mode editing, diddle, ignore carriage returns, user programmable end of line sequence, adjustable carriage width, multiple user-defined WRU, transmit delay (fixed, none or auto adaptive), break mode and more!

TRS-80 NORMAL DISPLAY

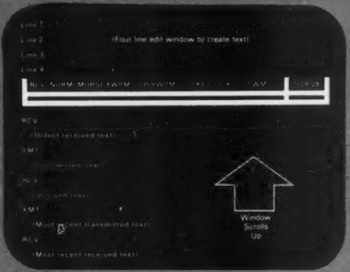

```
Line 1
Line 2              (Four line edit window to create text)
Line 3
Line 4
RCV
  (Oldest received text)
XMT
  (Transmitted text)
RCV
  (Received text)
XMT
  (Most recent transmitted text)
RCV
  (Most recent received text)
```

- **The all-in-one TERMINALL design** makes it great for use on HF or VHF, Ham, Commercial, SWL or MARS! SWL's: TERMINALL may be jumpered for either 425 or 850 Hz reception to copy news and weather services.

15 Day Money Back Trial Period on Factory Direct Orders

System Requirements

TERMINALL T1 Communications terminal for the TRS-80 Model I. Requires a Model I TRS-80, 16K RAM and Level II BASIC. Includes software on cassette and disk, assembled and tested hardware and an extensive instruction manual. **$499.**

TERMINALL T3 Communications terminal for the TRS-80 Model III. Requires a Model III TRS-80, 16K RAM and Model III BASIC. Includes software on cassette and disk, assembled and tested hardware and an extensive instruction manual. **$499.**

TERMINALL T2 Communications terminal for the APPLE II. Requires an APPLE II or APPLE II PLus with 48K RAM and disk. Software is provided on disk in DOS 3.2 format, Use MUFFIN utility to convert to DOS 3.3 format. Includes software on disk, assembled and tested hardware and an extensive instruction manual. **$499.**

Add $4.00 shipping U.P.S. reg. delivery - CA residents add 6% sales tax.

TO ORDER (209) 634-8888 or 667-2888

We are experiencing telephone difficulties. Please keep trying.

MACROTRONICS, inc.®
1125 N. Golden State Blvd.
Turlock, California 95380

✓44

master charge

VISA

***TRS-80 is a Registered Trademark of Tandy Corp.**
***Apple is a Registered Trademark of Apple Computer Inc.**
***Atari is a Registered Trademark of Atari Computer Inc.**
1 yr. parts & labor limited warranty.

FREE!

TO TERMINALL
T1 & T3 OWNERS
UPDATE TO DISK
VERSION 2.0

Adds save to Disk & more. Reg. $20.00. Send original distribution disk. We pay return postage. Offer expires 12-31-82

The communications terminal that does it all!

HAL'S CHRISTMAS SPECIALS

HAL 2304 MHz DOWN CONVERTERS (FREQ. RANGE 2000/2500 MHz)
2304 MODEL #1 KIT BASIC UNIT W/PREAMP LESS HOUSING & FITTINGS $19.95
2304 MODEL #2 KIT (with preamp) $29.95
2304 MODEL #3 KIT (with High Gain preamp) $39.95

MODELS 2 & 3 WITH COAX FITTINGS IN & OUT AND WITH WEATHER-PROOFED DIE CAST HOUSINGS

BASIC POWER SUPPLY $19.95
POWER SUPPLY KIT FOR ABOVE WITH CASE $24.95
FACTORY WIRED & TESTED $34.95

ANTENNAS & OTHER ACCESSORIES AVAILABLE. SEND FOR MORE INFO.

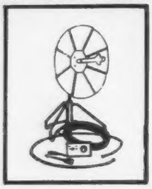

2100-2500 MHZ

*HMR-II COMPLETE UNIT
COMPLETE SYSTEM AS SHOWN. *NOT A KIT*. INCLUDES A PC BOARD, POWER SUPPLY, CABLES & CONNECTORS—PRE-ASSEMBLED AND TESTED. 24dB GAIN OR GREATER.
1 UNIT........ $149.95
2 UNITS........ $139.95 ea.
3 OR MORE UNITS........ $129.95 ea.
*HAM MICROWAVE RECEIVER

PRE-SCALER KITS

HAL 300 PRE .... (Pre-drilled G-10 board and all components) $14.95
HAL 300 A/PRE .... (Same as above but with preamp) $24.95
HAL 600 PRE .... (Pre-drilled G-10 board and all components) $29.95
HAL 600 A/PRE .... (same as above but with preamp) $39.95

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 × 5-1/2 INCHES. HAS 12 LINES OUT. ONLY $39.95

NEW—16 LINE DELUXE DECODER $69.95

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT UTILIZING THE NEW ICM 7206 CHIP PROVIDES BOTH **VISUAL** AND **AUDIO** INDICATIONS! COMES WITH ITS OWN TWO-TONE ANODIZED ALUMINUM CABINET MEASURES ONLY 2¾"x3¾" COMPLETE WITH TOUCH-TONE PAD. BOARD, CRYSTAL, CHIP AND ALL NECESSARY COMPONENTS TO FINISH THE KIT. **PRICED AT $29.95**

NEW—16 LINE DELUXE ENCODER $39.95

HAL ECD—16 LINE DELUXE ENCODER INCLUDES PC BOARD, ALL PARTS & CASE $39.95

HAL ECD—12 LINE DELUXE ENCODER COMPLETE WITH PC BOARD, ALL PARTS & CASE $29.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK $16.95

ACCUKEYER—MEMORY OPTION KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER. IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY $16.95

BUY BOTH THE MEMORY AND THE KEYER AND **SAVE**
COMBINED PRICE ONLY **$32.00**

PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (−3dB POINTS). 19 dB GAIN
FULLY ASSEMBLED AND TESTED $8.95

HAL-PA-1.4 WIDE BAND PRE-AMPLIFIER, 10 MHz TO 1.4 GHz. 12dB GAIN
FULLY ASSEMBLED $12.95

NEW!

CLOCK KIT—HAL 79 FOUR-DIGIT SPECIAL—$7.95. OPERATES ON 12-VOLT AC (NOT SUPPLIED) PROVISIONS FOR DC AND ALARM OPERATION.

6-DIGIT CLOCK•12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND COMM. CATH. READOUTS, 13 TRANS., 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSHBUTTON SWITCHES AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA. WILL RUN OFF ANY 12-VOLT AC SUPPLY. **PRICED AT $12.95**

CLOCK CASE AVAILABLE AND WILL FIT ANY ONE OF THE ABOVE CLOCKS. REGULAR PRICE... $6.50 **BUT ONY $4.50 WHEN BOUGHT WITH CLOCK.**

SIX-DIGIT ALARM CLOCK KIT FOR HOME, CAMPER, RV, OR FIELD-DAY USE. OPERATES ON 12-VOLT AC OR DC, AND HAS ITS OWN 60-Hz TIME BASE ON THE BOARD. COMPLETE WITH ALL ELECTRONIC COMPONENTS AND TWO-PIECE, PRE-DRILLED PC BOARDS. BOARD SIZE 4" × 3". COMPLETE WITH SPEAKER AND SWITCHES. IF OPERATED ON DC, THERE IS NOTHING MORE TO BUY*
PRICED AT $16.95

*TWELVE-VOLT AC LINE CORD FOR THOSE WHO WISH TO OPERATE THE CLOCK FROM 110-VOLT AC **WHEN PURCHASED WITH CLOCK KIT $2.95**

SHIPPING INFORMATION: ORDERS OVER $25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN $25, PLEASE INCLUDE ADDITIONAL $2.00 FOR HANDLING AND MAILING CHARGES. SEND 20¢ STAMP FOR FREE FLYER.

DISTRIBUTOR FOR
Aluma Tower• AP Products
(We have the new **Hobby-Blox System**)

VISA

"HAL" HAROLD C. NOWLAND
W8ZXH

HAL-TRONIX
P. O. BOX 1101
SOUTHGATE, MICH. 48195
PHONE (313) 285-1782

✓31

connected to the $\overline{K}$ (keying) line, and the output connected to the reset pin of Z7B, keying the tone for the ID. The $\overline{K}$ line is still used for logic purposes.

The remaining two gates of Z8 are not used in this design and their inputs are grounded. Don't forget to tie all inputs of the other half of the 74C76 high. Leave the outputs floating.

Although this circuit adds 2 ICs to the design, it subtracts one transistor, and if your ID is short enough, you may be able to leave out Z10 as well, thus saving that expense. And you get a tone generator, a more reliable clock, and other improvements in the bargain.

About the 74C series: I switched all of my TTL to CMOS/TTL (by National Semiconductor) some time back. The savings in current is worth it, and the voltage requirement is not finicky like TTL. I use 8 volts on all my CMOS and timers.

One *caveat*: The 74C ICs used here are pin-for-pin replacements for their TTL counterparts *except* for the 74C93. If you're planning to retrofit an existing circuit and convert your 7493 to CMOS, you will have to rewire that part of the circuit.

With these modifications, I feel that the K2OAW IDer is the ultimate ID circuit. If you have one in use now and update to the circuit described here, I think you'll agree that the best has been made better.■

References

1. Stark, "A Complete Repeater Control Circuit and ID," *73*, February and March, 1973.
2. Stark, "Update on the K2OAW ID Circuit," *73*, June, 1979.

Orbit

ORBIT is the Official Journal for the Radio Amateur Satellite Corporation (AMSAT), P.O. Box 27, Washington, DC 20047. Please write for application.

For a **FREE SAMPLE COPY** please send $1 to cover First Class Postage and handling to: Orbit, 221 Long Swamp Road, Wolcott, CT 06716.

YAESU FT-404R/TTP

450 MHz Hand-held with factory installed 16-button tone pad. Six crystal channels within a 3 mHz (tx) or 5 mHz (rx) spread; 430 to 450 MHz. 2.5w or 200mw output. NiCad pack, wall charger, flex antenna, case, strap, earphone & 446.0 mHz crystals. 7¼"h × 2⅝"w × 2¼"d, 1 lb..... *Regular $325*

Closeout - $\$189^{95}$

Crystal Certificates: (2/channel required) are **$5.00** each when purchased **WITH** FT-404R/TTP; purchased later, **$8.00** each.

FT-404R/TTP accessories:

NC-1A	15-hr drop-in charger............	**Sale** $44.95
NC-3A	Drop-in chgr/AC adaptor	**Sale** 79.95
FBA-1	Battery sleeve for NC-1A/3A..................	8.00
FNB-1	Extra NiCad battery pack..................	23.00
NC-9B	Extra 15-hr wall charger..................	10.00
PA-2	Mobile DC-DC adaptor & charger	39.00
YM-24A	Speaker/microphone..................	39.00
FTS-32E	32 tone CTCSS encoder..................	40.00
FTS-32ED	32 tone CTCSS enc/dec	75.00
LCC-3	Leather carrying case	38.00
MMB-10	Mobile bracket..................	15.00

FT-107/DMS Package Deal

YAESU FT-107M/DMS (WARC) 9-band Dig. Transceiver. Covers 160-10m, incl. WARC bands. 240w DC input SSB & CW; 80w AM & FSK. 12 channel memory circuit with Digital Memory Shift (tunable). 13.5vdc @ 20A. 5"h × 13"w × 10"d, 27 lbs...................... **Regular $1149.00**

YAESU FP-107 Internal Power supply. 115/230 VAC, for base. Mounts inside FT-107M .... **Regular $139.00**

YAESU SP-107P Speaker/Patch. Ext. speaker & hybrid phone patch in matching cabinet .... **Regular $65.00**

TOTAL REGULAR PRICE - $1359.00

PACKAGE PRICE - $\$899^{95}$

KENWOOD TR-7850 2m FM Transceiver. 144-147.995 Mhz; **40 watts**; 15 memories; UP/DN mic; 13.8vdc/9A.

Regular $\$419^{95}$ - ***Closeout $\$329^{95}$***

DRAKE Theta 7000E/TR-930 Combination Closeout

Theta 7000E (alone) - **$\$689^{95}$**

DRAKE Theta 7000E Communications Terminal. Complete, automatic send/receive of Morse code CW, Baudot & ASCII code (RTTY) .... **Regular $1095***

DRAKE TR-930 9" Video monitor..... **Regular 185***

Regular Combination Price - $1280*

Combination Closeout Price - $\$799^{95}$

*DRAKE'S Suggested List Price

HAL OVERSTOCK SALE

(The Boss ordered too many!)

CT2100 Communications Receive Terminal

Regular $\$845^{00}$ - ***Special Sale $\$689^{95}$***

KB2100 Keyboard (companion to CT2100)

Regular $\$175^{00}$ - ***Special Sale $\$149^{95}$***

CWR6850 Telereader Terminal/5" CRT/keyboard

Regular $\$995^{00}$ - ***Special Sale $\$849^{95}$***

CWR6700 Telereader Receive only, portable reader

Regular $\$495^{00}$ - ***Special Sale $\$429^{95}$***

ICOM IC-290A 2m SSB/CW/FM Mobile Transceiver. 143.8-148 MHz; 10 watts; T/T mic; 13.8vdc/3.5A

Regular $549 - ***Closeout $\$399^{95}$***

YAESU FT-708R

440 Mhz UHF Hand-Held. 440-450 Mhz; 1 watt output. Keyboard entry of all frequencies and splits for non-standard repeaters. 4-bit CPU, LCD display, Up/Down scanning, priority, memory scan, memory back-up, 16 tone DTMF encoder. Flex antenna and Ni-Cd battery pack.

Special - $\$269^{95}$

FT-708R accessories:

NC-7	15-hr desk charger	$\$53^{95}$
NC-8	15/4-hr desk chgr/AC ps	89^{95}
LCC-8	Leather carrying case.....	35^{00}
FBA-2	Battery sleeve	6^{25}
FNB-2	Extra battery	29^{00}
NC-9B	Extra wall charger........	10^{00}
SSY-32/FTS-32	32-tone encoder	33^{00}
TS-32/FTS-32AE	Enc./decoder	75^{00}

KLM VHF/UHF POWER AMPLIFIERS

Factory Sealed, late model units with one Year Warranty, including output devices.

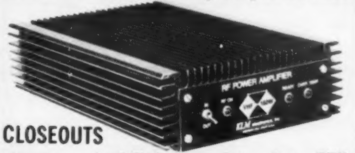

CLOSEOUTS

Model	Band/Mode	In	Out	Reg.	NOW
PA2-25B	2m FM	1-4w	25w	$ 99^{95}	$ 74^{95}
MA-35BL	2m FM/SSB	.1-4w	35w	129^{95}	99^{95}
PA10-170BL	2m FM/SSB	10w	170w	299^{95}	225^{95}
PA15-40BL	2m FM/SSB	5-15w	40w	149^{95}	112^{95}
PA15-80BL	2m FM/SSB	5-15w	80w	179^{95}	135^{95}
PA15-160BL	2m FM/SSB	5-15w	160w	269^{95}	199^{95}
MA-25BCL	220 FM/SSB	.1-4w	25w	129^{95}	99^{95}
PA45-120BC	220 FM	15-45	120w	279^{95}	209^{95}
PA4-40CL	450 FM/SSB	1-4w	40w	279^{95}	209^{95}
PA15-40CL	450 FM/SSB	5-15w	40w	199^{95}	149^{95}

RECEIVE PREAMPLIFIERS *(Regular $\$62^{95}$)*		NOW
PRA-50C	6m, 10 dB, 2.5 dB NF	$\$47^{95}$
PRA-144I	2m, 10db; for older KLM amps	47^{95}
PRA-144II	2m, 10db; for newer KLM amps....	47^{95}
PRA-220C	220 MHz, 15 dB......................	47^{95}

Echo 70 CM 432 Mhz SSB/CW Transceiver

Regular $\$449^{95}$ - ***Closeout $\$399^{95}$***

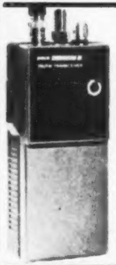

PACE Communicator MX

Compact, 2m hand-held FM Transceiver. 144-148 Mhz, 1 watt, 6 channels with 18 channel capability (6 simplex, 6 at +600 KHz, 6 at -600 KHz), 1 channel installed (146.52 simplex). Only one crystal per channel. Complete with flexible rubber antenna, nicad battery pack & charger. 2¾"w × 6⅛"h × 1¾"d, 16 oz

Closeout Price.. $\$119^{95}$

Crystal Certificates...... each $\$5^{00}$

TEN-TEC OVERSTOCK SALE

OMNI-C 9-band Digital Transceiver

Regular $1289 - ***Sale Price $\$899^{95}$***

ARGOSY 10/100w 6-band Transceiver

Regular $579 - ***Sale Price $\$449^{95}$***

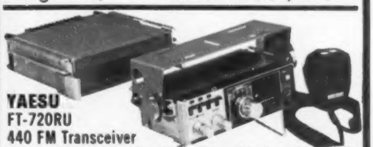

YAESU
FT-720RU
440 FM Transceiver

10w, 440-449.975 Mhz. Control head & detachable RF deck for remoting or use of optional **720RVH** 2m 25w RF deck. 13.8vdc/6½A; 6"w × 2"h × 10"d, 5½ lbs.

Regular $449 - ***Closeout $\$299^{95}$***

MasterCard

VISA

Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area)
1-800-242-5195

AMATEUR ELECTRONIC SUPPLY® Inc.

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES

WICKLIFFE, Ohio 44092
28940 Euclid Avenue
Phone (216) 585-7388
Ohio WATS 1-800-362-0290
Outside Ohio 1-800-321-3594

ORLANDO, Fla. 32803
621 Commonwealth Ave.
Phone (305) 894-3238
Fla. WATS 1-800-432-9424
Outside Florida 1-800-327-1917

CLEARWATER, Fla. 33515
1898 Drew Street
Phone (813) 461-4267
No In-State WATS
No Nationwide WATS

LAS VEGAS, Nev. 89106
1072 N. Rancho Drive
Phone (702) 647-3114
No In-State WATS
Outside Nevada 1-800-634-6227

Associate Store

CHICAGO, Illinois 60630
ERICKSON COMMUNICATIONS
5456 N. Milwaukee Avenue
Phone (312) 631-5181
Outside Illinois 1-800-621-5802

Paul Swearingen W9PJF
RR 1, Box 485
Benton IL 62812

The Bunesti Caper

The two British agents needed a power amp—fast. Could the American ham build one?

December 7, 1941, was a day of glory and achievement for the Japanese Empire because of the unbelievably effective attack upon military installations in Hawaii. In England, the long hoped-for involvement of America in the war now seemed assured. The "Day of Infamy," however, also brought a special sort of gloom and silence to one small segment of the American population—the amateur radio operators.

Photo A. The crew of Destiny Deb prior to its final combat mission to Ploesti, Rumania. (The little guy on the left in the front row is W9PJF.)

In the midwest that night, most of the ham bands were full of stations relaying the FCC announcement that all radio amateur activity was to cease immediately. It seemed that almost every ham in the country was trying to make as many contacts as possible that last night. I kept my 20-Watt AM rig (push-pull 45s modulated by 47s) going on 160 meters until well past midnight, but finally closed down when I got too sleepy to continue.

The next morning, I turned on my Howard 435A receiver and heard a couple of guys yakking away just as though the Pearl Harbor attack had never occurred. Naturally, I cranked up the rig and told them of the FCC notice. They claimed that my call was the first they had heard about it and that they thought their receivers had been "desensitized by a storm." Of course, I didn't believe them for even a second, but that short chat on 8 December 1941 was to be my last ham QSO until World War II was over.

As a normal, healthy, high-school senior, I had no illusions about what the future held for me. I was caught up in the tide of rising national indignation at the treachery of the attack and looked forward to becoming a member of our armed forces. I hoped that my great interest and skimpy skills in radio might be useful. They were, of course, but there was a time still about 2-1/2 years away in my future when they were useful in a way I could never have imagined.

After graduation from high school, I found that the Army Air Corps was glad to have my services, but they insisted that I go to Miami Beach for basic training. This was to introduce me to the finer points of the military organization, to teach me discipline and respect for authority, to enable me to distinguish between my left foot and my right foot, and to educate me in a host of related subjects such as KP, policing the area, saluting, scrubbing the barracks, why all relationships with females are dangerous, etc.

During my third day at basic, an announcement was made that all personnel who knew Morse code were to report to the administrative office at 1300 hours. I reported as ordered and was given a short code test that was sent at about 10 wpm. I don't think that I missed a letter, and the next day I was on a troop train bound for the radio school at Sioux Falls, South Dakota. In my hands were records showing that I had completed basic training (?) and a promotion order making me a PFC! Those long hours practicing code in order to pass the ham exam had finally paid off, since I avoided many miserable hours of close-order drill.

The Air Corps radio operator/mechanic school had a curriculum that covered basic theory, Morse code, and radio repair. It included an almost frightening amount of material in a very short time, but I was having a ball. The films, lectures, and demonstrations expanded and solidified my knowledge of the theories I had struggled with as a ham. The code classes were pretty much of a bore and I did not advance my speed very rapidly, but I did manage to pass 35 wpm. We were not allowed to use typewriters, however, so I felt that printing at 35 wpm wasn't too bad.

The practical part of the course was a snap, and I became reasonably proficient at the operation and maintenance of such items as the BC-221 frequency meter, BC-375 transmitter, BC-342 and BC-348 receivers, ARC-5-series HF transmitters and receivers, BC-610 transmitter, SCR-522 VHF transceiver, and miscellaneous aircraft electronic gear such as beacon receivers, the radio compass, interphone systems, etc. I was happy to be expanding my knowledge of electronics and was actually a bit sorry when I completed the course.

I declined an invitation to stay at Sioux Falls as an instructor and requested an assignment as a flight radio operator. Within a couple of days I was on another train, now enroute to Kingman, Arizona, this time to qualify as an aerial gunner. I spent some time on the train sewing on my new corporal stripes.

Gunnery school did not have the same fascination for me that I had felt at radio school. While all of the radio operators at gunnery school had to participate in weekly code practice sessions in order to maintain proficiency, I learned a lot more than I thought possible (or necessary) about the 50- and 30-caliber air-cooled machine guns, the 20 mm cannon, hydraulically- and electrically-operated gun turrets, and how to lead or lag moving targets in flight. We spent a few hours in the air shooting at airborne targets, but I enjoyed the skeet shooting part of the course most of all. We learned the basics of leading or lagging moving targets by shooting at clay pigeons from the back of a moving truck! On days off, we were encouraged to shoot regular skeet—the guns and ammo courtesy of Uncle Sam. After the moving truck training, the normal skeet seemed easy and I was soon 25 for 25 most of the time.

I was not sorry to finish the gunnery course although it had qualified me for the first "flight pay" of my life. I left Kingman as a brand new "Buck" Sergeant, and headed for a combat crew assignment at Tucson, Arizona.

It would take a whole

Photo B. Back in Italy just before returning to the USA, W9PJF points to the souvenir Rumanian Air Force pilot wings worn by "Charlie" Kourvelas, the tail gunner.

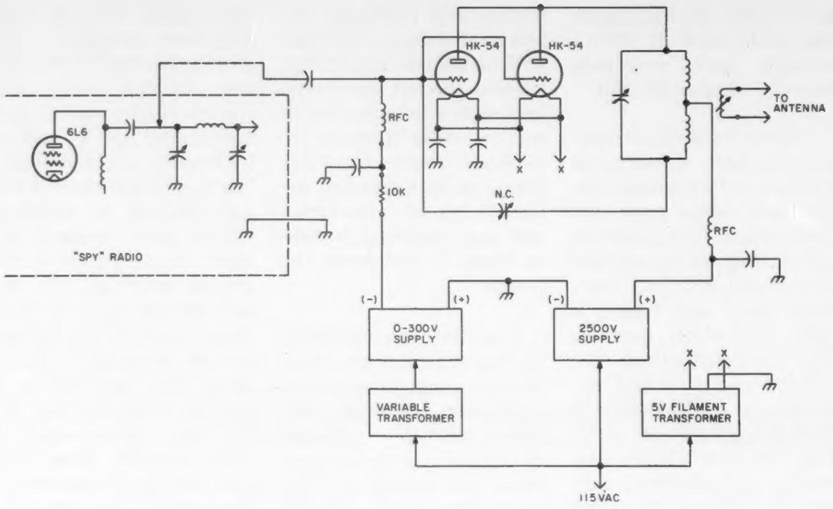

Fig. 1.

book to express my memories and feelings about our ten-man crew formed at Tucson. That crew became my family away from home, and a closeness developed between us that I have not experienced with any other group. Ten semi-trained civilians (four second lieutenants and six buck sergeants) became a reasonably competent crew for a B-24 Liberator, a heavy bomber. We soon were enroute overseas via Natal, Brazil, Dakar, West Africa, Marrakesh, and eventually to an austere base in southern Italy where our 450th Bomb Group joined the newly formed 15th Air Force.

I will always believe that aerial combat was at least as frightening as combat on the ground. Most of the time, our activities were conducted far inside enemy territory with the obvious risk of capture or death a long way from home base. We bombed a number of tough targets. We got shot at and were hit by fire from antiaircraft guns and fighter aircraft. We saw friends disappear in the cloud of an exploding aircraft, and we held back unmanly tears as corpsmen removed bodies from riddled airplanes. Our crew completed 34 missions with many close calls but with no physical wounds. Our flight engineer and I had been promoted to tech sergeant, and the other enlisted men now were staff sergeants. We were flying our third B-24, however: a nearly new one called *Destiny Deb*. Our first two aircraft had been totaled in crashes.

Our 35th mission was to bomb a target that was probably as well guarded as any in Europe. It was the oilfield/refinery complex at Ploesti, Rumania, which was a major source of petroleum products for the Nazi war effort. It was to be our second trip to Ploesti, and memories of the fighters and the intense antiaircraft fire were still fresh in our minds.

That mission turned out to be our last, as *Destiny Deb* was rocked by an enormous explosion just after we dropped our bomb load and while we were making a right descending turn to take up the return compass heading for Italy. An 88 mm shell had exploded between number two engine and the main fuselage, tearing a large hole in the fuselage and rupturing some fuel lines.

Only God knows why we were not immediately surrounded by flames. The number two engine quit immediately, and number three on the other side began to smoke. We fell well behind the squadron and obviously would soon be alone, an easy prey for any Luftwaffe fighters that saw our plight.

The Fates were again kind to us that day, however, and while the number one engine soon failed and power had to be reduced on number three, the old gal flew long enough for us to get well away from the target area. We realized that we would not see Italy very soon as reluctantly we parachuted out over open country near the small town of Bunesti, and soon we were uninvited and unwanted guests of the Rumanian government.

The life and times of a POW in that era cannot be described very well in a few sentences, but a great deal of my time was spent in planning what I might build as my postwar ham station. I was still constrained by my depression views, however, and my most grandiose design turned out to be a T-55 modulated by a pair of TZ-40s. For antennas, I considered the 8JK for 20 and 10 and perhaps a centerfed zepp for 80 and 40. Even the other radio operators in the Bucharest hospital POW camp considered my pages and pages of schematics to be a rather weird pastime.

The Allied invasion in June of 1944 gave quite a boost to our morale, and a spirit of cautious optimism began to spread. All that summer we treasured every scrap of information we could get about the Allied efforts in France. The Rumanians, however, were more concerned about their own future in view of the failures of the Nazi campaign in Russia.

The news of the war on the Eastern front reached us occasionally and, as the Russians advanced, our food improved measurably. The black bread was replaced by brown and the amount of meat in our thin stews seemed to be increased. The lieutenant in charge of our guards sometimes gave us copies of the local newspapers, and the rapid approach of the Russian troops to the Bucharest area was always a headline item. An aura of uncertainty and suspense appeared to envelope our captors and the element of fear could almost be felt. We heard rumors that British paratroopers had been captured, but it seemed hardly likely that any significant British airborne operation could be supported at this great distance from Italy.

One morning, an American major, accompanied by a Rumanian colonel and two men dressed in civilian clothes, entered our enlisted compound and asked if anyone had had any experience in building radio equipment. I explained my background in amateur radio and was told that two British agents had indeed parachuted into the area and that they needed a

Barry Electronics Corp.

WE SHIP WORLDWIDE

WORLD WIDE AMATEUR RADIO SINCE 1950

Your one source for all Radio Equipment!

Kitty Says: We Will Not Be Undersold! For **BEST VALUES** Call: **212-925-7000.** We Are The Hottest Li'l Ham House In Town. **For Orders Only Please Call: 1-800-221-2683.**

YAESU

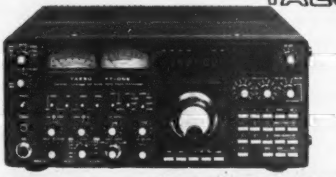

FT-ONE, FT-102, FT-101ZD, FT-707, FT-230R, FT-480R, FT-720RU, FT-290R, FRG-7700, FT-625RD

Land-Mobile H/T
Wilson Mini-Com II
Yaesu FTC-2203, FT-4703
Icom IC-M12 (Marine)
IC-H12

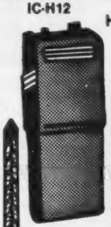

ICOM
IC2AT
IC3AT
IC4AT

SANTEC
HT-1200,ST-7/T
ST-144/UP

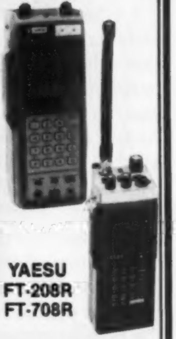

YAESU
FT-208R
FT-708R

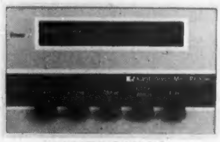

KANTRONICS
Mini-Reader Field Day
Code Tapes In Stock

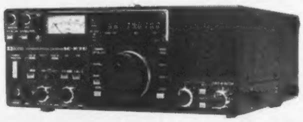

ICOM IC-R70, IC-720A, IC-730, IC-740, IC-25A, IC-251A, IC-2KL, IC-451A, IC-290H, IC-45A

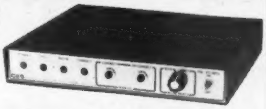

CES-Simplex Autopatch 510-SA Will Patch FM Transceiver To Your Telephone. Great For Telephone Calls From Mobile To Base. Simple To Use - $319.95.

DENTRON
Amplifiers,
Tuners &
Transceivers In
Stock

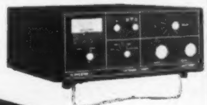

MFJ Keyboard

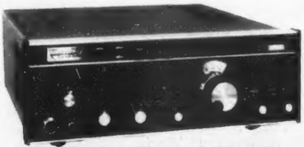

DRAKE TR-5, TR-7A, R-7A, L-7
L-15, Earth Satellite Receiver ESR-24
Digital Multimeter Model #8550-$95.00

MIRAGE
B-23, B-1016,
C-22 C-106,
D-24, D-1010

BIRD
Wattmeters &
Elements
in stock

EIMAC
3-500Z
572B, 6JS6C
12BYZA, 4-400A
6146

TEN-TEC
Omni "C"

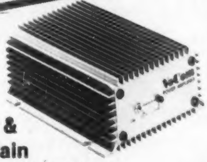

VoCom
Power
Amplifier &
5/8λHT Gain
Antennas IN STOCK

HY-GAIN
TOWERS
ANTENNAS
& ROTORS

ROBOT Slow Scan TV 400 & 800

MURCH
Model UT2000B

AEA 144 MHz,
AEA 440 MHz
ANTENNAS

MAIL ALL ORDERS TO **BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.**

New York City's LARGEST STOCKING HAM DEALER
COMPLETE REPAIR LAB ON PREMISES

Subways: IRT/LEX-"Spring St. Station"
BMT-"Prince St. Station"
IND-"F" Train-Bwy. Station"

BARRY INTERNATIONAL TELEX 12-7670 **212-925-7000.**
TOP TRADES GIVEN ON YOUR USED EQUIPMENT.

STORE HOURS: MON/FRI - 9 AM to 5:30 PM,
THURS. TILL 7:30 PM, SAT 10 AM to 3 PM.

"Aqui Se Habla Espanol"

WE STOCK: KLM ANTENNAS, UHF & VHF AMPLIFIERS, HENRY AMPLIFIERS, BIRD WATTMETER, HY-GAIN, LARSEN, SHURE, KDK-2015R, TURNER, ASTATIC, VOCOM, VHF ENG., MFJ, KANTRONICS, AVANTI, CORDLESS TELEPHONES, POCKET SCANNERS, NYE, BENCHER, VIBROPLEX, ALPHA.

AUTHORIZED DISTS. MCKAY DYMEK FOR SHORTWAVE ANTENNAS & RECEIVERS.

✓305

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS
DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED.

Amateur Radio Courses Given On Our Premises

Export Orders Shipped Immediately.

✓See List of Advertisers on page 130

power amplifier for use with their small suitcase-sized radio station. Their transmitter provided only about 20 Watts of power, and they had been unable to contact their station in Egypt.

I must admit that I was a little confused by a situation wherein an agent of a nation at war with Rumania was to be assisted by an American prisoner of war in establishing radio contact with an Allied radio station in Egypt. The Rumanian colonel told me that the rapidly approaching Russian forces had created serious political problems and that the British communications arrangements had been approved by "high government officials."

I said that I could build a suitable amplifier if I had the necessary parts, and one of the civilians replied that parts were available. After trading my flying suit for a pair of pants and a shirt, in order to appear less military, I gathered up my small collection of personal belongings and left the prison camp by car in the company of the civilians and two other radio operators, Charlie P. Brewer from Beaumont, Texas, and Ray Jones, RAF, from Sutton, Surrey, England.

We were taken to a large building which must have been part of a university physics department. I was escorted to a room that was full of electronic equipment and told to select whatever I needed. I found many American-made parts and some power supplies that appeared to be operational. I selected some triode transmitting tubes (they were either the HK-54 Gammatrons by Heintz and Kaufman or the 35TGs by Eimac—my memories have been somewhat dimmed by the passage of some 37 years), a 2500-volt power supply, a 300-volt power supply, tube sockets, variable capacitors, wire, solder, a variable transformer (Variac), and an assortment of rf chokes, resistors, insulators, and fixed capacitors.

There was no heavy solid wire available, and I could find no meters or test equipment. I explained my need for wire or tubing to make coils, and one of the civilians said that he would bring some later. The parts that I selected were placed on a bench, and the civilian said they would be delivered to the transmitter location that afternoon.

We left the building and were driven to the Banca Nationale A Romania (The National Bank of Rumania). In one of the basement rooms we were introduced to the two British agents. One was a British captain and the other a Rumanian national who also was a lieutenant in the British army. They showed me their small transmitter/receiver, and I was happy to see that they had several extra coil sets available which I could use in the amplifier circuit.

When the parts from the school were delivered, I assembled a simple power amplifier on a piece of pine board. Electrically, it was a pair of power triodes in parallel (see Fig. 1). The 2500-volt supply provided the plate voltage, and the 300-volt supply, Variac controlled, provided the bias. I used two of the spare coils from the "spy" radio for the amplifier-plate coil and checked for approximate tuning by coupling the output from the small transmitter to the antenna link on the plate coil. Resonance was easily established by tuning for maximum rf voltage in the tank coil.

Next, I capacity-coupled the grids of the power amplifier to the plate of the 6L6 output tube in the small transmitter. I hooked a flashlight bulb to the output link and carefully readjusted the amplifier plate, tuning for maximum output. Then the neutralizing capacitor was adjusted for minimum output, and the amplifier was ready for the first trial run. The flashlight bulb was replaced by a 300-Watt bulb, the bias voltage was set for maximum (−300 V) and the 2500-volt supply was turned on.

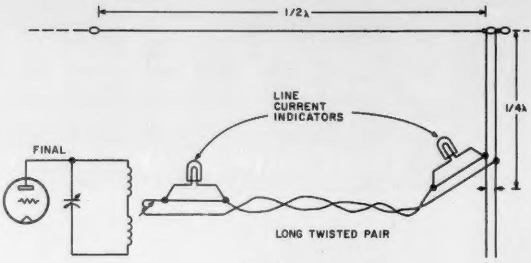

Fig. 2.

Surprisingly, nothing blew and no smoke appeared. By decreasing the bias voltage slowly and observing the intensity of the blue glow of the mercury-vapor rectifiers (866s) in the high-voltage supply, I could tell when the amplifier tubes began to draw plate current. I set the bias to a point where a definite plate current was evident and then keyed the small transmitter now being used as a driver for the amplifier. I was rewarded with a brilliantly glowing 300-Watt bulb and a large increase in the mercury-vapor glow.

The amplifier was indeed working and obviously was producing more radio energy than I had ever achieved with any of my ham gear. The only missing element now was an antenna, and the roof of the bank building was an awfully long way from the basement.

It was during this time period that a group of Rumanian leaders formed a provisional government, declared themselves the legal spokesmen, and agreed to cease combat activities against all Allied forces. I was introduced to Dr. Maniu who headed the provisional government and whose temporary abode was also in the basement of the bank. I understood that he had a long history of public service and was well thought of by the Rumanian people.

A man from the telephone company provided us with a large reel of twisted-pair telephone cable, a small reel of bare copper wire, and a great many glass insulators. Charlie, Ray, and I put a half-wave antenna with a quarter-wave matching stub on the roof and used the phone cable as a transmission line to the transmitter (see Fig. 2). The elevator shaft provided the shortest path for routing the cable between the roof and the basement.

During the installation of the antenna, the local German military authorities reacted immediately and harshly to the new government. Several Rumanian civilian facilities were bombed, and, for a few minutes one day while we were on the roof, we watched ME-109s dive-bomb nearby buildings. Luckily, the bank was not selected as a target.

I was concerned about the suitability of the phone cable as a radio-frequency transmission line because of the poor insulation and extreme length of the cable. (No one else there had ever heard about EO-1 cable). As it turned out, the phone cable was very lossy and the

Boman➤ A WORLD AHEAD OF THE COMPETITION

SAMPLE VOLUME DISCOUNT COUPON

Submit this coupon with your order, and/or payment, and receive one **EFH-75** POLAR-MATIC FEED for evaluation purposes at the **24** lot price (*Limit one per customer*) **$99.50**

NAME ____________

COMPANY ____________

ADDRESS ____________

CITY ________ STATE ______ ZIP ____

PHONE ____________

TOLL FREE INSIDE CA: (800) 352-2553 OUTSIDE CA: (800) 421-2533

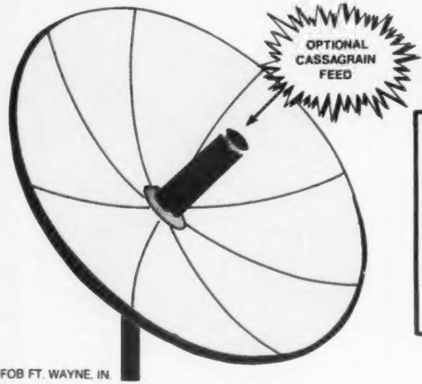

*FOB FT. WAYNE, IN.

PRODELIN

SUPER DISH

THERMO COMPRESSION MOLDED

$499.50 DISTR. PRICE

The BOMAN SA-3000 is a THERMOCOMPRESSION MOLDED Satellite Antenna . . . NO MORE GRIEF! FEATURES: • 3.0 meter diameter • 8 interlocking fiberglass sections for quick, precise assembly • Unique design allows for superior stress resistance to withstand extreme environmental changes . . . **NO MORE GRIEF!**

SR-800 RECEIVER

The **Boman SR-800B** Satellite Receiver uses advanced technology to provide high quality reception at a very affordable price. **Features:** ■ 24 channel capability ■ 6 audio channels ■ fine tuning control ■ AFC ■ illuminated signal strength meter ■ attractive design fits any decor.

ORDER WITH:
A - 100° Low Noise Converter (LNC)
B - 110° Low Noise Converter (LNC)
C - Down Converter

$399.50 DIST. PRICE

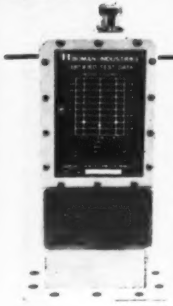

MODEL LNA-915
LOW NOISE AMPLIFIER

110° K OR BETTER

All BOMAN MICROWAVE AMPLIFIERS are **100%** tested and marked for each **guaranteed** test parameter before they are released. All measurements are taken with equipment calibrated and maintained in accordance with military standard MIL-C-45662.

QTY.	OPEN ACC'T	Pay w Order
10 UNITS	$443.89	$399.50
30 UNITS	$421.67	$379.50
60 UNITS	$388.33	$349.50
600 UNITS	$366.11	$329.50
1000 UNITS	$332.77	$299.50

BOMAN INDUSTRIES
SATELLITE PRODUCTS DIVISION
9300 HALL RD., DOWNEY, CA 90241
(213) 869-4041

✓157

The "NEW" Polar-matic Ultra Feed

Improve your system qualtiy with the EFH-75 Microwave Feed. It offers precision polarity selection using the attractive control shown here.

PRECISION CONTROL WITH ON OFF SWITCH AND L.E.D. INCLUDES "NO SLIP" CONTACT TAPE.

INSTALLATION FEATURES: 130 ft. of 3 conductor wire included -TERMINALS attach at each end - NO MORE SPLICING - Molded terminal posts on motor cover - Painted parts prevent corrosion - ON-OFF switch on control box - Power-on light on control box - All necessary hardware included.

ALL NEW

$99.50

DISTRIBUTOR PRICE

Toll Free Inside Ca.: (800) 352-2553 Outside (800) 421-2533

WEATHER PROOF TERMINAL STRIP TO INSURE YEAR AROUND CONNECTION. (NO MORE SPLICING)

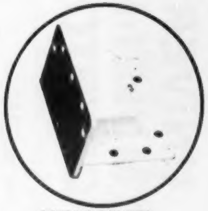

RIGHT ANGLE ADAPTER PERMITS VERTICAL OR RIGHT ANGLE L.N.A. MOUNTING current flow into the antenna matching stub was much less than the current flow from the amplifier into the cable. In the final version of the antenna, the telephone cable was used as a single conductor connected to a water-pipe ground through the amplifier-output link. The cable length to the antenna was adjusted for best loading. This worked very well, and the British agents were soon in contact with the Allied radio station in Egypt. I have no idea of the purpose or content of their conversations as the messages were all encrypted—by use of the Bucharest telephone book.

The opportunity to improvise electronic equipment had been a splendid diversion, however, and during the two or three day period involved, I was directly concerned in an urgent project that was of value to our allies. During this period, I slept in the basement of the bank and food was sent in from a nearby restaurant. This was overwhelming in it's quantity, and I was never able to eat the entire portion. I took particular delight in the dill pickles since I had not tasted any since being shot down.

Within a few days, Russian troops entered Bucharest and the British and American POWs were flown to Italy in B-17 bombers with the protection of many P-51 fighter aircraft. We spent a few days visiting our respective squadrons and then departed from Naples for a fantastic voyage to the USA. By October of 1944, I was home on leave. I planned to ask for an assignment to a B-29 group so that I could get to the Pacific. That would also give me a chance to tinker with that new Collins rig, the ART-13.■

UNIVERSAL M-600 MULTI-MODE AND CRYPTO-DECODER

— NEW —
DECODES:
TOR-SITOR
BIT INVERSION
WEATHER FORMAT
NON STANDARD SHIFT

The M-600 converts these Codes plus RTTY (Baudot & ASCII) to video and will drive a Serial or Parallel printer for hard copy. Baudot speeds from 60 to 132 WPM and ASCII from 110 to 1200 Baud rates. Morse reception, auto range up to 60 WPM. The M-600 has 3 fixed shifts and 1 tunable shift. Multiple scroll inhibit and un-shift on space are included along with a built-in self-test system. Isolated loop MIL-188 or RS232 and optional parallel ASCII.

CONTACT US FOR FURTHER INFORMATION

Phone: (614) 866-4605 $799.95
MC & VISA Accepted (shipping extra)

UNIVERSAL ELECTRONICS INC.
1280 AIDA DRIVE, REYNOLDSBURG, OHIO 43068

REMOTE -O- MIKE

FM Wireless Mike

$34.95

- **Range—up to 300 ft.**
- **FM Audio**
- **XTAL Controlled**
- **Simple Hook-up**
- **Reliable years of service**

FM RECEIVER

REMOTE-O-MIKE

Stop: The steering wheel mike cord tangle. Stop: Running back and forth to answer a call on your radio. Stop: The inconvenience of being tied to your radio during long QSO's. The Remote-O-Mike may be connected to any HF, VHF or UHF ham transceiver. Just connect the Remote-O-Mike receiver to the mike input jack and each time you press the PTT button on your cordless mike your ham rig will function as your normal mike. The Remote-O-Mike receiver will provide both the PTT and audio to your ham rig.

Use in and around the house, auto, boat, etcetera. Just like a repeater with a range of up to 300 ft. Each Remote-O-Mike includes a XTAL controlled wireless FM mike and FM receiver. How do you spell mike cord tangle relief (Remote-O-Mike) Order today for your mike cord relief.

WORKS ON ANY RADIO—MOBIL OR BASE

To Order Call (714) 268-8131—Free Shipping

✓57

Discount Ham Radio 9520 Chesapeake Dr., #606 A, San Diego, CA 92123

812-422-0231
MON-FRI 9AM-6PM • SAT 9AM-3PM

✓449

The HAM SHACK

master charge

VISA

808 N. Main • Evansville, IN 47711

AEA	
MBA-RO Reader	$269.00
MBA-RC Rcv/Code Conv. Xmt	395.00
MM-2 MorseMatic Ultimate Keyer	150.00
CK-2 Contest Memory Keyer	125.00
KT-2 Keyer/Trainer	99.00
BT-1 Trainer	72.00
Isopole 144 Jr/220 Jr	30.00
Isopole 144/220 MHz	40.00
Isopole 440 MHz	59.00
ALLIANCE	
HD73 (10.7 sq. ft.) Rotator	$99.00
U-100 Small Rotator	45.00
ARRL	
83 Handbook	$12.00
Antenna Book	8.00
License Manual	4.00
Large Assortment of Publications	call
ASTRON	
RS7A 5-7 Amp Power Supply	$49.00
RS12A 9-12 Amp Power Supply	69.00
RS20A 16-20 Amp Power Supply	89.00
RS20M 16-20 Amp w/meter	109.00
RS35A 25-35 Amp	135.00
RS35M 25-35 Amp w/meter	149.00
RS50M 37-50 Amp w/meter	225.00
AZDEN	
PCS 4000 2M Xcvr	call
PCS 300 Handheld	$285.00
Speaker/Mic	29.00
Leather Case	27.00
Battery	27.00
Mobile Operating Cord	35.00
Dual PL Tone encoder/decoder	39.00
B&W	
Folded Dipole 80-10 Meter	$135.00
375 6 pos. coax switch	21.00
376 5 pos. coax switch	21.00
593 3 pos. coax switch	19.00
595 6 pos. coax switch	22.00
SWL Antenna	37.50
BASH	
General, Advanced, Extra Theory Books	$9.95
Novice Study Guide	4.95
Code Tapes	9.95
BENCHER	
BY-1 Paddle	$36.00
BY-2 Chrome Paddle	45.00
BUTTERNUT	
HF6V 80-10 Meter vertical	$119.00
RM Kit Roof Mount w/radials	39.00
STR Stub Tuned Radials	23.00
TBR 160 Meter Coil Kit	49.00
CALLBOOK	
U.S.	$19.95
DX	18.95
Map Library	4.50
CUBIC	
Astro 103	$1,150.00
CN-102 CW Filter	72.00
1500ZA Amplifier	500.00
WM2000A HF PEP Meter	89.00
PSU-6A Power Supply	170.00
CUSHCRAFT	
A3 Tribander 3 EL	$179.00
A4 Tribander 4 EL	229.00
A743/744 40 Meter Add-on	69.00
R3 Motor Tuned Vertical	229.00
AV5 80-10 Meter Vertical	95.00
214B Boomer 14 EL 2M	69.00
214FB Boomer 14 EL FM	69.00
228FB Power Pack 28 EL 2M FM	189.00
32-19 Super Boomer 19 EL 2M	83.00
220B Boomer 17EL 220 MHz	75.00
ARX-2B Ringo Ranger II 2M	36.00
ARX450B Ringo Ranger II 450 MHz	38.00
A147-20T Vert. & Horiz. 10EL 2M	63.00
A144-10T Satellite 10EL 2M	45.00
A144-20T Satellite 20EL 2M	69.00
A432-20T Satellite 20EL 432 MHz	45.00
DAIWA	
CNA-2002 2.5KW Antenna Tuner	$399.00
CNA-1001 0.5KW Antenna Tuner	299.00
CWN-518 2.5KW Tuner	295.00
CWN-418 200W Tuner	179.00
CN 520 1.8-60 MHz SWR/Pwr Mtr.	63.00
CN-540 50-148 MHz SWR/Pwr Mtr.	72.00
CN-550 144-250 MHz SWR/Pwr Mtr.	80.00
CN-620B 1.8-150 MHz SWR/Pwr Mtr.	110.00
CN-630 140-450 MHz SWR/Pwr Mtr.	129.00
CN-720B 1.8-150 MHz SWR/Pwr Mtr.	149.00
CS-201 2-position switch	22.00
CS-401 4-position switch	62.00
RM-940 Wireless Mic	72.00
DRAKE	
TR7A Xcvr	$1,439.00
R7A Receiver	1,399.00
TR5 Xcvr	695.00
L7 2KW Amplifier w/tubes	1,149.00
L75 1.2KW Amplifier w/tube	729.00
MS7 Speaker	49.00
WH7 Watt Meter	109.00
RV75 VFO	269.00
ENCOMM (SANTEC)	
ST-144/μP	$285.00
ST-440/μP	309.00
Leather Case	29.00
Battery Pack	24.00
Base Charger	29.95
Charge Adapter	5.00
Sub Tone	29.95
Speaker/Mic	32.00
HAL	
DS3100 Terminal	$1,850.00
MSO3100	525.00
CT2100 Terminal	695.00
KB2100 Keyboard	159.00
RS2100 Scope	289.00
MSG2100 Message Storage ROM	25.00
DS2050 Terminal	569.00
MR2000	145.00
CWR685A TeleReader	870.00
ST-6000 Deluxe Demodulator	635.00
ST-5000 Demodulator	225.00
12″ Monitor	179.00
6700 Reader Terminal	435.00
HY-GAIN	
TH7 DXS 7EL Tribander	$375.00
TH5 MK2S 5EL Tribander	319.00
TH3 MK3S 3 EL Tribander	219.00
TH3 JRS 3 EL Tribander	159.00
402BAS 2EL 40 Meter Beam	199.00
205BA 5EL 20 Meter Long John	269.00
204 BAS 4EL 20 Meter Beam	229.00
203BA 3EL 20 Meter Beam	119.00
155BA 5EL 15 Meter Beam	159.00
66BS 6EL 6 Meter Beam	109.00
18HTS 80-10 Meter Vertical	339.00
18AVT/WBS 80-10 Meter Vertical	95.00
BN86 Balun	19.00
214 14EL 2 Meter Beam	36.00
208 8EL 2 Meter Beam	33.00
205 5EL 2 Meter Beam	23.00
CD45 8.5 sq. ft. Rotator	119.00
Ham IV 15 sq. ft. Rotator	195.00
T2X 20 sq. ft. Rotator	249.00
HDR300 25 sq. ft. Rotator	435.00
V2S 2 Meter Vertical	39.00
Procomm 200 Dual Headphones/Mic	89.00
Procomm 300 Headphone/Mic	79.00
C1210 Headphones	35.00
Free Shipping on all crank-up towers	
ICOM	
R70 General Coverage Receiver	$669.00
720A General Coverage Xcvr	1,140.00
730 Xcvr	call
740 Xcvr	call
251A 2 Meter All Mode	575.00
451A Oscar Xcvr	759.00
505 6 Meter Xcvr	395.00
25A 2 Meter	299.00
29H 2 Meter All Mode	475.00
PS15 Power Supply	135.00
PS20 Power Supply	195.00
SM2 Desk Mic	36.00
SM5 Desk Mic	36.00
SP3 Speaker	45.00
Phone Patch	125.00
MB-5 Mobile Mount	19.50
FL32 500 Hz CW Filter 720A	55.00
FL34 AM Filter 720A	45.00
FL30 SSB Filter 730	55.00
FL45 CW Filter 730	55.00
HM10 Scanning Mic	36.50
IC2KL Solid State Amp	13.95
AT500 Automatic Tuner	389.00
2AT/3AT/4AT Handhelds	235.00
BC-30 Base Charger	65.00
BP5 425ma 8.4v Battery	45.00
BP4 Battery Case	12.50
BP3 250ma 8.4v Battery	29.50
BP2 425ma 7.2v Battery	36.50
DC-1 DC Operating Module	17.50
HM-9 Speaker/Mic	32.00
KLM	
KT34A 4EL Triband Beam	$309.00
KT34XA 6 EL Triband Beam	465.00
144-148-13LBA 2M Long Boomer	79.00
143-150-14C 2M Oscar Ant	85.00
KANTRONICS	
Interface	$165.00
Mini-Reader Pkg	225.00
Mini-Terminal	249.00
Software for:	
Apple	27.00
Atari	45.00
TR80C	55.00
VIC20	45.00
KDK	
2030 2M Xcvr	275.00
LARSEN	
NLA-150-MM 5/8 Wave 2M Mag. Mt.	$39.00
NLA QMM 1/4 Wave 2M Mag. Mt.	23.00
MFJ	
989 3KW Roller Inductor Tuner	call
949B Tuner	$125.00
941C Tuner	81.00
940B Tuner	72.00
901 Tuner	54.00
900 Tuner	45.00
484B Keyer	125.00
482 Keyer	89.00
481 Keyer	81.00
408 Keyer	72.00
406 Keyer	63.00
405 Keyer w/paddle	59.00
401 Econokeyer	45.00
496 Super Keyboard	289.00
422 Keyer/BENCHER Paddle combo	89.00
722 Filter	63.00
624 Phone Patch w/meter	59.00
250 Dummy Load w/coil	32.00
812 VHF Meter	29.00
814 HF Meter	45.00
816 HF Meter	29.00
820 Meter	63.00
825 Deluxe Meter	105.00
959 Rcvr Tuner w/preamp	81.00
1040 Deluxe Preselector	89.00
MIRAGE	
B23 2/30 Amp	$80.00
B108	155.00
B1016	239.00
B3016	205.00
D1010 10/160 440 MHz	275.00
MP1/MP2 Watt Meters	100.00
C106 220 MHz	169.00
C22 220 MHz	80.00
NYE	
Phone Patch	$54.00
Straight Key	13.00
ROBOT	
400 SSTV Scan Converter	$675.00
800 ASCII/Baudot/CW Terminal	749.00
SHURE	
444D Desk Mic	$50.00
414A Hand Mic	36.00
TEN-TEC	
525 Argosy	call
645 Keyer	$77.00
227 Antenna Tuner	80.00
444 Hercules Amplifier	1,325.00
217, 218, 219, 220 Filters	54.00
229 2KW Tuner	250.00
TOKYO HY-POWER	
HL32V 25W Amp	$79.00
HL82V 80W Amp	149.00
HL160V 160W Amp	285.00
VOCOM	
Amplifiers/Ants	call

Send SASE for our new & used equipment list.

Penn Clower W1BG
459 Lowell Street
Andover MA 01810

The Tube Returns

Move over, ICs. This receiver is easy to build, cheap, and works like a dream.

Bored with cranking out the contacts on your expensive transceiver? Been looking for a simple construction project to put some of the thrill back into ham radio? Maybe you'd just like to build something for the fun of seeing what you can make with that collection of old parts wasting away in the basement? If the answer is yes then this is for you.

Believe it or not, here is a surprisingly effective one-tube shortwave receiver you can build in a weekend. The cost is 0 to 15 dollars, depending on your resourcefulness. No slouch on performance, it will pull in just about every signal on the 80-meter ham band that an expensive commercial receiver will hear. As described here, it tunes from 3.5 to 7.5 MHz but the frequency range is determined by plug-in coils and can be extended easily in either direction.

Old-timers have already recognized this project as a regenerative receiver. This type of detector has its roots in the misty past of radio lore and its reputation for high sensitivity is well earned. Early amateurs found that putting an adjustable amount of positive feedback around a detector had several benefits: An astounding amount of gain was available, the selectivity of the associated tuned circuit was vastly increased, and with proper adjustment either AM or CW signals could be copied easily. If a dual triode is chosen for the tube, then one section can be the regenerative detector and the other an audio amplifier. The resulting receiver is easy to construct, sensitive, and inexpensive. It was a very popular design in the 1920s and 30s.

Photos by W1GSL

The one-tube wonder at work.

There are, of course, several drawbacks. To receive code signals the feedback is adjusted so the detector is just barely oscillating, and with that setting a long antenna blowing around in the wind can cause frequency instability on the higher bands. Since the detector is oscillating, a steady carrier can be broadcast via the antenna. A few microwatts isn't going very far but the ham next door might hear it. Furthermore, any receiver with a single tuned circuit will tune rather broadly. While that isn't too much of a problem when all of the signals in the band are of similar strength, a really strong station on a nearby frequency (within 30 kHz or so) can cause problems.

All of these problems were eventually solved with the development of the superheterodyne receiver, but the regenerative detector continued to be used, if to a lesser extent, because of its simplicity and sensitivity. Until the mid 1950s there was always a one-tube regen featured as a good beginner's receiver in the ARRL *Handbook*. Even in the 60s there were designs for simple superhet receivers using regenerative detectors and controlled amounts of i-f regeneration to sharpen selectivity.

So much for history; let's turn to the project at hand. This circuit is a distillation from several described in the literature of the 50s. I tried not to use components that would be difficult to locate today and I'll point out a lot of circuit alternatives to take care of the most likely junk-box shortages.

The receiver uses a plug-in coil—wound on the glass bulb of an extra octal tube—and covers 3.5 to 7.5 MHz. With that coil, the 80-meter band is covered with plenty of bandspread and the 40-meter band tunes pretty rapidly. You can wind other coils easily to cover 40 and 20 meters with plenty of bandspread.

The 80-meter tuning range is a good place to start since that band is not too crowded and the shortcomings of this simple receiver will be more pronounced on the higher frequency bands. The construction is genuine breadboard: very simple and easily adapted to whatever parts you collect. The performance is remarkable. With a 30- to 50-foot endfed wire you will be able to copy just about everything on 80 meters, SSB included, without much problem. In fact, the 80-meter performance compares quite favorably with that of a 5- or 6-tube "all-wave" receiver. The regenerative detector won't tune as conveniently as the superhet, but with a little practice the results are the same.

The Circuit

The circuit diagram for my receiver is shown in Fig. 1. You can copy it exactly or use it as the starting point for your own version. Before getting into possible variations let's take a close look at Fig. 1.

The antenna is link-coupled to the detector coil through three or four turns of wire. This is the swinging coil visible in the photograph. There are two tuning knobs. One 365-pF section of the tuning capacitor from an old tube-type broadcast radio does the main tuning while a smaller, 140-pF variable, tapped down on the coil, is the slower tuning bandspread capacitor. A three- to four-turn feedback winding on the bottom end of the plug-in coil allows the detector to oscillate when the regeneration control is set high enough.

The plate lead from the detector triode is filtered clean of rf after running through that feedback winding and the audio is capacitively coupled into the grid of the audio-amplifier triode. An inductor (the primary of an audio-output transformer) keeps the audio from getting back to the power supply and a 25k pot sets the regeneration level by adjusting the detector's plate voltage.

The audio amplifier is pretty straightforward, except perhaps that the headphones are connected directly into the plate lead. This is simple and works well but please note that the B+ runs through the headphones and you should be mindful of the shock hazard. The headphone jack is wired so that the voltage doesn't appear on the external part of the jack (which is normally grounded) until the 'phones are plugged in and, of course, the jack is insulated completely from the front panel.

The power supply is correspondingly simple. Two small filament transformers feed each other back to back to provide both the 6.3 volts for the filament and a transformer-isolated 115 volts for the B+ supply.

Construction

The physical design is straight out of the 50s. A 7½- by 8-inch board is the base for the receiver, and most of the parts are mounted on terminal strips screwed to this board. The two tube sockets are mounted on 1-inch standoffs. The front panel is a piece of 1/16-inch aluminum to which are mounted the various controls. Most of the rf wiring is hung on the tuning capacitors, so it is important that the front panel be mechanically rigid and electrically shielding. These two conditions ensure a minimum of problems due to microphonics (audio noise in the headphones due to mechanical disturbance of the electrical parts) or hand effect (frequency shifts caused by circuit capacitance variations due to motion of the operator's hands near the receiver).

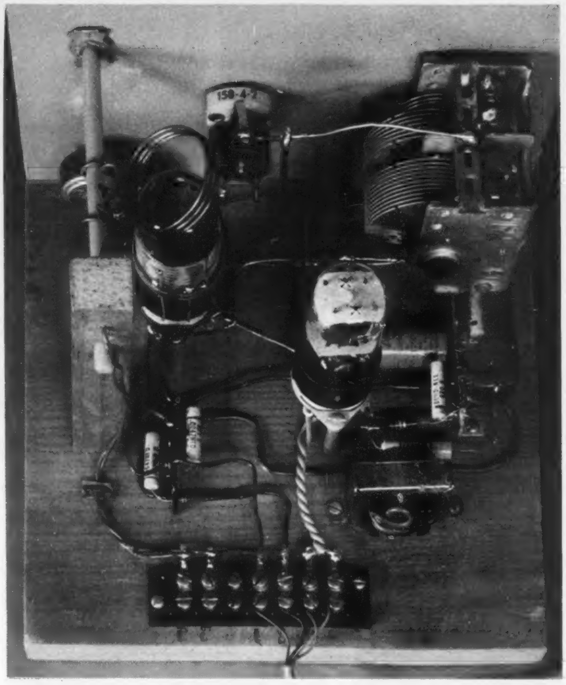

Behind the dials: A simple circuit and classic breadboard construction.

The antenna is coupled into the tuned circuit by means of a swinging link coil. As can be seen in the photograph, this link is mounted near the middle of a 5-inch length of 1/4-inch-

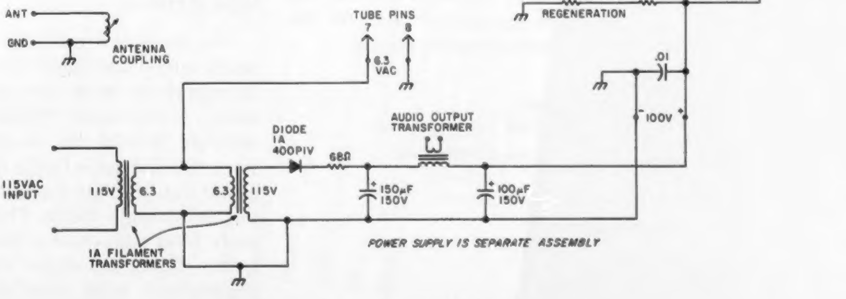
DETECTOR
AUDIO AMP
PLUG IN COIL ON SPARE OCTAL TUBE
4
5
1
8
2
2.2M
100
270
140
365
BAND-SPREAD
BAND-SET
1/2 6SN7
1.5K
.001 (2)
AUDIO OUTPUT TRANSFORMER
.01
510K
1/2 6SN7
1K
20μF
JACK FOR 2000Ω HEADPHONES
JACK INSULATED FROM PANEL B+ TO TIP CONNECTION
25K
REGENERATION
5.1K
ANT
GND
ANTENNA COUPLING
TUBE PINS
7
8
6.3 VAC
100V
115VAC INPUT
115V
6.3
6.3
115V
1A FILAMENT TRANSFORMERS
DIODE 1A 400PIV
68Ω
AUDIO OUTPUT TRANSFORMER
150μF 150V
100μF 150V
POWER SUPPLY IS SEPARATE ASSEMBLY

Fig. 1. One-tube receiver schematic.

diameter plastic rod. The rod need not be plastic—any insulating material will do, even wood. The rod is supported at the front panel by a bushing (which was salvaged from an old volume control in keeping with the spirit of the project) and at the other end by a wooden pillar having a 1/4-inch hole through it in the appropriate spot.

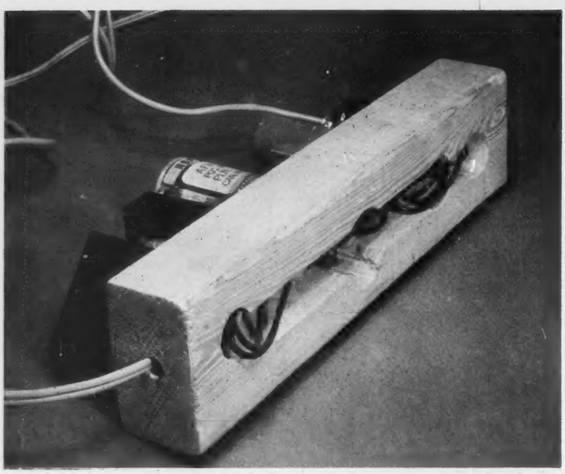

The power supply: built on a hollowed-out length of 2 × 3.

The link was formed by winding stiff wire around a wooden dowel slightly larger in diameter than the 6SN7 coil form. The wire is kept under as much tension as possible while winding. The time-honored method is to clamp one end of the length of wire in a vise and, with the wooden form held in both hands, lean back to put tension on the wire as you wind your way toward the vise.

The coil will spring out some when it is taken off the form and probably several turns at the start will be distorted. Save three or four good turns with an inch and a half or so of lead on them. When the rod and 6SN7 coil form are both mounted, you can measure where the antenna link will have to go on the shaft in order to swing over the coil. Drill a pair of wire-diameter-sized holes at the appropriate spots and mount the link through them.

The rest of the receiver layout is pretty well defined in the photographs. I used heavy wire for all of the rf wiring so that vibration-induced microphonic effects would be at a minimum. Your layout doesn't have to match mine exactly as you surely won't have a matching collection of parts.

The construction style of the power supply is also historically motivated. The supply is built as a separate unit to minimize 60-cycle pickup in the receiver. I used a 1-foot-long section of wooden 2 by 3 with a slot jigsawed down the middle to contain the wiring. One concession was made to modern electronic design in the form of a silicon rectifier mounted on a terminal strip hidden under the "chassis." In earlier years, there would have been a 5Y3 or type-80 rectifier tube in the supply.

Alternate Parts and Circuits

Half the fun of building the one-tube receiver is coming up with a suitable collection of parts. The circuits are so noncritical that the builder can substitute with wild abandon and still have excellent results. This is especially true of the power-supply circuit.

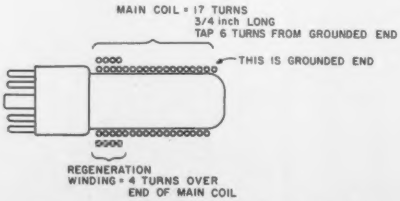

Fig. 2. Coil data for 3.5-7.5-MHz coil.

The receiver needs 6.3 volts ac at .6 Amps and 90 to 200 volts dc at 8 to 20 mA. If you're lucky, you will have a single small transformer providing these voltages and probably 5 volts as well (for a rectifier filament) that you won't need. I didn't have any suitable small power transformers, but I did have a collection of filament transformers. Two were wired back to back as indicated in Fig. 1.

Of course, it is all right to use a single large transformer if that's what's available. If the voltage is too high (250 volts or more), a 10 or 15k, 1-Watt resistor can always be used in place of the filter inductor. A really large transformer, like that from an old TV set, should probably be mounted on a metal chassis for safety's sake—an inverted cake pan will serve if the junk box lacks a chassis.

The rectifier I used is a small silicon unit rated at 1 Amp and 400 peak inverse volts. A full-wave bridge rectifier would be nicer since the 120-cycle ripple is easier to filter than the output of a single diode. The more filter capacitance the better. Don't be afraid to experiment with smaller amounts than I used, but be prepared to add more if hum is a problem. Be sure the capacitors are rated to work at voltages higher than they will see in the circuit. The filter inductor would ideally be a small 5- to 20-Henry unit rated at 20 mA or more. Small chokes, like small power transformers, are not too plentiful these days, so I used the primary of a salvaged TV set audio-output transformer instead.

An entire alternate receiver schematic is shown in Fig. 3. I haven't built a receiver using this schematic, but it is included here to illustrate a number of circuit variations. You can mix and match circuit features from Figs. 1 and 3 to make maximum use of the parts you have on hand. Note first how the antenna is capacitively coupled to the tuned circuit. If you have a small variable capacitor and a big knob, you may find this version easier to build than the swinging link. Both sides of the capacitor must be insulated from the panel and the large knob is desirable since placing your hand near the control shaft may influence the antenna coupling. This circuit arrangement was used in the 1952 ARRL *Handbook* receiver with a homemade capacitor constructed much along the lines of my swinging link—though plates were used instead of coils, of course.

If you have another small capacitor with a suitable shaft, you can use it as a bandspread capacitor. The smallest variable I had was 140 pF, so when I wound my coil I put a tap a few turns up from the ground end and connected that larger capacitor across only part of the coil. A 10- or 15-pF variable can go across the entire coil as shown in Fig. 3, and if you only have several 365-pF units, you can use a tap on the coil even closer to ground than mine. Don't overlook old FM radios as a

BOOKS

73 Magazine, Pine Street, Peterborough, N.H. 03458

Please send me the following 73 products:

Qty.	Catalog #	Title	Unit Price	Total

Please allow 4-6 weeks for delivery.
No C.O.D. orders accepted.
Enclosed $_______ ☐Check ☐M.O.
Bill: ☐ AE ☐ MC ☐ Visa

Shipping/handling _______
Total _______

Card # ____________________ Exp. date _______
Signature ________________ Interbank # _______
Name ____________________________
Address __________________________
City _____________________________
State ________________ Zip ___________

Shipping and handling charges:
$1.50 1st book, $1.00 each additional book
(UPS, use street address)
$10.00 each book overseas airmail

12-82

SUBSCRIPTIONS

73 Magazine, P.O. Box 931, Farmingdale, N.Y. 11737

73 subscribers save 30% off the newsstand price.

☐ New subscription ☐ 1 year $19.97

Enclosed $_______ ☐ Check ☐ M.O.
Bill: ☐ MC ☐ Visa ☐ AE ☐ me

Card # ____________________ Exp. date _______
Signature ________________ Interbank # _______
Name ____________________________
Address __________________________
City _______________ State ______ Zip _______

Canada & Mexico $22.97 1 year U.S. funds only.
Foreign surface—$39.97 1 year U.S. funds drawn on US bank only
Foreign airmail—please inquire.

32DR69

Please allow 6-8 weeks for delivery.

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO 73 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 MAGAZINE
Subscription Dept.
POB 931
Farmingdale NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO 73 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 MAGAZINE
Att. Mail Order
Peterborough
NH 03458

Albia Electronics

Season's Savings

LOW OHM METER MODULE, DM-10

Measures resistance from 10 milliOhms to 20 Ohms. Now you can measure resistance down to 10 milliOhms with this low cost, easy to use DVM module. Check coil resistance, transformers, relays, chokes, printed circuit board copper paths and ground cables. Special zero balance control nulls out input cable resistance to insure accurate readings. Your DVM has to be set to 2V range during operation.

DM-10 LOW OHM METER MODULE
TO DVM
ZERO CAL
20Ω
2Ω
.2Ω
RANGE
Rx
PUSH TO MEASURE
Albia Electronics

- Resistance range 10 milliOhms to 20 Ohms
- Zero Calibration control
- Battery powered (push to read battery saver circuit). Requires 9 Volt Battery (not included)
- Size 6.25"x3.75"x2"
- Incl. Model 336 Test Clips

$\$55^{95}$

ORDER BEFORE JAN. 15th AND GET A FREE GIFT!

REGULATED TRIPLE POWER SUPPLY, LOW PRICED! DM-6

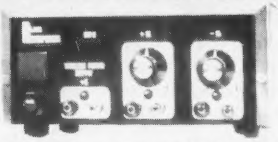

A fully assembled and tested triple benchtop power supply. Includes fixed 5V @ 1 Amp, 5V to 15V @ 0.5 Amp and −5V to −15V @ 0.5 Amp—all supplies regulated, short proof. Each supply has a power on indicator LED. Complete and ready for use in a durable (8" x 6" x 3½") metal case.

$\$99^{95}$

8 CHANNEL SCOPE MULTIPLEXER, DM-12

Convert your single channel scope into a 4 or 8 channel instrument; just connect the DM-12, 8 channel scope multiplexer to your scope, clip the 8 input probes to the signals you want to view. Simple, easy, fast—can handle logic level TTL signals from DC to 3MHz. Features separate spacing and trace amplitude controls and selectable sampling rate—all to insure easy clear scope display.

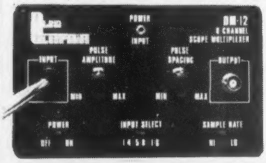

COMPLETELY ASSEMBLED AND TESTED! READY TO USE!

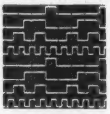

VIEW 8 CHANNELS AT ONCE!

- 8 TTL compatible input channels (1 TTL load per channel) can drive 50 Ohm scope cable
- Maximum full screen amplitude 1.6 Volts adjustable
- Trace amplitude and spacing controls
- 4 or 8 channel selector switch
- 8 color coded input cable, 24" long with insulated alligator clips
- External 9 VDC power supply included (Model MMAC-2)
- Size 6.25" x 3.75" x 2"
- BNC Output Cable Accessory (Model PSA-2 add $14.95)

$\$74^{95}$

LOW COST CAPACITANCE METER MODULE, DM-8

Connect this high quality low cost Capacitance Meter Module, DM-8 to your digital Volt Meter and turn it into a Digital Capacitance Meter—the Low Cost Way!

COMPLETELY ASSEMBLED AND TESTED! READY TO USE!

- 2V Output
- Accuracy better than 5%
- Push to read range (button) from 1 pF to 20,000 μF
- Zero Calibration control
- In one easy to use, self-contained package
- Battery powered, with "push to read" battery saver circuit (9V batteries not included)
- Size 6.25" x 3.75" x 2"
- Includes Model 336 Test Clips

$\$79^{95}$

PORTABLE SELF-CONTAINED CIRCUIT DESIGNER, DM-5

Contains 8 LEDs and 8 logic switches.

- Control switches and buffered LED logic indicators
- Plug your ICs into solderless breadboards, tie in power and ground, connect your logic switches and LED indicators
- All interconnections between LEDs, switches and circuits via 22-26 solid wire
- Self-powered, in compact, durable carrying case
- Battery (4 1½ Volt C cells*) or AC powered providing economical bench use or convenient portable use. Available in two models

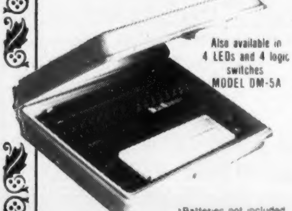

Also available in 4 LEDs and 4 logic switches MODEL DM-5A

$\$69^{95}$

*Batteries not included

MENTION THIS MAGAZINE AND GET A FREE GIFT!

LOW COST HIGH FREQUENCY COUNTER

49902250
550 MHz FREQUENCY COUNTER

MODEL NO. DM-7

The Albia Model DM-7, 8 Digit High Frequency Counter is easy to use, switch selectable time base input by a single BNC, nothing to build!

- 5 Hz to 550 MHz
- 8 big easy-to-read .43" high intensity LED display
- Crystal (±3 ppm @ 25 C) controlled 0.1 or 1.0 sec. gate times
- Convenient benchtop size (7"x10"x3") durable attractive case

COMPLETELY ASSEMBLED PRE-CALIBRATED PRE-TESTED

$\$149^{95}$

PRICES & SPECIFICATIONS SUBJECT TO CHANGE • SPECIAL ENDS JAN 30th

MasterCard AMERICAN EXPRESS VISA

FOR FASTER SERVICE USE YOUR CREDIT CARD.

MOST ORDERS SHIPPED NEXT DAY.

Albia Electronics
44 KENDALL STREET
NEW HAVEN, CT. 06512

✓475

BACKED BY ALBIA'S FAMOUS WARRANTY.

CALL TOLL FREE 1-800-243-6953 9 AM 5 PM EST source of small-value variable tuning capacitors. UHF TV tuners are another possibility and they often have a built-in vernier dial as well.

The 100-pF coupling capacitor can be any value from 50 to 250 pF and the grid-leak resistor can range from 1 to 10 megohms. Even the tube itself can be changed; a 12AU7 or 6CG7 will work as well as the 6SN7, though the base wiring and filament needs will be different. Naturally a real plug-in coil form will work as well as the spare 6SN7 I used, and any straight-sided glass octal tube will do the job as well as a 6SN7. Be careful not to use both filament pins of a tube for coil connections unless the filament is burnt out. I used #24 solid insulated wire for winding the coils. The coil ends are brought down over the outside of the tube base and soldered to the ends of the pins. A dab of cement holds the wires in place on the glass.

One big change in the circuit of Fig. 2 is that the regeneration control has been replaced by a 365-pF variable capacitor. There is a good reason for this circuit change: lower adjustment noise. The trouble with the 25k pot used in Fig. 1 is that it has dc flowing through it. Carbon pots, unlike wirewound ones, develop contact noise when used this way and eventually sound scratchy when rotated. I used the carbon pot because wire-wound ones are hard to find, but the variable-capacitor approach is a better solution to the problem and you may want to try it.

A 1- or 2.5-mH rf choke is used in the plate circuit and an audio-interstage transformer provides coupling to the audio amplifier. The audio-output transformer used for this purpose in Fig. 1 could also be replaced with any power-supply-type choke rated at more than 10 mA and 2 H or so inductance. Also shown in Fig. 2 is an audio transformer or supply choke used as a dc feed path for the audio amplifier. This permits ac coupling to the headphones and gets them out of the dc side of the circuit. If your main interest is in CW work, you may want to add some audio selectivity by placing a capacitor across the transformer winding as shown. The resulting tuned circuit can be set to the desired audio frequency by adjusting the capacitor value on a cut-and-try basis. The actual value will depend on the inductance of the transformer you have. Try starting with .01 or .05 uF and listen for an audio peak as you tune across a CW signal. Use a larger- or smaller-value capacitor to lower or raise the peak frequency as necessary.

Operation

Getting the most out of this little receiver is going to require some practice because the controls interact more than they do on a modern superhet. Peaking the preselector control on a transceiver may change the speaker volume a little, but you don't expect it to alter the i-f bandwidth or receiver tuning! Basic operation of the receiver is as follows: The main tuning is set to the approximate frequency of interest and the bandspread control to the middle of its range. The antenna-coupling link is positioned over the top of the coil and the regeneration control advanced. A "plop-hiss" noise in the headphones announces that the detector has started to oscillate. The control is positioned just after the oscillation starts and the receiver is tuned to a signal with the two tuning capacitors.

You will find that the sensitivity and selectivity are greatest with the regeneration set so the detector is close to the oscillation threshold. CW and SSB signals are copied with the detector oscillating, while for AM reception the regeneration is backed down just below the threshold. Often it is easiest to find a signal with the regeneration turned a bit to one side of the critical setting. Increasing the antenna coupling brings up the headphones volume but also reduces the amount of regeneration present and changes the received frequency slightly. The regeneration setting needed to maintain oscillation will vary some with frequency as well. All of this sounds more difficult than it really is. After a little experimentation, you'll find yourself pulling in an amazing number of signals.

Troubleshooting and Calibration

One side benefit of this design is that there is so little to go wrong. If the receiver is built according to the schematic and with good parts, it will most likely work when turned on. If it doesn't, and a series of circuit and voltage checks indicates that everything is OK, then the problem is probably with the regeneration coil. Try reversing the connection of the link winding. If the receiver cannot be made to oscillate on the lower end of the tuning range, then slide the feedback winding closer to the main coil. The coil dimensions recommended in Fig. 2 will surely get you off to a good start but you may wish to experiment with different geometries.

Once the receiver is pulling in signals, you will want to calibrate the dials. This is easy to do with the help of another receiver since the oscillating regenerative detector generates a weak carrier on the frequency to which it is tuned. Set the calibrated receiver to a given frequency, turn up the regeneration control on the little set, then sweep its bandset knob until you hear its carrier in the other receiver. At that setting the two receivers are listening to the same frequency. I glued a paper scale behind my tuning knobs and marked the bandset-dial

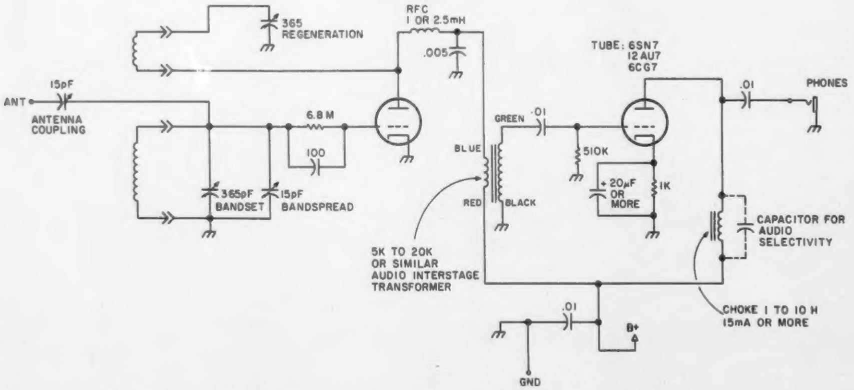

Fig. 3. Alternate schematic showing some possible circuit variations.

position at every half megahertz. The bandspread dial was marked for the 80-meter Novice band and the whole 40-meter band. Of course, the bandspread calibration is only accurate when the bandset knob is set properly.

Other Coils

Changing the tuning range means winding other plug-in coils. Simply use more turns to go down in frequency and fewer to go up. On the higher bands, space out the turns so the whole coil is 1/2 to 3/4 of an inch long. The number of regeneration turns should also increase or decrease one or two, in step with the main coil change. If your main tuning capacitor has two sections, you can place jumpers across otherwise unused coil pins and wire the socket to use both capacitor sections on low bands and only one on the higher frequencies.

A Word of Warning

This little receiver is really a lot of fun to operate. It is cheap to build and can be thrown together in a weekend. If there are a few spare octal tubes on hand, the frequency range can easily be extended in either direction. One word of caution is necessary though. The time will come when you tune across 80 meters with this set and realize that you *can* hear just about every signal on the band. In fact, you could actually use this little gem to make some real contacts (and enjoy shaking up the ham on the other end with a description of your receiver)! After you do that several times you'll naturally start to think about one-tube QRP transmitters. So when nosing around the local flea market for 6SN7s keep an eye out for a slightly larger power transformer, a 6AG7, some 80-meter crystals, and maybe a few old B&W plug-in coils. ■

1900 – 2500 MHZ KITS

DOWN CONVERTER KIT
$19.95

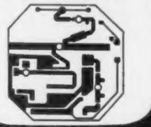

ANTENNA KIT
$19.95

POWER SUPPLY KIT
$19.95

1 P.C. BOARD PRE-DRILLED AND SOLDER FLOWED
3 MRF901 TRANS.
2 HP DIODES
6 CHIP CAPS "LARGE"
8 RESISTORS
4 PREPAIRED COILS, FACTORY WOUND
1 10 MFD CAP.

33 WASHERS
32 SPACERS
1 3 FOOT ROD
2 NUTS
1 8" PVC PIPE
2 4" END CAPS
1 MOUNTING BAR
1 "F" CONNECTOR
1 NUT AND BOLT

1 P.C. BOARD
1 POWER TRANSF.
1 317L ADJUSTABLE REGULATOR
1 FINE TUNING POT. WITH SWITCH
1 COARSE TUNING POT.
2 KNOBS
3 "F" CONNECTORS
4 POWER DIODES
1 RF CHOKE
3 RESISTORS
3 DISK CAPS.
1 1000 MFD CAP.
1 DPDT MINI TOGGLE SWITCH
1 LED WITH HOLDER

SUPPLY CABINETS
ALUMINUM CABINETS PREPUNCHED TO FIT POWER SUPPLY KIT..........$9.95

MANUFACTURED CABLE SETS
100FT. PLUS 3FT..........$19.95
75FT. PLUS 3FT..........$15.95
50FT. PLUS 3FT..........$12.95

DISCOUNTS
2 TO 4..........10%
5 TO 9..........15%
10 TO 24..........20%
25 TO 49..........25%
50 TO 99..........30%
100 TO 999..........35%
1000 UP..........40%
DIFFERENT KITS CAN NOT BE ADDED FOR QUANITY DISCOUNTS.

MAIL ORDERS
ADD $5.00 FOR SHIPPING AND HAN-DLING.
INDIANA RESIDENTS ADD 4% SALES TAX.

MasterCard
American Express Cards Welcome
VISA

TRIONYX IND. INC.
6219 COFFMAN RD.
INDIANAPOLIS, IND.
46268 ✔ 104
(317) 291-7280
(317) 291-2995

Big TEN-TEC OMNI-C & ARGOSY Overstock Sale

TEN-TEC Model 546 OMNI/Series-C All solid-state, 200w SSB/CW HF Transceiver. 9 HF bands, 160-10m including 10, 18 & 24.5 Mhz & 10 MHz WWV; 40 KHz VFO overrun. Instant band change, no tune-up. Digital readout, six 0.43" LEDs - read to 100 Hz. 8-pole 2.4 KHz SSB filter and audio active filter. Select standard SSB filter, optional 1.8 KHz SSB filter or optional CW filter plus 450 Hz or 150 Hz of audio filtering. 50 dB notch filter, ± 500 Hz & ± 4 KHz offset tuning, QSK CW break-in, VOX or PTT, adj. ALC, S/SWR meter, sidetone, built-in spkr. 13.8vdc @ 18A; 5½"h × 14½"w × 14"d, 14½ lbs... **SAVE $389**

Regular $1289 - ***Sale Price $899*** ^{95}

Common OMNI-C/ARGOSY accessories:
215PC Ceramic microphone w/coil cord.......... \$39^{00}
217 500 Hz 8-pole CW filt. *(Reg. $59)*.. SALE 54^{95}
218 1.8 KHz 8 pole SSB filt. *(Reg. $59)* SALE 54^{95}
219 250 Hz 6-pole CW filter *(Reg. $59)* SALE 54^{95}
234 Speech Processor (Reg. $139).......... SALE \$124^{95}
214 Electret microphone.......... 45^{00}

OMNI-C accessories:
280 18A power supply *(Reg. $169)*..... SALE \$154^{95}
255 Deluxe ps w/speaker *(Reg. $199)* SALE 179^{95}
243 Remote VFO *(Regular $189)*........ SALE 169^{95}
1140 DC circuit breaker.......... 10^{00}
645 Dual paddle keyer (Reg. $85).......... SALE 79^{95}

ARGOSY accessories:
225 9A power supply *(Regular $129)*... SALE \$119^{95}
220 2.4 KHz 8 pole SSB filt. *(Reg. $59)* SALE 54^{95}
222 Mobile mount.......... 25^{00}
223A Noise blanker.......... 34^{00}
224 Audio CW filter.......... 34^{00}
226 25 KHz crystal calibrator.......... 39^{00}
670 Single paddle keyer.......... 39^{00}
1125 DC circuit breaker w/cable.......... 18^{00}

TEN-TEC Model 525 ARGOSY All solid-state, 10/100 watt SSB/CW HF Transceiver. 6 HF bands 80-10m, including 30 meter band & 10 MHz WWV; 40 kHz VFO overrun on each band edge. Instant band change, broadbanded, no receiver front end or final tuning. Analog dial accurate to ± 2 kHz. 4-pole 2.5 KHz crystal SSB filter, sensitivity 0.3 uV for 10 db S + N/N ratio. Meter shows forward/reverse power, SWR & received signal strength. Offset tuning ± 3 KHz, notch filter, QSK CW break-in & PTT on SSB, sidetone, adjustable ALC. 13.8vdc/9A; 4½"h × 9"w × 15"d, 12½ lbs.......... **SAVE $129**

Regular $579 - ***Sale Price $449*** ^{95}

Order Toll Free: 1-800-558-0411
In Wisconsin (outside Milwaukee Metro Area)
1-800-242-5195

AMATEUR ELECTRONIC SUPPLY® Inc.
4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES

WICKLIFFE, Ohio 44092
28940 Euclid Avenue
Phone (216) 585-7388
Ohio WATS 1-800-362-0290
Outside Ohio 1-800-321-3594

ORLANDO, Fla. 32803
621 Commonwealth Ave.
Phone (305) 894-3238
Fla. WATS 1-800-432-9424
Outside Florida 1-800-327-1917

CLEARWATER, Fla. 33515
1898 Drew Street
Phone (813) 461-4267
No In-State WATS
No Nationwide WATS

LAS VEGAS, Nev. 89106
1072 N. Rancho Drive
Phone (702) 647-3114
No In-State WATS
Outside Nevada 1-800-634-6227

Associate Store

CHICAGO, Illinois 60630
ERICKSON COMMUNICATIONS
5456 N. Milwaukee Avenue
Phone (312) 631-5181
Outside Illinois 1-800-621-5802

MICROLOG
INNOVATORS IN DIGITAL COMMUNICATION

Just in time for Santa to get the word!

Here's where to check out the Microlog of your choice:

Santa's Microlog Workshop
18713 Mooney Drive
Gaithersburg, MD 20879
(301) 258-8400
TELEX: 908153

EASTERN UNITED STATES

Amateur Electronic Supply
28940 Euclid Avenue
Wickliffe, OH 44092
(216) 585-7388
800-321-3594

The Comm Center
Route 198
Laurel, MD 20810
(301) 792-0600 Jerry

EGE Inc.
13646 Jeff Davis Highway
Woodbridge, VA 22191
(703) 643-1063 John

EISCO
11305 Elkin Street
Wheaton, MD 20902
(301) 946-1088 Rolando

G & G Electronics
16424 Grande Vista Drive
Rockville, MD 20855
(301) 948-7388 Jeff

Hamtronics/Trevose
4033 Brownsville Road
Trevose, PA 19047
(215) 357-1400 Jim

Tufts Electronic Dept. Store
61 Lowell Road
Hudson, NH 03051
(603) 883-5005 Chuck

MIDWEST

Amateur Electronic Supply
4828 West Fond Du Lac Avenue
Milwaukee, WI 53216
(414) 442-4200 Paul
800-558-0411

The Ham Shack
808 North Main Street
Evansville, IN 47711
(812) 422-0231 Dan

Madison Electronic Supply
1508 McKinney
Houston, TX 77010
(713) 658-0268 Don

Midcom Electronics
8516 Manchester Road
St. Louis, MO 63144
(314) 961-9990 Dolores

SOUTHERN

Amateur Electronic Supply
1898 Drew Street
Clearwater, FL 33515
(813) 461-4267

Amateur Electronic Supply
621 Commonwealth
Orlando, FL 32803
(305) 894-3238
800-327-1917

Amateur Radio Center
2805 N E 2nd Avenue
Miami, FL 33137
(305) 573-8383 Arturo

Amateur Radio Supply of Nashville
615 South Gallatin Road
Madison, TN 37115
(615) 868-4956 Frank

Britts 2-Way Radio
2508 N Atlanta Road
Smyrna, GA 30080
(404) 432-8006 Dan

High Technology Electronics
3229A S Andrews Avenue
Ft. Lauderdale, FL 33316
(305) 764-8308 Jeff

HELP Radio
1055 Liberty Street
Jacksonville, FL 32206
(904) 356-8546 Al

WESTERN

Amateur Electronic Supply
1072 North Rancho Drive
Las Vegas, NV 89106
(702) 647-3114
800-634-6227

Burghardt Amateur Center
208 East Kemp Avenue
Watertown, SD 57201
(605) 886-7314 Jim

Conley Radio Supply
318 N 16th Street
Billings, MT 59101
(406) 259-9554 Ron

CW Electronic Sales
800 Lincoln Street
Denver, CO 80203
(303) 832-1111 Pete

Ham Radio Outlet
2620 West La Palma
Anaheim, CA 92801
(714) 761-3033 Earl
800-854-6046

Ham Radio Outlet
999 Howard Avenue
Burlingame, CA 94010
(415) 342-5757

Ham Radio Outlet
2811 Telegraph Avenue
Oakland, CA 94609
(415) 451-5757

Ham Radio Outlet
5375 Kearny Villa Road
San Diego, CA 92123
(714) 560-4900

Ham Radio Outlet
6265 Sepulveda Blvd.
Van Nuys, CA 91401
(213) 988-2212

CANADA

Colmay Products
14902 Beachview Avenue
White Rock, BC V4B 1N8
(604) 536-3058 Colin

Current Microlog Equipment and Accessory Price List

ATR-6800 System, 9" B&W Video, Application Module, Cable Kit	$ 2495
As Above, Less Video	$ 2370
Morse Trainer Module	$ 189
ARQ Mode B Receive Module	$ 189
Data Ecryption Board	$ 1000
BASIC/Mailbox/16K Bat	$ 599
Epson MX 80 Print, Custom Cable & Ser. Board	$ 600
Okidata 82A Print, With Custom Cable	$ 600
Extra ATR-6800 Manual Set	$ 25
ACT-1 System	$ 995
Bat Backup/Print (new) Add $25 for Previously Shipped Unit	$ 125
RF Video Modulator	$ 30
Monitor Ext. Legs	$ 7.50
Custom Interface Cable for MX80 or 82A Printer (Specify ATR or ACT-1)	$34.36
9" B&W Video	$ 199
12" B&W Video	$ 229
9" Green Video	$ 229
Extra ACT-1 Manual	$ 10

SANYO
VM 4509
MICROLOG CORPORATION/ACT-1
TONE
TUNE
POWER

MICROLOG

ACT-1

$995*

MEMORY BACK-UP

AND HIGH SPEED PRINTER OUTPUT*

Never Lose Your Memory Again!

All "Here-is" memories, ID's **and** all keyboard input parameters are retained for 2 weeks by the internal Ni-Cad battery & charging circuit. Load up the memories, carry the ACT-1 out to your field-day site and be ready to go as if you never turned it off! Also included in this option package is the high speed code converted RS-232 serial printer output.

The best gets better at MICROLOG Corp.
18713 Mooney Dr., Gaithersburg, MD 20879
Tel. 301-258-8400 TELEX 908153.

MICROLOG 51

INNOVATORS IN DIGITAL COMMUNICATION

• SIMPLE DIRECT CONNECTION to your Transceiver. • COMPLETE SYSTEM, built-in Demodulator & AFSK Modulator with keyboard programmable tone pairs from 500 to 3000 Hz. • SPLIT-SCREEN operation with keyboard selectable line location • 1400 character text buffer. • TEN, 40 CHAR. programmable message memories (doubles with BATT. BACKUP), plus ID's WRU & SELCALs. • RANDOM CODE generator & hand key input for practice. • Baudot 60 to 132 WPM. • ASCII 110 & 300 baud. • SYNC-LOC MODE for improved ASCII operation. • RECORDER INTERFACE for "BRAG-TAPE" or recording off-the-air. • CODE CONVERTED printer output in Baudot or ASCII. • SSTV/GRAPHICS transmit. • FULL 63 KEY Computer grade keyboard.

---

*9" monitor $199. Battery Backup & RS232 print $125.

Jack Martin W8XW
701 Radar Squadron
Box 1774
Kure Beach NC 28449

The Program That Knows It All

Repeater info, third-party agreements, you name it—this TRS-80 BASIC program knows it.

"Hey, OM. Shall I QRQ?"

"Er, uh, yeh. I guess." Boy, I sure wish I knew what he meant! Where did I put that list of Q-signals?

I operate contests quite a bit. I keep a dupe sheet in front of me, but I sure wish I could search through those calls faster!

Has it been ten minutes since I last IDed? Six minutes? Or 12?

Just showed that FCC examiner a few things and upgraded my license. Now let's explore this new territory . . . umm, how far down can I go? Am I in the phone portion of this new band?

Familiar situations? Well, now you can relax. This versatile program will put fun and pleasure back into your hamming. Just by inputting a bit of information about a repeater station (last three letters of its call, its frequency pair, or its location), the program will provide all the information concerning that repeater. If you are a contest operator, this program was made for you. It provides dupe sheet capability with memory and fast recall. No more lost contacts while you check your log to see if you worked that station. Those infrequently used Q-signals are now available when you need them and there is no more wondering whether that country has a third-party agreement before running the phone patch.

```
MENU OF COMMANDS
1. REPEATER INFO
2. CONTEST OPERATOR
3. Q-SIGNALS
4. THIRD-PARTY AGREEMENTS
5. IDER
6. FREQUENCY CHECK
7. EXIT
COMMAND?
```

Fig. 1. Sample run of commands available for user.

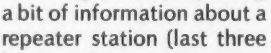

Fig. 2. Frequency check display showing 3.5-MHz band with operating frequency of 3.7 MHz. A display is provided for each band, 80-2 meters.

I remember when I upgraded and was operating on new and unfamiliar bands, I was constantly referring to a chart to see where the band limits were and if I was still in the phone or CW portion of the band. Before using this program, I still had to resort to that chart when I would occasionally operate on a seldom used band. Now the computer will verify the legality of my operating frequency and visually display where I am operating within that band.

Last but not least, the program provides a visual reminder to satisfy the station identification requirement and will give a flashing reminder when it is time to identify.

Written for the Radio Shack Level II TRS-80 with 16K memory, the program requires about 9K to run. Since there are no unique statements, it should readily adapt to other BASICs. The overall program is actually composed of seven different subprograms. By compartmentalizing it in this manner, the user may choose all or portions of the program to fit his particular needs or memory capability.

Program action is simple to follow. Just respond to the computer's requests and you cannot go astray. The program should be loaded and ready to use when the operator sits down for a hamming session. Then he will have all these capabilities at his fingertips.

Program Introduction: Statement lines 1 through 52 graphically introduce the program and ask the user to input his choice of subprograms. I have made extensive use of the INKEY$ function throughout the program. This allows faster responses and saves wasted effort by not having to use the ENTER key to input data. Safeguards have been incorporated to prevent the program from crashing if a wrong key is inadvertently hit.

Favorite Repeater: Statement lines 100 through 288 comprise the repeater infor-

MFJ ANTENNA TUNERS 16 MODELS

MFJ-941C 300 Watt Versa Tuner II

Has SWR/Wattmeter, Antenna Switch, Balun. Matches everything 1.8-30 MHz: dipoles, vees, random wires, verticals, mobile whips, beams, balanced lines, coax lines.

TRANSMITTER
SENS./POWER
MFJ
INDUCTANCE
ANTENNA
MFJ VERSA TUNER II
MODEL MFJ-941C

Ham Radio's most popular antenna tuner. Improved, too.

$89.95 (+ $4)

Fastest selling MFJ tuner . . . because it has the most wanted features at the best price.

Matches everything from 1.8-30MHz: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balanced and coax lines.

Run up to 300 watts RF power output.

SWR and dual range wattmeter (300 & 30 watts full scale, forward/reflected power). Sensitive meter measures SWR to 5 watts.

Flexible antenna switch selects 2 coax lines, direct or through tuner, random wire/balanced line, or tuner bypass for dummy load.

12 position efficient airwound inductor for lower losses, more watts out.

Built-in 4:1 balun for balanced lines. 1000V capacitor spacing.

Works with all solid state or tube rigs.

Easy to use, anywhere. Measures 8x2x6", has SO-239 connectors, 5-way binding posts, finished in eggshell white with walnut-grained sides.

4 Other 300W Models: MFJ-940B, $79.95 (+ $4), like 941C less balun. **MFJ-945, $79.95** (+ $4), like 941C less antenna switch. **MFJ-944, $79.95** (+ $4), like 945, less SWR/Wattmeter, **MFJ-943, $69.95** (+ $4), like 944, less antenna switch. Optional mobile bracket for 941C, 940B, 945, 944, $3.00.

MFJ-900 VERSA TUNER

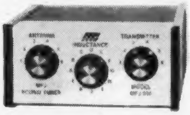

MFJ-900

$49.95 (+ $4)

Matches coax, random wires 1.8-30 MHz.

Handles up to 200 watts output; efficient airwound inductor gives more watts out. 5x2x6".

Use any transceiver, solid-state or tube.

Operate all bands with one antenna.

2 OTHER 200W MODELS:

MFJ-901, $59.95 (+ $4), like 900 but includes 4:1 balun for use with balanced lines.

MFJ-16010, $39.95 (+ $4), for random wires only. Great for apartment, motel, camping, operation. Tunes 1.8-30 MHz.

MFJ-949B VERSA TUNER II

MFJ-949B

$139.95 (+ $4)

MFJ's best 300 watt Versa Tuner II.

Matches everything from 1.8-30 MHz, coax, randoms, balanced lines, up to 300W output, solid-state or tubes.

Tunes out SWR on dipoles, vees, long wires, verticals, whips, beams, quads.

Built-in 4:1 balun. 300W, 50-ohm dummy load. SWR meter and 2-range wattmeter (300W & 30W).

6 position antenna switch on front panel, 12 position air-wound inductor; coax connectors, binding posts, black and beige case 10x3x7".

MFJ-962 VERSA TUNER III

MFJ-962

$229.95 (+ $10)

Run up to 1.5 KW PEP, match any feed line from 1.8-30 MHz.

Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected.

6 position antenna switch handles 2 coax lines (direct or through tuner), wire and balanced lines.

4:1 balun. 250 pf 6KV cap. 12 pos. inductor. Ceramic switches. Black cabinet, panel.

ANOTHER 1.5 KW MODEL: MFJ-961, $189.95 (+ $10), similar but less SWR/Wattmeter.

MFJ-10, 3 foot coax with connectors, $4.95.

MFJ-984 VERSA TUNER IV

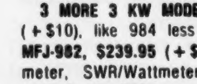

MFJ-984

$329.95 (+ $10)

Up to 3 KW PEP and it matches any feedline, 1.8-30 MHz, coax, balanced or random.

10 amp RF ammeter assures max. power at min. SWR. SWR/Wattmeter, for./ref., 2000/200W.

18 position dual inductor, ceramic switch.

7 pos. ant. switch. 250 pf 6KV cap. 5x14x14".

300 watt dummy load. 4:1 ferrite balun.

3 MORE 3 KW MODELS: MFJ-981, $239.95 (+ $10), like 984 less ant. switch, ammeter. **MFJ-982, $239.95 (+ $10),** like 984 less ammeter, SWR/Wattmeter. **MFJ-980, $209.95 (+ $10),** like 982 less ant. switch.

MFJ-989 VERSA TUNER V

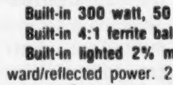

MFJ-989

$329.95 (+ $10)

New smaller size matches new smaller rigs — only 10-3/4Wx4-1/2Hx14-7/8D".

3 KW PEP. 250 pf-6KV caps. Matches coax, balanced lines, random wires 1.8-30 MHz.

Roller inductor, 3-digit turns counter plus spinner knob for precise inductance control to get that SWR down.

Built-in 300 watt, 50 ohm dummy load.

Built-in 4:1 ferrite balun.

Built-in lighted 2% meter reads SWR plus forward/reflected power. 2 ranges (200 & 2000W).

6 position ant. switch. Al. cabinet. Tilt bail.

↙47

To order or for your nearest dealer

CALL TOLL FREE

800-647-1800

For tech. info., order or repair status, or calls outside continental U.S. and inside Miss., call 601-323-5869.

- **All MFJ products unconditionally guaranteed for one year (except as noted).**
- **Products ordered from MFJ are returnable within 30 days for full refund (less shipping).**
- **Add shipping & handling charges in amounts shown in parentheses.**

Write for FREE catalog, over 80 products

MFJ ENTERPRISES, INCORPORATED
Box 494, Mississippi State, MS 39762

↙*See List of Advertisers on page 130*

Program listing.

```
1 REM JACK MARTIN - W8XW
2 REM MAY 1980
9 CLEAR1000
10 DIMF$(10)
11 DIMC$(100)
12 CLS:PRINTCHR$(23)
14 PRINT@448,"*** H A M  H E L P E R ***"
16 FORY=1TO5
18 PRINT@710,"C Q  -  C Q  -  C Q"
20 FORX=1TO200:NEXTX
22 PRINT@710,"                       "
24 FORX=1TO200:NEXTX
26 NEXTY
28 CLS:PRINT"MENU OF COMMANDS"
30 PRINTSTRING$(55,"=");
32 PRINT:PRINT
34 PRINT"1. REPEATER INFO"
36 PRINT"2. CONTEST OPERATOR"
38 PRINT"3. Q - SIGNALS"
40 PRINT"4. THIRD - PARTY AGREEMENTS"
42 PRINT"5. ID 'ER"
44 PRINT"6. FREQUENCY CHECK"
46 PRINT"7. EXIT"
48 PRINT:PRINT"COMMAND?"
50 GOSUB10000:IFVAL(KB$)<1ORVAL(KB$)>8GOTO50
52 ONXGOTO100,300,500,700,900,1100,2100
100 CLS:PRINT"FAVORITE REPEATER INFO"
102 PRINT
104 PRINT"THIS PROGRAM WILL PROVIDE INFORMATION ABOUT"
106 PRINT"YOUR FAVORITE REPEATER(S). ENTER THE LAST"
108 PRINT"THREE LETTERS OF ITS CALL OR THE FREQUENCY"
110 PRINT"PAIR (13/73) OR THE NAME OF THE CITY WHERE"
112 PRINT"REPEATER IS LOCATED."
114 PRINT:PRINT
116 INPUT"STATION";S$
118 X=0:D$="DEG."
120 IFS$="ACO"ORS$="34/94"ORS$="BECKLEY"GOSUB200
121 IFS$="AER"ORS$="22/82"ORS$="CHARLESTON"GOSUB201
122 IFS$="AFE"ORS$="28/88"ORS$="ROANOKE"GOSUB202
198 IFX>0THEN282
199 GOTO280
200 PRINT"WR8ACO,34/94,350 ";D$;" ,BECKLEY,WV":X=1:RETURN
201 PRINT"WR8AER,22/82,345 ";D$;" ,CHARLESTON,WV":X=1:RETURN
202 PRINT"WR4AFE,28/88,76 ";D$;" ,ROANOKE,VA":X=1:RETURN
280 PRINT:PRINT"THAT STATION IS NOT ON FILE"
282 PRINT:PRINT"ANOTHER STATION (y/N)?"
284 GOSUB10005
286 IFKB=89GOTO114
287 IFKB<>78GOTO284
288 IFKB=78GOTO28
300 CLS
302 PRINT"JUST ENTER CALL SIGN AND COMPUTER WILL LET"
304 PRINT"YOU KNOW IF IT IS A DUPLICATE."
306 PRINT:PRINT
308 INPUT"STATION (INPUT 'S' TO STOP):";A$
310 IFA$="S"GOTO28
312 LETX=0
314 X=X+1
316 IFC$(X)=""THEN322
318 IFC$(X)=A$THEN336
320 GOTO314
322 PRINT:PRINT"THAT IS A NEW ONE -- CALL IT"
324 PRINT:PRINT"WANT IT LOGGED (Y/N)?"
326 GOSUB10005
327 IFKB=89GOTO332
328 IFKB<>78GOTO326
330 IFKB=78GOTO306
332 LETC$(X)=A$
334 GOTO306
336 PRINT"ALREADY WORKED HIM --"
338 GOTO306
470 ,":"
475 ,":"
500 CLS:INPUT"Q - SIGNAL (ENTER 'S' TO STOP):";Q$
502 IFQ$="S"GOTO28
504 X=0
506 RESTORE
508 FORJ=1TO24
510 READA$
512 IFA$="END"GOTO550
514 IFA$=Q$GOTO520
516 NEXTJ
518 IFX>0THEN552
520 ONJGOSUB525,526,527,528,529,530,531,532,533,534,535,536,537,538,539,
     540,541,542,543,544,545,546,547:GOTO518
525 PRINT"QRL: ARE YOU BUSY?":X=1:RETURN
526 PRINT"QRM: AM I BEING INTERFERED WITH?":X=1:RETURN
527 PRINT"QRN: IS THERE STATIC?":X=1:RETURN
528 PRINT"QRO: SHALL I INCREASE POWER?":X=1:RETURN
529 PRINT"QRP: SHALL I DECREASE POWER?":X=1:RETURN
530 PRINT"QRQ: SHALL I SEND FASTER?":X=1:RETURN
531 PRINT"QRS: SHALL I SEND SLOWER?":X=1:RETURN
532 PRINT"QRT: SHALL I STOP SENDING?":X=1:RETURN
533 PRINT"QRU: HAVE YOU ANYTHING FOR ME?":X=1:RETURN
534 PRINT"QRV: ARE YOU READY?":X=1:RETURN
535 PRINT"QRX: WHEN WILL YOU CALL AGAIN?":X=1:RETURN
536 PRINT"QRZ: WHO IS CALLING ME?":X=1:RETURN
537 PRINT"QSB: ARE MY SIGNALS FADING?":X=1:RETURN
538 PRINT"QSK: DO YOU HAVE BREAK-IN?":X=1:RETURN
539 PRINT"QSL: DO YOU ACKNOWLEDGE RECEIPT?":X=1:RETURN
540 PRINT"QSM: SHALL I REPEAT LAST MESSAGE?":X=1:RETURN
541 PRINT"QSP: WILL YOU RELAY?":X=1:RETURN
542 PRINT"QSV: SHALL I SEND A SERIES OF V'S?":X=1:RETURN
543 PRINT"QSY: SHALL I CHANGE FREQUENCY?":X=1:RETURN
544 PRINT"QTB: WORD COUNT AGREE?":X=1:RETURN
545 PRINT"QTC: HOW MANY MESSAGES DO YOU HAVE?":X=1:RETURN
546 PRINT"QTH: WHAT IS YOUR LOCATION?":X=1:RETURN
547 PRINT"QTR: WHAT IS YOUR TIME?":X=1:RETURN
550 PRINT:PRINT"THAT ONE IS NOT ON FILE"
552 PRINT:PRINT"ANOTHER ONE (Y/N)?"
554 GOSUB10005
556 IFKB=89GOTO500
557 IFKB<>78GOTO554
558 IFKB=78GOTO28
600 DATA"QRL","QRM","QRN","QRO","QRP","QRQ","QRS","QRT"
601 DATA"QRU","QRV","QRX","QRZ","QSB","QSK","QSL","QSM"
602 DATA"QSP","QSV","QSY","QTB","QTC","QTH","QTR"
603 DATA"END"
700 CLS:PRINT"THIRD - PARTY AGREEMENTS"
702 PRINTSTRING$(55,"=");
704 PRINT
706 PRINT"(LU) ARGENTINA       (HC) ECUADOR         (EL) LIBERIA"
708 PRINT"(CP) BOLIVIA         (YS) EL SALVADOR     (XE) MEXICO"
710 PRINT"(PY) BRAZIL          (TG) GUATAMALA       (YN) NICARAGUA"
712 PRINT"(VE) CANADA          (8R) GUYANA          (HP) PANAMA"
714 PRINT"(CE) CHILE           (HH) HAITI           (ZP) PARAGUAY"
716 PRINT"(HK) COLUMBIA        (HR) HONDURAS        (OA) PERU"
718 PRINT"(TI) COSTA RICA      (4X4) ISRAEL         (9Y4) TRINIDAD"
720 PRINT"(CM) CUBA            (6Y5) JAMAICA        (CX) URUGUAY"
722 PRINT"(HI) DOMINICAN REP.  (JY) JORDAN          (YV) VENEZUELA"
724 PRINTSTRING$(55,"=");
726 PRINT:PRINT"HIT 'C' TO CONTINUE"
728 GOSUB10005
730 IFKB=67GOTO28
732 IFKB<>67GOTO728
900 CLS:PRINTCHR$(23)
902 PRINT@128,"HIT 'S' TO STOP"
904 PRINT@192,"HIT 'R' TO RESET"
906 A=1:B=0:C=0:D=0
908 PRINT@448,A;"    ";B;"  ";C;"    ";D
910 B=10
911 E=60
913 PRINT@470," ";
914 FORX=1TO320:NEXTX:E=E-1
915 PRINT@470,": ";
918 LETQ$=INKEY$
920 IFQ$="R"GOTO906
922 IFQ$="S"GOTO28
928 IFE=-1GOTO932
930 GOTO913
932 A=0:B=B-1:C=0:D=0
934 PRINT@448,A;"    ";B;"  ";C;"    ";D
936 IFB=0GOTO940
938 GOTO911
940 LETQ$=INKEY$
942 IFQ$="R"GOTO906
944 IFQ$="S"GOTO28
950 PRINT@832,"I D E N T I F Y ! !":FORX=1TO200:NEXTX
952 PRINT@832,"                   ":FORX=1TO200:NEXTX
954 GOTO940
1100 CLS:PRINT"CLASS OF LICENSE"
1102 PRINTSTRING$(55,"=");
1104 PRINT
1106 PRINT"<N>OVICE"
1108 PRINT"<T>ECHNICIAN"
1110 PRINT"<G>ENERAL (OR CONDITIONAL)"
1112 PRINT"<A>DVANCED"
1114 PRINT"<E>XTRA"
1116 PRINT
1118 PRINT"WHICH CLASS ARE YOU?"
1119 GOSUB10005
1120 IFKB=78ORKB=84ORKB=71ORKB=65ORKB=69GOTO1122
1121 IFKB<>78ORKB<>84ORKB<>71ORKB<>65ORKB<>69GOTO1119
1122 LETC=KB
1124 CLS:PRINT"BANDS OF OPERATION"
1126 PRINTSTRING$(55,"=");
```

mation program. When the user responds with the last three letters of the repeater's callsign, its frequency pair (e.g., 13/73), or the city where it is located, the computer will display pertinent information concerning that repeater. One helpful bit of data provided is the proper beam heading for that repeater. Lines 120 through 197 and 200 to 279 are reserved for the user to insert information pertaining to his favorite repeaters. I have put data in these lines just to provide formatting examples.

Contest Logger: This routine is the answer to the contester's prayers. It resides from lines 300 to 338. It will ask for the callsign of the station, check memory, and, if not already logged, will tell the operator that it is a new contact and to call it. If contact is made, the call can be saved in memory for recall later. If the station was previously logged, the user will be informed so that a different station can be checked. Searching action is completed in seconds—a lot easier than trying to find a callsign in a stack of dupe sheets! Statement line 11 is initialized for 100 contacts. This can be adjusted if desired.

Q-Signals: How many times have you heard a Q-signal used and tried to remember its meaning? Statement lines 500 through 603 provide instant recall. The user enters his own catalog of Q-signals into DATA statements beginning on line 600. I have already inserted 23 signals. These can be altered to suit individual needs. The only program modification required is changing the DATA statements and lines 525 through 547 to support the changes made. Be sure the last DATA element is "END".

Third-Party Agreements: This program will display the list of countries with which the United States has third-party agreements. Statement lines 700 to 732 support this function. The list includes call letter prefixes. If the country is not listed, do not make that phone patch!

Station Identification: The operator can initiate this program when the QSO

```
1128 PRINT
1130 PRINT"1. 3.5 (80M)                  5. 28.0 (10M)"
1132 PRINT"2. 7.0 (40M)                  6. 50.0 (6M)"
1134 PRINT"3. 14.0 (20M)                 7. 144.0 (2M)"
1136 PRINT"4. 21.0 (15M)                                  "
1138 PRINT
1140 PRINT
1142 PRINT"WHICH BAND ARE YOU OPERATING ON?"
1144 GOSUB10000:IFVAL(KB$)<1ORVAL(KB$)>7GOTO1144
1146 LETB=X
1148 IFC=78GOTO1152
1150 IFC=84GOTO1154
1151 IFC=71ORC=65ORC=69GOTO1156
1152 IFB=3ORB=6ORB=7THENPRINT"NOVICES CANNOT OPERATE THERE":GOTO1182
1153 IFB=1ORB=2ORB=4ORB=5GOTO1156
1154 IFB=1ORB=2ORB=3ORB=4ORB=5THENPRINT"TECHS ARE NOT ALLOWED":GOTO1182
1156 CLS:PRINT"MODE OF OPERATION: <C>W  OR  <P>HONE?"
1157 GOSUB10005
1158 IFKB=67ORKB=80GOTO1160
1159 IFKB<>67ORKB<>80GOTO1157
1160 LETM=KB:IFC=84ANDM=67THENPRINT"TECHNICIANS CANNOT USE CW":GOTO1182
1161 IFC=78ANDM=80THENPRINT"NOVICES DO NOT HAVE PHONE PRIVILEGES":GOTO1182
1162 PRINT:PRINT
1164 PRINT"WHAT IS YOUR PRESENT OPERATING"
1166 INPUT"FREQUENCY (I.E., 14.32)";F
1168 IFC=78GOTO1300
1170 IFC=84GOTO1320
1172 IFC=71GOTO1330
1174 IFC=65GOTO1370
1176 IFC=69GOTO1410
1178 LETX=INT(RND(5))
1180 ONXGOSUB1190,1192,1194,1196,1198
1182 PRINT:PRINT"DO YOU WISH A NEW FREQUENCY CHECK (Y/N)?"
1184 GOSUB10005
1186 IFKB=89GOTO1124
1188 IFKB<>78GOTO1184
1189 IFKB=78GOTO28
1190 PRINT"SORRY - YOU'RE ILLEGAL!!":RETURN
1192 PRINT"BETTER GET BACK IN THE BAND.":RETURN
1194 PRINT"CHECK YOUR VFO. YOU'RE OUT OF THE BAND!":RETURN
1196 PRINT"HERE COMES THE PINK SLIP!":RETURN
1198 PRINT"GOTCHA YOU!!":RETURN
1300 IFF>=3.70ANDF<=3.75GOTO1310
1302 IFF>=7.10ANDF<=7.15GOTO1310
1304 IFF>=21.10ANDF<=21.20GOTO1310
1306 IFF>=28.10ANDF<=28.20GOTO1310
1308 GOTO1178
1310 IFM=80THENPRINT"NOVICES DO NOT HAVE PHONE PRIVILEGES":GOTO1182
1312 GOTO1500
1320 IFF>=50.10ANDF<=54.00GOTO1500
1322 IFF>=145.00ANDF<=148.00GOTO1500
1324 GOTO1178
1330 IFF>=3.525ANDF<=3.775GOTO1358
1332 IFF>=3.89ANDF<=4.00GOTO1500
1334 IFF>=7.025ANDF<=7.15GOTO1358
1336 IFF>=7.225ANDF<=7.30GOTO1500
1338 IFF>=14.025ANDF<=14.20GOTO1358
1340 IFF>=14.275ANDF<=14.35GOTO1500
1342 IFF>=21.025ANDF<=21.25GOTO1358
1344 IFF>=21.35ANDF<=21.45GOTO1500
1346 IFF>=28.00ANDF<=28.50GOTO1358
1348 IFF>=28.51ANDF<=29.70GOTO1500
1350 IFF>=50.10ANDF<=54.00GOTO1500
1352 IFF>=144.0ANDF<=144.10GOTO1358
1354 IFF>=144.11ANDF<=148.00GOTO1500
1356 GOTO1178
1358 IFM=80THENPRINT"YOU ARE NOT IN THE PHONE PORTION":GOTO1182
1360 GOTO1500
1370 IFF>=3.525ANDF<=3.775GOTO1400
1372 IFF>=3.80ANDF<=4.00GOTO1500
1374 IFF>=7.025ANDF<=7.150GOTO1400
1376 IFF>=7.151ANDF<=7.30GOTO1500
1378 IFF>=14.025ANDF<=14.200GOTO1400
1380 IFF>=14.210ANDF<=14.35GOTO1500
1382 IFF>=21.025ANDF<=21.25GOTO1400
1384 IFF>=21.275ANDF<=21.45GOTO1500
1386 IFF>=28.00ANDF<=28.50GOTO1400
1388 IFF>=28.51ANDF<=29.70GOTO1500
1390 IFF>=50.00ANDF<=50.10GOTO1400
1392 IFF>=50.11ANDF<=54.00GOTO1500
1394 IFF>=144.00ANDF<=144.10GOTO1400
1396 IFF>=144.11ANDF<=148.00GOTO1500
1398 GOTO1178
1400 IFM=80THENPRINT"YOU ARE OUT OF THE PHONE BAND":GOTO1182
1402 GOTO1500
1410 IFF>=3.50ANDF<=3.775GOTO1440
1412 IFF>=3.776ANDF<=4.00GOTO1500
1414 IFF>=7.00ANDF<=7.15GOTO1440
1416 IFF>=7.16ANDF<=7.30GOTO1500
1418 IFF>=14.00ANDF<=14.20GOTO1440
1420 IFF>=14.21ANDF<=14.35GOTO1500
1422 IFF>=21.00ANDF<=21.250GOTO1440
1424 IFF>=21.251ANDF<=21.45GOTO1500
1426 IFF>=28.00ANDF<=28.50GOTO1440
1428 IFF>=28.51ANDF<=29.70GOTO1500
1430 IFF>=50.00ANDF<=50.10GOTO1440
1432 IFF>=50.11ANDF<=54.00GOTO1500
1434 IFF>=144.00ANDF<=144.10GOTO1440
1436 IFF>=144.11ANDF<=148.00GOTO1500
1438 GOTO1178
1440 IFM=80THENPRINT"BETTER GET BACK IN THE PHONE BAND":GOTO1182
1442 GOTO1500
1500 ONBGOTO1510,1550,1570,1590,1600,1610,1620
1510 GOSUB1700
1512 X=835:A=3.5:H=3.6:M=3.7:D=3.8:E=3.9:G=4.0:J=127
1514 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E:PRINT@X+50,
     G
1515 X=832
1516 GOTO1900
1550 GOSUB1700
1552 X=835:A=7.0:H=7.1:M=7.2:D=7.3:J=127
1554 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D
1555 X=828
1556 IFF>=AANDF<HTHENZ=(F-A)+A:Y=0:GOSUB1800:GOTO1182
1558 IFF>=HANDF<MTHENZ=(F-H)+H:Y=10:GOSUB1800:GOTO1182
1560 IFF>=MANDF<DTHENZ=(F-M)+M:Y=20:GOSUB1800:GOTO1182
1561 IFF=DTHENZ=(F-M)+M:Y=28:GOSUB1800:GOTO1182
1570 GOSUB1700
1572 X=835:A=14.0:H=14.1:M=14.2:D=14.3:E=14.35:J=127
1574 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E
1575 X=821
1576 GOTO2000
1590 GOSUB1700
1592 X=835:A=21.0:H=21.1:M=21.2:D=21.3:E=21.4:G=21.45:J=127
1594 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E:PRINT@X+50,
     G
1595 X=814
1596 GOTO1900
1600 GOSUB1700
1602 X=835:A=28.0:H=28.5:M=29.0:D=29.5:E=29.7:J=127
1604 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E
1605 X=807
1606 GOTO2000
1610 GOSUB1700
1612 X=835:A=50.0:H=51.0:M=52.0:D=53.0:E=54.0:J=127
1614 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E
1615 X=785
1616 GOTO2000
1620 GOSUB1700
1622 X=835:A=144.0:H=145.0:M=146.0:D=147.0:E=148.0:J=127
1624 PRINT@X,A:PRINT@X+10,H:PRINT@X+20,M:PRINT@X+30,D:PRINT@X+40,E
1625 X=691
1626 GOTO2000
1700 CLS:Y=36
1702 FORX=10TO110
1704 SET(X,Y)
1706 NEXTX
1708 Y=37
1710 SET(10,Y)
1712 SET(30,Y)
1714 SET(50,Y)
1716 SET(70,Y)
1718 SET(90,Y)
1720 SET(110,Y)
1722 RETURN
1800 PRINT@(X+Y+Z)-J," V";
1808 PRINT@128,"HIT 'C' TO CONTINUE"
1810 LETQ$=INKEY$
1812 IFQ$="C"RETURN
1900 IFF>=AANDF<HTHENZ=(F-A)+A:Y=0:GOSUB1800:GOTO1182
1902 IFF>=HANDF<MTHENZ=(F-H)+H:Y=10:GOSUB1800:GOTO1182
1904 IFF>=MANDF<DTHENZ=(F-M)+M:Y=20:GOSUB1800:GOTO1182
1906 IFF>=DANDF<ETHENZ=(F-D)+D:Y=30:GOSUB1800:GOTO1182
1908 IFF>=EANDF<GTHENZ=(F-E)+E:Y=40:GOSUB1800:GOTO1182
1909 IFF=GTHENZ=(F-E)+E:Y=48:GOSUB1800:GOTO1182
2000 IFF>=AANDF<HTHENZ=(F-A)+A:Y=0:GOSUB1800:GOTO1182
2002 IFF>=HANDF<MTHENZ=(F-H)+H:Y=10:GOSUB1800:GOTO1182
2004 IFF>=MANDF<DTHENZ=(F-M)+M:Y=20:GOSUB1800:GOTO1182
2006 IFF>=DANDF<ETHENZ=(F-D)+D:Y=30:GOSUB1800:GOTO1182
2007 IFF=ETHENZ=(F-D)+D:Y=38:GOSUB1800:GOTO1182
2100 CLS:PRINTCHR$(23)
2102 PRINT@448,"7 3   &   G O O D   D X ! !"
2104 FORX=1TO1000:NEXTX
2106 CLS:END
10000 KB$=INKEY$:IFKB$=""GOTO10000
10001 LETX=VAL(KB$):RETURN
10005 KB$=INKEY$:IFKB$=""GOTO10005
10015 KB=ASC(KB$):RETURN
```

(where's that Q-signal program!) begins. A visual timer will be displayed, updated each minute, and provide a flashing reminder when the time limit has expired and station identification must be made. When the ID has been made, the time can be reset and the sequence repeated. Reset can occur any time by hitting the "R" key. Hitting "S" returns the program to the menu of commands. This IDer routine is in statement lines 900 to 954. The timing sequence is software controlled (FOR . . . NEXT loop) and may have to be adjusted to allow for differences in machines. Line 914 controls this timing.

Frequency Check: The largest and most complex subprogram, it resides from lines 1100 to 2007. Don't let that scare you, though. If you answer all prompts and data requests when required, the computer will provide the proper response. The program is designed to give the operator the security of knowing his operation is within the band limits established for his license. This verification is supported as the program is run and then reinforced by graphically displaying the operating frequency.

The frequency program can be customized for specific requirements. For example, if you always intend to remain a General, eliminate lines 1102 through 1121 and change lines 1100 and 1122 to read:

```
1100 CLS
1122 LET C=71
```

This eliminates answering the class of license question each time the program is run. If your operation is confined to one band, make variable B at line 1146 the applicable value. Also, if you never use CW, make M=80 at line 1160 to establish phone-only operation (also delete lines 1156 and 1157).

As previously stated, this is a highly versatile and useful program, either piecemeal or in its entirety. I believe it contains some routines which every ham will find helpful. I hope it will take some of the paperwork out of your operation and give you more time to rag-chew! ■

Edward W. Crandell WD8CBE
Rte. 8, Box 79
Warsaw IN 46580

Berserk Direction-Finding

Zero in on transmitters in seconds with this TRS-80 program. It will tell you how to get there, too.

In any radio direction finding operation, whether it be tracking a jammer or a distress signal, the time factor is important. The Radio Amateur RDF Assistant minimizes the time involved in tracking a transmitter. The program allows the operator to determine the general location of the transmitter instantly by entering the headings to the transmitter from two stations whose locations are known. The advantages of this method over the standard map, protractor, and straightedge approach are speed and accuracy. The high speed of the operation allows for comparison of headings from different stations and for quick, repeated calculations if the transmitter is moving.

Other features of the program include the giving of directions to the transmitter for field units and providing a listing of the DF committee members and repeater users, with their calls, phone numbers, and distances and directions to the transmitter, allowing the RDF net control to coordinate the efforts of the stations in reaching the transmitter site. The data for this listing is stored on tape, so the user may have different tapes for different repeaters or bands.

Instructions

After you have CLOADed the program and entered RUN, the computer will ask you if you want the data tape loaded before continuing with the program. You would normally do this when stations will not be giving you bearings immediately, such as right after a jammer or ELT has appeared on frequency. If you need to determine the transmitter's location immediately and have the appropriate information, enter N and the program will continue. You may load the tape later if needed by selecting that option from the menu.

Next, the computer will ask you for the coordinates of station A. Type in the horizontal coordinate, a comma, and the vertical coordinate of the first station that you will be taking a bearing from. (This information can be found by preparing an RDF Map and a Station Data Sheet described later.) Press ENTER and the computer will then ask you the bearing that that station has on the transmitter. Type in this and press ENTER. Repeat the procedure for station B, using a second station. It should be noted that you should not enter two stations that have the same bearings or whose bearings have a difference of 180°. This will result in a divide-by-zero error. This situation is rare and even if the computer were not used the results would be meaningless. The user should simply select another station to replace one of these.

Once this has been done, the transmitter's location is printed along with directions and distances from stations A and B to the transmitter. To see the list of options available, press ENTER.

The first option is DF-Fix Calculations, which was just described. You would select this option if you want to enter a new set of headings to the transmitter. This is the only option that affects the transmitter's location. The other options only use this data to provide related information.

The second option provides directions to the transmitter for a field unit. The computer will ask you for the coordinates of the

RTTY/CW
For the TRS-80*

* A Trademark of the Tandy Corp.

ROM-116
Now includes:
•TEXT EDITING
•RTTY PICTURES
•SAVE TEXT TO DISK *Detailed brochure available on request.*

Featuring:

1200 BAUD OPERATION. Not limited to 110 baud because of timing loops. 60, 66, 75 & 100 W.P.M. Plus 110, 150, 300, 600 & 1200 baud operations possible.
FLEXIBILITY OF OPERATION. Instantly change: Baud Rates; Program Mode (ASCII/Baudot); Program Status.
SPLIT SCREEN VIDEO. Transmit & receive data displayed separately.
REAL TIME. Automatic CW/ID without user intervention. Automatically updates at end of month or year.

Other features include:
- Two Serial Ports
- Fourteen Buffers
- Automatic CW/ID
- Transmit Control
- Selective Call Feature
- Error Correction & Editing
- Word Wraping
- Easy to Interface
- 30 Day Unconditional Guarantee
- Hardware Requirements: TRS-80 Model I or III 16K EXTERNAL TERMINAL UNIT REQUIRED

CROWN MicroProducts
606 State Street, P.O. Box 892-R • Marysville, WA 98270 • (206) 659-4279

CRAIG
Star View Systems™

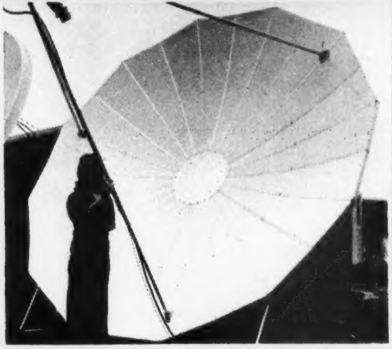

STAR VIEW MODEL 12K
- Complete System
- Easy to Install
- Reasonably Priced
- UPS Shippable Weight 125 Pounds
- More than 100 Channels Accessible

THE STAR VIEW 12K SYSTEM KIT CONTAINS:
- 12 Foot Antenna
- Azimuth Elevation Mount
- 24 Channel Receiver
- 120° Low Noise Amplifier
- Feed Horn
- Cables & Connectors
- No Modular Included (May be ordered separately for $79.95)

$2595.00

Available through your local Craig Star View dealer • Call or write for information • Dealership inquiries welcome • Price subject to change without notice.

H&R COMMUNICATIONS, INC. Subsidiary of Craig Corp.
Route 3, Box 103G
Pocahontas, Arkansas 72455
Call 800-643-0102
or 501-647-2291
✓86

MFJ
24 HOUR
CLOCKS

Your choice: dual 24 hour LCD display, or 24/12 hour with ID timer, or 12 inch quartz analog.

$39.95 DUAL 24 HOUR LCD MFJ-104

Two independant 24 hour LCD displays! Read both GMT and local times at a glance.
Six digit main display has seconds readout. Four digit auxiliary. Switch reverses main/aux.
Alarm plays 4 selectable melodies. Alarm "ON" indicator. Snooze button.
Quartz timing. Synchronizable to WWV.
Flip-top cover serves as stand.
Night light. Forward/reverse, fast/slow set buttons. Lock function prevents mis-setting. Display main time only, main/auxiliary or main/alarm time. Includes battery. 4x2x1/2 inches.

24/12 HOUR, ID TIMER MFJ-102 $32.95

Switchable 24 hour GMT or 12 hour format.
ID timer sounds every 9 minutes after reset.
Switchable seconds readout.
Observed timer. Just start clock from zero and note time of event up to 24 hours.
Bright blue 0.6" vacuum fluorescent digits.
Alarm with snooze function. Synchronizable with WWV. Fast/slow set buttons. Lock function prevents mis-setting. Power out, alarm "ON" indicators. 110 VAC, 60 Hz (50 Hz with simple modification). UL approved.
Black, brushed aluminum top/front. 6x2x3".

24 HOUR QUARTZ MFJ-105 $49.95

True 24 hour quartz wall clock has huge 12 inch diameter face. Gives excellent visability across computer/radio room.
Fifteen seconds per month accuracy.
Single "AA" battery provides over one year operation, immunity from power line failure and eliminates power cord.
Sweep second hand. Brown hi-impact case. Glass front. 24 hour military time format.

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping).
One year unconditional guarantee.
Order yours today. Call toll free 800-647-1800. Charge VISA, MC. Or mail check, money order. Add $4.00 each for shipping and handling.

CALL TOLL FREE 800-647-1800

Call 601-323-5869 in Miss., outside continental USA, tech/repair info. Telex 53-4590 MFJ STKV

MFJ ENTERPRISES, INCORPORATED
Box 494, Mississippi State, MS 39762 ✓47

field unit. Enter these coordinates. The coordinates can be found by finding the field unit on the RDF Map and finding its corresponding coordinates. The computer will then display the transmitter's location and the distance and directions to the transmitter from the field unit. This information is presented in two forms to allow for different types of field units. If the field unit is a car restricted to streets, the north/south and east/west directions are more appropriate. On the other hand, if the field unit is on foot or in open country, distance and bearing information is more relevant.

The third option is the DF-Net Listing. To use this option, you must have loaded the data tape in or inserted new data (option 5.2) during the current run of the program. The computer will first ask you for a maximum report range. The computer will list only those stations which are within the number of miles you entered to the transmitter. The computer will then ask if you want only DF committee members (those with asterisks at the front of their calls) to be listed. Enter either Y or N. The computer will then list the stations on the screen. It will only show eleven stations at one time, so merely press ENTER to see the next set of eleven. After the computer has listed all of the stations that have met the given requirements, it will tell how many stations were within the given range. You must press ENTER to see the list of options.

The fourth option is to load the data tape. The computer will guide you through the process of loading the tape. The menu will be displayed after the tape has been loaded.

The fifth option allows you to modify the data tape of the DF-Net stations (callsign, phone number, and location). How to determine the station's location will be discussed later. This option has five options of its own. The first merely lists the data. This allows you to check the data and see what, if anything, needs to be changed. The number displayed on the extreme left is a record number. This is the record number you will use in options 2 and 3. Before using options 2 and 3, it is a good idea to check the listing to make sure that you select the right number. To insert a new record, first determine after which record you would like the new record inserted. If it is the first record to be inserted, insert it after 0.

The third option is the delete option. If you have a station which is no longer active or needs to be deleted for some other reason, find it on the listing (option 1) and note its record number. Then select option 3. Enter this number in response to the computer's question about which record number should be deleted. If you choose to de-

```
4 REM RADIO AMATEUR RDF ASSISTANT
5 REM PROGRAM BY EDWARD W. CRANDELL
6 REM             RT B BOX 79
7 REM             WARSAW, IN  46580
10 CLEAR5000
11 M=100
12 DIM D$(M),E$(M),X(M),Y(M)
15 CLS:PRINT"RADIO AMATEUR RDF ASSISTANT":PRINT
20 INPUT"DO YOU WANT TO LOAD THE DATA TAPE NOW (Y OR N)";G$:CLS
21 IF G$="Y"THEN GOSUB240
39 REM DF-FIX CALCULATIONS
40 CLS:PRINT"STATION A":INPUT"COORDINATES";A,B
45 INPUT"BEARING";C:PRINT
50 PRINT"STATION B":INPUT"COORDINATES";D,E
60 INPUT"BEARING";F:PRINT
75 C=450-C:F=450-F
90 C=TAN(C*3.14159/180):F=TAN(F*3.14159/180)
100 G=((F*D)+B-E-(C*A))/(F-C):H=C*(G-A)+B
105 G=INT(G*10+.5)/10:H=INT(H*10+.5)/10
110 X=A:Y=B:GOSUB2000:CLS:PRINT"TRANSMITTER'S COORDINATES: ";G",";H
111 PRINT:PRINT"DISTANCE FROM STATION A:";U"MILES":GOSUB1900
113 X=D:Y=E:GOSUB2000:PRINT"DISTANCE FROM STATION B:";U"MILES":GOSUB1900:INPUT"PRESS ENTER TO CONTINUE";P:CLS:GOTO300
140 REM FIELD UNIT ROUTINE
145 INPUT"FIELD UNIT'S COORDINATES";X,Y
150 PRINT"TRANSMITTER'S COORDINATES: "G","H:GOSUB2000
160 PRINT:PRINT"BEARING TO TRANSMITTER:"Z
165 PRINT"DISTANCE TO TRANSMITTER:"U:GOSUB1900:GOTO300
180 REM DF-NET LISTING
181 IFDF=0THENPRINT"***DATA TAPE HAS NOT BEEN LOADED***":PRINT"PLEASE LOAD DATA TAPE OR SELECT ANOTHER OPTION"ELSE185
182 GOTO300
185 INPUT"MAXIMUM REPORT RANGE";L
190 INPUT"DF-COMMITTEE MEMBERS ONLY";H$
191 R=0:V=0:RN=1
195 CLS:PRINT"  CALL     PHONE #   DISTANCE  BEARING         DIRECTIONS":PRINT
198 IFRN>TRTHEN230
200 D$=D$(RN):E$=E$(RN):X=X(RN):Y=Y(RN)
205 RN=RN+1
210 IFASC(H$)<>89THENGOSUB2000:GOTO220
215 IF ASC(D$)=42THENGOSUB2000ELSE224
220 IFU<=LTHENPRINT;D$;TAB(9);E$;TAB(20);U;TAB(31);Z;TAB(39);S;A$TAB(52)T;B$ELSE224
221 R=R+1:V=V+1:IFV<11THEN224
222 PRINT:INPUT"PRESS ENTER TO CONTINUE";P:V=0
223 GOTO195
224 GOTO198
230 PRINT:PRINTR;"STATIONS WITHIN"L"MILES OF TRANSMITTER":INPUT"PRESS ENTER TO CONTINUE";P:CLS:GOTO300
239 GOSUB240:GOTO300
240 REM DATA INPUT ROUTINE
241 PRINT"INSERT DATA TAPE":PRINT"PRESS PLAY":PRINT"PRESS ENTER WHEN READY TO LOAD":INPUTP
242 RN=1:DF=1:CLS:PRINT"FILE LOADING"
243 INPUT#-1,D$(RN),E$(RN),X(RN),Y(RN)
246 IF D$(RN)="END"THEN248
247 RN=RN+1:GOTO243
248 TR=RN-1:RETURN
250 REM MODIFY DATA TAPE
252 PRINT"1) LIST RECORDS":PRINT"2) INSERT RECORD":PRINT"3) DELETE RECORD":PRINT"4) WRITE DATA TAPE":PRINT"5) RETURN TO MAIN PROGRAM
":PRINT
253 INPUT"ENTER SELECTION";Q1:CLS
254 ON Q1 GOTO256,263,277,283,300
255 GOTO252
256 V=0
257 FOR RN=1TOTR
258 PRINT;RN;" ";D$(RN);" ";E$(RN);" ";X(RN);" ";Y(RN)
259 V=V+1:IFV<14THEN261
260 PRINT:INPUT"PRESS ENTER TO CONTINUE";P:CLS:V=0
261 NEXT RN
262 PRINT:INPUT"PRESS ENTER TO CONTINUE";P:CLS:GOTO252
263 DF=1:INPUT"ENTER CALL LETTERS OF STATION";D$
264 INPUT"ENTER STATION'S TELEPHONE NUMBER";E$
265 INPUT"ENTER STATION'S COORDINATES";X,Y
270 INPUT"AFTER WHAT RECORD NUMBER SHOULD THIS RECORD BE INSERTED (0 IF THIS IS THE FIRST RECORD)";NR:IFNR<>0THEN271:GOTO275
271 NR=NR+1:FOR FR=TR TO NRSTEP-1
273 NN=FR+1:D$(NN)=D$(FR):E$(NN)=E$(FR):X(NN)=X(FR):Y(NN)=Y(FR)
274 NEXTFR
275 D$(NR)=D$:E$(NR)=E$:X(NR)=X:Y(NR)=Y
276 TR=TR+1:CLS:GOTO252
277 INPUT"WHICH RECORD NUMBER SHOULD BE DELETED";DR
278 IF DR<=TR THEN 280
279 PRINT"RECORD NOT FOUND":GOTO277
280 FOR FR=(DR+1)TO TR
281 NN=FR-1:D$(NN)=D$(FR):E$(NN)=E$(FR):X(NN)=X(FR):Y(NN)=Y(FR):NEXTFR
282 TR=TR-1:CLS:GOTO252
283 RN=1:LR=0
284 PRINT"INSERT DATA CASSETTE IN RECORDER AND PRESS PLAY AND RECORD":PRINT"PRESS ENTER"
285 INPUTP
286 FORRN=1TOTR
287 PRINT#-1,D$(RN),E$(RN),X(RN),Y(RN):NEXTRN
288 PRINT#-1,"END","END",0,0
289 PRINT"TAPE WRITTEN"
300 REM MENU
305 PRINT:PRINT"1) DF-FIX CALCULATIONS"
310 PRINT"2) FIELD UNIT CALCULATIONS"
315 PRINT"3) DF-NET LISTING":PRINT"4) LOAD DATA TAPE":PRINT"5) MODIFY DATA TAPE":PRINT"6) END"
320 PRINT:INPUT"ENTER SELECTION";Q:CLS
325 ON Q GOTO39,140,180,239,250,9999
326 GOTO300
1900 PRINT"DIRECTIONS TO TRANSMITTER:"S;"MILES "A$"    "T;"MILES "B$:PRINT:RETURN
2000 REM CALCULATIONS SUBROUTINE
2001 S=G-X:T=H-Y
2005 U=SQR((S*S)+(T*T))
2006 IFS<>0THEN2015
2007 IFT>=0THEN2215ELSE2220
2015 Z=ATN(T/S)
2025 Z=Z*180/3.14159
2030 IF(S>=0)*(T>=0)THEN2195
2035 IF(S<0)*(T>=0)THEN2100
2040 IF(S>=0)*(T<0)THEN2205
2045 IF(S<0)*(T<0)THEN2210
2050 S=ABS(INT((S*10)+.5)/10):T=ABS(INT((T*10)+.5)/10):U=INT(U*10)/10:Z=INT(Z+.5)
2055 RETURN
2100 A$="WEST":B$="NORTH":Z=270-Z:GOTO2050
2195 A$="EAST":B$="NORTH":Z=90-Z:GOTO2050
2200 A$="WEST":B$="NORTH":Z=90-Z:GOTO2050
2205 A$="EAST":B$="SOUTH":Z=90-Z:GOTO2050
2210 A$="WEST":B$="SOUTH":Z=270-Z:GOTO2050
2215 A$="EAST":B$="NORTH":Z=0:GOTO2050
2220 A$="EAST":B$="SOUTH":Z=180:GOTO2050
9999 END
```

Program listing.

WORLD TIME WATCH
the first microprocessor watch made especially for hams

24 hr. timer
microprocessor water resistant
solar assist
New Low Price –$59.95

The HAM-1 functions include local time, world time, (G.M.T. too) count-up and count down chronometer, day, month, date, alarm and hourly chime. It's ideal for log-keeping, DX time conversion and 10 minute I.D. timing. The HAM-1 features a high contrast Seiko display and solar cell battery assist. Battery life is better than 4 years. The HAM-1 is water resistant to 20 meters, the case is 100% solid stainless steel and the crystal is scratch resistant mineral glass. The HAM-1 is rugged and durable and has a 1 year warranty.

2 METER AMPLIFIER
$39.95

• 2 Watts In, 10 Watts Out • V.S.W.R. Protected • Can be Used for F.M. & S.S.B. • Led Status Indicators • Low Loss SO-239 Connectors • Current Drain Less Than 2.5A at 13.6 V.D.C. • Massive Heatsink • Built In T/R Switch

TEMPO S-1 UPGRADE KITS
$39.95

Upgrade your early Tempo S-1 to current Production Specifications, kits include: • 450 M.A.H. Battery Pack • New Case Assembly • All New Escutcheons • Spkr./Mic. Jack w/Dust Cap • New Earphone & Jack • P.C.B. and Parts for Easy Installation • Detailed Instruction Manual • For Radios With & Without T.T. Pad.

Other Accessories Available:
Spkr/Mic. Designed for S-1's. . . $24.95
Heavy Duty Belt Clip. 7.50
Flex Antenna 6.00

To Order Call or Write to:
ADVANCED COMMUNICATIONS INTERNATIONAL ✓448
2411 Lincoln Avenue
Belmont, CA. 94002 U.S.A.
(415) 595-3949

Add $3.00 per order for shipping & handling. California residents add 6% sales tax. Visa, Master Charge accepted.

WHY COMPROMISE

Others claim more gain for their antennas than the IsoPole™ antennas, but none can beat the IsoPole for HONEST on-the-horizon omni-directional gain unless you are willing to spend at least THREE TIMES AS MUCH!!! The IsoPole is easiest of ALL competitive models to assemble, has a weather protected, factory-tuned matching network, (no more aggravating SWR variations with weather changes), uses all stainless steel hardware, and is designed to withstand severe icing and wind conditions. The IsoPole antenna is UPS shippable without the standard 10 foot 1¼ inch TV mast. You can buy the mast from your local ham dealer, hardware store, or Radio Shack™ store for less than the shipping costs of a single mast. When good strong, low cost 10 foot sections of mast are so easily available, why compromise by using several shorter pieces that have to be joined together?

For more details, please write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation.

ADVANCED ELECTRONIC APPLICATIONS, INC. ✓2
P.O. Box C-2160,
Lynnwood, WA 98036
(206) 775-7373
Telex: 152571 AEA INTL

AEA Brings you the Breakthrough!

Hear Police/Fire Weather
on 2 Meter Handhelds with this MFJ VHF Converter.

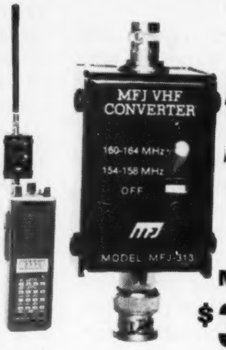

Scanning Handhelds become Police/Fire Scanners

MFJ-313
$39.95

New MFJ VHF converter turns your synthesized scanning 2 meter handheld into a hot Police/Fire/Weather band scanner.

144-148 MHz handhelds receive Police/Fire on 154-158 MHz with direct frequency readout. Hear NOAA weather, maritime coastal plus more on 160-164 MHz.

Mounts between handheld and rubber ducky.

Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No missed calls.

Highpass input filter and 2.5 GHz transistor gives excellent uniform sensitivity over both bands. Crystal controlled.

Bypass/OFF switch allows transmitting. Won't burn out if you transmit (up to 5 watts) with converter on. Low insertion SWR. Uses AAA battery. 2¼x1½x1½ in. BNC connectors.

Enjoy scanning, memory, digital readout, etc. as provided by your handheld on Police/Fire band.

220 MHz Converter for 2 M Handheld

MFJ-314
$59.95

MFJ-314, like MFJ-313 but lets you receive 221-225 MHz on your 2 meter handheld.

Police/Fire/Weather Band Converter for 2 Meter Mobile Rigs.

MFJ VHF BAND EXPANDER
160-164
ON
154-158 MHz
OFF-BYP
MFJ-312

MFJ-312
$59.95

MFJ-312, like MFJ-313 but for mobile 2 meter rigs. Transmit up to 40 watts thru converter without damage. SO-239 connectors. Mobile mounting brackets. Rugged. "ON" LED. Use 12 VDC or AAA battery. 3x4x1 in.

Order from MFJ and try it-no obligation. If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus $4.00 each shipping.

Hear police/fire/weather. Order now. ✓47

CALL TOLL FREE . . . 800-647-1800

Call 601-323-5869 in Miss..outside continental USA, tech/order/repair info. Telex 53-4590.

MFJ ENTERPRISES, INCORPORATED
Box 494, Mississippi State, MS 39762

lete a record number that does not exist, the computer will print RECORD NOT FOUND and ask you for the record number to be deleted again. If a record has some incorrect information on it, you must insert the complete correct record and then delete the incorrect one.

The fourth option will write a new data tape with all of the new changes or duplicate the old data tape if it has been loaded in and no changes have been made. To use this option, place the tape you want to put the data on in the recorder. Press the Play and Record buttons on the recorder and then press ENTER on the computer. After the data tape has been written, the computer will return to the main program and display the menu.

The fifth option simply returns you to the main program and displays the menu. You would select this in case you did not want to write a new tape or did not want to write immediately after making the changes.

RDF Map

In order to use this program, you must prepare a map with a coordinate system on it. First obtain a map of the coverage area. This map should have an appropriate scale for RDF use, that is, it should not be so small that one inch equals twenty miles. After the map has been obtained, you should determine what length on the map corresponds to a distance of one mile; for example, 0.5 inch=1 mile. Then, starting in the left-hand corner, you should make a mark every mile along the bottom edge of the map (see Fig. 1). Do the same along the top edge, starting in the upper left-hand corner. Repeat this procedure for the sides, starting in the lower left- and right-hand corners. Next, label them, starting with 0 and going from left to right and bottom to top. The markings on the side of your map should be similar to those in Fig. 1 (different scales and more numbers of course).

After you have prepared the map, you are ready to prepare the DF-Net station data sheet (see Fig. 2). Fill in the call and phone number columns with appropriate information. The first coordinate is the number on the top or bottom of the map which corresponds to the horizontal position of the station. The second coordinate is the number on the sides of the map which corresponds to the vertical position of the station. This sheet is sufficient for using options 1 and 2 of the program.

As has been stated before, in order to use the DF-Net Listing option, you must have previously inserted stations onto the data tape using option 5.2. The option will guide you through the procedure, but a few things should be mentioned before you use the option. First, answer all of the questions the computer asks about the station. Do not leave any answer blank. If a radio direction finding station does not have a call, (e.g., a future ham or SWL), type his name (if it is six or less letters) or his initials in response to the question about the station's callsign. If a station does not have a phone or his number is not known, type in NO PHONE or N/A in response to that question. If you would like a station to be included in a selective printout in the DF-Net Listing, put an asterisk in front of the station's callsign. The asterisk can be used to denote a station who is part of the DF committee or to denote those who have special RDF equipment in their cars, etc.

As well as using the program to find stations, it can be used to calibrate the members' antenna-heading indicators. To use the program for this purpose, RUN the program and load the data tape. Next, you need to insert the coordinates of the station that everyone will be aiming at. To do this, enter station A's coordinates as follows: first coordinate of station being aimed at, 0. For the bearing, enter 0. Enter B's coordinates as follows: 0, the second coordinate of the station being aimed at. For the bearing, enter 90. Press ENTER to get to the menu, and select the DF-Net Listing option. Answer the questions as you normally would. The number in the bearing column of the listing is the direction that each station's heading indicator should show. This information should be relayed to each station so that he can either correct his indicator or make a note of the error and correct for it when he is tracking a station. A good station to calibrate on would be the repeater.

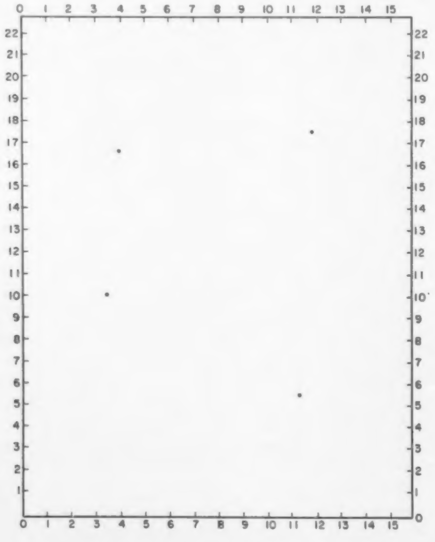

Fig. 1. RDF map.

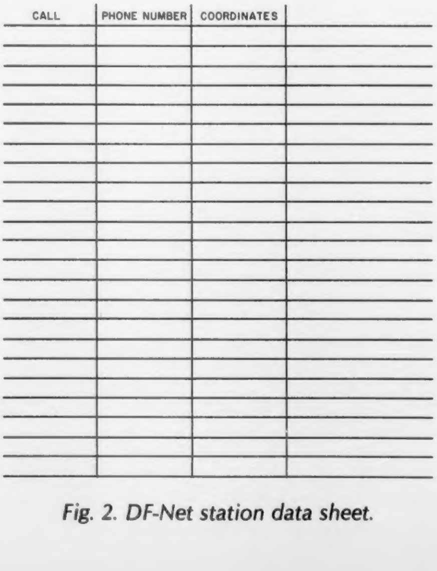

CALL	PHONE NUMBER	COORDINATES	

Fig. 2. DF-Net station data sheet.

DO ANTENNAS WORRY YOU?

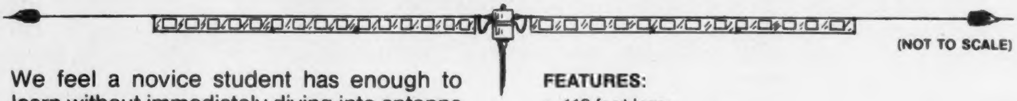

(NOT TO SCALE)

We feel a novice student has enough to learn without immediately diving into antenna construction. Our new novice antenna is fully assembled and covers **all** the novice bands and beyond. One of its better features is the price. *(At last glance the competition wanted $123.50 for their fully assembled antenna with coax fitting that covers the four novice/tech bands.)*

MODEL ND-4
only $69.95

FEATURES:

- 118 feet long
- Heavy Copperweld® construction
- 100 feet of 450# test Nylon rope included
- Waterproof center connector with female coax fitting
- No antenna tuner needed
- 2 KW PEP input rated (750 W on 21 mHz)
- Retunable when you upgrade
- Installs as low as 25 feet

Average Bandwidths for 2:1 VSWR:

- 80 meters = 200 KHz plus
- 40 meters = 125 KHz
- 15 meters = 600 KHz plus
- 10 meters = 700 KHz plus

ALL PRICES ARE UPS PAID CONTINENTAL USA

Available at your favorite dealer or order direct from:

Van Gorden Engineering
P.O. Box 21305 • South Euclid, Ohio 44121
Dealer Inquiries Invited

Organize your shack with a

CLUTTERFREE MODULAR CONSOLE $203.35

- Large, 42" H x 57" W x 29"D
- Strong groove-construction
- Mar-resistant wood grain finish
- Options, drawers & face plate
- For ham or home computer
- Visa and Master Charge

CLUTTERFREE MODULAR CONSOLES

P.O. Box 5103 Tacoma, WA 98405
(206) 272-0713 ✓89

MFJ/Bencher Keyer Combo

Deluxe MFJ Keyer fits on Bencher Paddle. Curtis 8044 IC. Iambic. Adjustable weight, tone, volume, speed. Semi and automatic modes. Solid state keying. RF proof.

MFJ-422 Combo $99.95

MFJ-422X Keyer only $69.95

The best of all CW worlds - a deluxe MFJ Keyer in a compact configuration that fits right on the Bencher iambic paddle! You can buy the combination or just the keyer for your Bencher.

New MFJ Keyer—small in size, big in features. Curtis 8044 IC, adjustable weight and tone, front panel volume and speed controls (8-50 wpm). Built-in dot-dash memories. Speaker, sidetone, and push button selection of semi-automatic/tune or automatic modes.

Ultra-reliable solid state keying: grid-block, cathode and solid state transmitters (-300 V, 10 mA max., +300 V, 100 mA max.). Fully shielded. Uses 9 V battery or 110 VAC with optional adapter, MFJ 1312, $9.95.

Beautiful functional engineering. The keyer mounts on the paddle base to form a small (4 1/8 x 2 5/8 x 5 1/2") attractive combination that is a pleasure to look at and use. ✓47

The Bencher Paddle is a best seller. Fully adjustable gold-plated silver contacts, lucite paddles, chrome plated brass, heavy steel base with non-skid feet.

Order from MFJ and try it - no obligation. If not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus $4.00 each shipping and handling.

Enjoy CW. See dealer or call MFJ now.

CALL TOLL FREE . . . 800-647-1800

Call 601-323-5869 in Miss., outside continental USA **or** for technical info., order/repair status.

MFJ ENTERPRISES, INCORPORATED
Box 494, Mississippi State, MS 39762

You also may want to include the repeater in your DF-Net Listing so you can estimate the station's transmitter power by comparing the distance to the repeater with the signal strength into the repeater.

Technical Data

The program is divided into six subprograms (DF-fix calculations, field-unit calculations, DF-Net Listing, loading the data tape, modifying the data tape, and the menu) and one major subroutine.

Statements 5 through 12 merely initialize the program. String space (5000 bytes) is set aside and the arrays are DIMensioned to a value of 100. Statements 15 through 21 give the user the option to load the data tape before he actually starts to use the program.

The DF-fix routine (lines 39 through 113) determines the location of the transmitter from the information entered by the user. This location (G,H) is used in all of the other routines for determining the transmitter's relationship to the positions of the other stations.

Statements 40 through 60 prompt the user to input the tracking station locations and beam headings. Statement 75 converts these headings from compass bearings (0° = North, increasing in a clockwise direction) to polar bearings used by the computer. Statement 90 converts these headings from degrees to radians and takes the tangent. Statement 100 solves the simultaneous equations representing the lines from the tracking stations at the given bearings. Statement 105 rounds the results of the calculations (G,H—the transmitter's coordinates) to the nearest tenth. Statement 110 passes station A's coordinates to the variables used in the calculations subroutine. The results are then printed out.

Subroutine 1900 is called to print the directions, since it is used many times. This is again done for station B in line 113. The last half of line 113 is a dummy input used to pause the program and allow the user to continue when he is ready. This is done frequently throughout the program.

The field-unit routine prompts the user to input the field-unit's coordinates, calls the calculations subroutine, and displays the results. It then jumps to the menu. This routine is straightforward in that all it does is format the input and output of the calculations subroutine.

The DF-Net Listing first checks the data flag (DF) to see if data has been loaded in (line 181). The computer then prompts the user to input different parameters for the listing (lines 185 and 190). RN is the record number and specifies which element of the array is to be read. The computer compares the record number with the total number of records (TR). When RN exceeds TR, the listing routine then summarizes the results of the listing. If the user selects the selective printout, the program then checks to see if the first character of the callsign string (D$) is an asterisk (line 215). R is the "stations within range" counter and V is a line counter for limiting the number of stations printed on the screen at one time so that the results do not go flying off the screen before they can be read.

The data tape input routine is also straightforward. DF=1 sets the data flag. One record, D$,E$,X,Y, is input off the tape and stored in an array, with the subscript being incremented after each record. The computer checks D$ for the end of file indicator, END. TR is found by taking the total number of records read (RN) and decreasing it by one to remove the end-of-file indicator from the count.

The modify data tape routine has five options. The first option merely prints out the contents of the arrays. The second option (263 through 276) inserts a new record into the file. First, the user types the information in, then the computer moves all of the records after where the new one is to be inserted up one record number. The new record then is put in the hole left by the records moved.

The delete routine merely moves all of the records above the record to be deleted down one. This destroys that record by writing over it. The program checks to make sure the user does not try to delete records that do not exist.

The fourth option (283 through 289) just outputs the arrays to the tape recorder, using a similar approach to the way they are read in. The fifth option is merely a jump to the menu.

The menu is straightforward, using an ON/GOTO statement to branch. Line 326 takes care of inputs that are not covered in line 325.

The calculations subroutine calculates the distance to the transmitter (lines 2001 and 2005), bearings to the transmitter, and directions to the transmitter (lines 2006-2220). The subroutine is made up of different branches used to correct the ambiguity of the ATN function.

It is hoped that this program and the presence of a good RDF committee will reduce the amount of jamming and be a valuable tool in locating emergency locator transmitters quickly.■

Variable List

A—First coordinate of station A's location
B—Second coordinate of station A's location
C—Bearing to transmitter from station A
D—First coordinate of station B's location
E—Second coordinate of station B's location
F—Bearing to transmitter from station B
G—First coordinate of transmitter's location
H—Second coordinate of transmitter's location
L—Maximum report range
M—DIMension of arrays
P—Dummy variable for pausing program
Q—Menu selection
R—Number of stations within given radius of transmitter
S—Horizontal distance between a station and transmitter
T—Vertical distance between a station and transmitter
U—Distance from transmitter
V—Line counter in listing
X—First coordinate of station's location when using calculation subroutine
Y—Second coordinate of station's location when using calculation subroutine
Z—Bearing to transmitter
DR—Record number to be deleted
DF—Data flag
FR—Former record number
NN—New number of record after being renumbered
NR—New record number (inserted record number)
Q1—Option selection under option 5
RN—Record number
TR—Total number of station records in arrays
A$—"EAST" or "WEST"
B$—"NORTH" or "SOUTH"
G$—"Y" or "N" to load data tape at beginning of program
H$—"Y" or "N" to "DF-COMMITTEE MEMBERS ONLY?"
D$—Station's call
E$—Station's telephone number

Communications Specialists TE-64

Food for thought.

Our new Universal Tone Encoder lends its versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequency-just dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers' repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

- All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak
- Instant start-up.
- Off position for no tone output.
- Reverse polarity protection built-in.

Group A

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 1A	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 M1

- Frequency accuracy, ± .1 Hz maximum - 40°C to + 85°C
- Frequencies to 250 Hz available on special order
- Continuous tone

Group B

TEST-TONES:	TOUCH-TONES:		BURST TONES:			
600	697	1209	1600	1850	2150	2400
1000	770	1336	1650	1900	2200	2450
1500	852	1477	1700	1950	2250	2500
2175	941	1633	1750	2000	2300	2550
2805			1800	2100	2350	

- Frequency accuracy, ± 1 Hz maximum - 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

Model TE-64 **$79.95**

COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, California 92667
(800) 854-0547/ California: (714) 998-3021

✓15

Shack from Scratch

Building a ham shack in a new home can be a breeze. Just plan ahead.

Thomas R. Sundstrom W2XQ
Box 175
Vincentown NJ 08088

A man's home may be his castle, but have you tried to install a 6-element, 20-meter beam on a parapet lately? Most homes built or renovated today are not conducive to installing an amateur radio station.

The problem of what to do with the radio equipment confonted me when my wife and I opted to have a new home built in a semi-rural area. In our old home on a suburban lot, it had been make-do in a third bedroom with the attendant problems of running antenna feedlines, supplying adequate electrical power, and establishing decent grounds for the equipment.

My solutions will not necessarily be your solutions, but variations of these ideas may help you in solving your installation problems. Funds were a consideration—the overall objective was, after all, to build the house! But when it was all done, I wound up with a fair amount of operating room, all the electrical power I needed, and a TVI-free environment for less than two percent of the total cost of the house and property.

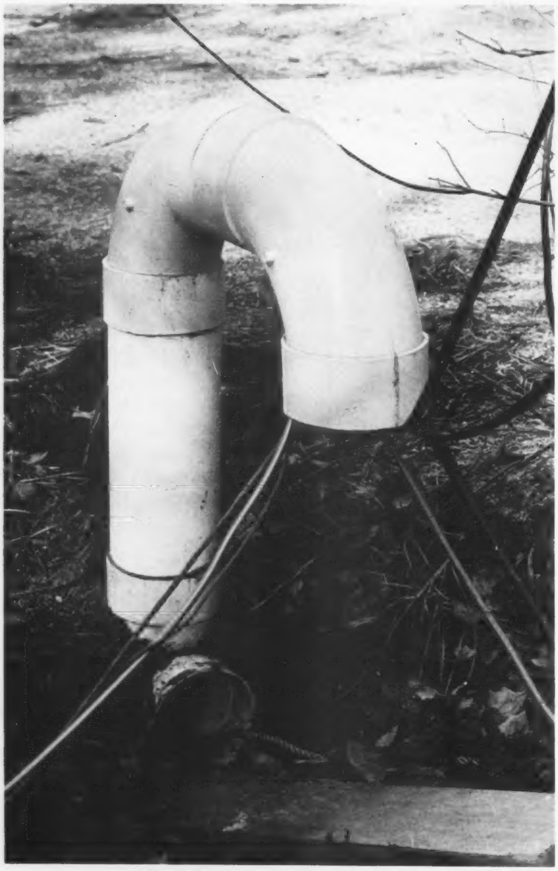

Photo A. The PVC pipe has a couple of elbows on the end of it to keep out rain and snow. A pull rope is left in the pipe to move additional antenna and rotor cables through; otherwise, the open end is capped and covered with dirt.

Review the Plans

Once you have selected the location (no zoning restrictions on towers, right?) and a builder, look over the plans carefully to determine options for the radio room.

In our case, the locale dictated no basement because of the water table. We chose an L-shaped ranch on a slab of concrete. The options were to put the equipment into a bedroom or in the back of the garage. Neither option was desirable.

The solution was relatively simple. The garage was on one end of the house on the long side of the L. We had the builder expand the long side of the L by adding a 6-foot-wide room between the living area and the garage and adding one wall and door. See Fig. 1.

The additional room provided space for the amateur radio equipment, enabled my wife to get the washer-dryer out of an interior closet in the living area, and gave us a mudroom in which to leave boots, raincoats, and other items that should not be trailed across carpeting.

In solving your installation problem, factors to consider would be (1) accessibility to the back yard (or the side yard) for antennas, with a minimum feedline run, (2) keeping the station away from the sleeping areas of the house so that late night and early morning DXing sessions don't disturb the rest of the family, (3) keeping the family TV antenna, TV, and audio equipment apart from the radio equipment, and (4) the location of overhead power lines coming into the house.

If you opt to expand the house or add an addition to solve the location problem of your equipment, you can hold costs down by doing it in such a way that no new corners are created, needing additional forms for concrete and framing. For example, it would have been more costly for us to tack a room on to the back of the garage, extending that by 10 feet or so. Additional costs would have been incurred for laying forms around two additional corners, a redesign of the roof and supporting rafters in that part of the house, and a reconfiguration of the heating and cooling systems; considerably more concrete, lumber, and siding would have been needed.

Antenna Feedthroughs

Because space for antennas was available in the back yard, I agreed not to punch holes in the sides or roof of the new house and to see that everything was put in the back and out of sight.

Before the slab was poured, I had the builder lay down 4-inch PVC pipe extending from beyond the foundation of the house to the rear of the proposed station operating area. A 90-degree elbow and a short section of pipe at the desk end put that end above the floor level. The poured concrete anchored the 10-foot sections; a board temporarily capped the end outside the house.

Later, I purchased additional sections of PVC pipe and extended the run further into the backyard, bringing it above ground beyond the normal traffic patterns and behind some ground cover. Two 90° elbows are needed so that rain and snow do not enter the pipe. See Fig. 2.

In retrospect, I probably should have put two runs of PVC pipe into the shack area. While one handles a number of RG-8 and RG-8/X and control cables, hardline takes up a lot of room in a hurry.

Factors to consider in planning your own installation include (1) keeping runs of PVC pipe as straight as possible to minimize difficulties in routing cable, (2) leaving a "pull" rope in the pipe so that cable can be fed through from either end at any time (and don't forget to anchor it so that it's not accidentally pulled into the pipe beyond your reach), and (3) consideration of how many antennas and types of feedlines will be installed in the coming years.

Variations on the theme of using PVC pipe to route cable might include using PVC pipe inside the house to route cable to an exterior wall. Place the pipe inside the walls before the sheetrock is hung. Depending upon the design of the house, you may choose to route the pipe and cable to the attic from an interior first- or second-floor room chosen as the "shack," or route it to the basement or the garage before entering the underground run to the antenna tower.

Another variation, for those setting up the operating station in a basement or family room below ground level, would be to bring the PVC through the exterior wall to a point flush with the inside wall. Make up an appropriate bulkhead with connectors and label the lines. In times of electrical storms, shorting plugs can be put on each of the antenna feedthroughs and grounded through the ground attached to the bulkhead plate.

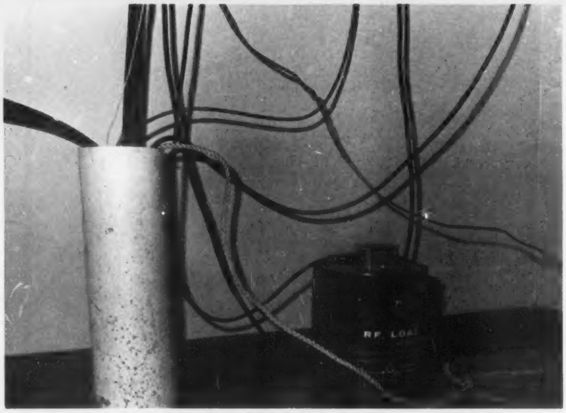

Photo B. The PVC pipe comes up under the operating desk. One of the two ground rods is visible on the right.

Grounds

At the same time that the PVC pipe was laid for the antenna cable runs and before the floor was poured, I installed 10-foot, ¾-inch ground rods at the rear of the area where the operating desk was to be placed. I left them about 8 inches above the finished floor.

That simple move has paid off handsomely in the reduction of in-house TVI and RFI on the operating desk compared with what I had been used to in the previous house. Ground leads are a maximum of 3 feet now.

In your installation, consider the shortest run possible. If you are setting up in an interior room, drop the ground leads through the walls directly to the basement. Use ground rods as long as possible; those 4-foot lengths just won't do the job. Run heavy wire; #4 would be fine. As the heavier wire is a bit difficult to work with, consider tying the heavy ground lead to a heavy-gauge metal plate that has been drilled and tapped with 3/8- or 1/2-inch bolts and place that behind the operating desk. The individual ground leads from the several pieces of equipment can be terminated with spade lugs and bolted to the plate.

Electrical

Before the wall between the added utility room/ham shack and the garage was closed, I had an electrician wire a separate electrical panel for the radio equipment. At the main electrical panel in the garage, a 70-Amp circuit breaker was installed. A three-wire line was run into the shack wall; another panel was installed with a 70-Amp main circuit breaker, and separate circuit breakers were installed to provide 220 and 110 V ac to a number of outlets.

Perhaps this was overkill, but the family members have instructions on how to turn off either main breaker in case of an emergency. Everything goes down when

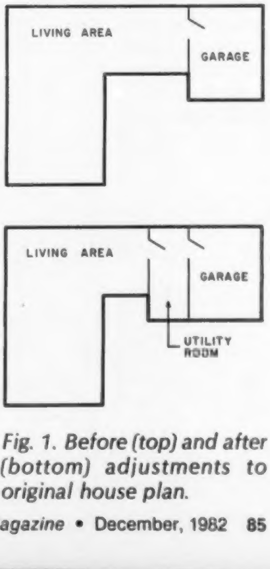

Fig. 1. Before (top) and after (bottom) adjustments to original house plan.

SATELLITE
TELEVISION
SYSTEMS

WE WILL NOT BE UNDERSOLD!!
Complete Systems, Antennas,
Receivers, LNA's & Accessories
CALL US TODAY! ✓320
812-238-1456

hoosier
electronics

"Nation's Largest Total Communications Distributor"
P.O. BOX 3300 • TERRE HAUTE, INDIANA 47803

that switch is thrown. (That panel is low enough for even my youngster to reach.)

Plan your needs carefully. I had eight 110 V ac outlets installed, and still I ran out. Also consider height and placement of the outlets. Don't install outlets at tabletop height if the surface of the operating area runs wall-to-wall; put them above or below the tabletop.

Odds and Ends

Some other planning-ahead activities to consider as the house is framed and before the sheetrock is hung are all based around pre-wiring the house for a variety of items.

Don't forget to get the telephone installer at work before the sheetrock goes on. The job is a lot easier and cleaner. Run a telephone line into the shack, and consider having the house wired for two (or more) telephone lines. If you change your mind at the time the installer returns to fish out the lines to telephone jacks, there is no problem reverting to one line. There is no charge for pre-wiring the framed house.

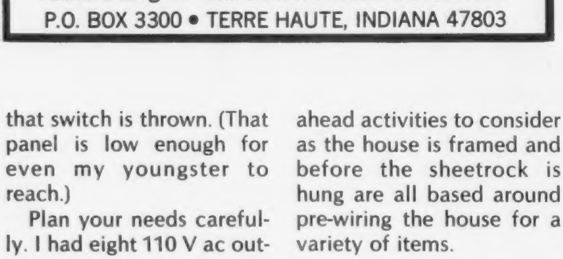
90° ELBOWS AND A T-CONNECTION ARE USED HERE TO KEEP RAIN AND SNOW OUT OF PIPING.
CAP THIS END EXCEPT TO PULL ANTENNA AND ROTOR CABLES.
LENGTH OF PIPE RUN IS DETERMINED BY YOUR NEEDS: KEEP THE RUN STRAIGHT.
LEAVE A "PULL" ROPE IN THE PIPE TO PULL ADDITIONAL CABLES FROM EITHER END.

Fig. 2. Details of PVC pipe arrangement which contains coax and control cables

Want to install a burglar alarm system? A wired perimeter system tends to be the cheapest, and it's easy to do yourself. Supplies can be acquired from a number of wholesale and retail outlets. Pick the system best for you; it may be easiest to install before the walls are closed. Don't forget about electrical power to the system (most systems also have a battery backup).

Also consider pre-wiring for your stereo system. It's a lot easier to run speaker leads in the walls and over ceilings than under rugs or behind wall moldings. Use some larger-size electrical zip cord, such as #12 or #14, rather than the light stuff. Plan ahead for the day when you upgrade to a larger, more powerful amplifier and have speakers in other areas of the house. You can always leave the wires in the walls until you actually have speakers in hand.

An intercom system is also very easy to put in before the walls are closed. Plan ahead. (It's your choice to put one in the shack so that you can be called to do chores in the middle of a contest!)

Be sure to install 75-Ohm coaxial cable for the household TV and FM antenna system before closing the walls. Consider the placement of the antennas with respect to the ham equipment when routing the cable. I opted to install an antenna to take care of both the TV and the FM stereo receiver under the roof of the house, rather than outside, and hung it in the end of the house away from the shack. Plan ahead if you want multiple outlets for multiple TV sets, and don't forget an electrical source for a distribution amplifier if your plans require one. Using shielded cable and picking the right spot for your TV/FM antenna(s) will go a long way to eliminating in-house TVI.

I also took advantage of the open walls to install a coaxial cable which was later hooked up to an attic-mounted scanner antenna and a scanner in the family room; my wife and I eavesdrop on one or two police and fire frequencies, some remote broadcast stuff, and one or two 2-meter frequencies.

In Closing

The building of a new home or of a major addition to an existing home is a massive undertaking. Attention has to be given to everything, and the smallest detail has to be reviewed on a continuing basis. If you tell the builder *before* he begins that you want to install certain wires and pipes for the amateur radio station, there shouldn't be any problems. In my case, the builder gave me a schedule of construction and permission to come in to install the ground rods and the pre-wiring described above; he placed the PVC pipe for me, and the electrician came after I took title to the house.

Keep receipts on everything you purchase and install. That's all part of your tax records for calculating the adjusted cost of the house and the improvements, depending upon the dates involved.

Some of the ideas described above are not necessarily new or original, but they are intended as food for thought. Your needs are different from mine, but if I have reminded you to think about a particular installation problem before you begin a project, then I have been successful. Good luck in your building. ■

AZDEN PCS-300
6.820
M-ADRS
S/RF
UP MHz
100K
5K
DOWN
BAND SCAN
M ADRS
M SCAN
M WRITE
M CALL
MT CALL
KEY LOCK
SCAN MODE
LAMP
OFF ON

Shown Actual Size

The Standard for Comparison

New AZDEN® PCS-300
2-M Handheld FM Transceiver

8 MHZ COVERAGE • 142 to 149.995 MHz in 5 kHz steps, including CAP and MARS.

IDEAL SIZE & WEIGHT DISTRIBUTION • 7.3" high by 2.5" wide by 1.8" deep; 1.4 lbs.

MICROCOMPUTER CONTROL • All frequency operations are done by means of a microcomputer keyboard with acquisition tone.

LCD DISPLAY WITH TIMED LAMP • Draws almost no current. Lamp times out automatically after 20 seconds.

16 KEY AUTOPATCH • Keyboard works as a Touchtone® pad while transmitting.

PL TONE SWITCH • Actuates optional subaudible tone module.

PROGRAMMABLE "ODD SPLITS" • Transmit and receive on any possible frequency combination. Reset in seconds.

9 CHANNEL MEMORY WITH SCAN • Eight addressable channels and one externally accessible up/down channel retain frequency and standard offset. Backup drain is a scant 10 microamps!

AUTOMATIC INCLUSIVE OR EXCLUSIVE PROGRAMMABLE BAND SCAN • Limits may be reset in seconds. Scans either inside or outside the limits.

BUSY AND VACANT SCAN MODES • Scan for either an occupied or empty frequency.

KEYBOARD LOCK • Prevents accidental change of frequency or scan status.

TRANSMIT LOCK • Avoids unintentional transmission.

DIGITAL S/RF AND MEMORY ADDRESS METER • Shows relative signal strength on receive, relative power on transmit. Also shows memory address.

HIGH OR LOW POWER • 3 watts high, 1 watt low. Low power is continuously adjustable from 0.5 to 3 watts.

TRUE FM • Not phase modulation – Unparalleled audio quality.

AUTOMATIC FRONT END TUNING • RF stage is varactor tuned for superior sensitivity and selectivity.

RUGGED COMMERCIAL-GRADE MODULAR CONSTRUCTION The PCS-300 is built to take years of the toughest operating conditions.

SUPERIOR RECEIVER • Sensitivity is 0.25 uV for 20 dB quieting, 0.2 uV for 12 dB SINAD.

BNC ANTENNA CONNECTOR •

STANDARD ACCESSORIES • Heavy duty NICAD battery pack (500 mAh), belt clip, hand strap connector, flexible rubber antenna, earphone, ac charging unit, and special stand for table-top operation.

OPTIONAL ACCESSORIES • Deluxe leather case, mobile dc charging cord, external speaker/microphone, and PL tone module.

MANUFACTURER: **AZDEN** JAPAN PIEZO CO., LTD.
No. 12-17, 1-chome, Kami-Renjaku, Mitaka, Tokyo, Japan, Telex: 781-2822452

EXCLUSIVE DISTRIBUTOR: **AMATEUR-WHOLESALE ELECTRONICS, INC.**
8817 S.W. 129 Terrace, Miami, Florida 33176 Telephone (305) 233-3631 Telex: 80-3356 Toll-free (800) 327-3102

COMPUTERIZED MORSE KEYERS

AEA, the first company to introduce microcomputerized products to the Amateur Radio market, is proud to announce the second generation of computerized electronic keyers. Each keyer is preprogrammed, no computer language is required of the operator. The easy to use keypads eliminate up to 75 switches or potientiometers, thereby greatly simplifying the operation of such sophisticated keying systems. We invite you to compare the features of our keyers (shown below) to ANY others.

IMPORTANT KEYER AND/OR TRAINER FEATURES	AEA MM-2	AEA KT-2	AEA CK-2
Speed Range (WPM)	2-99	1-99	1-99
Memory Capacity (Total Characters)	500	N/A	500
Message Partitioning	Soft	N/A	Soft
Automatic Contest Serial Number	Yes	N/A	Yes
Selectable Dot and Dash Memory	Yes	Yes	Yes
Independent Dot & Dash (Full) Weighting	Yes	Yes	Yes
Calibrated Speed, 1 WPM Resolution	Yes	Yes	Yes
Calibrated Beacon Mode	Yes	N/A	No
Repeat Message Mode	Yes	N/A	Yes
Front Panel Variable Monitor Frequency	Yes	Yes	Yes
Message Resume After Paddle Interrupt	Yes	N/A	Yes
Semi-Automatic (Bug) Mode	Yes	Yes	Yes
Real-Time Memory Loading Mode	Yes	N/A	Yes
Automatic Word Space Memory Load	Yes	N/A	Yes
Instant Start From Memory	Yes	N/A	Yes
Message Editing	Yes	N/A	Yes
Automatic Stepped Variable Speed	No	No	Yes
2 Presettable Speeds, Instant Recall	No	No	Yes
Automatic Trainer Speed Increase	Yes	Yes	N/A
Five Letter or Random Word Length	Yes	Yes	N/A
Test Mode With Answers	Yes	Yes	N/A
Random Practice Mode	Yes	Yes	N/A
Standard Letters, Numbers, Punctuation	Yes	Yes	N/A
All Morse Characters	Yes	Yes	N/A

MM-2

MorseMatic

MorseMatic™

KT-2

Keyer Trainer

Keyer Trainer

CK-2

Contest Keyer

For more information write AEA, or better yet see your favorite dealer for a demonstration.

Software ©copyright by AEA.

PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION.

ADVANCED ELECTRONIC APPLICATIONS, INC.
P.O. Box C-2160,
Lynnwood, WA 98036
(206) 775-7373
Telex: 152571 AEA INTL

AEA
Brings you the breakthrough!

2

Preamplifiers

The famous Palomar Engineers preamplifier has been updated and packaged in an attractive new cabinet.

For the SWL there is the P-305 (9-v DC powered) and the P-308 (115-v AC powered) featuring full shortwave coverage, selection of two antennas, 20 db attenuator, 15 db gain control and on-off-bypass switch.

For transceivers, the P-310X (115-v AC powered) and the P-312X (12-v DC powered) feature automatic bypass on transmit, adjustable delay for return to receive, and 350 watt transmit capability.

All models have these features:

- **Up to 20 db gain.**
- **Covers 1.8 to 54 MHz in four bands.**
- **Low noise figure.**
- **Reduces image and spurious response.**
- **8" x 5" x 3". Brushed aluminum control panel. Black vinyl cover.**
- **SO-239 connectors.**
- **LED pilot.**

Order direct or from your favorite dealer. Model P-305 Receiver Preamplifier for 9-v DC $99.95. Model P-308 for 115-v AC $109.95. Transceiver Preamplifier Model P-310X $129.95. Model P-312X $129.95. Add $3 shipping/handling. Calif. residents add sales tax.

master charge VISA

Don't wait any longer to pull out weak, rare DX.

Send for FREE catalog describing the Preamplifiers and our complete line of Noise Bridges, SWR Meters, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

Palomar Engineers
1924-F West Mission Rd.
Escondido, CA 92025
Phone: (619) 747-3343

1983 CALLBOOKS

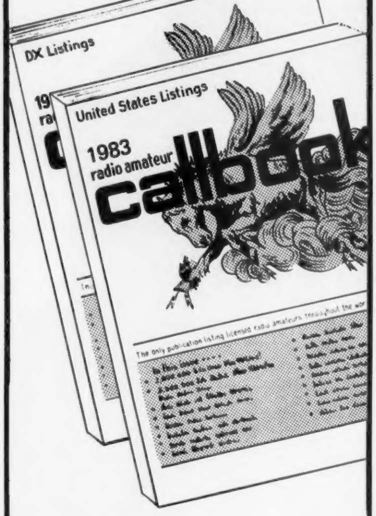

Order today!
NEW 1983
RADIO AMATEUR CALLBOOKS
READY DECEMBER 1ST!

The latest editions of the world-famous Radio Amateur Callbook will be available soon. The U.S. edition features over 400,000 listings, with over 75,000 changes from last year. The Foreign edition has over 370,000 listings, over 50,000 changes. Each book lists calls and the address information you need to send QSL's. Special features include call changes, census of amateur licenses, world-wide QSL bureaus, prefixes of the world, international postal rates, and much more. The new 1983 Callbooks will be published December 1, 1982. Order your copies now.

	Each	Shipping	Total
☐ US Callbook	$19.95	$3.05	$23.00
☐ Foreign Callbook	$18.95	$3.05	$22.00

Order both books at the same time for $41.95 including shipping.

Order from your dealer or directly from the publisher. All direct orders add shipping charge. Foreign residents add $4.55 for shipping. Illinois residents add 5% sales tax.

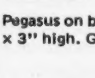

SPECIAL OFFER!
Amateur Radio Emblem Patch
only $2.50 postpaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on jackets and caps.

✓61

RADIO AMATEUR callbook INC.
Dept. B
925 Sherwood Drive
Lake Bluff, IL 60044, USA

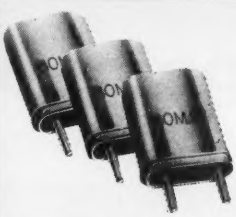

WE'RE ROLIN IN CRYSTALS!
✓418

2 Meter Crystals — $3.95 each
(10 or More — $3.50 each)
Quick Delivery

We Stock Crystals For:

Clegg
Kenwood
Standard
Lafayette

Drake
Midland
Wilson
Tempo

Icom
Regency
Yaesu
VHF Eng

(Custom Crystal Orders Accepted.)

Rolin Distributors
P.O. Box 436 Department 7
Dunellen, N.J. 08812
201-469-1219

Precision Cut Land Mobiles Available

The Code Reader That Sends

Tune
Rcv
Xmit
ID
Mini-Terminal
Lo
Filter Hi
Power

Mini-Terminal™
suggested price $299.95

All in one package—CW, RTTY, ASCII send/receive and hard copy capability for under $300. Unbelievable, but true! Again, **Kantronics** puts all the features you want in a single unit: The **Kantronics Mini-Terminal.**™

You send CW with your key or keyboard, and the **Mini-Terminal**™ converts to RTTY or ASCII. **Mini-Terminal**™ also reads all incoming CW, RTTY, and ASCII messages and reads out on a bright green 10-digit display. For hard copy simply attach any Centronix compatable printer, such as the Epson MX-80 or the Paper Tiger, and watch the **Mini-Terminal**™ do the rest.

A complete code reader and RTTY terminal, with printer compatability all in one package only 2½"x5"x5¼". Get all you can for your dollar; get the **Kantronics Mini-Terminal.**™

See your local **Kantronics** dealer, or contact

Kantronics
(913) 842-7745 1202 E. 23rd Lawrence, Kansas 66044

Winning the Coax War

The electrical length of feedline depends on its velocity factor. Don't get caught short.

Paul Swearingen W9PJF
RR #1, Box 485
Benton IL 62812

A review of the basic theory sections of many radio handbooks will reveal references to "dielectric constant" and "velocity factor" as interrelated characteristics that describe real-world influences upon the velocity of an electromagnetic wave and upon the capacitance existing between two conductors.

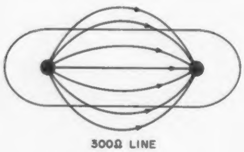

Fig. 1(a).

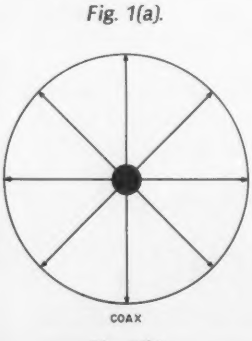

Fig. 1(b).

We don't need to be physicists or to even understand the actions of dielectric molecules to observe that capacitors come in a variety of sizes and shapes. The basic capacitor consists of two conductors separated by an insulator. When the capacitor is charged, the insulator becomes a dielectric because it is then permeated by the electric field between the conductors.

The value of the capacitance depends upon the area of the conductors, the spacing between them, and just what sort of dielectric occupies that space. For example, two sheets of aluminum about 3′ on a side and spaced about 3/16″ apart in a vacuum would form a capacitance on the order of 1500 micromicrofarads, or 1500 picofarads as some may prefer to call it.

If the vacuum between the plates were replaced with glass, the capacitance might increase by a factor of 5 to a new value of 7500 pF. The factor "5" in this case would be the "dielectric constant" of that kind of glass. The thickness of the metallic plates has little effect on the capacitance. For the smaller capacitance values with increased conductor spacings, the "edge effect" requires consideration. This effect is a result of non-linearities in the electric field near the conductor edges. Manufacturers use a variety of dielectric materials to produce the capacitors for today's electronic systems.

Radio signals and other electromagnetic waves travel at a velocity of about 300 × 10^6 meters per second in a vacuum and just a bit slower in air. This velocity of propagation is equal to about 186,000 miles per second. In liquid or solid materials, the velocity of electromagnetic waves is decreased by an amount depending upon the specific characteristics of the material. A signal travels a distance of one wavelength through space in a period of time depending upon its frequency. Under the (ugh!) metric system, the formula for a wavelength (λ) in space is: λ(meters) = 300/frequency (MHz). In terms more familiar to some of us, a free-space wavelength (λ) in feet is equal to 984/frequency (MHz).

If the same signal had to

Introducing Corsair

SWR
FWD
PROCESS
Corsair
TEN-TEC
PHONES
MIC
SPOT
USB
AGC
XTAL
OFFSET SELECT
VOX
FAST
SLOW
OFF
OUT

A New No-Compromise HF Transceiver

The CORSAIR is an extraordinary new HF transceiver. Every function operates without compromise. New unique features make it a delight to operate.

A new front end provides extreme sensitivity, low internal noise and high dynamic range to bring weak signals to life. For even greater overload prevention, the integral rf preamplifier can be switched out. More effective than the usual rf attenuator.

The filtering system, a TEN-TEC exclusive, virtually switches to privacy. It starts with a superb 2.4 kHz 12-pole ladder sideband filter system, standard. It provides variable bandwidth for ssb, great for today's crowded phone bands. A novel pass band tuning circuit allows a received signal to be moved within the pass band to its optimum position with respect to QRM. Optional narrow band filters are available for ssb, cw and RTTY, all switched from the front panel. The ultimate in QRM reduction.

Full cw break-in opens a window on the band while transmitting, turning monologues into conversation. Or, if conditions dictate, just switch to semi-break-in. And no VOX adjustment when changing modes.

A versatile offset tuning system allows the receiver and transmitter to be tuned separately with a ± 1 kHz range for fine tuning or ± 4 kHz for working off frequency. For net operation, both can be moved simultaneously.

Reliability is designed in. The CORSAIR system is so rugged it will operate into infinite SWR. And we guarantee it unconditionally (except for lightning) for one year. The CORSAIR is designed for 100% duty cycle, ideal for RTTY, SSTV and of course, contests.

Beauty is more than skin deep. The contemporary styling with the blackout LED frequency display (last digit in green), the baked-on textured bronze/black finish with aluminum trim will retain its handsome appearance permanently. Beneath its sleek exterior is a carefully crafted chassis packed with performance.

There are many other features, each with superb performance. An effective speech processor, notch filter, adjustable noise blanker, signal spotter, three position AGC, threshold ALC, simplified VOX, all controlled from the front panel. In addition, the CORSAIR has a compression loaded speaker, less than 2% audio distortion, and full accessory connections including remote bandswitch output. It even has a volume equalizing headphone output.

The CORSAIR is a total system of pure operating pleasure—it really must be put through its paces to be fully appreciated. Its smooth controls, comfortable and logically spaced, give it the feel of a superlative transceiver. One that will be a faithful companion for the years ahead.

All TEN-TEC products are completely manufactured in the U.S.A., in the foothills of the Great Smoky Mountains.

Model 560, CORSAIR transceiver.......... $1169.
See your TEN-TEC dealer or write for full information.

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862

travel through glass having a dielectric constant of 5, the distance it would move during the time period of one wavelength would be much shorter. In fact, one wavelength would be only 44.72% of the equivalent length in space. When converted to a decimal figure, .4472, this dielectric correction is the "velocity factor" (VF) of the glass. It is equal to the reciprocal of the square root of the dielectric constant or VF = $1/\sqrt{5}$ = 1/2.236 = .4472. This formula describes the mathematical relationship between "dielectric constant" and "velocity factor."

So, what can we do with dielectric constants or velocity factors? Actually, I can think of very few occasions when changing the dielectric in a capacitor would be necessary, desirable, or feasible. It would be fairly easy, though, to make a low-capacity variable capacitor by using two pieces of aluminum and to insert a variable amount of a plastic dielectric via a shaft and a dial system.

The velocity factor, though, is a much used and occasionally misused factor.

All of the coaxial and parallel-wire feedlines using solid dielectrics are characterized by higher losses than found in equivalent air-insulated lines and by having velocity factors of less than 1. These velocity factors mean that radio waves are propagated along these lines at velocities less than in free space. When the electrical length of the feedline to be used is critical, the velocity factor must be considered in calculating the physical length. If you wanted an electrical length of 1/2λ and the velocity factor was .80, then the desired formula for the physical length in feet would be: 1/2λ = (492 × .80)/frequency (MHz).

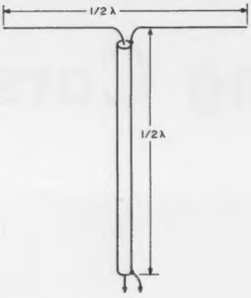

Fig. 2(a).

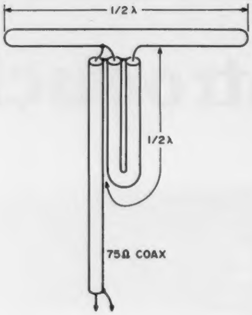

Fig. 2(b).

The velocity factors for some common coaxial feedlines range from .80 for polyethylene foam dielectrics to .66 for solid polyethylene. Some 300-Ohm parallel-conductor feedlines using a solid dielectric of polyethylene have a velocity factor of about .82. Why should that be? Fig. 1(a) shows a cross-sectional view of a piece of 300-Ohm line. The oval represents the solid dielectric and the dots represent the conductors. The arrowed lines represent an instantaneous electric field that might exist at a given moment in time. The fact that a portion of this field exists outside the solid dielectric is the reason that the 300-Ohm line velocity factor of about .82 lies between the .66 factor of solid polyethylene and the value of 1.0 for air. This also explains the sensitivity of oval 300-Ohm line to external influences such as rain, snow, and ice, or to the proximity of metallic objects.

Fig. 1(b) shows the cross section of a 100%-shielded coaxial cable. In this case, the electric field is wholly contained within the shield, and surrounding influences are minimal. That's why coaxial cable can be taped to your tower, run along gutters, or even buried with little observable effect upon its performance.

The velocity factor is used to determine the physical length of the line whenever a particular electrical length of feedline is required, and when in the feedline's use an electric field will exist between the feedline conductors as a result of current flow along the conductors. Fig. 2 shows some of the typical cases wherein the velocity factor would be used in calculating the physical length of the required feedline. In Fig. 2(a), a feedline 1/2λ long is used so that the impedance at the center of the antenna will be repeated at the ground end for easy impedance measurements. The desired physical length of a 1/2λ line would be the free-space length times the velocity factor, or 1/2λ (ft.) = (492 × VF)/frequency (MHz). In this case, the line could be made any whole number multiple of the correct length if a single 1/2λ wasn't long enough.

Fig. 2(b) shows a 4:1 coaxial balun connected to a folded dipole radiator. The length of the 1/2λ U-shaped piece of coax is calculated with VF. Fig. 2(c) shows broadside radiating elements, each fed through a gamma match. Any equal lengths of cable could be used for pieces X and Y to satisfy the phasing requirements of the broadside array. The 3/4λ sections, however, also serve as impedance transformers between the radiators and the feedline junction. The physical length of the 3/4λ lines should be computed with the VF.

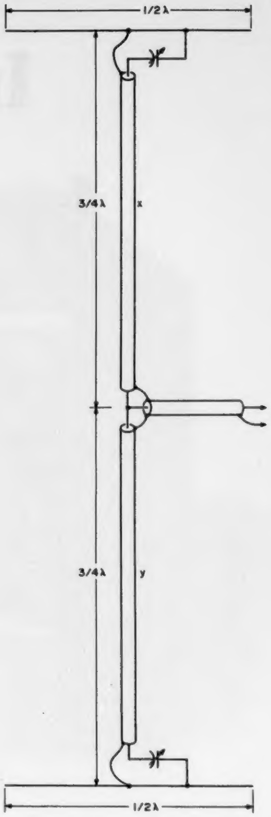

Fig. 2(c).

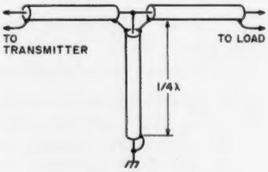

Fig. 2(d).

Fig. 2(d) shows a 1/4λ section of coaxial cable used as an rf choke. The shorted end of the 1/4λ section is transformed into a very high impedance at its connection point to the coaxial feedline. It has no effect upon the feedline as far as the operating frequency is concerned, but it keeps both sides of the coax at ground potential for dc or lightning protection. In addition, the 1/4λ section will act as a dead short across the coaxial cable at the second harmonic!

Fig. 2(e) shows 1/4λ ver-

FT-230R: QUITE A SIGHT! (AND EASY TO SEE, TOO!!)

Sporting an all-new Liquid Crystal Display, the FT-230R is Yaesu's high-performance answer to your call for a very affordable 2 meter mobile rig with an easy-to-read frequency display! The FT-230R combines microprocessor convenience, a sensitive receiver, a powerful yet clean transmitter strip, and the new dimension of LCD frequency readout. See your Authorized Yaesu Dealer today — and go home with your new FT-230R!

YAESU
SALE SUBJECT
FCC CERTIFICATION

- LCD five-digit frequency readout with night light for high visibility day or night.
- Two VFOs for quick QSY across the band.
- Ten memory slots for storage and recall of favorite channels.
- Selectable synthesizer steps (5 kHz or 10 kHz) in dial or scanning mode.
- Priority channel for checking a favorite frequency for activity while monitoring another.
- Unique VFO/Memory Split mode for covering unusual repeater splits.
- Up/Down band scan plus memory scan for busy or clear channel. Scanning microphone included in purchase price.
- Full 25 watts of RF power output from extremely compact package.
- Built-in automatic or manual tone burst.
- Optional synthesized CTCSS Encode and Encode/Decode boards available.
- Lithium memory backup battery with estimated lifetime of five years.
- Optional YM-49 Speaker/Microphone and YM-50 DTMF Encoding Microphone provide maximum operating versatility.

And don't forget! Yaesu has a complete line of VHF and UHF handheld and battery portable transceivers using LCD display!!!

FT-208R
FM Handheld
2 Meters

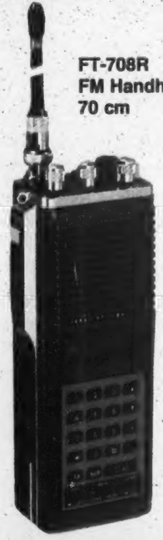

FT-708R
FM Handheld
70 cm

FT-290R - 2 Meters
SSB/CW/FM Portable
FT-690R - 6 Meters
USB/CW/AM/FM Portable

YAESU
The radio.

482

Price and Specifications Subject To Change Without Notice or Obligation

YAESU ELECTRONICS CORP. 6851 Walthall Way, Paramount, CA 90723 • (213) 633-4007
Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246 • (513) 874-3100

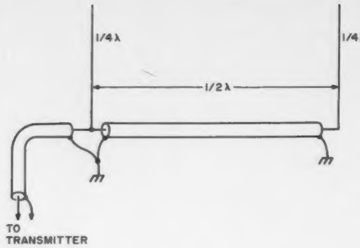

Fig. 2(e).

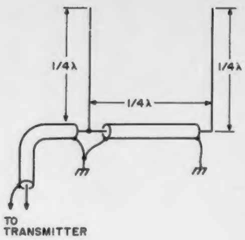

Fig. 2(f).

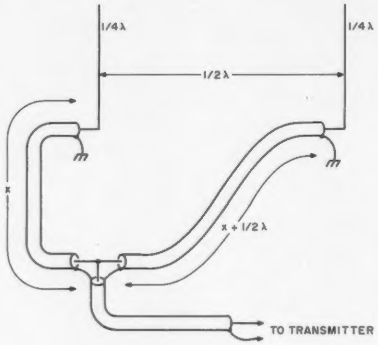

Fig. 2(g).

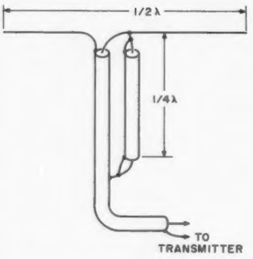

Fig. 3(a).

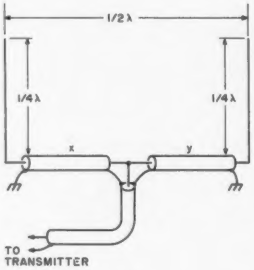

Fig. 3(b).

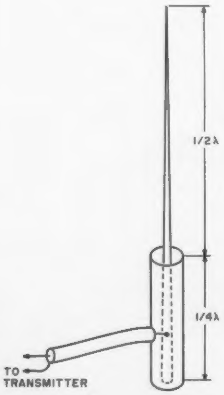

Fig. 4.

tical antennas spaced 1/2λ apart and fed 180° out of phase through a 1/2λ line to achieve a figure-eight radiation pattern. Fig. 2(f) shows similar antennas spaced 1/4λ apart and fed 90° out of phase to produce a unidirectional pattern. The velocity factor would apply to these phasing lines. Please note that Figs. 2(e) and (f) are just basic representations of an antenna system and not a practical arrangement.

How could you make a 1/2λ of coax (free space 1/2λ × VF) stretch between two verticals spaced a 1/2λ (free-space value) apart? It would be impossible unless you used an *air-dielectric* coax and then, of course, its proper length would be equal to the antenna spacing.

The proper phasing with solid-dielectric coax can be achieved as shown in Fig. 2(g). Dimension X is any convenient length of coax. The 1/2λ portion is computed with the VF. While this feedline system provides the proper phasing, it doesn't provide the necessary impedance matching. The same scheme could be used to provide the correct phasing for Fig. 2(f), but then the lines would be X, and X + 1/4λ.

Fig. 3 shows some cases where the velocity factor is *not* used in determining the physical length of solid-dielectric cables. In Fig. 3(a), a 1/4λ of coaxial cable is paired with a portion of the feedline to act as a decoupling stub or balun. Its length is approximately equal to the free-space length of a 1/4λ. The VF of the coax does *not* apply because no electric field exists between the inner conductor and the shield of the 1/4λ of coax. In fact, the inner conductor could be cut off flush with the dielectric, or even removed, as it has no function in this application other than to provide increased physical rigidity. In Fig. 3(b), line segments X and Y could be of any equal lengths and still provide the correct phasing for the broadside array. VF does not apply because a particular electrical length of feedline is not required.

The effects of velocity factor/dielectric constant in places other than feedlines can sometimes be important to the correct functioning of antennas or resonant circuits. For example, a coaxial version of a "J" antenna is shown in Fig. 4. The lower 1/4λ could be an air-insulated high-Q resonant section which matches the high end impedance of the 1/2λ radiator to the coaxial feedline.

This is a good, simple antenna for VHF. If it were to be built, though, you might be tempted to fill the lower 1/4λ section with plastic potting compound for improved physical rigidity or to minimize the effects of weather. Any dielectric added, however, would change the electrical length of the section, thereby detuning the system. A better approach would be to use the velocity factor of the plastic filler beforehand to determine the correct length of a plasticized 1/4λ section.

Why have I persisted in using the free-space formulas times the velocity factor to compute specific physical lengths? What's wrong with the old, tried and true formula, 468/frequency (MHz), to find the length of a 1/2λ? The reason is that antenna design is influenced by something called "end effect." This necessitates just about a 5% reduction of the free-space lengths when calculating the physical length of wire antennas. This phenomenon does not occur in transmission lines, so for these applications we just have to adjust the free-space figures with the velocity factor.

There is no doubt that coaxial cable is the most-used amateur feedline today. Its ease of use more than compensates for its small losses. If you need a critical electrical length, however, don't forget to use the velocity factor established by the cable manufacturer.■

step up to the best...

Without doubt LR-1 is the repeater value leader! Compare its outstanding performance with any repeater -- then look at its price. LR-1 features include individual die-cast shielding of receiver and transmitter plus a separately shielded 6-stage receiver prefilter for peak performance in harsh RF environments • Front panel metering of all vital functions • CW identifier • Symmetric hard limiting for clean natural audio • Low power MOS control logic • Even the cabinet is included -- just plug in and go! The price? Only $1095 (US amateur club net).

NEW

LR-1
REPEATER AMPLIFIER
MICRO CONTROL SPECIALTIES
PA-75

LINKING? The LR-1 is also available with control circuitry for Link Transceiver operation. Now link repeater sites with the flexible control capability you've always wanted.

HIGH POWER? Our PA-75 power amplifier is the champion! Ruggedly built to give years of dependable operation in continuous duty repeater service.

NEW

MARK 3-C CONTROLLER
MICRO CONTROL SPECIALTIES
POWER
RESET
STATUS INDICATORS
MARK 3-CR REPEATER
MICRO CONTROL SPECIALTIES
VOLUME
SQUELCH
STATUS INDICATORS

Mark 3C repeaters and controllers have no equal in performance. Both units feature auto patch, reverse autopatch, autodial, 13 Morse messages and a total of 39 functions. Both feature microprocessor control and both have been proven in the field from icy Alaska to tropical Brazil. A Mark 3C supercontroller can make any repeater a super performer. The Mark 3CR repeater is in a class by itself. It combines superbly designed RF circuitry in one handsome package. It is without doubt the world's most advanced repeater!

• SEE US AT DAYTON •

CALL OR WRITE FOR FULL DETAILS

✓49

MICRO CONTROL SPECIALTIES

23 Elm Park • Groveland, Massachusetts 01834 • Telephone (617) 372-3442

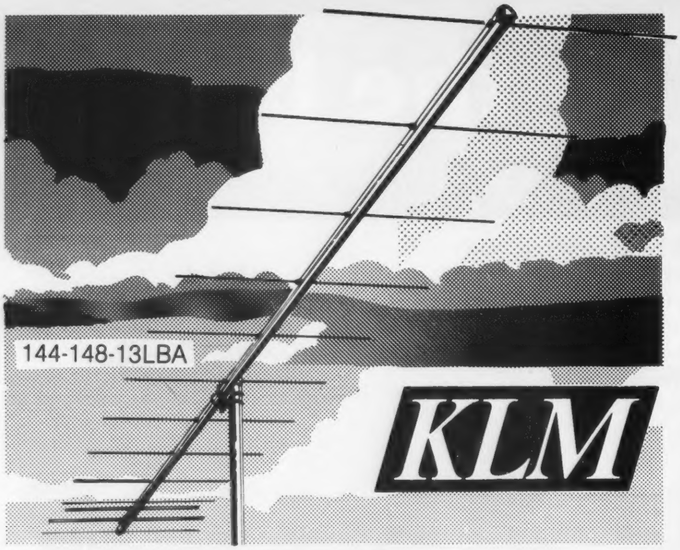

WHY SETTLE FOR HALF THE BAND?
Enjoy super-gain, low VSWR, and FULL COVERAGE, 144 through 148 MHz, with less weight and windload. Dual-driven elements, balanced feed for a better match and clean pattern.

Bandwidth:	144-148 MHz	Balun:	2KW 4:1
Gain:	15.5 dBd	Boom:	21' .5/1½"
VSWR:	1.2:1 & less	Windload:	1.6 sq ft
Beamwidth:	28°	Weight:	9 lbs

CIRCULAR POLARIZED For the Phase IIIB satellite and terrestrial DX, ATV, and FM. Minimizes multipath and flutter fading. Rugged symmetrical construction.

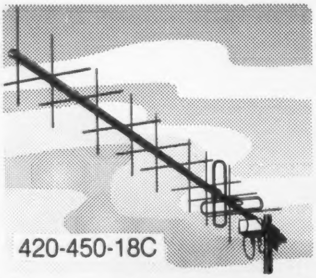

Bandwidth:	420-450 MHz		
Gain:	12 dBdc		
VSWR:	1.5:1 & less		
F/B:	20 dB		
Baluns:	2KW, 4:1 (2)	Windload:	.5 sq ft
Boom:	88"/1"	Weight:	3.6 lbs

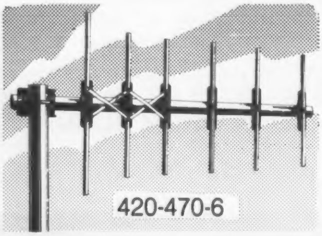

IDEAL for point-to-point and repeater control. Rear-mounted, vertically polarized, compact. Continuous coverage, 420-470 MHz. Direct coax feed suitable for most installations.

		Bandwidth:	420-470 MHz
		Gain:	8dBd
		VSWR:	1.2:1 & less
Boom:	2'/1" O.D.	Beamwidth:	60°
Weight:	1.2 lbs	F/B:	20 dB, min

SEE YOUR KLM DEALER:

KLM Electronics, Inc. P.O. Box 816, Morgan Hill, CA 95037
(408) 779-7363

HURDLE THE HUMP
WITH TWIN OAKS CW TRAINING PROGRAM

CW TEACHING SYSTEMS

Twin Oaks Associates is a partnership of mental health professionals who are hams interested in helping others to learn CW. Twin Oaks has developed three Morse code teaching systems on tape which represent the careful application of psychological principles to learning. They help students learn to recognize and copy Morse characters at a very high speed.

The first set of tapes is called System 12©. It is designed for the ham who may have a Novice or Technician class license but can't "get over the hump" to pass the General class code test. System 12 takes students past 15 words per minute on five carefully-structured, successive-demand, 60-minute cassettes.

The second training program is called System 24©. It assumes that the student is able to copy comfortably at 9 or 10 words per minute but would like to go after the amateur Extra class license. This program is on five 60-minute cassettes and carries the student past 30 words per minute.

The third teaching system, the System 12 Alphabet Book©, is designed for persons who know absolutely nothing about Morse code. It may be used, however, by persons who are not thoroughly comfortable at 5 words per minute, and it is useful for either classroom or self-instruction.

Each program, or system, comes with its own carefully-written study guide. Systems 12 and 24 cost $30 each, and the System 12 Alphabet Book costs $15.

GET HUMPIN'—
ORDER TODAY!

TWIN OAKS ASSOCIATES
ROUTE 5,BOX 37 ✓197
KNOXVILLE IA 50138.

FAST SCAN

***$249**

A modular approach. . . for your own custom-designed ATV system. . . . Here's how

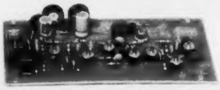

TXA5-4 ATV EXCITER/MODULATOR.$89 ppd

This wired and tested module is designed to drive the Motorola MHW-710 module in the PA5 10 watt linear amp. The crystal in the 100 mHz region keeps harmonics out of two meters for talk back. The video modulator is full 8 mHz for computer graphics and color. Requires 13.8 vdc reg @ 70 ma. Tuned with xtal on 439.25, 434.0, or 426.25 mHz. Provision for sync expanding. Two frequencies available.

PA5 10 WATT ATV POWER MODULE $89 ppd

The PA5 will put out 10 watts RMS power on the sync tips when driven with 80 mw by the TXA5 exciter. 50 ohms in and out, plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 vdc regulated @ 3 amps.

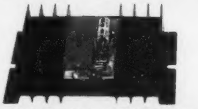

FMA5 AUDIO SUBCARRIER GENERATOR .... $29 ppd

Puts audio on with your camera video just as broadcast TV does at 4.5 mHz. Puts out up to 1 v p-p to drive the TXA5 or VM-2, 3, or 4 modulators. Requires low Z mic (150 to 600 ohms), and + 12 to 18 vdc @ 25 ma. Works with any xmtr with 5 mHz video bandwidth.

TVC-2 ATV DOWNCONVERTER. . . . $55 ppd

Stripline MRF901 (1.7 db NF) preamp and double balanced mixer module digs out the weak ones but resists intermods and overload. Connects between uhf antenna and TV set tuned to channel 2 or 3. Varicap tunes 420 to 450 mHz. Requires + 12 to 18 vdc @ 20 ma. Super sensitive TVC-2L with NE64535 preamp (.9db NF) stage. . . $69 ppd.

***TXA5, PA5, FMA5 and TVC Basic Module Pkg.**

Call or write for our complete list of specifications, station set-up diagrams, and optional accessories which include antennas, modulators, detectors, test generators, cameras, etc. **WE ARE A FULL-LINE SUPPLIER OF ALL YOUR ATV NEEDS.**

TERMS: VISA or MASTER CARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Allow three weeks after order for delivery.

(213) 447-4565 Charge card orders only

P.C. ELECTRONICS **2522 Paxson Lane,**
Arcadia, California 91006
Tom W6ORG Maryann WB6YSS

The New Standard in High Performance Repeater Control...

☐ FRIENDLY, POWERFUL, EASY TO USE – Human engineered to be your "assistant" at the repeater, with capability second to none.

☐ REMOTELY CONFIGURABLE – Change command codes, messages, tone characteristics, timing, and more, remotely! Reliable storage in E²PROM.

☐ Room to grow: BUILT IN! – Features intelligent remote control and meter readback. Interfaces to synthesized remote bases and links. Planned software upgrade path.

☐ SUPPORT –We invented the "Computer Controlled Talking Repeater," so we know how to provide the applications assistance, and long term support so crucial to a computer based product.

☐ BRING YOUR REPEATER SYSTEM INTO THE 80'S – Starting at less than $1200!

The RC-850 Repeater Controller!

Call or write for detailed specifications.

Manual and demonstration cassette tapes available separately.

acc advanced computer controls

10816 Northridge Square
Cupertino, CA 95014
(408) 253-8085

124

ROTATE YOUR BEAM

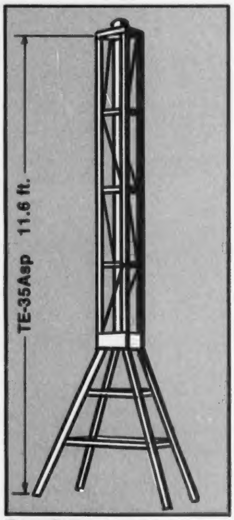
TE-35Asp 11.6 ft.

Roof Tower
11.6 ft. $194.95
6½ ft. extension sections $70.00

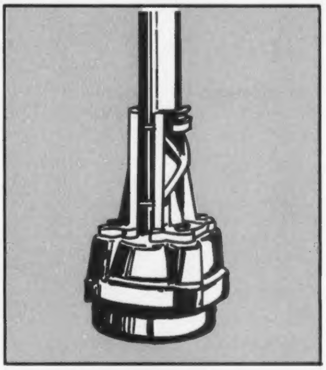

KR400
Azimuth Rotator*
8½ sq. ft. $119.95

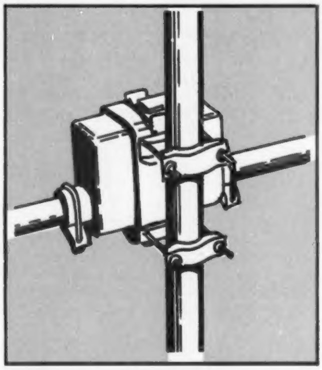

KR500
Elevation Rotator*
7½ sq. ft. $189.95

* *Rotators come complete with an attractive control box that indicates beam heading.*

Send for free catalog describing our rotators, towers, thrust bearings, VHF beams, Swiss Quads, Tribanders, and more.

BY MAIL:
TET Antenna Systems
1924-E W. Mission Road
Escondido, CA 92025

BY PHONE: 714-743-7025 170

TET ANTENNA SYSTEMS

HAL COMMUNI
RTTY & CW

PROFESSIONAL SYSTEM!

The DS3100ASR Terminal and ST6000 Demodulator are the choice of professional RTTY operators the world over. Some of the advanced features offered by this equipment are:

DS3100ASR:

● True ASR capabilities ● 200 line display storage ● 150 lines receive ● 50 lines transmit ● Baudot, ASCII, and Morse Codes ● 45 to 9600 baud RTTY ● 5 to 175 WPM CW ● WORD, LINE, and CONTINUOUS modes ● SYNC idle ("diddle") ● Unshift on space (USOS) ● WRU answerback ● Selective call printer control (SELCAL) ● Serial ASCII printer output for received text in any code ● Four keyboard controlled accessory switches ● RS232 or loop RTTY I/O ● 10 user-programmable HERE IS messages ● EAROM non-volatile storage of 4 HERE IS messages and operating conditions ● On-screen status indicators ● Custom labeled 3-legend keytops for non-confusing control operations ● Built-in 12 inch P31 display ● 120/240V, 50/60 Hz AC ● 13.5" × 20.5" × 15.25" ● 60 lbs. (two cartons)

MSO3100:

● Inserts into DS3100 ● Adds "electronic mail box" to DS3100 ● Extends DS3100 storage by 32K ● Works with all codes, Baudot, ASCII, or CW ● User-programmable call-up code ● May be used with 'KOS to switch TX and RX on/off ● Inserts CW ID when required ● Sends user "HELP" and "RYRY" and "QBF" test messages when requested ● Lists directory contents, size, and date created ● Allows password for delete or read protection of files ● Use for brag tapes as well as for message storage ● Commands include: ".DIR .SDIR .READ .WRITE .ENDFILE .HELP .SEND .FILE-HELP .KY1ON .KY1OFF .KY2ON .KY2OFF .PRINTON .PRINTOFF .QBF .RYS .DELETE .EXIT" ● Factory installation only

ST6000:

● Super RTTY demodulator ● Perfect companion to DS3100 in "dream station" ● All three standard RTTY shifts (170-425-850 Hz) ● Receive and Transmit circuitry ● Transmit tones crystal controlled ● Transmit CW ID - 100 Hz shift down in frequency ● Available for "high" or "low" tones (*High tones recommended for United States* - 2125 Hz mark) ● Wide bandwidth limiter for superior signal capture ● FM or AM operation ● Multipole active filter front-end ● Active filter discriminator ● Active low pass filter ● Synthesized transmit tone outputs ● ATC (automatic tone threshold control) ● DTH (decision threshold hysteresis) ● RS232, MIL188, CMOS, and current loop I/O ● Built-in 175 VDC, 60 ma neutral loop supply ● Motor control relay for autostart ● Antispace ● Built-in tuning oscilloscope ● 120/240V, 50/60 Hz AC ● Table or Rack cabinet (specify which) ● 3.5" × 9" × 17" ● 15 lbs.

PORTABLE RTTY and CW

The HAL CWR6850 brings a new dimension to amateur RTTY operation - PORTABILITY! Even though the size is small, the features are many:

CWR6850:

● Built-in display screen and demodulators ● 5" green CRT display ● 32 character display lines ● 4 pages of display ● 6 user-programmable HERE IS messages ● Internal RTTY demodulator for both "high" and "low" RTTY tones, three shifts each (170-425-850) ● Baudot or ASCII baud rates of 45 to 300 baud ● Morse code send and receive 3 to 40 wpm ● Parallel ASCII printer output for received text ● Separate, small keyboard ● Tape input/output connections ● Requires 12 VDC, 1.8 Amperes ● 12.75" × 11.75" × 5" (CWR6850); 13.75" × 2" × 7.25" (Keyboard) ● 20 lbs, including keyboard

LOW COST AND COMPACT!

The DS2050KSR is a time-proven RTTY terminal, combining the best of the popular HAL DS2000 and ST5000. Some of the DS2050 features are:

DS2050KSR:

● One cabinet for keyboard, display generator, and demodulator ● Full 72 character line by 24 line screen ● 2 programmable HERE IS messages ● Built-in RTTY demodulator for two shifts (170 or 850 Hz) ● Send and receive Baudot RTTY at 45 to 100 baud and ASCII RTTY at 110 to 300 baud ● Send CW at 5 to 100 wpm ● Receive CW (with MR2000 option) from 5 to 100 wpm ● RTTY CW ID is built-in ● KOS (Keyboard operated switch) ● Full current loop interface for send and receive RTTY loop (external loop supply required) ● SYNC idle ● USOS ● WORD mode ● Bright-dim video to distinguish TX and RX text ● 120/240V, 50/60 Hz AC ● 14.1" × 8.8" × 4.7" ● 18 lbs ● Two-tone tan cabinet ● External TV monitor required (HAL KG12 or ESM914 recommended).

CATIONS CORP.
EQUIPMENT

COMMUNICATIONS TERMINAL

The CT2100 and KB2100 make up a very versatile and convenient RTTY and CW communications terminal. The CT2100 offers capabilities available in no other single-unit RTTY system. Some of these features are:

Communications Terminal
CT2100
HAL
RS2100
HAL

CT2100 & KB2100:

● KSR or split-screen operation ● Large or small character video ● 72 or 36 character display lines ● 24 lines per display page ● 2 pages of 72 character per line display or 4 pages of 36 character lines ● 12 line split screen transmit pretype buffer ● 2 user-programmable HERE IS messages ● Very large brag tape storage in MSG2100 (2K characters) ● 4 Built-in RTTY demodulators ● "High" tone RTTY (170-425-850 shift) ● "Low" tone RTTY (170-425-850 shift) ● 103 Modem RTTY (1070-1270 Hz; to 300 baud) ● 202 Modem RTTY (1200-2200 Hz; to 1200 baud) ● Baudot, ASCII, or Morse code ● 45 to 1200 baud Baudot or ASCII RTTY ● 5-100 WPM CW ● Crystal controlled synthesized transmit tones match receive filters ● RS232, Loop, or audio I/O interface ● Tape in/out connections ● KOS (keyboard operated switch) for auto TX/RX ● HDX or FDX ● Transmit data from loop device (paper tape distributor, etc.) ● Small separate keyboard with flexible cord for comfortable lap operation ● On-screen status line and tuning indicator ● Serial ASCII printer output to print all received text ● 120/240V, 50/60 Hz AC ● 16.75″ × 3.625″ × 10.375″; 19 lbs (CT2100) ● 14″ × 2.375″ × 7″; 7 lbs (KB2100) ● Two-tone gray cabinet with color front panel graphics ● External monitor required - HAL KG-12 or ESM914 recommended.

RS2100 - NEW RTTY TUNING SCOPE:

HAL
RS2100
RTTY SCOPE

● Matches CT2100 cabinet ● Gives crossed-ellipse type of RTTY tuning indication for CT2100 ● Also includes built-in 175 VDC, 60 ma current loop supply ● Connects directly to CT2100 rear panel ● Also may be used with these other HAL products: DS2050, DS2000, ST5000, CWR685, CWR6850, CWR670, CWR6700, and ST5 or ST6 (with modification) ● One inch green phosphor CRT ● Front panel positon, focus, and intensity controls ● 120/240V, 50/60 Hz AC ● 3.5″ × 8.25″ × 10.156″ ● 12 lbs.

MSG2100 - Message Storage ROM Option:

● Installs in CT2100 ● Stores 7 - 256 character and 1 - 192 character "brag-tape" or reply messages ● Also stores contents of both HERE IS messages ● Non-volatile storage is not lost when power is turned off ● Type 2716 EPROM programmed by HAL or by anyone with EPROM programmer ● Have several made - one for home, one for field day, etc. ● Coding forms included with each CT2100 - KB2100 system.

WORLD PRESS SERVICES FREQUENCIES
HAL TELEREADER

SWL - RTTY and CW, TOO!

Now you can also enjoy shortwave listening to RTTY and Morse code transmissions with a unit designed for that purpose. The CWR6700 offers many advance features, previously available only in more expensive transmit-receive terminals. Some of these features are:

CWR6700:

●Receive ASCII, Baudot, or Morse code transmissions and see the decoded characters on the TV monitor screen ●RTTY speeds from 45 to 300 baud (60, 66, 75, 100, and 300 wpm) ●CW speeds from 4 to 50 wpm ●Unshift on space (UOS) for Baudot reception ●Parallel ASCII printer output ●Printer prints received ASCII, Baudot, or Morse signals ●Requires external TV monitor (HAL KG12 or ESM914 recommended) ●Runs on 12 VDC, 0.8 Ampere ●8″ × 2.85″ × 12.6″ ●8 lbs

RTTY DEMODULATORS:

HAL has long been a leader in the RTTY demodulator market. Our first two demodulator products, the ST5K and ST6K, are still in use all over the world and are still available on special order from HAL Communications (kit form only). The ST6000, as mentioned above, is a "standard of comparison" for performance and reliability. The ST5000 is a simplified version of the ST6000, particularly suited for limited budget installations where high performance is still a requirement. Some of the ST5000 features are:

ST5000:

●Two shifts - 170 and 850 Hz (others available on custom order) ●Internal 175 VDC, 60 ma current loop supply ●Motor control autostart with motor relay and outlet ●Built-in AFSK transmit tone generator with narrow-shift CW ID ●Meter tuning indicator with provision for external tuning scope (RS2100 recommended) ●2.75″ × 8″ × 12″ ●9 lbs shipping ●Two-tone blue and beige cabinet.

HAL COMMUNICATIONS, YOUR RTTY COMPANY:

HAL Communications Corp.
P.O. Box 365
Urbana, Illinois 61801
(217) 367-7373
✓345

Since 1969, we have been designing and selling RTTY equipment for amateur and commercial use. We can claim many firsts in this business, including the first amateur video display of RTTY (RVD1001 and RVD1002) and the first commercial electronic amateur Baudot keyboard (DKB2010). The HAL people are proud of the equipment they sell and have a lot of experience in interfacing many types of equipment for RTTY and CW. Yes, RTTY can be confusing, but we'll be glad to help you if you give us a call.

ICOM HF

Three Choices—Three Great Radios

HF ALL BAND TRANSCEIVER IC-720A
ICOM

IC-720A

Listen to signals from around the world with a 100 KHz — 30 MHz receiver. Talk with a 160 — 10 meter transceiver — ready to go WARC 79 bands, dual VFO's — split operation. ICOM's DFM (Direct Feed Mixer), passband tuning, speech compressor, 100 watts, SSB, CW, AM, RTTY (FSK), computer compatible tuning, 12 volt operation, all features standard except CW & AM narrow filters. *ICOM system** accessories are available for a complete station.

ICOM HF TRANSCEIVER IC-740
SOLID STATE ALL BANDER

IC-740

Versatility plus! ICOM's newest addition to HF offers features most asked for by ham operators. 160 — 10 meters, variable noise blanker and AGC with off position, IF shift and passband tuning, automatic SSB mode selection, notch filter, switchable CW filter, 8 memories, SWR meter, XIT, speech compressor, 100 watts and 12 volt operation. Options are FM, automatic keyer, internal AC power supply and 5 IF filters. *ICOM system** compatible.

IC-730

Go portable/mobile with ICOM's small HF. *ICOM system** compatible. 100dB dynamic range, +19.5dBm intercept point receiver utilizing ICOM's DFM, SSB, CW, AM, dual VFO's — split operation, one memory per band, CW/SSB filter options, 100 watts, 12 volt operation.

**ICOM system.* *The same accessories work with all three HF transceivers — IC-2KL autobandswitching broadbanded linear amplifier, AT-500 or AT-100 autobandswitching, autotuning antenna tuners, IC-PS15 power supply, BC-10A memory backup, IC-SP3 external speaker, IC-HP1 headphones, IC-AH1 autobandswitching mobile antenna, IC-MB5 mobile mount and IC-SM5 desk microphone (condesenser type).*

ICOM

The World System

ICOM America, Inc., 2112-116th Ave NE, Bellevue, WA 98004 **(206)454-8155**/3331 Towerwood Drive, Suite 307, Dallas, TX 75234 **(214)620-2780.**

All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions.

Evert Fruitman W7RXV
2808 West Rancho Drive
Phoenix AZ 85017

Red-Hot and Ready to Go

Anyone who has ever soldered knows that the cord gets in the way. Find freedom with this home-brew cordless iron.

Here's a simple, one-evening project that has proved to be very worthwhile. The end result is an instant portable soldering iron that is heavy enough for most soldering jobs short of antenna and chassis work. Since the tip can be changed from high to low power, the battery life may be extended when only light duty work is involved.

A 6-1/2" × 2" × 1-5/8" box neatly holds the parts, which consist of two size D nicads, two barrier strips, an on/off switch, a pilot lamp, a replacement soldering gun tip, and a diode to facilitate recharging the batteries. The pilot lamp is a #222 (2.25 V, 0.25 A).

Do use the lamp, as it is a very practical visual voltmeter and will give an indication as to when the battery needs a recharge. The tip still will get hot even if one of the cells is run down, and that can lead to deep discharge of the cell. Besides that, the lamp helps you to see where the solder is supposed to go inside of those dark and mysterious projects. (With 3.5-Ah cells and the tip removed, the thing makes an excellent 14-hour emergency flashlight.)

Without a doubt, there are better ways than the one shown to secure the tip, but this method is adequate and allows the business end of the instrument to get into tight places. If you wish to duplicate this mess, use a convenient length of #12 wire. The two-inch length shown has a voltage drop of about 10 millivolts per leg.

The heavy-duty tip, Wahl #7546, draws 8.5 A at 2.5 volts. The regular tip draws 6.5 A. With that kind of current, it is no surprise to find less than 2.5 V at the tip. The measured voltage is close to 2.1. The batteries fell to 2.25 volts.

With that kind of current, the on/off switch must be a heavy-duty type. The least expensive on/off switch that I could get happened to be a push-on/push-off type. Since the iron stands by itself, this allows both hands to be used for bringing the work to the iron—which is often the most convenient way to do it. With the lamp glowing and the point smoking, you are not likely to go off and leave the thing turned on.

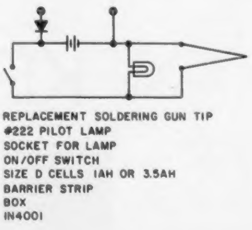

Fig. 1.

A quick word concerning the batteries is now in order. With 1.2-Ah size D cells, expect about 8 minutes operating time. Allowing 10 seconds to reach operating temperature and another 10 seconds to make the connection, that would figure out to be about 25 connections (that's the high-power tip). With 3.5-Ah batteries, the arithmetic says to expect about 73 connections. The lighter tip should give about 23% more operating time.

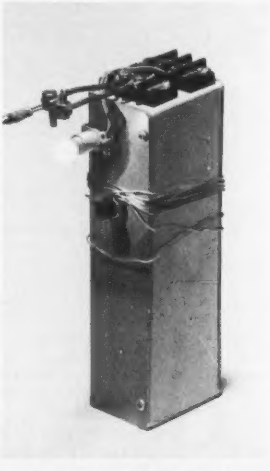

Instant soldering iron.

The batteries may be recharged by means of a suitable current source connected to the second barrier strip. The battery manufacturers normally state on the battery how much current should be used and for how long. The diode is included to ensure that the current is not fed in backwards.

Since this is a cordless iron, there is no cord to use for storing solder. (You do keep a chunk of solder on your regular iron handle or cord, don't you?) The way the solder is stored here ensures an adequate supply and is almost self-feeding.

All of the parts for this project, except the batteries, were purchased new! (Don't faint!) The heavy-duty 3-4 Ah nicads are quite expensive if purchased from the regular wholesale outlets, so try to get them from one of the surplus sources.

The unit has proved itself after many hours of reliable operation.■

NEW

"DX-traordinary."

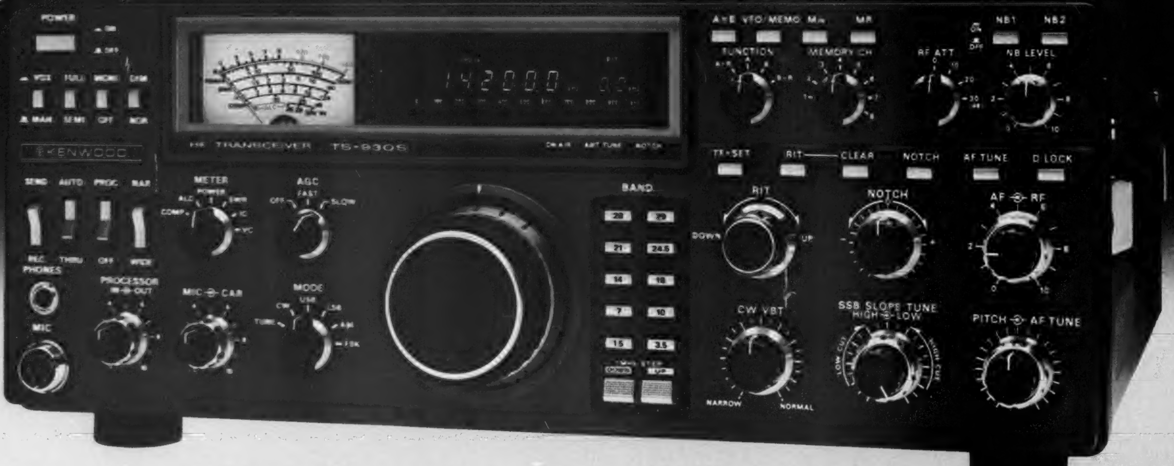

Superior dynamic range, auto. antenna tuner, QSK, dual NB, 2 VFO's, general coverage receiver.

TS-930S

The TS-930S is a superlative, high performance, all-solid state, HF transceiver keyed to the exacting requirements of the DX and contest operator. It covers all Amateur bands from 160 through 10 meters, and incorporates a 150 kHz to 30 MHz general coverage receiver having an excellent dynamic range.

Among its other important features are, SSB slope tuning, CW VBT, IF notch filter, CW pitch control, dual digital VFO's, CW full break-in, automatic antenna tuner, and a higher voltage operated solid state final amplifier. It is available with or without the AT-930 automatic antenna tuner built-in.

TS-930S FEATURES:

- **160-10 Meters, with 150 kHz-30 MHz general coverage receiver.** Covers all Amateur frequencies from 160-10 meters, including new WARC bands, on SSB, CW, FSK, and AM. Features 150 kHz-30 MHz general coverage receiver. Separate Amateur band access keys allow speedy band selection. UP/DOWN bandswitch in 1-MHz steps. A new, innovative, quadruple "UP" conversion, digital PLL synthesized circuit provides superior frequency accuracy and stability, plus greatly enhanced selectivity.
- **Excellent receiver dynamic range.** Receiver two-tone dynamic range, 100 dB typical (20 meters, 50-kHz spacing, 500 Hz CW bandwidth, at sensitivity of 0.25 μv, S/N 10 dB), provides the ultimate in rejection of IM distortion.
- **All solid state, 28 volt operated final amplifier.** The final amplifier operates on 28 VDC for lowest IM distortion. Power input rated at 250 W on SSB, CW, and FSK, and at 80 W on AM. Final amplifier protection circuits with cooling fan, SWR/Power meter built-in.
- **CW full break-in.** CW full break-in circuit uses CMOS logic IC plus reed relay for smooth, quiet operation. Switchable to semi-break-in.
- **Automatic antenna tuner, built-in.** Covers Amateur bands 80-10 meters, including the new WARC bands. Tuning range automatically pre-selected with band selection to minimize tuning time. "AUTO-THRU" switch on front panel.
- **Dual digital VFO's.** 10-Hz step dual digital VFO's include band information. Each VFO tunes continuously from band to band. A large, heavy, flywheel type knob is used for improved tuning ease. T.F. Set switch allows fast transmit frequency setting for split-frequency operations. A=B switch for equalizing one VFO frequency to the other. VFO "Lock" switch provided. RIT control for ±9.9 kHz.
- **Eight memory channels.** Stores both frequency and band information. VFO-MEMO switch allows use of each memory as an independent VFO, (the original memory frequency can be recalled at will), or as a fixed frequency. Internal Battery memory back-up, estimated 1 year life. (Batteries not Kenwood supplied).
- **Dual mode noise blanker ("pulse" or "woodpecker").** NB-1, with threshold control, for pulse-type noise. NB-2 for longer duration "woodpecker" type noise.
- **SSB IF slope tuning.** Allows independent adjustment of the low and/or high frequency slope of the IF passband, for best interference rejection. HIGH/LOW cut control rotation not affected by selecting USB or LSB modes.
- **CW VBT and pitch controls.** CW Variable Bandwidth Tuning control tunes out interfering signals. CW pitch controls shifts IF passband and simultaneously changes the pitch of the beat frequency. A "Narrow/Wide" filter selector switch is provided.
- **IF notch filter.** 100 kHz IF notch circuit gives deep, sharp, notch, better than -40 dB.
- **Audio filter built-in.** Tuneable, peak-type audio filter for CW.
- **AC power supply built-in.** 120, 220, or 240 VAC, switch selected (operates on AC only).
- **Fluorescent tube digital display.** Six digit readout to 100 Hz (10 Hz modifiable), plus digitalized sub-scale with 20-kHz steps. Separate two digit indication of RIT frequency shift. In CW mode, display indicates the actual carrier frequency of received as well as transmitted signals.
- **RF speech processor.** RF clipper type processor provides higher average "talk-power," improved intelligibility.
- **One year limited warranty on parts and labor.**

Other features:

- SSB monitor circuit, 3 step RF attenuator, VOX, and 100-kHz marker.

Optional accessories:

- AT-930 automatic antenna tuner.
- SP-930 external speaker with selectable audio filters.
- YG-455C-1 (500 Hz) or YG-455CN-1 (250 Hz) plug-in CW filters for 455-kHz IF.
- YK-88C-1 (500 Hz) CW plug-in filter for 8.83-MHz IF.
- YK-88A-1 (6 kHz) AM plug-in filter for 8.83-MHz IF.
- SO-1 commercial stability TCXO (temperature compensated crystal oscillator). Requires modifications.
- MC-60A deluxe desk microphone with UP/DOWN switch, pre-amplifier, 8-pin plug.
- TL-922A linear amplifier (not for CW QSK).
- SM-220 station monitor (not for pan-adapter).
- HS-6, HS-5, HS-4, headphones.

More information on the TS-930S is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.

KENWOOD

...pacesetter in amateur radio

Specifications and prices are subject to change without notice or obligation.

LOAD
PLATE
DRIVE
KENWOOD TS-830S
HF SSB TRANSCEIVER

TS-830S

"Top-notch"...VBT, notch, IF shift, wide dynamic range

The TS-830S has every conceivable operating feature built-in for 160-10 meters (including the three new bands). It combines a high dynamic range with variable bandwidth tuning (VBT), IF shift, and an IF notch filter, as well as very sharp filters in the 455-kHz second IF.

TS-830S FEATURES:

- LSB, USB, and CW on 160-10 meters, including the new 10, 18, and 24-MHz bands. Receives WWV on 10 MHz.
- Wide receiver dynamic range, Junction FETs in the balanced mixer, MOSFET RF amplifier at low level, and dual resonator for each band.
- Variable bandwidth tuning (VBT). Varies IF filter passband width.
- Notch filter high-Q active circuit in 455-kHz second IF.
- IF shift (passband tuning).
- Noise-blanker threshold level control.
- Built-in digital display, (fluorescent tube), with analog dial.
- 6146B final with RF negative feedback. Runs 220 W PEP (SSB)/180 W DC (CW) input on all bands.
- Built-in RF speech processor.
- Narrow/wide filter selection on CW.
- SSB monitor circuit.
- RIT and XIT (transmitter incremental tuning).

Optional accessories:

- SP-230 external speaker.
- VFO-230 external digital VFO with five memories, digital display.
- VFO-240 external analog VFO.
- AT-230 antenna tuner.
- YG-455C (500 Hz) or YG-455CN (250 Hz) CW filter for 455 kHz IF.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filter for 8.83 MHz IF.
- KB-1 deluxe heavyweight knob.

LOAD
PLATE
DRIVE
KENWOOD TS-530S
HF TRANSCEIVER

TS-530S

"Cents-ational"...IF shift, digital display, narrow-wide filter switch

The TS-530S SSB/CW transceiver covers 160-10 meters using the latest, most advanced circuit technology, yet at an affordable price.

TS-530S FEATURES:

- 160-10 meters, LSB, USB, CW, all amateur frequencies, including new 10, 18, and 24 MHz bands. Receives WWV on 10 MHz.
- IF shift tunes out interfering signals.
- Built-in digital display (six digits, fluorescent tubes), with analog dial.
- Narrow/wide filter selector switch for CW and/or SSB.
- Built-in speech processor, for increased talk power.
- Wide receiver dynamic range, with greater immunity to overload.
- Two 6146B's in final, allows 220W PEP/180 W DC input on all bands.
- Advanced single-conversion PLL, for better stability, improved spurious characteristics.
- Adjustable noise-blanker, with front panel threshold control.
- RIT/XIT front panel control allows independent fine-tuning of receive or transmit frequencies.

Optional accessories:

- SP-230 external speaker with selectable audio filters.
- VFO-240 remote analog VFO.
- VFO-230 remote digital VFO.
- AT-230 antenna tuner/SWR/ power meter.
- MC-50 desk microphone
- KB-1 deluxe VFO knob.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filter.
- YK-88SN (1.8 kHz) narrow SSB filter.

TS-660

The TS-660 "QUAD BANDER" covers 6, 10, 12, 15 meters.

- FM, SSB (USB), CW, and AM
- Dual digital VFO's
- Digital display
- IF shift built-in
- 5 memories with memory scan
- UP/DOWN microphone
- All-mode squelch
- Noise blanker
- CW semi break-in/sidetone
- 10 W on SSB, CW, FM; 4 W on AM.

Optional accessories:

- PS-20 power supply
- VOX-4 speech processor/VOX
- SP-120 External speaker
- MB-100 Mobile mount
- YK-88C, YK-88CN CW filters
- YK-88A AM filter.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut, Compton, California 90220

MODE
NARROW
WIDE
AM
USB
LSB
CW
15.195
COMMUNICATIONS RECEIVER
POWER
RF ATT
AF GAIN
TONE
BAND
KENWOOD
MODEL R-600

R-600

"Now hear this"...digital display, easy tuning

The R-600 is an affordably priced, high performance general coverage communications receiver covering 150 kHz to 30 MHz in 30 bands. Use of PLL synthesized circuitry provides maximum ease of operation.

R-600 FEATURES:
- 150 kHz to 30 MHz continuous coverage, AM, SSB, or CW.
- 30 bands, each 1 MHz wide, for easier tuning.
- Five digit frequency display, with 1 kHz resolution.
- 6 kHz IF filter for AM (wide), and 2.7 kHz filter for SSB, CW and AM (narrow).
- Up-conversion PLL circuit, for improved sensitivity, selectivity, and stability.
- Communications type noise blanker eliminates "pulse-type" noise.
- RF Attenuator allows 20 dB attenuation of strong signals.
- Tone control. • Front mounted speaker.
- "S" meter, with 1 to 5 SINPO "S" scale, plus standard scale.
- Coaxial and wire antenna terminals.
- 100, 120, 220, and 240 VAC, 50/60 Hz. Selector switch on rear panel.
- Optional 13.8 VDC operation, using DCK-1 cable kit.
- Other features include carrying handle, headphone jack, and record jack.

Optional accessories for R-600 and R-1000:
- DCK-1 DC Cable kit. • SP-100 External Speaker.
- HS-6, HS-5, HS-4 Headphones.
- HC-10 Digital World Clock.

R-1000

High performance, easy tuning, digital display

The R-1000 high performance communications receiver covers 200 kHz to 30 MHz in 30 bands. An up-conversion PLL synthesized circuit provides improved sensitivity, selectivity, and stability.

R-1000 FEATURES:
- Covers 200 kHz to 30 MHz.
- 30 bands, each 1 MHz wide.
- Five-digit frequency display with 1-kHz resolution and analog dial with precise gear dial mechanism.
- Built-in 12-hour quartz digital clock/timer.
- RF step attenuator.
- Three IF filters for optimum AM, SSB, CW.
- Effective noise blanker. • Tone control.
- Built-in 4-inch speaker. • Dimmer switch.
- Wire and coax antenna terminals.
- Voltage selector for 100, 120, 220, and 240 VAC. Operates on 13.8 VDC with optional DCK-1 kit.

14.215.0
KENWOOD
MODE
SEND
CW
SSB
REV
REC
PHONES
PROC
VOX
ALC
FIX
OFF
MAN
Ic
VFO
MIC
FIX
VFO
MIC CAR
AF GAIN RF GAIN
CAL ON
RIT IF SHIFT
BAND
POWER
RIT
NAR
RF ATT
NB
ON
OFF
WIDE

TS-130SE

"Small talk"...IF shift, Processor, N/W switch, affordable.

A compact, all solid-state HF SSB/CW transceiver for mobile or fixed base station, covering 3.5 to 29.7 MHz.

TS-130SE FEATURES:
- 80-10 meters including the new 10, 18, and 24 MHz bands. Receives WWV on 10 MHz.
- TS-130SE runs 200 W PEP/160 W DC input on 80-15 meters, 160 W PEP/140 W DC on 12 and 10 meters. TS-130V version at 25 W PEP/20 W DC, all bands, also available.
- Digital display, built-in.
- IF shift circuit.
- Speech Processor, built in.
- Narrow/wide filter selection on CW and SSB with optional filters.
- Automatic SSB mode selection (LSB on 40 meters and below, USB on 30 meters and up). SSB reverse switch provided.
- RF attenuator, built-in.
- Effective noise blanker.
- Final amplifier protection circuit assures maximum reliability. Output power is reduced if abnormal operating conditions occur. For very severe operations, optional cooling fan, FA-4, is available.
- Dimensions: 3-3/4 H x 9-1/2 W x 11-9/16 D (inches). Weight: 12.3 lbs.
- Other features: VOX, CW semi break-in with sidetone, one fixed channel, and 25 kHz marker.

Optional DFC-230 Digital Frequency Controller
Frequency control in 20-Hz steps with UP/DOWN microphone (supplied with DFC-230). Four memories and digital display. (Also operates with TS-120S, TS530S, and TS-830S.)

Optional accessories:
- PS-30 matching power supply (TS-130SE).
- KPS-21 power supply (TS-130SE).
- PS-20 power supply (TS-130V).
- SP-120 external speaker.
- VFO-120 remote VFO.
- FA-4 fan unit (TS-130SE).
- YK-88C (500 Hz) and YK-88CN (270 Hz) CW filters.
- YK-88SN (1.8 kHz) narrow SSB filter.
- AT-130 antenna tuner.
- MB-100 mobile mounting bracket.

KENWOOD
TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut, Compton, California 90220

TR-2500

The TR-2500 is a compact 2 meter FM handheld transceiver with every conceivable operating feature.

TR-2500 FEATURES:

- Weighs 540 g, (1.2 lbs). 66 (2-5/8) W x 168 (6-5/8) H x 40 (1-5/8) D, mm (inches).
- LCD digital frequency readout.
- Ten memories includes "MO" for non-standard split repeaters.
- Lithium battery memory back-up, built-in, (est. 5 year life).
- Memory scan.
- Programmable automatic band scan, and upper/lower scan limits; 5-kHz steps or larger.
- Repeater reverse operation.
- 2.5 W or 300 mW RF output. (HI/LOW power switch).
- Built-in tunable (with variable resistor) sub-tone encoder.
- Built-in 16-key autopatch encoder.
- Slide-lock battery pack.
- Keyboard frequency selection.
- Covers 143.900 to 148.995 MHz.

KENWOOD 2m FM TRANSCEIVER
TR-2500

CONVENIENT TOP CONTROLS

SQUELCH
POWER VOL

AC charger/supply for operation while charging.

- Battery status indicator.
- Complete with flexible antenna, 400 mAH Ni-Cd battery, and AC charger.

Optional accessories:

- ST-2 Base station power supply/charger (approx. 1 hr.)
- MS-1 13.8 VDC mobile stand/charger/power supply.
- VB-2530 2-M 25 W RF power amps., (TR-2500 only).
- TU-1 Programmable CTCSS encoder (TR-2500 only).
- TU-35B Programmable CTCSS encoder (mounts inside TR-3500 only).
- PB-25H Heavy-duty 490 mAH Ni-Cd battery pack.
- DC-25 13.8 VDC adapter.
- BT-1 Battery case for AA manganese/alkaline cells.
- SMC-25 Speaker microphone.
- LH-2 Deluxe leather case.
- BH-2A Belt hook.
- RA-3 2 m 3/8 λ telescoping antenna (for TR-2500).
- WS-1 Wrist strap.
- EP-1 Earphone.

TR-3500

70 CM FM Handheld

- Covers 440-449.995 MHz in 5-kHz steps.
- Hi-1.5 W, Low-300 mW.
- TX OFFSET switch, ±5 kHz to ±9.995 MHz programmable.
- Auto/manual squelch control.
- Tone switch for opt. TU-35B
- Other outstanding features similar to TR-2500.

TR-7950/7930

Big LCD, Big 45 W, Big 21 memories, Compact.

Outstanding features providing maximum ease of operation include a large, easy-to-read LCD display, 21 multi-function memories, a choice of 45 watts (TR-7950) or 25 watts (TR-7930), and the use of microprocessor technology throughout.

TR-7950/TR-7930 FEATURES:

- New, large, easy-to-read LCD digital display. Easy to read in direct sunlight or dark (backlighted). Displays TX/RX frequencies, memory channel, repeater offset, sub-tone number, scan, and memory scan lock-out.
- 21 new multi-function memory channels. Stores frequency, repeater offset, and optional sub-tone channels. Memory pairs for non-standard splits. "A" and "B" set band scan limits. Lighted memory selector knob. Audible "beep" indicates channel 1 position.
- Lithium battery memory back-up. (Est. 5 yr. life.)
- 45 watts or 25 watts output. HI/LOW power switch for reduction to 5 watts.
- Automatic offset. Pre-programmed for simplex or ±600 kHz offset, in accordance with the 2 meter band plan. "OS" key for manual change in offset.
- Programmable priority alert. May be programmed in any memory.
- Programmable memory scan lock-out. Skips selected memory channels during scan.
- Programmable band scan width.
- Center stop circuit for band scan, with indicator.
- Scan resume selectable. Selectable automatic time resume-scan, or carrier operated resume-scan.
- Scan start/stop from up/down microphone.
- Programmable three sub-tone channels with optional TU-79 unit (encoder).
- Built-in 16-key autopatch encoder, with monitor (Audible tones).
- Front panel keyboard control.
- Covers 142.000-148.995 MHz in 5-kHz steps.
- Repeater reverse switch. (Locking)
- "Beeper" amplified through speaker.
- Compact lightweight design.

Optional accessories:

- TU-79 three frequency tone unit.
- KPS-12 fixed-station power supply for TR-7950.
- KPS-7A fixed-station power supply for TR-7930.
- SP-40 compact mobile speaker.

KENWOOD 2m FM TRANSCEIVER
MEMORY
VOL SQL
TR-7950
1 2 3 OS
4 5 6 PS
7 8 9 LO
M 0 C SC
REV TONE HIGH SCAN ALERT OPER
LOW
PRIORITY
SELECT

NEW

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut, Compton, California 90220

KENWOOD 2m ALL MODE TRANSCEIVER
TR-9130

TR-9130

All mode (FM/SSB/CW) 25 watts, plus...!!!

The TR-9130 is a powerful, yet compact, 25 watt FM/USB/LSB/CW transceiver. Available with a 16-key autopatch UP/DOWN microphone (MC-46), or a basic UP/DOWN microphone.

TR-9130 FEATURES:

- 25 Watts RF output on all modes, (FM/SSB/CW).
- FM/USB/LSB/CW all mode. Selectable tuning steps of 100-Hz, 1-kHz, 5-kHz, 10-kHz.
- Six memories. On FM, memories 1-5 for simplex or ±600 kHz offset, using OFFSET switch, Memory 6 for non-standard offset. All six memories may be simplex, any mode.
- Memory scan.
- Internal battery memory back-up, using 9 V Ni-Cd battery, (not KENWOOD supplied). Memories are retained approx. 24 hours, adequate for the typical move from base to mobile. External back-up terminal on the rear.
- Automatic band scan.
- Dual digital VFO's.
- Transmit frequency tuning for OSCAR operations.
- Squelch circuit for FM/SSB/CW.
- Repeater reverse switch.
- Tone switch.
- CW semi break-in; sidetone.
- Compact size and lightweight.
- Covers 143.9 to 148.9999 MHz.
- High performance noise blanker.

TR-9500

70 CM SSB/CW/FM transceiver

- Covers 430-440 MHz, in steps of 100-Hz, 1-kHz, 5-kHz, 25-kHz or 1-MHz.
- CW-FM Hi—10 W, Low—1 W. SSB 10 W.
- Automatic band/memory scan. Search of selected 10-kHz segments on SSB/CW.
- 6 memory channels.
- HI/LOW power switch, 25 or 5 watts on FM or CW.
- RF gain control. • RIT circuit.

Optional accessories:

- KPS-7A AC power supply.
- PS-20 AC power supply (TR-9500 only).
- BO-9A system base with memory back-up supply.
- SP-120 external speaker.
- TK-1 AC adapter for memory back-up.

TR-7730

Dyna-"mite"... miniaturized, 5 memories, memory/band scan.

The TR-7730 is an incredibly compact, reasonably priced, 25 watt, 2 meter FM mobile transceiver, with five memories, memory scan, automatic band scan, plus other convenient operating features. It is available with a 16-key autopatch UP/DOWN microphone, (MC-46), or with a basic UP/DOWN microphone.

TR-7730 FEATURES:

- Dimensions: 5-3/4 W x 2 H x 7-3/4 D, inches. Weighs 3.3 lbs.
- Extended frequency coverage, 143.900-148.995 MHz, in 5 or 10-kHz steps.
- 25 watts RF output power, with HI/LOW power switch.
- Five memories. Simplex or repeater operation, with transmit offset switch. The 5th memory stores receive and transmit frequencies independently, for non-standard splits. Memory back-up terminal on rear panel.
- Memory scan, plus automatic band scan. Locks on busy channel, resumes when signals disappear, or when scan switch is pressed. Scan HOLD or PTT switch on microphone cancels scan.
- UP/DOWN manual scan on microphone, either version.
- Four digit LED frequency display.
- S/RF bar meter. LED indicators for BUSY, ON-AIR, REPEATER operation.
- Tone switch for internal tone encoder (not Kenwood supplied).
- Offset switch ±600 kHz, or simplex. Fifth memory for non-standard offset.

Optional Accessories:

- MC-46 16-key autopatch UP/DOWN microphone.
- SP-40 Compact mobile speaker.
- KPS-7A Fixed station power supply.

KENWOOD 2m FM TRANSCEIVER
TR-7730

TR-8400

Synthesized 70-cm FM mobile rig

- Covers 440-450 MHz, in 25-kHz steps, with two VFOs.
- Transmit offset switch for ±5 MHz. Non-standard offset uses fifth memory.
- HI/LOW power switch selects 10 or 1 watt RF output.
- Similar to TR-7730 in other features, including five memories, memory scan, automatic band scan, UP/DOWN manual scan, four digit display, S/RF bar meter, LED indicators, tone switch, and same optional accessories.
- Basic UP/DOWN microphone supplied with unit.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut, Compton, California 90220

TL-922A

Maximum legal power on 160-15 meters

The TL-922A linear amplifier provides maximum legal power on the 160-15 meter Amateur bands.

TL-922A FEATURES:

- 2000 W PEP (SSB)/1000 W DC (CW, RTTY) input power on 160, 80, 40, 20, and 15 meters, with 80 W drive.
- Excellent IMD characteristics.
- Pair of EIMAC 3-500Z high-performance transmitting tubes.
- Safety protection.
- Blower with automatic turnoff-delay circuit.
- Variable threshold level type ALC.
- Two meters, one indicating plate current, and the other indicating grid current, relative RF output, and high voltage.

SM-220

High-performance oscilloscope for various monitoring functions

The SM-220 Station Monitor provides a variety of waveform-observing capabilities, and an optional pan display.

SM-220 FEATURES:

- Monitors transmitted SSB and CW waveforms from 1.8 to 150 MHz.
- Monitors signal waveforms in receiver's IF stage.
- Functions as high-sensitivity, wide-frequency-range (up to 10 MHz) oscilloscope.
- Tests linearity of linear amplifiers (provides trapezoid pattern).
- Allows observation of RTTY tuning points (cross pattern).
- Built-in two-tone (1000-Hz and 1575-Hz) generator.
- Expandable to pan-display capability for observing the number and amplitude of stations within a switchable ±20 kHz/±100 kHz bandwidth.

Optional accessories:

- BS-8 pan-display module for TS-180S, TS-830S, and TS-820 Series.
- BS-5 pan-display module for TS-520 Series.

ACCESSORIES

A wide selection of optional accessories is offered for optimum operating flexibility. In addition to the optional items listed with each piece of equipment described in this catalog, the following accessories are also available:

(FCC Part 68 registered)

PC-1A Phone Patch

PC-1A Phone Patch with hybrid circuit and VU meter for null and audio gain measurements.

BO-9A System Base (for TR-9130, TR-9500, TR-9000).
With memory backup supply, speaker sound port, ST-BY switch, power switch, headphone jack.

VB-2530 25 W RF Power Amplifier (for TR-2500).
BNC-BNC cable, and mounting bracket supplied.

DM-81 Dip Meter

The DM-81 dip meter is highly accurate and features, in addition to the traditional inductive-coupling technique, capacitive coupling for measuring metal-enclosed coils and toroidal coils.

DM-81 FEATURES:

- Measuring 700 kHz-250 MHz in seven bands.
- Capacitance probe for measuring resonant frequencies without removing coil shields, and also for measuring resonant frequencies of toroidal coils.
- Built-in storage compartment for coils, and accessories.
- All solid-state and built-in battery.
- HC-25U and FT-243 sockets for checking crystals and marker-generator function.
- Amplitude modulation.
- FET for good sensitivity.
- Absorption frequency meter function.
- Earphone for monitoring transmitted signals.

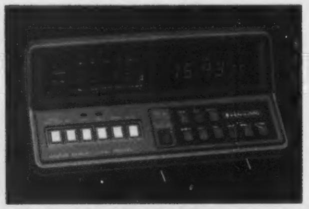

HC-10 Digital Quartz Clock

The HC-10 digital world quartz clock with dual 24-hour display shows local time and the time in 10 preprogrammed plus two programmable time zones.

MICROPHONES:

- **MC-60A** Deluxe desk microphone with UP/DOWN switch, pre-amplifier. 50 kΩ/500Ω, 8-pin. Adapter cords PG-4A (4-pin), PG-4B (6-pin), available. PG-4C, supplied with MC-60A.
- **MC-60N4** Deluxe desk microphone. 50 kΩ/500Ω, 4-pin. (UP/DOWN switch, pre-amp. (not included). PG-4C available.
- **MC-50** Desk microphone, 50 k/500Ω, 4-pin.
- **MC-46** 16-key autopatch UP/DOWN microphone, 6-pin.
- **MC-42S** Hand microphone with UP/DOWN switch, 500Ω, 8-pin.
- **MC-30S** Hand microphone, 500Ω, noise-cancelling, 4-pin.
- **MC-35S** Hand microphone, 50 kΩ, noise-cancelling, 4-pin.

Microphone Plug Adapters:

- MJ-48 (4-pin microphone to 8-pin transceiver).
- MJ-84 (8-pin microphone to 4-pin transceiver).
- MJ-86 (8-pin microphone to 6-pin transceiver).

HEADPHONES:

- **HS-5** Deluxe headphones.
- **HS-6** Lightweight headphones.
- **HS-4** Standard headphones.

GENERAL PURPOSE AC POWER SUPPLIES:

- **KPS-7A** 13.8 VDC, 7A intermittent.
- **KPS-12** 13.8 VDC, 12A intermittent.
- **KPS-21** 13.8 VDC, 21A intermittent.

OTHER ACCESSORIES:

- **SP-40** Compact external mobile speaker.
- **RD-20** Dummy load, 50Ω, DC-500 MHz, 50 W intermittent, 20 W continuous.
- **PG-3A** DC line noise filter for mobile.

SERVICE MANUALS:

- Available for most transceivers, receivers, and major accessories.

NOTE: Prices and specifications of all Trio-Kenwood products are subject to change without prior notice or obligation.

KENWOOD
TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut, Compton, California 90220

Cutting Current to Size

Measuring large ac currents can be difficult unless you know a trick or two. W7CRY explains how.

Larry T. Wier W7CRY
1068 149 Pl. SE
Bellevue WA 98007

Have you ever tried to measure large ac currents and found your trusty VOM somewhat short? Welcome to the club. I was stuck with the problem of finding the current used by an electric hot water heater but no way of measuring it. I also found my wallet short after letting my fingers walk through several instrument catalogs. Several hours of thrashing around the workbench yielded a simple and, best of all, inexpensive way of measuring large ac currents using an ordinary 88-mH choke, a trick or two, and Ohm's law.

Theory

Perhaps a little transformer theory should be covered before Ohm's law and the tricks are applied.

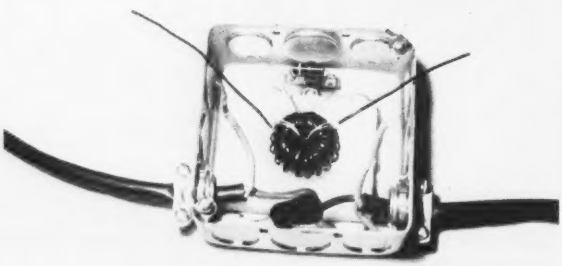

The almost-completed ac current transformer. The transformer is mounted on a piece of styrofoam™ which is glued to the box. Contact or rubber cement can be used for both the foam and transformer. The signal wires (not shown) can be routed out through any of the knockouts.

By definition, a transformer is exactly what its name implies: It transforms one voltage (or current) to a different level. The major differences between a voltage transformer and current transformer are the turns ratio and power-transfer characteristics. Depending on design, the voltage transformer has a low turns ratio, i.e., approximately 19 to 1 (118/6.3) for a filament transformer. The current transformer, on the other hand, has a turns ratio from around 300 to greater than 10,000 to 1, depending on the burden (load) on the secondary.

The current transformer always has the burden specified along with the current ratio. For example, a typical 50-Amp to 5-Amp current transformer will require a burden of .25 Ohms. If the secondary burden were to open or be removed, the transformer would be destroyed because the voltage developed across the resulting open circuit would cause arcing within the windings.

An additional consideration is that the current transformer should not introduce significant changes in the circuit being measured.

Hybrid Current Transformer Design

Fig. 1 shows the basic technique in utilizing the 88-mH choke as a current transformer. The term hybrid is used because in using the choke, a "halfway in-between" turns ratio will result. The approximate number of turns is determined by measuring the resistance of the coil, finding

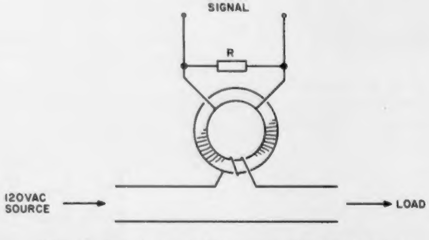

Fig. 1. Basic hybrid current transformer.

More Transceiver

Contest or rare DX – the world is waiting to hear from a new breed of HF operators who'll have the power of a microcomputer at their instant command. The Heath SS-9000 signals a new era in Amateur Radio, full of exciting promise. Challenge. And opportunity...

MORE WORLD HORIZONS

In the SS-9000, we met a major design goal: *provide the highest-tech, most versatile transceiver possible.* Our objective? Nothing less than setting the pace for transceiver performance in the next decade. And transforming the state-of-the-art in amateur telecommunications potential.

As a microprocessor-based, fully-synthesized nine band Transceiver, your SS-9000 leads the new revolution in computer-enhanced hamshacks – with an array of applications yet to be discovered. At your command under direct or RS-232 control, it could break all known records for station performance.

MORE MICRO CONTROL

Harness the SS-9000 to a video terminal, ASCII teletype or home computer. Commands are available to select, display and change all 27 operating and memory frequencies, assign and toggle T/R/Tr status on the dual readout, and freely manipulate the three stored frequencies on each band, with full diagnostic error-prompting.

Keyboard command also allows you to set and switch the band, mode, passband shift, baud and scan rates, plus switch to one of five antennas *automatically.*

MORE POWER AS A PAIR

The PS-9000 AC Power Supply has an in-cabinet speaker and two digital 12 or 24-hour clocks. Both units benefit from thermal and over-current protection with high VSWR cutback. Test-prove the assembled System 9000. Get a hands-on tryout at your nearby Heathkit Electronic Center.*

MORE DETAILS IN CATALOG

Heathkit
AM-429

FREE! For complete details and specs, get a copy of the latest Heathkit catalog. **Write:** Heath Company, Dept. 011-964, Benton Harbor, MI 49022.

There's more for the Ham at Heath

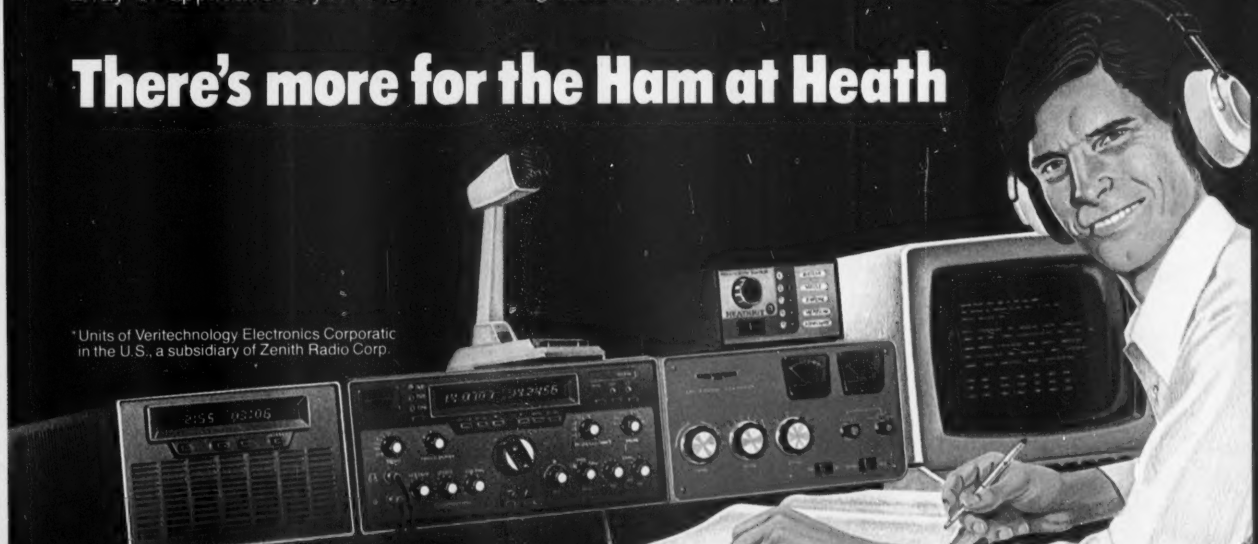

*Units of Veritechnology Electronics Corporatic in the U.S., a subsidiary of Zenith Radio Corp.

Heathkit
Heath
Company

the wire size, and, from a wire table, finding the resistance per foot. By taking the average diameter of the donut and average cross section, a rough turns count can be calculated.

For those not willing to take the time to play with the math, a quick test can be found in the calibration section. If the ratio is found to be in excess of about 300, the choke is a good candidate.

Apparently, there are several so-called surplus 88-mH-type chokes. I found some with and some without center tap. I have also found some with two separate windings. These can be used if the windings are connected in series adding. Even though the choke defined here was intended for the audio frequencies, it works well at 60 Hz if the power levels are kept low.

Construction

The only construction required is covering the existing windings with tape. Once the value of R is determined, it can be soldered to the windings and taped to the body of the coil or mounted as shown in Fig. 3. The signal wires are attached across the resistor and routed where necessary. Wire length is not critical, but wires should be routed away from high-noise areas.

Calibration

Fig. 2 shows the test setup used to calibrate the current transformer. It is not necessary to use the 120-volt, 60-Hz line to do the calibration. As shown, a low-voltage, high-current voltage transformer with an adjustable input is the quickest and safest.

For calibration purposes, R can be a quality pot. The 100-Ohm resistor is used to prevent shorting the transformer, but is part of the burden. The source and load will depend on what is available. Use the following steps to calibrate the transformer:

1) Make sure that there are ten complete turns of #18 insulated wire wound as shown in Fig. 2.

2) Adjust the load for 10.0 Ohms.

3) Adjust the voltage to the load for 10.0 V ac.

4) Adjust R (1k pot) for an even value of voltage—preferably 0.1 V ac. Remove power.

(If 0.1 volt was not obtainable, replace R with a 2k pot. If the measured voltage was higher than 0.1 V ac, set the value to any even value above 0.1 V, e.g., 0.3 V ac.

(The current ratio is calculated as follows: I = E/R, where E was set to 10.0 V ac and R was set to 10.0 Ohms. Therefore, I = 10 V/10Ω = 1 Amp.

(Then 1 Amp through 10 turns equals 10 Amp/turns which is also equal to 10 Amps with 1 turn through the transformer. With one turn in the primary and the measured value across R of 0.1 V ac, the ratio becomes 10 to 0.1. By Ohm's law, E is equal to I times R, and if R is held constant, then E must be proportional to I.

(What this boils down to is that the current through the transformer will generate a proportional voltage across R as long as R stays constant. If the ratio has been set correctly, adjusting the load to 1.0 Ohms and again adjusting the voltage across the load to 10.0 V ac, a value of 1 V ac should be measured across R.)

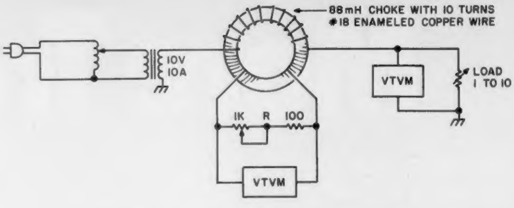

Fig. 2. Calibration test setup.

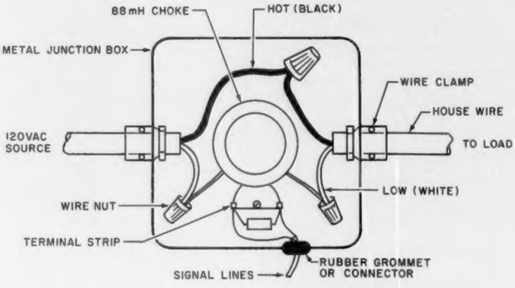

Fig. 3. Mounting fixture.

5) Determine the wattage for R by measuring the value of R and calculating as follows: $P_{Watts} = E^2/R$. Generally, a ½-Watt resistor will be more than sufficient. Replace the pot and 100-Ohm resistor with a fixed value equal to the combination of the two in series.

Application

Obviously, this combination can be used with any current range. It is limited only by the size of wire capable of being wound (1 turn) through the donut. Note that at least one turn is necessary to excite the transformer core. Passing the wire through the hole is not sufficient. Practically speaking, a #5 (solid enameled) wire is about the maximum-size wire which can be formed into one turn around the donut. This limits the upper current range to around 50 Amps.

The number of turns wound on the current transformer will depend on the current range to be measured and wire size. As an example, suppose a motor rated at 15 Amps (running) is to be monitored. We know from our calibration that 10 Amps gave us 0.1 V ac across R. Therefore, one turn of #12 wire through the donut should give us 0.15 V ac across R. The #12 was chosen because it is the smallest size generally used for motors in this range.

Another example is the case where only 1 Amp is to be measured. In this case, the wire size (assumed to be #14) is too large to pass a large number of turns through the donut. If you can assume also that nothing larger than approximately 5 Amps will be

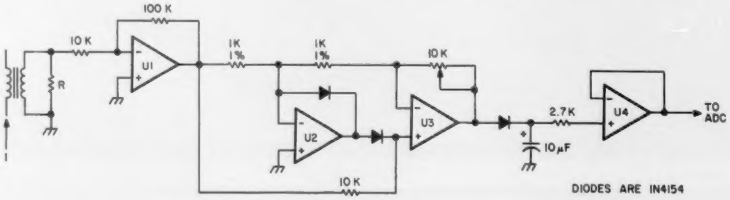

Fig. 4. Precision rectifier/buffer.

The ultimate team... the new Drake "Twins"

The TR7A and R7A offer performance and versatility for those who demand the ultimate!

TR7A Transceiver

- **CONTINUOUS FREQUENCY COVERAGE** — 1.5 to 30 MHz full receive coverage. The optional AUX7 provides 0 to 1.5 MHz receive plus transmit coverage of 1.8 to 30 MHz, for future Amateur bands, MARS, Embassy, Government or Commercial frequencies (proper authorization required).
- **Full Passband Tuning (PBT)** enhances use of high rejection 8-pole crystal filters.

New! **Both 2.3 kHz ssb and 500 Hz cw crystal filters, and 9 kHz a-m selectivity are standard,** plus provisions for two additional filters. These 8-pole crystal filters in conjunction with careful mechanical/electrical design result in realizable ultimate rejection in excess of 100 dB.

New! **The very effective NB7 Noise Blanker is now standard.**

New! **Built in lightning protection** avoids damage to solid-state components from lightning induced transients.

New! **Mic audio available** on rear panel to facilitate phone patch connection.

- **State-of-the-art design** combining solid-state PA, up-conversion, high-level double balanced 1st mixer and frequency synthesis provided a no tune-up, broadband, high dynamic range transceiver.

R7A Receiver

- **CONTINUOUS NO COMPROMISE 0 to 30 MHz frequency coverage.**
- **Full passband tuning (PBT).**

New! **NB7A Noise Blanker supplied as standard.**

- **State-of-the-Art features** of the TR7A, plus added flexibility with a low noise 10 dB rf amplifier.

New! **Standard ultimate selectivity choices** include the supplied 2.3 kHz ssb and 500 Hz cw crystal filters, and 9 kHz a-m selectivity. Capability for three accessory crystal filters plus the two supplied, including 300 Hz, 1.8 kHz, 4 kHz, and 6 kHz. The 4 kHz filter, when used with the R7A's Synchro-Phase a-m detector, provides a-m reception with greater frequency response within a narrower bandwidth than conventional a-m detection, and sideband selection to minimize interference potential.

- **Front panel pushbutton control** of rf preamp, a-m/ssb detector, speaker ON/OFF switch, i-f notch filter, reference-derived calibrator signal, three agc release times (plus AGC OFF), integral 150 MHz frequency counter/digital readout for external use, and Receiver Incremental Tuning (RIT).

The "Twins" System

- **FREQUENCY FLEXIBILITY.** The TR7A/R7A combination offers the operator, particularly the DX'er or Contester, frequency control agility not available in any other system. The "Twins" offer the only system capable of no-compromise DSR (Dual Simultaneous Receive). Most transceivers allow some external receiver control, but the "Twins" provide instant transfer of transmit frequency control to the R7A VFO. The operator can listen to either or both receiver's audio, and instantly determine his transmitting frequency by appropriate use of the TR7A's RCT control (Receiver Controlled Transmit). DSR is implemented by mixing the two audio signals in the R7A
- **ALTERNATE ANTENNA CAPABILITY.** The R7A's Antenna Power Splitter enhances the DSR feature by allowing the use of an additional antenna (ALTERNATE) besides the MAIN antenna connected to the TR7A (the transmitting antenna). All possible splits between the two antennas and the two system receivers are possible.

Specifications, availability and prices subject to change without notice or obligation.

DRAKE

See your Drake dealer or write for additional information.

COMING SOON: **New RV75 Synthesized VFO Compatible with TR5 and 7-Line Xcvrs/Rcvrs**

- **Frequency Synthesized** for crystal-controlled stability • **VRTO (Variable Rate Tuning Oscillator*)** adjusts tuning rate as function of tuning speed. • **Resolution to 10 Hz** • **Three programmable fixed frequencies** for MARS, etc. • **Split or Transceive** operation with main transceiver PTO or RV75

R. L. DRAKE COMPANY • 540 Richard Street, Miamisburg, Ohio 45342 • Phone (513) 866-2421 • Telex 288-017

* Patent pending

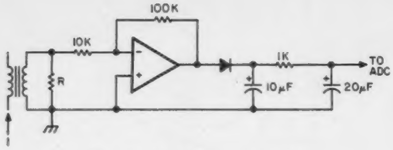

Fig. 5. Half-wave rectifier.

passed through the donut, then ten turns of #18 (solid enameled) will generate 0.1 V ac across R. In most cases, the number of turns will be determined by the measurement requirements.

Installation

According to most electrical codes, any splices of power lines must be located in a box. An outlet or junction box will work equally well. The transformer should not touch the metal box, and make sure that only the circuit being measured is in the box. It is best to use the low side (white wire) because the voltage between the low side and ground will not exceed the voltage rating of the enameled wire.

When measuring a 220-V ac line it will be necessary to use either of the two hot (red or blue) lines. In this case, the donut should have at least one layer of electrical (plastic) tape between the two sets of windings. Fig. 3 shows one method of mounting the donut and resistor R. Any method which meets your local code requirements will work.

Use

Now that you have a current transformer, how can it be used? The answer to that depends on why it was built. The easiest use of the current transformer is with an ac voltmeter. In my case, it is being used in a computer-controlled power system. Since a computer does not know ac from dc (or much else), the ac signal across R must be signal conditioned. There are many ways to signal-condition, but the method I chose was determined by the analog-to-digital converter (ADC) used with my computer. It has ±15 V dc available, so that the use of operational amplifiers seemed to be the best solution.

Fig. 4 is an example of how the ac signal is conditioned from ac to dc for the ADC. It is beyond the scope of this article to dissect the operation of Fig. 4 except to note that U2 and U3 form an absolute value (precision-rectifier) circuit. U1 is an inverting amplifier and U4 is used as a unity-gain buffer. U1 and U4 are in one LM747 and U2 and U3 are in another. Any general-purpose operational amplifier will work. (More information on this particular absolute-value circuit may be found in the November 8, 1979, issue of *Electronic Design*, page 94.)

A simple amplifier and diode arrangement also will work if accuracy and response time are unimportant. Fig. 5 is the method used in this case.

Summary

No matter what the requirement, a simple arrangement such as described here will provide a reasonably accurate measurement of ac line current. Sources of 88-mH chokes are found in the back of most electronic magazines and cost around $3.00.

Now I need to look into a method of measuring the gas pressures in my heat pump! ■

ASSOCIATED RADIO **913-381-5900**
8012 CONSER BOX 4327
OVERLAND PARK, KANSAS 66204

BUY—SELL—TRADE

All Brands New & Reconditioned

YOU WANT A DEAL — WE WANT TO DEAL
CALL NOW!!!

MasterCard **SAVE—SAVE—SAVE** VISA®

NOTE: SEND $1.00 FOR OUR CURRENT CATALOG OF NEW AND RECONDITIONED EQUIPMENT
SEND $1.00 FOR OUR WHOLESALE LIST OF UNSERVICED & OVERSTOCK ITEMS.
SEND $2.00 FOR BOTH. THEY WILL BE MAILED SEPARATELY.

COM-SPEC
IC-107
SEND
BATTERY
VOL
SQL
ON
MHz
10kHz
PWR

At Last.

A microthin, synthesized, programmable, sub-audible tone encoder that fits inside the ICOM IC-2AT.

Need we say more?

$29.95

COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, CA 92667
800/854-0547 California: 714/998-3021

VISA

Santa's Gone Soft!

Today is DEC. 25th
J. GRAVES '82

With Help From Instant Software

BUSINESS AND APPLICATIONS

0222RD	Electronic Breadboard 32K, Mod I & III, disk	$59.95
0228R	Electronic Breadboard 16K, Mod I & III, tape	$49.95
0428AD	Electronic Breadboard 32K, Apple, disk	$59.95
0369RD3	Easy Calc 48K, Mod III only, disk	$49.95
0269RD	Easy Calc 48K, Mod I only, disk	$49.95
0103R	Personal Bill Paying 16K, Mod I & III, tape	$14.95
5005RD	Master Directory 32K, Mod I only, disk	$29.95
0152RD	Business Analysis 32K, Mod I & III, disk	$99.95
0140R	Business Analysis 32K, Mod I & III, tape	$75.00
0380RD	Scriptr 48K, Mod I only, Disk	$34.95

EDUCATION

0099R	Typing Teacher 16K, Mod I & III, tape	$17.95
0100R	Video Speed Reading 16K, Mod I & III, tape	$14.95
0309R	Triangle Trig 16K, Mod I & III, tape	$19.95
0071RD	Geography Explorer: USA 32K, Mod I & III, disk	$49.95
0276RD	Geography Explorer: Mid East, 32K, Mod I & III, disk	$49.95
0111R	Word Watch 16K, Mod I & III, tape	$14.95
0257R	Math Master 16K, Mod I & III, tape	$17.95
0127R	Surveyors Apprentice 16K, Mod I & III, tape	$14.95

GAMES

0332R	Space Shuttle 16K, Mod I & III, tape	$19.95
0017R	Air Flight Simulation 16K, Mod I & III, tape	$14.95
0148A	Air Flight Simulation 16K, Apple, tape	$14.95
0159R	Jet Fighter Pilot 16K, Mod I & III, tape	$14.95
0329AD	Jet Fighter Pilot 32K, Apple, disk	$24.95
0223R	Cosmic Patrol 16K, Mod I & III, tape	$19.95
0224RD	Cosmic Patrol 16K, Mod I & III, disk	$24.95
0237R	Danger in Orbit 16K, Mod I & III, tape	$19.95
0247RD	Danger in Orbit 16K, Mod I & III, disk	$24.95
0051R	Ball Turret Gunner 16K, Mod I & III, tape	$14.95
0240R	Alien Attack Force 16K, Mod I & III, tape	$14.95
0171R	Flight Path 16K, Mod I & III, tape	$14.95
0043R	Santa Paravia 16K, Mod I & III, tape	$14.95
0229AD	Santa Paravia 48K, Apple, disk	$24.95
0273TI	Santa Paravia 16K, TI 99/4, tape	$14.95
0174A	Santa Paravia 48K, Apple tape	$14.95
0312R	Swamp War 16K, Mod I & III, tape	$14.95
0141R	Battleground 16K, Mod I & III, tape	$14.95
0378RD	Master Reversi 16K, Mod I only, disk	$24.95
0117R	Night Flight 16K, Mod I & III, tape	$14.95
0183A	Skybombers III 32K, Apple, tape	$14.95
0271AD	Skybombers II 32K, Apple, disk	$24.95
5020RC	Tower of Fear 16K, Color Computer, tape	$19.95
0084R	Music Master 4K, Mod I & III, tape	$14.95
0106R	Air Mail Pilot 16K, Mod I & III, tape	$14.95
0205RD	Flying Circus 32K, Mod I only, disk	$39.95
0163AD	Paddle Fun 32K, Apple, disk	$19.95
0219R	House of 30 Gables 16K, Mod I & III, tape	$14.95
0325RD	Mission: Mud 32K, Mod I & III, disk	$19.95
0387RD	Sparrow Commander 32K, Mod I & III, disk	$19.95
0386RD	Kitchen Sink 32K, Mod I & III, disk	$19.95
0161AD	Apple Fun 32K, Apple, disk	$19.95

UTILITIES

0230R	TLDIS 16K, Mod I & III, tape	$19.95
0231RD	DLDIS 32K, Mod I only, disk	$24.95
5700RD	Super>>Terminal 32K, Mod I & III, disk	$95.00
5003R	Ultra-Mon 16K, Mod I & III, tape	$24.95
0232R	The Disassembler 16K, Mod I & III, tape	$14.95
0245R	Programmer's Primer 16K, Mod I & III, tape	$14.95
0139RD	Disk Scope 32K, Mod I only, disk	$24.95
0184R	TRS-80 Tests 16K, Mod I only, tape	$14.95

TO ORDER:

See your local Instant Software dealer or call toll-free 1-800-258-5473 Dept. A-65 In New Hampshire 1-603-924-9471 Dept. A-65

Mon.-Fri. 8:00 am-4:30 pm E.S.T.

Include $2.50 for Shipping & Handling

***TRS-80 is a trademark of Radio Shack a division of Tandy Corporation**
****APPLE is a trademark of Apple Computer Inc.**

Instant Software™

Peterborough, N.H. 03458 USA
A subsidiary of Wayne Green Inc.

PRICES SUBJECT TO CHANGE

Westland Electronics
INCORPORATED

Microprocessor & Interface

1771	24.50	6845	12.95	DAC-0800	3.99
1791	34.95	6850	4.49	INS8250	14.90
21L02	1.49	8085A	8.95	MM58167	12.75
2112	1.65	8212	2.75	TMS9900	29.95
2516	4.75	8214	3.95	TR1602B	2.49
2532	7.95	8216	2.75	SC-01	55.00
2651	12.95	8224	3.29	Z80A-CPU	7.95
4044L-2	2.49	8226	2.79	Z80ACTC	7.49
6502	8.99	8228	4.49	Z80ADart	19.95
6800	6.99	8251	6.95	Z80APIO	7.49
6802	11.95	8255	6.49	Z80ASIO	17.95
6809	19.95	AY5-1013A	4.95	Z8603	74.95
6821	4.95	AY5-2376	12.39	Z8671	29.95

1 Amp TO-220 Voltage Regulators

PART #	1-24	25-99	100-499
7805 (LM340T-5)	.85	.75	.65
7812 (LM340T-12)	.85	.75	.65
7815 (LM340T-15)	.85	.75	.65
7818 (LM340T-18)	.85	.75	.65

Linear Integrated Circuits

8038	3.95	LM393	.97	MC3302	.90
LF351	.75	LM733	99	MC1458	.59
LF353	1.29	LM741-8	35	MC1514	1.39
LF357	1.39	LM741-14	.35	NE555	.45
LM301	45	LM747	.77	NE556	.98
LM307	49	LM748	.49	NE565	1.25
LM311	95	LM1310	1.69	NE5534	1.99
LM318	1.75	LM1458	.69	NE5538	2.25
LM324	90	LM1800	2.49	SSM2010	7.50
LM339	79	LM1818	3.49	SSM2020	7.50
LM358	90	LM1889	2.99	SSM2030	7.50
LM377	2.49	LM2900	.69	SSM2040	7.50
LM380N-14	1.25	LM3900	.89	SSM2044	5.75
LM381	1.89	LM3905	1.49	SSM2055	6.50
LM383	3.29	LM3914	3.79	XR2206	5.19
LM384	1.95	LM3915	3.79	XR4136	.99
LM386	99	LM3916	3.79	XR4741	1.95
LM387	1.49	LM4500	3.29	XR558	1.99

5% Carbon Film Resistors

We stock all 5% standard values between 1 Ohm and 1 Meg Ohm.

¼ Watt

Package of 5	.20
Package of 100 (one value)	1.50
Package of 1000 (one value)	9.75

½ Watt

Package of 5	.25
Package of 100 (one value)	1.75
Package of 1000 (one value)	15.00

Sampler box consisting of 5 each of all 169 standard 5% values between 1 Ohm and 10 Meg Ohm (845 pieces total).

¼ Watt Sampler Box	25.00
½ Watt Sampler Box	28.00

We Also Stock ⅛ Watt Resistors

1% ¼ Watt Metal Film Resistors

We now stock all 481 Standard EIA values between 10 Ohms and 1 Meg Ohm.

Package of 5	.45
Package of 100 (one value)	5.50
Box of 1000 (one value)	28.00

Send for our full line catalog of IC's, Resistors, Capacitors, Diodes, Regulators, Crystals, Trim Pots, Switches, Sockets, Connectors, RF Chokes, and more.

Minimum Order $10.00

Shipping

10-24.99	3.00	Above 50.00	FREE
25-49.99	1.50	C.O.D.	Add 1.50

WESTLAND ELECTRONICS
37387 Ford Rd. • Westland, MI 48185
Order Line – 1-800-521-0664
In Michigan – 313-728-0650 ✓154

DISPLAY YOUR STUFF

With the AEA MBA-RO Reader

Automatic display of transmitted and received Morse and RTTY coded signals has come of age. It is proving to be most worthwhile for improving one's own transmitted "fist" and for allowing SWL's or visitors the opportunity to experience the thrill of Amateur Radio coded transmission.

While no machine can yet match the ability of a skilled CW operator in copying poor fists or signals buried in the noise, the MBA-RO by AEA excels even when compared against units costing much more. The large 32 character display allows much easier reading than shorter displays, especially at higher speeds such as 60 WPM or 100 WPM RTTY. The MBA-RO also features dual filters for RTTY decoding of either 170 Hz or 425 Hz (easily changed to 850 Hz) shift transmissions.

For more details, write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation.
Software ©copyright by AEA.

ADVANCED ELECTRONIC APPLICATIONS, INC. ✓2
P.O. Box C-2160,
Lynnwood, WA 98036
(206) 775-7373
Telex: 152571 AEA INTL

AEA Brings you the Breakthrough!

Attention radio amateurs!

8-LEVEL ASCII TELEPRINTER SALE!

Model 33ASR SF
Good Working Condition

~~$400~~
Now
$300!
plus tax and shipping.

Code: ASCII
Speed: 10 cps, 100 baud.
Interface: 20/60 mA,
EIA optional
Data Set Optional
From RCA Service Company.
Nationwide Service Available.

RCA

K-248

Write:
J. H. Bell
RCA Service Company
Bldg. 204-2, Route #38
Cherry Hill, New Jersey 08358
Or call collect the RCA Data Services Region Office in your area:

New York	212-267-1550
Philadelphia	609-234-8900
Atlanta	404-934-9333
Dallas	817-640-0900
Chicago	312-595-4910
Los Angeles	213-728-7473

Alexander MacLean
WA2SUT/NNN0ZVB
18 Indian Spring Trail
Denville NJ 07834

Construct This All-American Audio Signal Generator

The perfect project for starting a test bench or rounding one out.

It is still possible for the average builder to design and make equipment that is competitive in cost and effectiveness with that which is store-bought. Many simple, standard design concepts can be applied to modern technology.

The Circuit

This FET audio signal generator is an easy project derived from the audio oscillator circuit presented in "Working with FETs—part 1," in *73* in November, 1979. There are some simple additions in the finished circuit which make it far more useful than just the basic circuit (see Fig. 1).

I could have used a switch and a selection of fixed values, but it would have cost more and built in a fixed limit. The easy way out was to put the frequency-determining capacitor outboard so that it can be changed quickly. You can use a substitution box or your junk-box selection with ease, but most of the time you can just leave the fixed value in place. I have rarely needed more than the one tone for testing.

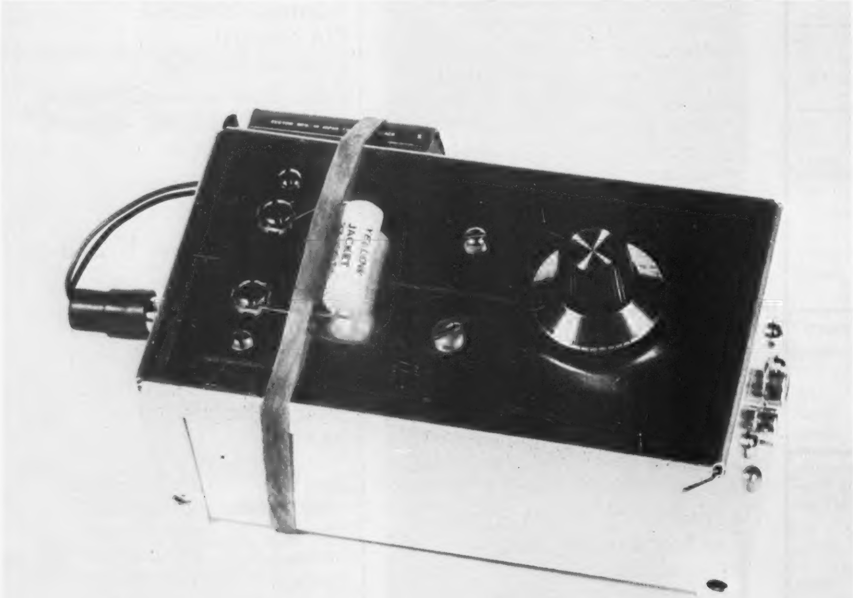
Top view of FET audio signal generator.

Potentiometer R2 gives you an adjustable output level. This is very handy for testing or troubleshooting. Resistors R3 and R4 form an output attenuator network that gives you a low-level adjustable output. This is useful when working with high-gain circuits. Using an attenuator network gives you a cleaner low-level signal than trying to use a high-level signal at the lowest setting.

A 9-volt transistor radio battery or a power supply can be plugged in at J3. This way you can change quickly between battery and fixed supply, or use your battery or supply with other equipment. It's handy. The low power drain, about 2.2 mA, makes this a really practical project for battery and portable operation.

There are only a few parts values that are at all critical. The design center was for 10% tolerance and in most cases it is much wider. Except in one important case, the voltage rating is anything reasonable over 20 WV dc.

L1 is an 88-mH unpotted toroid. It is a common surplus item, but you may have to look around. They are often used for filters in RTTY equipment.

C1 in combination with L1

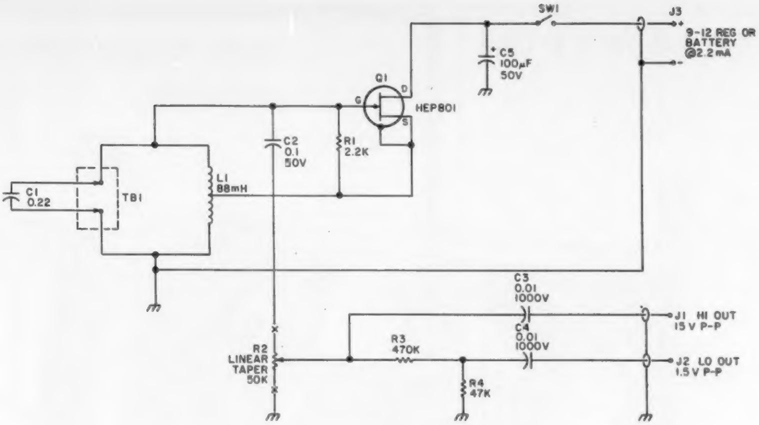

Fig. 1.

is what actually sets the audio tone. My substitution box gave usable tones from 0.22 uF up, but the highest tones were out of the comfortable audio range. I think that 0.1 uF to 0.22 uF would be a good starting point. Get out the junk box and play around.

R1 limits the voltage swing of the output waveform at the gate of Q1. If it were not there, under some conditions the signal might be large enough to damage the transistor. The value is not critical; 3.3k or more will do, but have something there for protection.

Q1 is a Motorola HEP-801, a commonly available audio FET. It has four pins, the fourth being a connection to the outer case. When I made the prototype circuit, the matrix board automatically connected the case to the source pin. It worked well that way so I left it in the finished circuit.

Drain bypass capacitor C5 is not critical. Anything from 20 to 100 uF at 20 volts or more should do. The circuit worked well without it, but it might be needed to keep any noise from getting in from your supply. Keep in mind that to further decouple the circuit you can also add a 2.2k or so resistor in series with the drain line if you have a stubborn noise problem. The greater the capacitance of output coupling capacitor C2, the better the low frequency response. I used a 0.1-uF 50-V-dc disc ceramic that was on hand.

Output level control R2 is a 50k linear-taper potentiometer. A linear taper is used because it is a voltage divider application, not a true volume control. Mine has an ac switch (SW1) right on the back, but you can use a separate switch.

R3 (470k) and R4 (47k) form the attenuator network. The textbook values would be different, but since I aimed for a wide 10% tolerance, it worked out well. The measured output is very close to a 10:1 ratio. My resistors happen to be 5% values as they were available in the store. Output coupling capacitors C3 and C4 have the only critical ratings: Both are 0.01 uF at 1000 volts disc ceramics.

The voltage rating is critical. They block any dc voltage in the test circuit (such as a tube-type amplifier) from getting back into the generator and frying all the little parts. Use at least 500-volt capacitors, preferably higher. You should not be using equipment like this in really high-voltage circuits. It's unhealthy. But a good safety margin will keep you going when you work with most tube-type equipment.

These two capacitors also will determine the frequency response of your generator and it's hard to find high capacitance at high working voltage. This means that your lowest audio tones will have less output voltage than mid or high tones.

I should stress that the low-frequency loss comes from the coupling capacitors in the circuit, not the oscillator, which will provide far flatter output across the audio spectrum.

Construction

Construction is easy. There are only a few mechanical problems to watch for. The photos show the parts layout and there are a few tricks to make it easier.

I used cardboard at the top and bottom of toroid L1 and a short length of insulation over the screw where it went through the toroid to prevent any shorting.

There is one potential trouble area. Clean the enamel off the magnet wire ends of the toroid very carefully. I mean really get in there with a sharp penknife and *scrape it off*. I was sloppy the first time. It looked good but it didn't work. It took me a while to find the problem. Check for a good clean contact with your ohmmeter. It doesn't matter which end is grounded when you install it, but when you make the center-tap, look for the two ends that are closest together.

Use a good quality transistor socket. The cheap one I tried at first fell apart. I soldered the leads to the socket first and then wired it to the terminal strip. I was going to tack it down with silicone sealer, but the wire was stiff enough that it didn't wander.

RCA jacks were used throughout. They are not the last word in connectors, but they are cheap and easy to get.

There are many styles of enclosure available; it just has to all fit. I did not try

Parts List

C1—0.22-uF, 20-volt or greater
C2—0.1-uF, 50-volt disc ceramic
C3,C4—0.01-uF, 1000-volt disc ceramic (voltage rating critical)
C5—100-uF, 50-volt electrolytic
J1, J2, J3—RCA jacks
L1—88-mH toroid
R1—2.2k, ½-Watt 5 or 10%
R2—50k, linear-taper pot. (Radio Shack 271-1716)
R3—470k, ½-Watt 5 or 10%
R4—47k, ½-Watt 5 or 10%
SW1—ac switch, part of R2 (Radio Shack 271-1740)
Q1—Motorola HEP-801 n-channel FET

Miscellaneous

Minibox—5-1/4" × 3" × 2-1/8" (Radio Shack 270-238)
Knob—Radio Shack 274-413
TB1—2-screw terminal strip
Solder terminal strip (see photo)
Transistor socket
Mounting hardware

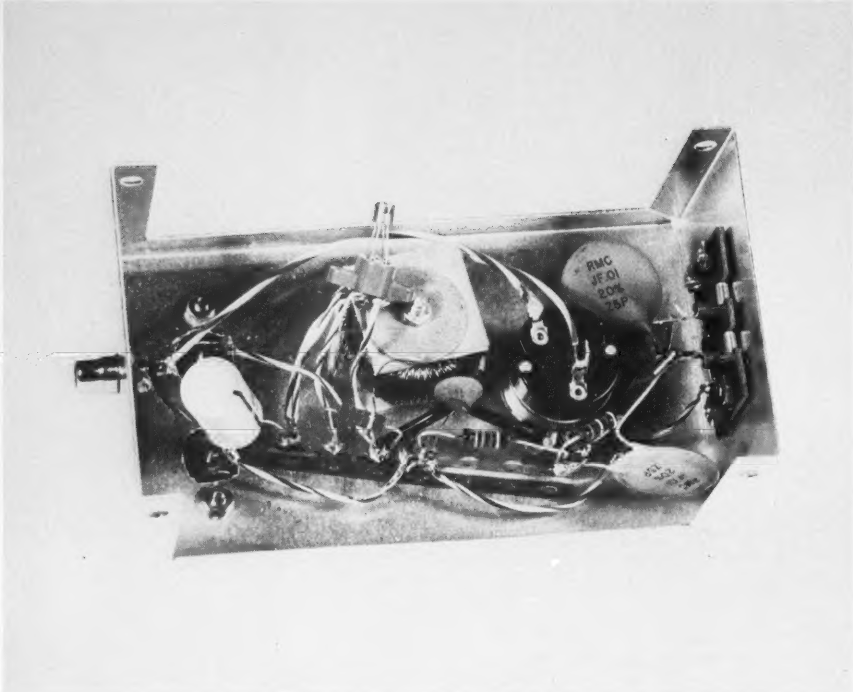

Bottom view.

to miniaturize. It's small enough now to be handy but large enough to service easily. Notice that the leads are not as short as they could possibly be. It's neat, but there is room and length to work with.

The only part that might be a problem to buy is the toroid. They are still common mail-order items if you check the RTTY supply houses. Get a few; they're useful. Almost any of the other parts are common enough that you may be able to use some of them to make up a minimum order requirement.

I spent a little under $9 to build the signal generator. I had the toroid, transistor, and some of the small parts, but I bought the rest new to get the prices. I would estimate that it can be built for about $12 if you are careful, and within $15 without too much trouble.

Testing

When you have it put together, check for wiring errors and shorts. Put your milliammeter in the power lead and check the current as you turn it on. Don't forget to put some capacitance value at TB1 (C1) so there will be a complete LC circuit.

Use your scope or high-impedance headphones to check for a tone. If it works, use your scope or VTVM to measure the output voltage at both output jacks as it may vary between units. Don't try to use a VOM on the low-level output. It will load it down to almost nothing. Check for proper operation of the level control and the on-off switch. If you get past all that, you are in business.

The first time I tried mine it didn't work and I designed it! Here are the most likely troubles to look for:

1) Transistor inserted incorrectly in the socket, or you have the wrong pin configuration to the circuit.

2) Weak or dead battery. Check yours under load with meter.

3) Wiring error. Recheck schematic.

4) Coil doesn't make connection with rest of circuit. Unsolder and clean again. Ohmmeter might help here.

The signal should be at the gate of the FET. Lifting one lead of C2 will isolate the output circuit. If there is still no signal at the gate, then the trouble is in the oscillator circuit itself.

Performance

I checked the performance of mine with my usual assortment of ancient and out-of-tolerance test gear and got the following.

The output voltage varies only slightly over the supply-voltage range of 9 to 20 volts. This is a fringe benefit of R1. It holds the output voltage constant over a wide range of supply voltages.

The output drops off slightly with a supply voltage between 9 and 5 volts. At the design center of 9 to 12 volts, the drain current is about 2.2 mA.

The output voltage at the HI output jack (J1) is 15 volts peak-to-peak on the scope. At the LO jack (J2), it is 1.5 volts p-p. Pretty good for a rough and ready attenuator network.

The calculated rms voltage by formula was not what one meter showed. The VOM indicated 4.2 volts rms. The LO range was loaded down too much by the meter. The output across the "output" jack was about +15 dBm—enough for many purposes.

The minimum signal voltage available is about 0.01 volt p-p on the scope. The voltage is still controllable below this level, but you are at the extreme end of the range and there is a higher level of hum vs. signal. Some noise will get in from any test setup, but at very low levels, noise and crud are a higher percentage of your actual test signal.

Your performance measurements will probably vary from mine because of differences in the unit and test equipment used. The absolute values are not as significant as knowing the relative values as measured by your own equipment. This gives you a way to check the performance against a recorded value.

Always keep records on the operating characteristics of equipment you make when you complete it. Then you will have figures to use for comparison when you need them. It won't be guesswork or vague memory.

Odds and Ends

There are a few little odds and ends to really finish the project properly.

Make a full-size schematic diagram of the circuit showing all parts and values, voltage and current, and the actual output at both jacks (use scope if available). A clear drawing of the parts layout will help if you ever have to work on yours. You may not remember it that well in time. You might even make a copy of this article for your service package.

. . . at last - everything at your fingertips ! ! !

Bring ORGANIZATION & CONVENIENCE to your HAM Station! Eliminate clutter and provide lots of space for everything you need - Tuners, VFO, CW Keyers, Filters, Telephone, Log Book, Etc...

- *ANGLED REAR SHELF*
- *ALL PARTS FITTED*
- *STURDY CONSTRUCTION*
- *WALNUT or PECAN FINISH*

Floor space: 39"w by 30"d.
Also: 51"w by 30"d - $199.50
Dealers Inquiries Invited

$184.50
Radio Equipment
NOT Included
F.O.B. Culver City
(CA Residents add 6% sales tax)

A Finely Crafted Piece of Furniture With a REAL Purpose . . .

Call : (213) 837-4870 or Write for Information

S-F Amateur Radio Services ✓65
4384 Keystone Ave., Culver City, CA 90230

HI·Q BALUN

- For dipoles, yagis, inverted vees & doublets
- Replaces center insulator
- Puts power in antenna
- Broadbanded 3-40 MHz
- Small, lightweight and weatherproof
- 1:1 Impedance ratio
- For full legal power and more
- Helps eliminate TVI
- With SO 239 connector

only $12.95

HI·Q ANTENNA CENTER INSULATOR

Small, rugged, lightweight, weatherproof
Replaces center insulator
Handles full legal power and more
With SO 239 connector

$6.95

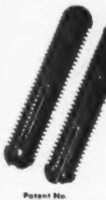

HI·Q ANTENNA END INSULATORS

Patent No
4 091 350

Rugged, lightweight, injection molded of top quality material, with high dielectric qualities and excellent weatherability. End insulators are constructed in a spiral unending fashion to permit winding of loading coils or partial winding for tuned traps.

May be used for
- Guy wire strain insulators
- End or center insulators for antennas
- Construction of antenna loading coils or multiband traps

$4.95

DIPOLES

MODEL	BANDS	LENGTH	PRICE WITH HI-Q BALUN	WITH HI-Q CENTER INSULATOR
Dipoles				
D-80	80,75	130	$31.95	$27.95
D-40	40,15	66	28.95	24.95
D-20	20	33	27.95	23.95
D-15	15	22	26.95	22.95
D-10	10	16	25.95	21.95
Shortened dipoles				
SD-80	80,75	90	35.95	31.95
SD-40	40	45	32.95	28.95
Parallel dipoles				
PD-8010	80,40,20,10,15	130	43.95	39.95
PD-4010	40,20,10,15	66	37.95	33.95
PD-8040	80,40,15	130	39.95	35.95
PD-4020	40,20,15	66	33.95	29.95
Dipole shorteners - only, same as included in SD models				
S-80	80,75			$11.95 pr
S-40	40			$10.95 pr

All antennas are complete with a HI-Q Balun or HI-Q Antenna Center insulator, No. 14 antenna wire, ceramic insulators, 100 nylon antenna support rope (SD models only 50) rated for full legal power. Antennas may be used as an inverted V and may also be used by MARS or SWLs.

Antenna accessories—available with antenna orders

Nylon guy rope 450# test 100 feet	$4.49
Ceramic (Dogbone Type) antenna insulators	$1.50 pr
SO-239 coax connectors	.55

All prices are postpaid USA 48
Available at your favorite dealer or order direct from

Dealer Inquiries Invited

Van Gorden Engineering

BOX 21305 B, SOUTH EUCLID, OHIO 44121

RIDGE
SYSTEMS
CO., INC.

4511 RTTY Interface for TRS-80* Color Computer Owners

- Simply plug into Program Pak* slot.
- No software to load, it is in ROM.
- Split screen features word wrap and continuously displays status.
- Selective calling stores incoming messages on casette tape.
- Baudot and ASCII modes.
- Standard EIA signals to your T.U.
- Complete documentation supplied.

4511 RTTY Interface
✓171 **$169.95**

RIDGE
SYSTEMS
CO., INC.

Tested & assembled; 90 day warranty; we pay shipping. Mass. residents add 5% sales tax.

*A trademark of Tandy Corp.

P.O. Box 772, Acton, MA 01720 (617) 264-4251

WACOM

DUPLEXERS

U.S.Patent No.4,080,601

OUR NEW BANDPASS-
REJECT DUPLEXERS WITH EXCLUSIVE
B_pB_r CIRCUIT FILTERS ®

. . . provides superior performance,
especially at close frequency spacing.

Models available for all commercial and ham bands.
Special prices for amateur repeator clubs.
✓79

WACOM PRODUCTS, INC.

P.O. BOX 7127 • WACO, TEXAS 76710
817/848-4435

Put all this in the file of service information you keep for your other gear. You do have one, don't you? Then it will be there when you need it. No guesswork.

This is one of the simpler pieces of test gear to use, but there are a few cautions I would like to stress.

If you have been used to working with transistor equipment, you may not be street-wise to the dangers of working in higher voltage tube circuits. This unit will help troubleshoot tube receivers and audio amplifiers, but make sure you observe all safety precautions for working with high voltage. Tube voltage levels are lethal.

Working with transistor equipment is a lot safer for you, but the oscillator has a husky output that easily can blow many transistor stages. Observe all safety precautions for working with transistor circuits, too.

As a general rule, set the controls of the unit under test as they would be for normal operation. Start with the lowest level signal you have and use the least signal that will do the job. You can damage a transistor stage with too much signal or even a static charge. It would be hard to damage a tube stage with this unit, but too much signal can cause distortion. You could be trying to fix a problem that you are causing while testing.

This unit will do a lot for you, but to use it safely and effectively you have to know what you are doing and why.

A good book or two on troubleshooting and repair will give you lots of ways to get the most out of your test equipment. Make sure your library covers both tube and solid-state gear.

A little hands-on experience working with this unit also will tell you a lot about its capabilities. ■

COM-RAD'S SPACE BEATERS

RUGGED LOW PROFILE ANTENNAS
FOR RESTRICTED SPACE USE

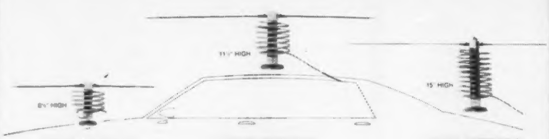

15/12 METERS
MODEL CR1512A

20/17 METERS
MODEL CR1720A

40/30 METERS
MODEL CR4030A

The Three Mobile-ears!*

REPEATER BEATER*

2 METER
DDRR
CR2A

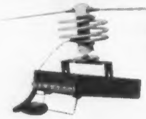

10 METER
CR1011A

ALSO
6 METER
CR6A

THE HI-RIZER

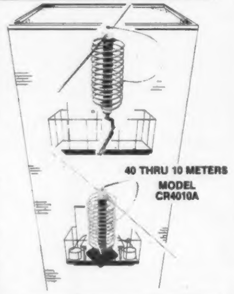

40 THRU 10 METERS
MODEL
CR4010A

*AS REVIEWED IN 73 MAGAZINE OCTOBER AND NOVEMBER, 1982

YOU CAN BE AS PROUD OF YOUR SIGNAL FROM THESE ANTENNAS AS WE ARE PROUD OF OUR PRODUCTS!

✓163

COM-RAD, INC. 1635 WEST RIVER PARKWAY
GRAND ISLAND, NEW YORK 14072 • (716) 773-1445

WORK THE U.H.F. BANDS

Add a transverter or converter to your existing 10m, 6m or 2m equipments. Choose from the largest selection of modules available for DX, OSCAR, EME, ATV.

TRANSVERTERS

MMT 50-144 $209.95
MMT 144-28 $199.95
MMT 432-28 (S) $299.95
MMT 439-ATV $349.95
MMT 1296-144 $374.95
OTHER MODELS AVAILABLE
write for details

POWER AMPLIFIERS

all models include RF VOX & Low Noise RX Pre-Ampl.
(no pre-amp in MML432-100)

2 Meters:	100W output	MML144-100-LS	1W or 3W in	$284.95
	100W output	MML144-100-S	10W input	$264.95
	50W output	MML144-50-S	10W input	$239.95
	30W output	MML144-30-LS	1W or 3W in	$124.95
	25W output	MML144-25	3W input	$114.95
432 MHz:	100W output	MML432-100	10W input	$444.95
	50W output	MML432-50	10W input	$239.95
	30W output	MML432-30-L	1W or 3W in	$ ask
1268-1296 MHz:		Coming soon. Watch for details.		

ANTENNAS (incl. 50 ohm balun)

2 Meter J-Beams: 12.3 dBd gain

8 over 8 Horizon'l pol	D8-2M	$63.40
8 by 8 Vertical pol	D8-2M-vert	76.95
1250-1300 MHz Loop-Yagi	1296-LY	$49.75

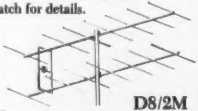

D8/2M

Send 36¢ stamps for full details of all our VHF/UHF items.

Pre-selector filters
Low-pass filters
Varactor triplers
Pre-amplifiers

Transverters
Converters
Antennas
Crystal Filters

VISA
master charge

si

Spectrum International, Inc.
Post Office Box 1084S
Concord, Mass. 01742 USA

✓436

2 GHz Microwave Receiving Systems

The new **Micro-System** features a machined 18" parabolic reflector for maximum efficiency, a linear feed-point downconverter with ceramic high performance RF preamplifier transistor, a variable 12 to 18 volt regulated power supply and 50' of 75Ω coaxial downlead, including a 3' jumper and matching transformer. The **Micro-System** includes a full 6 month warranty.

Micro-System (MS-021)	$159.95
Micro-System (MS-578)	$169.95
Micro-System (MS-645)	$179.95

Shipping & Handling: USA . . . $4.00 AK, HI & PR . . . $10.00

Data Service Company 612-636-9469

✓346 3110 Evelyn Street
Roseville, MN • 55113

MasterCard VISA

LIMITED SPECIAL $555.00

HAMEG Oscilloscopes

to meet every need

20 MHz
DUAL TRACE

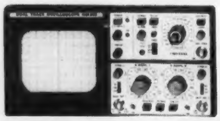

MODEL HM-203

WITH PROBES: × 1 & × 10
- ONE YEAR FULL WARRANTY
- SOLID STATE
- ASSEMBLED & CALIBRATED

NEW RECTANGULAR CRT

(603)434-5371

DEALER INQUIRIES INVITED

✓133 Rivendell Assoc.

RFD-5 DERRY, N.H. 03038 WARNER HILL

Alaska Microwave Labs

4335 E. 5TH STREET ANCHORAGE, ALASKA 99504
(907) 338-0340 DEPT 73

CHIP CAPACITORS	
1.2, 2.2, 3.3, 4.7, 6.8, 10, 18, 22, 27, 47, 100, 120, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1.2K 1.8K, 3.9K, 8.2K, 10K, 100K	$.60
GaAs FETS	
MGF1400 NF 2.0DB @ 4GHZ MAG 15DB	$19.00
MGF1412 NF 0.8DB @ 4GHZ MAG 18DB	$85.00
MCF1200 NF 1.0DB @ 1GHZ, NF 2.2DB & MAG 14DB @ 4GHZ	$14.00
COAX CONNECTORS	
BNC CHASSIS MOUNT SQUARE FLANGE	$1.95
BNC PLUG FOR RG-58	$1.95
SMA CHASSIS MOUNT SQUARE FLANGE	$6.10
SMA CHASSIS MOUNT PLUG SQ. FLANGE	$8.50
SMA CHASSIS MOUNT STRIP-LINE TAB	$6.75
SMA PLUG FOR RG-58	$6.75
SMA PLUG FOR RG-174	$6.75
SMA PLUG FOR .141 SEMI RIGID	$3.98
TYPE N CHASSIS MOUNT SQUARE FLANGE	$3.75
TYPE N PLUG FOR RG-9/RG-8	$3.75
TYPE N DOUBLE MALE	$7.25
TYPE N FOR .141 SEMI-RIGID	$15.00
TYPE N CHASSIS MOUNT PLUG SQUARE FLANGE	$14.00
SILVER PLATING KIT	
Will plate Copper, Brass, Bronze, Nickel, Tin, Pewter, Gold, and most white metal alloys.	$36.00
VTO	
V72T-1 2.7GHZ TO 3.2GHZ MIN POWER OUT 10 MW TUNING VOLTAGE 0 TO 20V Vcc +15 VDC @ 60 MA	$98.00
V82T-1 SAME AS V72T-1 BUT FREQ.3.6GHZ TO 4.2GHZ	$98.00
TEFLON CIRCUIT BOARD DBL SIDED 1 OZ	
APPROX. 3.25"× 5.0"× .010	$5.50
APPROX. 3.25"× 5.0"× .0312	$6.50
APPROX. 3.25"× 5.0"× .0625	$10.50
FEED-THRU CAPACITORS	
1000 PF SOLDER TYPE	$.50
470 PF SOLDER TYPE	$.50
LEADLESS CERAMIC CAPACITORS	
1000 PF	$.25

NO WARRANTEE ON SEMICONDUCTORS

OPEN AT 8 PM EST CLOSED 8PM PST
ORDERS ARE POSTAGE PAID
COD - VISA - MASTERCHARGE

CW MORSE for the TRS-80* COLOR COMPUTER

Our Plug-in Morse-Pak© interfaces the Color Computer to your transceiver and allows you to communicate in CW Morse Code through the computer.

★Installs in minutes★
★Simple to operate★
★Handles code speeds up to 60 wpm★
many more features

●●●●●●●●●●●●●●●●●

We stock a complete line of color computer accessories, including:

•Floppy disk controllers •Serial I/O Ports • Add-on EPROM kits • Plug-in Breadboards • RAM Expansion kits, 16K-64K • and more

Write for brochure to:

ATOMTRONICS ✓186
3195 ARIZONA AVE.
LOS ALAMOS, NM 87544

**™Tandy Corporation*

IRON POWDER and FERRITE PRODUCTS

AMIDON Associates ✓334

Fast, Reliable Service Since 1963

Small Orders Welcome **Free 'Tech-Data' Flyer**

Toroidal Cores, Shielding Beads, Shielded Coil Forms
Ferrite Rods, Pot Cores, Baluns, Etc.

12033 OTSEGO STREET, NORTH HOLLYWOOD, CALIFORNIA 91607

ALL BAND TRAP ANTENNAS!

PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. INPUT FOR NOVICE AND ALL CLASS AMATEURS! IMPROVED DESIGN!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6"- you just switch to band desired for excellent worldwide operation - transmitting and recleving! Low SWR over all bands -Tuners usually NOT NEEDED! Can be used as inverted V's - slopers - in attics, on building tops or narrow lots. The ONLY ANTENNA YOU WILL EVER NEED FOR ALL DESIRED BANDS - WITH ANY TRANSCEIVER - NEW - EXCLUSIVE! NO BALUNS NEEDED!

80-40-20-15-10-6 meter - 2 trap --- 104 ft. with 90 ft. RG58U - connector - Model 998BUC . . . $89.95
40-20-15-10 meter --- 2 trap --- 54 ft. with 90 ft. RG58U - connector - Model 1001BUC $88.95
20-15-10 meter --- 2 trap --- 26ft. with 90 ft. RG58U - connector - Model 1007BUC. $87.95

SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is $5.00 extra for postage - clerical - customs etc.)or order using VISA - MASTER CARD - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES MAY INCREASE . . SAVE - ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM
WESTERN ELECTRONICS Dept. A7-12 Kearney, Nebraska, 68847 ✓80

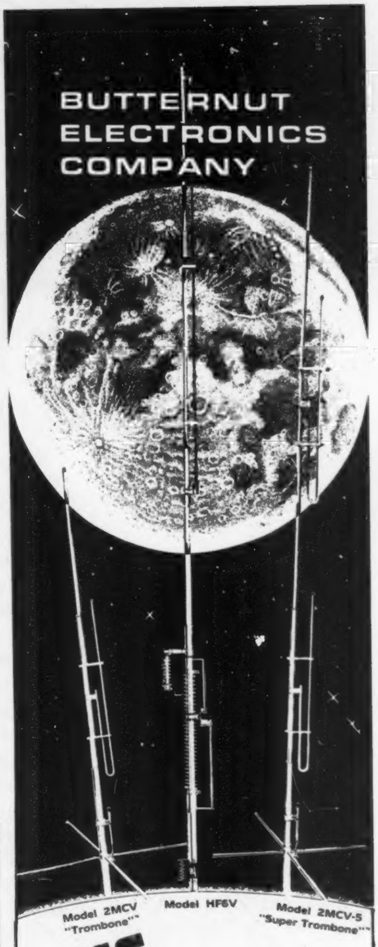

BUTTERNUT ELECTRONICS COMPANY

THE WINNERS

Model HF6V—Completely automatic bandswitching 80 through 10 **plus** 30 meters. Outperforms **all** 4- and 5-band "trap" verticals of comparable size. Thousands in use worldwide since December '81! 160 meter option available now; retrofit kits for remaining WARC bands coming soon. Height: 26 ft/7.8 meters; guying not required in most installations.

Model 2MCV "Trombone"™—omnidirectional collinear gain vertical for 2 meters having the same gain as "double-⅝λ" types, but the patented "trombone" phasing section allows the radiator to remain unbroken by insulators for maximum strength in high winds. No coils "plumber's delight" construction and adjustable gamma match for complete D.C. grounding and lowest possible SWR. Height: 9.8 ft/2.98 meters

NEW Model 2MCV-5 "Super-Trombone"™—Same advanced features as the basic 2MCV but a full wavelength taller with additional "Trombone"™ phasing section for additional gain. Height: 15.75 ft/4.8 meters

All BUTTERNUT ANTENNAS use stainless steel hardware and are guaranteed for a full year. For further information on these and other BUTTERNUT products write for our FREE CATALOG!

BUTTERNUT ELECTRONICS
GARY AIRPORT BOX 356 E RTE 2
SAN MARCOS, TEXAS 78666

Roger Stigney AJ0P
8400 Eastwood Rd.
Minneapolis MN 55432

Maximum Modulation for CB Conversions

Many CB rigs lack the gain for full modulation. This preamp will help.

If you have recently converted a CB for 10-meter operation or if your present ham rig has insufficient mike gain, you may be interested in building this simple microphone preamplifier. The majority of CB rigs in the lower to middle price ranges do not provide adequate mike gain for optimum modulation. Typical modulation levels obtained are from 30 to 60 percent. The addition of a preamplified mike can significantly increase the "talk power" of these rigs; just ask any CBer.

There are several commercially-available preamplified mikes on the market that will provide the added audio gain for a price tag of $25.00 to $50.00. A much cheaper alternative is the single field-effect transistor (FET) circuit shown in Fig. 1. I purchased all components for under $5.00 at a local Radio Shack store.

The circuit can be constructed in a separate minicabinet by using mating microphone connectors to match those used by your CB or it can be mounted inside the CB. When mounting within the CB, the additional mike connectors, switch, cabinet, and 9-volt battery are not required. You probably won't have enough room to install the potentiometer (R4) inside the CB, but it can be replaced with two fixed resistors once the proper mike gain adjustment level is established.

To provide similar circuit-operating parameters when installing inside a CB, substitute a 33k-Ohm resistor for R3 and connect it to a +12-volt power point in the CB. Also connect the common ground point of the preamplifier circuit to CB ground. Unsolder the existing microphone lead from the printed circuit board and connect it to the input of the FET circuit. Use a short piece of shielded wire to connect the output of the FET circuit to the printed circuit board and ground the shield to minimize hum pickup.

Adjustment is simply a matter of setting the potentiometer for optimum modulation level. This can be accomplished through the use of a modulation meter connected to the antenna feedline connector of the CB or during an actual QSO. Don't forget that the FCC limits the maximum permissible modulation level at 100 percent, so make sure that the gain setting used does not cause audio distortion or splatter.

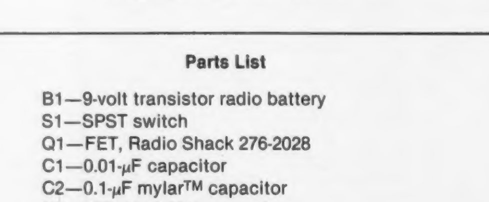

Fig. 1. Mike preamp circuit.

Parts List

B1—9-volt transistor radio battery
S1—SPST switch
Q1—FET, Radio Shack 276-2028
C1—0.01-μF capacitor
C2—0.1-μF mylar™ capacitor
C3—100-μF, 10-V-dc capacitor
R1—2-megohm, ½-Watt resistor
R2—3300-Ohm, ½-Watt resistor
R3—10k-Ohm, ½-Watt resistor
R4—50k-Ohm (or 100k) audio-taper potentiometer
J1,J2—Phone jacks to match equipment

When you have established the optimum level setting, the potentiometer can be replaced by two fixed resistors connected as a series voltage divider. To determine the proper resistor values, measure the resistance between the center lug of the potentiometer and each outside lug. Obtain two resistors having the same approximate values, connect them in series, and substitute these in place of the potentiometer. Connect the mike lead to the junction between the two resistors. Check that the resistors are installed in the circuit so that they have the same relationship as the measured resistance values on the potentiometer.

The circuit can be constructed on any suitable piece of insulating material. I used a piece of cardboard measuring about 1-1/2" by 3" and mounted the components on one half of the area. I then folded and taped the cardboard under to protect against possible shorting of the circuit connections. ■

"BEEPER III"

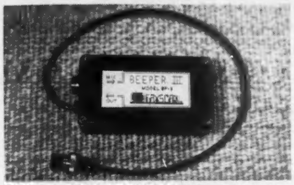

"THE PROFESSIONAL TOUCH COMES TO AMATEUR RADIO!"

"BP-3 automatically provides a gentle high frequency beep at the beginning of each transmission and a low beep at the end. Virtually eliminates "talk-over"! Operates for up to one year on a single 9-V battery (not supplied). Can be directly interfaced to any transceiver which is keyed by grounding the PTT line (the PTT line voltage must be positive, not greater than 24 VDC, nor the current greater than 100 ma.) Works with virtually all modern gear. You've heard it; now you can have it!"

"ADD THE BEEP!"

"BP-3A	Complete with case, cable, Standard 4-pin connectors	**39.95 pp**
BP-3B	As above except without connectors. Add your own	**36.95 pp**
BP-3C	Circuit-board version for custom installation	**29.95 pp**

All units assembled/tested. OH residents add 6% Sales Tax"

FAXSCAN INC. ✓85

3148 Dorf Drive • Dayton, Ohio 45418

TM

SUPER-RATT™

The Complete RTTY Communications Program for the 80's

ONLY $59.95 POSTPAID!

- For your 48K Apple II with one disc drive
- Works with all tuning units.
- Verified File Transfer™ assures error-free communication
- Full Radio Bulletin Board System™
- "Open" Program—easy for you to modify

UNIVERSAL SOFTWARE SYSTEMS, INC.
9 SHIELDS LANE · RIDGEFIELD, CT 06877
(203) 438-3117
VISA/M.C. OK

✓189

***QUALITY**
***PRICE**
***PERFORMANCE**

SATELLITE

Tunable Audio Demodulator — Tunes from 5.4 to 8.2 MHz. Switchable 5 KHz. LP filter for Canadian birds. Varactor tuning diodes included. Use two for MTV.

Bare Board (M81-020B)	**$24.95**
Two Boards (M81-021B)	**$39.95**

Canadian Audio Descrambler — Takes the normal audio output from your receiver and decodes the 'chirping' sub-carriers heard on Anik A/B.

Kit (R81-010K)	**$59.95**
Assembled & Tested (R81-010T)	**$94.95**

NEW! Canadian Audio Filter — A very sharp low-pass filter designed to remove the 'chirping' from the Canadian audio.

Kit (R82-020K)	**$19.95**
Assembled & Tested (R82-020T)	**$29.95**

Developed for high performance in weak signal areas:

Discrete 70 MHz PLL — Replaces NE 564 video demodulator without the need for an ECL divider (70 MHz I.F.). Guaranteed tracking to 85 MHz. Wide bandwidth. Lower C/N, reduced 'tearing'. May be remotely tuned.

Kit (M82-010K)	**$124.95**
Assembled & Tested (M82-010T)	**$159.95**

All prices include complete and comprehensive documentation, U.S. postage & handling. For overseas postage & handling, add $2.00.

P.O. Box 1656
Kodiak, Alaska 99615
(907) 486-5118
(907) 486-6215

DCE

DigiCom Engineering, Inc.

MOR-GAIN

1/2-size (75M only 66')

Multi-Band (5, 4, 3 bands) 80/75M thru 10M

Broadbanded - no traps used

Prices start at $82.50

MOR-GAIN

THE MOR-GAIN HD DIPOLES are the most advanced, highest performance multi-band HF dipole antennas available. Patented design provides length one-half of conventional dipoles. 50 ohm feed on all bands, no tuner or balun required. Can be installed as inverted VEE. Thousands in use worldwide. 22 models available including two models engineered for optimum performance for the novice bands. The Mor-Gain HD dipoles N/T series are the only commercial antennas specifically designed to meet the operational requirements of the novice license. Our 1-year warranty is backed by nearly 20 years of HD dipole production experience.

For detailed 10-page brochure, write or phone directly to **MOR-GAIN**, P.O. Box 329T, Leavenworth, Ks. 66048, Tel. (913) 682-3142.

MOR-GAIN

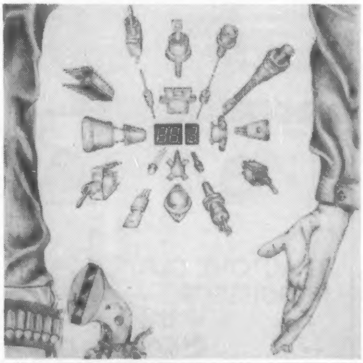

READY...WHEN YOU ARE

OVER 150,000 TYPES OF MRO ITEMS ON THE SHELF NOW FOR IMMEDIATE OVER THE COUNTER SALES.

Besides the world's largest selection of semiconductors, we also stock hard-to-find RF connectors, caps, chip caps, trim caps, trim pots, chokes, tantalums, feed-thru's, fuses, precision caps & resistors, indicator lamps, etc.

For the common items, anywhere will do . . . for the darn near impossible, CALL US!!

SEMICONDUCTOR SUPERMART
1042 E. GARVEY AVENUE
WEST COVINA, CALIFORNIA 91790
(213) 967-4611 • (213) 967-3846

✓194

✓*See List of Advertisers on page 130*

TRAC

TRAC • ONE + DELUXE CMOS KEYER
SPEED
VOLUME
LOCK
FREQ
DELAY
GAIN
TONE

TRAC*ONE + DELUXE CMOS KEYER

$119.95

Features: **Model TE-464**

- *True CW signal reproduction—Single signal reception
- *Removes all QRM and QRN
- *Digs out CW signal, decodes it with Phased Lock Loop Tone Decoder then reproduces it with full operator control over Gain, Freq, Tone, Delay.
- *All controls on front panel
- *Freq control variable 300 Hz to 2500 Hz will match any rig.
- *LED flashes during decoder operation
- *Operates in line with rig audio--leave in line on OFF/BYPASS
- *Built in speaker
- *Headphones jack rear panel
- *Battery or AC-adaptor, 9VDC operation

PLUS:

- *Deluxe CMOS Keyer—"State-of-the-art" CMOS circuitry
- *Self-completing dots and dashes
- *Both dot and dash memory
- *Iambic keying with any squeeze paddle
- *5-50 w.p.m.
- *Speed, Volume, Tone, Tune and Weight controls
- *Sidetone and speaker
- *Semi-auto switch for bug or straight key
- *Deluxe quarter-inch jacks for keying and output
- *Keys grid block or solid state rigs

TRAC • ONE
CW PROCESSOR
LOCK
FREQ
DELAY
GAIN
TONE

TRAC*ONE CW PROCESSOR

$89.95

Features: **Model TE 424**

- *True CW signal reproduction—Single signal reception
- *Removes all QRM and QRN
- *Digs out CW signal, decodes it with Phased Lock Loop Tone Decoder then reproduces it with full operator control over Gain, Freq, Tone, Delay.
- *All controls on front panel
- *Freq control variable 300 Hz to 2500 Hz will match any rig.
- *LED flashes during decoder operation
- *Operates in line with rig audio—leave in line on OFF/BYPASS
- *Built-in speaker
- *Headphones jack rear panel
- *Battery or AC-adaptor, 9 VDC operation ✓76

SEND FOR BROCHURE ON OUR FULL PRODUCT LINE

TRAC ELECTRONICS, INC.
1106 RAND BLDG.
BUFFALO, NY 14203
(716) 852-8188

M² ENGINEERING'S
VHF H.T. CONVERTERS

- •DOUBLE BAND HC-V, HC-U2
- •SINGLE BAND HC-V220
- •BI-LATERAL PROTECTION AGAINST ACCIDENTAL TRANSMISSON FOR UP TO 5 WATTS
- •STANDARD BNC CONNECTORS
- •HC-V 154-158 159-163
- •HC-U2 460-464 480-484
- •HC-V220 221-225
- • USES SINGLE AAA CELL
- • LOW LOSS COUPLING TO ANTENNA
- • "OFF" RETURNS TO NORMAL TRANSCEIVER OPERATION
- • SIZE: approx. 2x1.5x1.5
- • WEIGHT: 3.9 ozs.

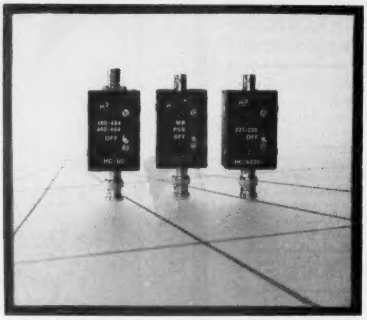

HC-U2 **$59.95**
HC-V **$47.45**
HC-V220 **$54.95**

✓77
M-SQUARED ENGINEERING, INC.
1446 LANSING AVE.
SAN JOSE, CA. 95118
CALL *SANDY* 408-266-9214

DEALERS WELCOME

Shipping included

Calif. residents add 6.5% sales tax

DIRECTION FINDING?

- ★ Doppler Direction Finding
- ★ No Receiver Mods
- ★ Mobile or Fixed
- ★ Kits or Assembled Units
- ★ 135-165 MHz Standard Range
- ★ Circular LED Display
- ★ Optional Digital Display
- ★ Optional Serial Interface
- ★ 12 VDC Operation
- ★ 90 Day Warranty

New Technology (patent pending) converts any VHF FM receiver into an advanced Doppler Direction Finder. Simply Plug into receiver's antenna and external speaker jacks. Use any four omnidirectional antennas. Low noise, high sensitivity for weak signal detection. Kits from $270. Assembled units and antennas also available. Call or write for full details and prices.

DOPPLER SYSTEMS, 5540 E. Charter Oak, Scottsdale, AZ 85254 ✓425 (602) 998-1151

PORTAPEATER™
M100 A INSTANT REPEATER
ANY BAND ANY MODE

$179.00 assembled unit

$99.00 assembled board

- *4Channel PROM CW I Der
- *VOX or COR operation
- *250 volt switching capability
- *An Instant Repeater
- *Works with any type radios
- *Complete Timer Functions
- *Built In Test Functions
- *20 Page Technical Manual

PORTA PEATER

(Fully tested, programmed, assembled) ✓302

W-S ENGINEERING P.O. BOX 58, PINE HILL, N.J. 08021
(201-852-0269)

Better by the dozen.

1. **NEVER SAY DIE**—If you want controversy, Wayne Green W2NSD/1 will give it to you. His popular column ranges from travelogue to tirade and is guaranteed to entertain, inspire and enlighten you.

2. **DX**—This globe-trotting column keeps you informed about the news of the DX world from Kingman Reef to Bahrain.

3. **CONTESTS**—You get all the news on the contest world from Robert Baker WB2GFE. He'll give you information on upcoming events and results from recent contests.

4. **FUN**—Just for fun, John Edwards KI2U provides you with wacky puzzles, quizzes, and games that test your ham mettle.

5. **FCC**—If you're looking to the future, these outtakes from the Federal Register chronicle changes in policy and regulations that relate to amateur radio.

6. **RTTY LOOP**—To keep you abreast of radioteletype developments, Marc Leavey WA3AJR explains the new RTTY equipment, the increasing role of computers in RTTY, and other matters of interest to digital communications fans.

7. **REVIEWS**—Before you buy, save yourself some money . . . check *73*'s in-depth evaluation of the latest gear.

8. **HAM HELP**—As a service to you, *73* prints your questions in our magazine. This helps you to obtain hard-to-get parts, schematics, and owner's manuals.

9. **SATELLITES**—From Phase III to TVRO, *73 Magazine* covers the news of the satellite world like no other radio amateur magazine.

10. **NEW PRODUCTS**—This brief look at the latest ham equipment on the market keeps you on top of new developments in amateur radio.

11. **AWARDS**—To find out what certificates are available where, read Bill Gosney KE7C's coverage of all the ham radio awards.

12. **CONSTRUCTION**—The builder's magazine . . . that's *73*. You get the best projects from the best authors every month.

Send me a dozen issues of
73 MAGAZINE
for the dozen reasons listed!

☐ Check enclosed for 1 year for only $19.97
Bill: ☐ MC ☐ VISA ☐ AMEX ☐ ME
Card#__________ Interbank#__________
Exp. date ________ Sig. __________
Name __________
Address __________
City________ State________ Zip________

Canada & Mexico $22.97 1 year U.S. funds.
Foreign surface $39.97 1 year U.S. funds drawn on US bank only
Foreign airmail—please inquire.

32DR6

73 Magazine•PO Box 931•Farmingdale, NY•11737
Please allow 6-8 weeks for delivery

73 MAGAZINE
FOR RADIO AMATEURS

Subscription Department
P.O. Box 931
Farmingdale, NY 11737

1-800-258-5473

For orders only please.
Foreign air mail, please inquire.

73 MAGAZINE
73 MAGAZINE FOR RADIO AMATEURS
73 MAGAZINE FOR RADIO AMATEURS

FLEXI-BILITY

MORSE BAUDOT ASCII CONVERTER 32
INPUT
OUTPUT
FILTER

AEA once again breaks new ground in the code communications field with the new model MBA-RC reader/-code converter. The MBA-RC decodes Morse, Baudot or ASCII signals off the air and displays them on a large 32 character alphanumeric vacuum fluorscent display. In addition, it will output Morse code for keying your transmitter. It will also generate RTTY (Baudot or ASCII AFSK two tone output. (170 or 850 Hz shifts.) Any of the acceptable input codes can be converted to any of the specified output codes (any speed to any speed). If you have any of the common Baudot RTTY terminals as an example, you can now send and receive Morse and ASCII with your keyboard and printer. You can even generate ASCII or BAUDOT RTTY using your Morse hand key or memory keyer.

Get the details. Write for our free product catalogue or better yet, see your favorite dealer.

Prices and Specifications subject to change without notice or obligation. Software ©copyright by AEA.

ADVANCED ELECTRONIC APPLICATIONS, INC.
P.O. Box C-2160,
Lynnwood, WA 98036
(206) 775-7373
Telex: 152571 AEA INTL

~2

AEA Brings you the Breakthrough!

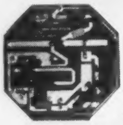

Christmas Sale

EM-3 **2300 MHz MICROWAVE DOWNCONVERTER KIT.** Includes high quality PC board, NE02137 & NE02136 transistors, thermal drift stabilizer, silver solder, .141 hardline, matched diodes, F-connectors, molded coils, instructions. **19.95**

EM-4 The EM-3 with NE64535 high performance RF transistor; Adds 3db gain to EM-3 and reduces noise figure. **25.95**

DO IT RIGHT THE FIRST TIME
WITH SUPERIOR QUALITY — *WITHOUT* HIDDEN COSTS

THOSE OTHER "DEALS" **DON'T** HAVE IT ALL —
WE DO!

- Detailed Instructions
- Post-Paid Delivery
- Thermal Drift Stabilizer
- F-Connectors
- Hardline Antenna Probe
- High Gain RF Stage
- Matched Diodes
- Molded Coils
- Silver Solder
- Toll-Free Number

Send SASE for Catalogue

Sale!

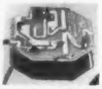

DA-3 **46.95**
EM-3 & RFA-1

Sale!

TU-8 Power Supply **32.95**

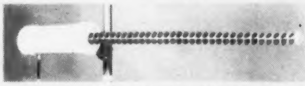

ANT-4 Antenna **24.95**
with Adjustable Bracket

Sale!

RFA-1 **29.95**
Preamplifier

SMP
Superior Microwave Products, Inc.
P.O. Box 1241
Vienna, VA 22180

Orders Only: **1-800-368-3028**
Info., VA & D.C.: **1-703-255-2918**
Discounts
All Orders Postpaid & Shipped in 48 Hours

VISA MasterCard

We Don't Compromise On Quality

Radio World

CENTRAL NEW YORK'S MOST COMPLETE HAM DEALER

ROBOT 800
ICOM IC-720
KENWOOD TS830S
DRAKE TR7-DR7
YAESU FT707

Featuring Kenwood, Yaesu, Icom, Drake, Ten-Tec, Swan, Dentron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Grain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Bird, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure, Collins, AEA. *We service everything we sell!*

Write or call for quote. **You Won't Be Disappointed.**
We are just a few minutes off the NYS Thruway (I-90) Exit 32

VISA master charge

OUT OF STATE
ORDER TOLL FREE
800-448-9338

ONEIDA COUNTY AIRPORT TERMINAL BUILDING
ORISKANY, NEW YORK 13424
N.Y. Res. Call (315) 736-0184

~397

Warren - K2IXN
Bob - WA2MSH
Al - WA2MSI

AFFORDABLE CW KEYBOARD FROM $69.95

Transmits perfect Morse Code * Built-in 16 character buffer * Internal speaker and side-tone * Reed relay output eliminates keying problems * All solid state circuits and sockets for reliability * Speed range 5—45 WPM * Perfect companion to our CODE★STAR all-mode code reader.

MORSE-A-KEYER KIT, model MAK-K, Complete kit of parts & manual	$159.95
MORSE-A-KEYER, model MAK-F, Factory wired & tested	$199.95
MORSE-A-KEYER ESSENTIAL PARTS KIT, model EPK-K	$ 69.95

(Essential parts kit for home-brewers consists of pc board, board parts and manual. You supply ASCII keyboard, cabinet, power supply & miscellaneous parts.)

Send check or money order. Use your VISA or MasterCard. Add $5.00 shipping and handling for Continental U.S. Wisconsin residents add 4% Wisconsin State Sales Tax.

Microcraft Corporation **Telephone: (414) 241-8144**
Post Office Box 513G, Thiensville, Wisconsin 53092 ~50

RADIO BOOKSHOP

FOR THE NOVICE

New, updated editions

of our famous novice

license study guide and novice study tapes.

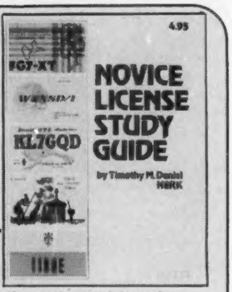

● **NOVICE LICENSE STUDY GUIDE**—by Timothy M. Daniel N8RK. Here is the most up to date novice guide available. It is complete with information about learning Morse Code, has the latest FCC amateur regulations and the current FCC application forms. This guide *is not* a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price. SG7357 $4.95.*

● **NOVICE STUDY TAPES**—If you are just getting started in ham radio, you'll find these tapes indispensable! This up-to-the-minute revision of the 73 Study Course is the perfect way to learn everything you need to breeze through the Novice written exam. Theory, FCC regulations, and operating skills are all covered, and you'll be amazed at how fast you learn using these tapes!

Once the test is behind you, these tapes will go right on being useful, because they are packed with the latest information on setting up your own ham station, and getting on the air.

Thousands of people have discovered how easy learning from cassette can be—order now and enter the fascinating world of ham radio! CT7300 Set of 3—$15.95.*

Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time—even while you're driving! You get more and more info each time you hear it. You can't progress without solid fundamentals. These three hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to these tapes?

Special Offer! Both Novice License Study Guide and Novice Study Tapes $19.95 Order NP7300.

GENERAL LICENSE STUDY GUIDE

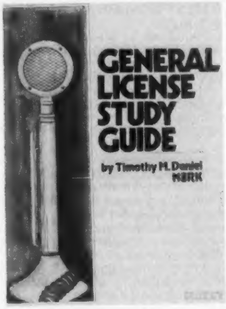

GENERAL LICENSE STUDY GUIDE—By Timothy M. Daniel N8RK This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-and-answer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world. SG7358 $6.95

Style W

Style Y

Style X

● **QSL CARDS**—*73* turns out a fantastic series of QSL cards at about half the cost of having them done elsewhere because they are run as a fill-in between printing books and other items in the 73 Print Shop. 250 Style W—QW0250—for $8.95*; 500 Style W—QW0500—for $13.95*; 250 Style X—QX0250—for $8.95*; 500 Style X—QX0500; 250 Style Y—QY0250—for $8.95*; 500 Style Y—QY0500—for $13.95.* Allow 6-12 wks. for delivery.

● **LIBRARY SHELF BOXES**—These sturdy white, corrugated, dirt-resistant boxes each hold a full year of *73, Kilobaud Microcomputing or 80 Microcomputing*. With your order, request self-sticking labels for any of the following: *73, Kilobaud Microcomputing, 80 Microcomputing, CQ, QST, Ham Radio, Personal Computing, Radio Electronics, Interface Age*, and *Byte*. Order 1—BX1000—for $2.00*; order 2-7—BX2002—for $1.50 each*; order 8 or more—BX1002—for $1.25 each*.

For Your Ham Shack 73 Magazine Binders

● Preserve and protect your collection for a lifetime! Order these handsome red binders with gold lettering. $7.50 for 1, 3 for $21.75, 6 for $42.00. (Postpaid within USA, please add $2.50 per order outside USA.) *Check or money orders only, no phone or C.O.D. orders.* **73 Binders, P.O. Box 5120, Philadelphia, PA 19141.**

***NOTE—Above address for Binders only.**

73

Code Tapes

any four tapes for $15.95! $4.95 each

"GENESIS"

5 WPM—CT7305—This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people—including kids of ten—are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

"THE STICKLER"

6+ WPM—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly—under pressure—faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.

"BACK BREAKER"

13+ WPM—CT7313—Code groups again, at a brisk 14 per so you will be at ease when you sit down in front of the steely-eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heaven you had this backbreaking tape.

"COURAGEOUS"

20+ WPM—CT7320—Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape.

"OUTRAGEOUS"

25+ WPM—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered it. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."

● **BACK ISSUES**—Complete your collection; many are prime collectables now, classics in the field! A full collection is an invaluable compendium of radio and electronics knowledge!

73300	73 BACK ISSUE—BEFORE JULY 1980	$ 3.00
73350	73 BACK ISSUE JULY 1980 THRU OCT. 1981	$ 3.50
73350P	73 BACK ISSUE NOV. 1981 TO PRESENT	$ 3.50
73005	73 BACK ISSUE—5 YOUR CHOICE	$10.75
73010	73 BACK ISSUE—10 YOUR CHOICE	$16.00
73025	73 BACK ISSUE—25 YOUR CHOICE	$27.00
73125	73 BACK ISSUE—25 OUR CHOICE	$14.00

Shipping: Please add $1.00 per magazine. Orders of ten magazines or twenty-five magazines add $7.50 per order.

*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop ● Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. $1.50 for the first book, $1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail $10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

RADIO BOOKSHOP

HAND BOOKS FOR THE HAMSHACK

THE COMPLETE SHORTWAVE LISTENER'S HANDBOOK, 2nd EDITION by Hank Bennett and Harry L. Helms. This comprehensive volume contains loads of new information from all over the world on the latest developments in SWL technology clubs, associations, practices and stations. A thorough guide to stations of the world by general continental area and frequency is included. BK1241 $9.95

THE TEN METER FM HANDBOOK—by Bob Heil K9EID. This handbook has been published to help the ten meter enthusiast learn more about the many methods of conversions and tricks that are used to make existing units work better. Join the great "tinkerers" of the world on ten FM and enjoy the fantastic amount of fun in communicating with amateur stations worldwide on ten meter FM. BK1190 $4.95.*

THE PRACTICAL HANDBOOK OF AMATEUR RADIO FM REPEATERS—by Bill Pasternak WA6ITF (author of 73 Magazines monthly column "Looking West") This is the book for the VHF/UHF FMer, compiled from material submitted by over a hundred individuals, clubs, organizations and equipment manufacturers. A "must have" for your ham shack shelf. BK1185 $12.95.*

THE NEW WEATHER SATELLITE HANDBOOK
TOOLS & TECHNIQUES FOR ELECTRONICS

TOOLS & TECHNIQUES FOR ELECTRONICS—by A. A. Wicks is an easy-to-understand book written for the beginning kit-builder as well as the experienced hobbyist. It has numerous pictures and descriptions of the safe and correct ways to use basic and specialized tools for electronic projects, as well as specialized metalworking tools and the chemical aids which are used in repair shops. BK7348 $4.95.*

BEHIND THE DIAL—This book explains, in detail, what's going on on all the frequencies, from shortwave up to microwave. It gives the reader a good idea of what he can find and where to find it, including some of the secret stations such as the C.I.A. and the F.B.I. Everything is covered short of microwave monitoring. Anyone interested in purchasing a shortwave receiver should have a copy of this book. surveillance, station layout consideration, antenna systems, interface, and the electromagnetic spectrum. are included. BK7307 $4.95

THE NEW WEATHER SATELLITE HANDBOOK—by Dr. Ralph E. Taggart WB8DQT. Here is the completely updated and revised edition containing all the information on the most sophisticated and effective spacecraft now in orbit. This book serves both the experienced amateur satellite enthusiast and the newcomer. It is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Solid hardware designs and all the instructions necessary to operate the equipment are included. For experimenters who are operating stations, the book details all procedures necessary to modify equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment. BK7383 $8.95.*

THE 73 TEST EQUIPMENT LIBRARY

VOL. II AUDIO FREQUENCY TESTERS—Jam-packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you . . . a good book for hi-fi addicts and experimenters, too! LB7360 $1.95.*

VOL. III RADIO FREQUENCY TESTERS—Radio frequency waves, the common denominator of amateur radio. Such items as SWR, antenna impedance, line impedance, RF output, and field strength; detailed instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads, and much more. LB7361 $1.95.*

VOL. IV IC TEST EQUIPMENT—Become a troubleshooting wizard! Here are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes for the *73* TEST EQUIPMENT LIBRARY. LB7362 $1.95.*

ALL THREE OF THE ABOVE ONLY $4.95 ORDER LB7365

RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD—BK1044—Rf burst, function, square wave generators, variable length pulse generators—100 kHz marker, i-f and rf sweep generators, audio osc, af/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. BK1044 $5.95.*

THE 73 TECHNICAL LIBRARY

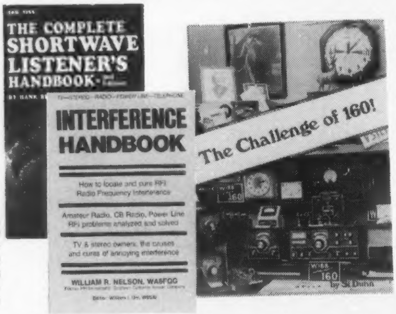
THE COMPLETE SHORTWAVE LISTENER'S HANDBOOK
INTERFERENCE HANDBOOK
The Challenge of 160!
WILLIAM R. NELSON, WA6FQG

THE CHALLENGE OF 160—The growth of amateur radio today is encouraging the use of 160 meters. All the information necessary to get started on this unique band, the all-important antenna and ground systems are described in detail. Also, how to get on, top-band operating tips, top-band transmitters, propagation, weather receiving equipment, and more are covered in full. The introduction contains interesting photos of Stew Perry's (the King of 160) shack. This reference is useful to new and experienced top-band operators. BK7309 $4.95

INTERFERENCE HANDBOOK—by William R. Nelson, WA6EQG—This timely handbook covers every type of RFI problem and gives you the solutions based on practical experience. Covers interference to TV, radio, hi-fi, telephone, radio amateur, commercial and CB equipment. Power line interference is covered in depth —how to locate it, cure it, work with the public, safety precautions, how to train RF/I investigators. Written by an RFI expert with 33 years of experience, this profusely illustrated book is packed with practical easy-to-understand information. BK1230 $8.95.*

OWNER REPAIR OF RADIO EQUIPMENT—by Frank Glass K6RQ. Here's a book that will teach you an approach to troubleshooting without a shack full of test equipment. Written in a narrative, non-mathematical style, it will encourage you to successfully fix your own rig problems 80 to 90% of the time. Even if you don't want to fix, you can learn a lot about how things work and fail. Add to your library and personal expertise. BK7310 $7.95.*

FOR THE CONTESTER

THE CONTEST COOKBOOK—This book reveals the secrets of that elite group of operators who top the list when the contest results are published. It contains detailed suggestions for the first-time contester as well as tips for the advanced operator. Domestic, DX, and specialty contests are all discussed, complete with photographs and diagrams showing the equipment and operating aids used by the top scorers. For the serious contester. BK7308 $5.95.

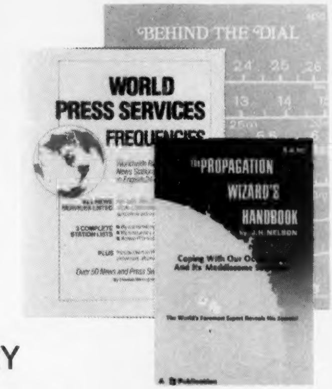
BEHIND THE DIAL
WORLD PRESS SERVICES FREQUENCIES
THE PROPAGATION WIZARD'S HANDBOOK
by J.H. NELSON

NEW

EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TELEVISION, (but were afraid to ask) —By Mike Stone WB0QCD. This book is a complete guide to setting up your own amateur radio television station. It contains—A history, what equipment you need, video theory, cameras, recorders, lighting, special effects, sound ATV DXing, mobile FSTV, ATV repeaters, ATV groups, building projects, test equipment, dealer directory, a cumulative index of over 1000 articles on amateur TV and much more. **This is the new, 1982 edition.** From the publishers of *Amateur Television Magazine*. $9.95 BK1244

WORLD PRESS SERVICE FREQUENCIES—by Thomas Harrington Can't wait to hear the evening news, or are you wondering about the news that you *aren't* hearing? Receive by Radio Teletype (RTTY) *all* the world news and financial happenings from the world capitols on a 24 hour a day basis. This book gives you the frequencies and times of broadcast of such news services as AP, UPI, Reuters, TASS, VOA and London Press. Also included is an introduction to RTTY with information on equipment, antennas, abbreviations—everything you need to get started in RTTY. BK1202 $7.95*

SSB . . . THE MISUNDERSTOOD MODE—by James B. Wilson. Single Sideband Transmission . . . thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. BK7351 $5.50.*

PROPAGATION WIZARD'S HANDBOOK— by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940s, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reliable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. BK7302 $6.95.*

IC OP-AMP COOKBOOK—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, liberally illustrated. 592 pages, 5½ × 8½, softbound. BK1028 $14.95.*

*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. $1.50 for the first book, $1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail $10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

RADIO BOOKSHOP

ANTENNA BOOKS

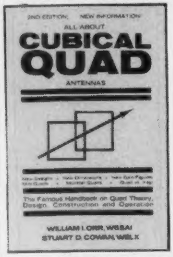
2ND EDITION · NEW INFORMATION
ALL ABOUT
CUBICAL QUAD
ANTENNAS
The Famous Handbook on Quad Theory, Design, Construction and Operation
WILLIAM I. ORR, W6SAI
STUART D. COWAN, W2LX

BEAM ANTENNA
WILLIAM I. ORR, W6SAI
STUART D. COWAN, W2LX

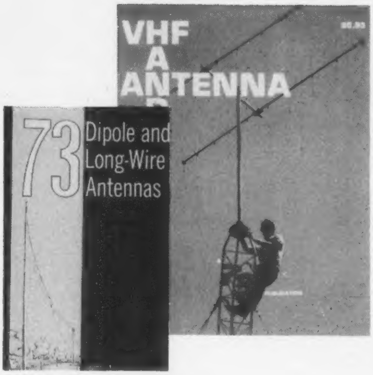

VHF ANTENNA HANDBOOK—The new *VHF Antenna Handbook* details the theory, design, and construction of hundreds of different VHF and UHF antennas . . . a practical book written for the average amateur who takes joy in building, not full of complex formulas for the design engineer. Packed with fabulous antenna projects you can build. BK7368 $5.95.*

BEAM ANTENNA HANDBOOK (New 5th edition)—by William I. Orr & Stuart D. Cowan. Yagi beam theory, construction and operation. Information on wire beams, SWR curves and matching systems. A "must" for serious DXers. BK1197 $5.95.

VHF HANDBOOK FOR RADIO AMATEURS—BK1198—Contains information on FM theory, operation and equipment, VHF antenna design and construction, satellite-EME, and the newest solid-state circuist $6.95*

THE RADIO AMATEUR ANTENNA HANDBOOK—BK1199—All about wire antennas, beams, tuners, baluns, coax, radials, SWR and towers. Clear and complete information. $6.95

SIMPLE, LOW-COST WIRE ANTENNAS FOR RADIO AMATEURS—All new data and everything you want to know about low-cost, multi-band antennas, inexpensive beams, "invisible" antennas for hams in "tough" locations. $6.95

73 DIPOLE AND LONG-WIRE ANTENNAS—by Edward M. Noll W3FQJ. This is the first collection of virtually every type of wire antenna used by amateurs. Includes dimensions, configurations, and detailed construction data for 73 different antenna types. Appendices describe the construction of noise bridges, line tuners, and data on measuring resonant frequency, velocity factor, and swr. BK1016 $5.50.*

ALL ABOUT CUBICAL QUAD ANTENNAS (2nd edition)—The "Classic" on Quad design, theory, construction, and operation. New 2nd edition contains new feed and matching systems and new data. BK1196 $5.95.*

HOW TO DEFEND YOURSELF AGAINST RADAR—BK1201—by Bruce F. Bogner and James R. Bodnar, a lawyer and radar expert. This book gives you the ammunition to challenge the radar "evidence" that usually leads to a speeding conviction. The major part of the book details the inner workings of radar—you'll become more of an expert than most police officers and judges. The remainder of the book outlines how to defend yourself against a speeding ticket—the observations, measures and testimony you must obtain to defend yourself without the help of a lawyer. The price is a lot less than a fine! $6.95.*

COOK BOOKS

TTL COOKBOOK—by Don Lancaster. Explains what TTL is, how it works, and how to use it. Discusses practical applications, such as a digital counter and display system, events counter, electronic stopwatch, digital voltmeter and a digital tachometer. BK1063 $9.50.*

CMOS COOKBOOK—by Don Lancaster. Details the application of CMOS, the low power logic family suitable for most applications presently dominated by TTL. Required reading for every serious digital experimenter! BK1011 $10.50.*

TVT COOKBOOK—by Don Lancaster. Describes the use of a standard television receiver as a microprocessor CRT terminal. Explains and describes character generation, cursor control and interface information in typical, easy-to-understand Lancaster style. BK1064 $9.95.*

MICROCOMPUTER BOOKS

ANNOTATED BASIC—A NEW TECHNIQUE FOR NEOPHYTES. VOL 1 & 2—*Annotated BASIC* explains the complexities of modern BASIC. It includes complete TRS-80* Level II BASIC programs that you can use. Each program is annotated to explain in step-by-step fashion the workings of the program. Programs are flowcharted to assisted you in following the operational sequence. And—each chapter includes a description of the new concepts which have been introduced.
Volume 1 BK7384 $10.95 Volume 2 BK7385 $10.95

HOBBY COMPUTERS ARE HERE!If you want to come up to speed on how computers work—hardware and software—this is an excellent book. It starts with fundamentals and explains the circuits and the basics of programming, along with a couple of TVT construction projects, ASCII, Baudot, etc. This book has the highest recommendations as a teaching aid. $2.47. BK7322

KILOBAUD KLASSROOM—By George Young and Peter Stark. Learning electronics theory without practice isn't easy. And it's no fun to build an electronics project that you can't use. *Kilobaud Klassroom* the popular series first published in *Kilobaud Microcomputing*, combines theory with practice. This is a *practical* course in digital electronics. It starts out with very simple electronics projects, and by the end of the course you'll construct your own working microcomputer! BK7386 $14.95

● **40 COMPUTER GAMES**—BK7381—Forty games in all in nine different categories. Games for large and small systems, and even a section on calculator games. Many versions of BASIC used and a wide variety of systems represented. A must for the serious computer gamesman. $7.95*

● **UNDERSTANDING AND PROGRAMMING MICROCOMPUTERS**—BK7382—A valuable addition to your computing library. This two-part text includes the best articles that have appeared in 73 and Kilobaud Microcomputing magazines on the hardware and software aspects of microcomputing. Well-known authors and well-structured text helps the reader get involved. $10.95*

TEXTEDIT—A Complete Word Processing System in kit form—by Irwin Rappaport. *TEXTEDIT* is an inexpensive word processor that you can adapt to suit your needs, from writing form letters to large texts. It is written in modules, so you can load and use only those portions that you need. Included are modules that perform right justification, ASCII upper/lowercase conversion, one-key phrase entering, complete editorial functions, and much more! *TEXTEDIT* is written in TRS-80* Disk BASIC, and the modules are documented in the author's admirably clear tutorial writing style. Not only does Irwin Rappaport explain how to use *TEXTEDIT*; he also explains programming techniques implemented in the system. *TEXTEDIT* is an inexpensive word processor that helps you learn about BASIC programming. It is written for TRS-80 Models I and III with TRSDOS 2.2/2.3 and 32K. *TRS-80 and TRSDOS are trademarks of the Radio Shack Division of Tandy Corporation. BK7387 $9.97

● **SOME OF THE BEST FROM KILOBAUD/MICROCOMPUTING**—BK7311—A collection of the best articles that have recently appeared in Kilobaud/ MICROCOMPUTING. Included is material on the TRS-80 and PET systems, CP/M, the 8080/8085/Z80 chips, the ASR-33 terminal. Data base management, word processing, text editors and file structures are covered too. Programming techniques and hardcore hardware construction projects for modems, high speed cassette interfaces and TVTs are also included in this large format, 200 plus page edition. $10.95.*

THE NEW HOBBY COMPUTERS—This book takes up from where "HOBBY COMPUTERS ARE HERE!" leaves off, with chapters on Large-Scale Integration, how to choose a microprocessor chip, an introduction to programming, low-cost I/O for a computer, computer arithmetic, checking memory boards . . . and much, much more! Don't miss this tremendous value! Only $2.47. BK7340

THE WELL EQUIPPED HAM SHACK

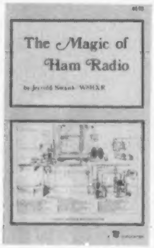

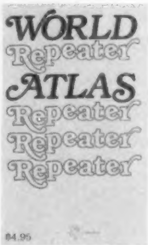

WORLD REPEATER ATLAS—Completely updated, over 230 pages of repeater listings are indexed by location and frequency. More than 50 maps pinpoint 2000 repeater locations throughout the USA. Foreign listings include Europe, the Middle East, South America, and Africa. $4.95* BK7315

THE MAGIC OF HAM RADIO—by Jerrold Swank W8HXR. Under various callsigns, W8HXR has been heard on the ham bands since 1919. He has watched amateur radio grow from the days of Model A spark coils to an era of microprocessors and satellite communications. Jerry has responded to calls for help from earthquake-striekn Managua and tornado-ravaged Xenia. Antarctica, one of man's loneliest outposts, has been a bit less lonely, thanks to Jerry's tireless phonepatching efforts. Drawing on his own colorful experiences and those of many other hams, Jerry has compiled this word-picture of ham radio during the past six decades. BK7312 $4.95

A GUIDE TO HAM RADIO—by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC license. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. $4.95.* BK7321

WORLD RADIO TV HANDBOOK 1982, 25TH EDITION—This book is the bible of international broadcasters, providing the only authoritative source of exact information about broadcasting and TV stations world wide. This 1981 edition is completely revised, giving comprehensive coverage of short, medium and long wave, 560 pages of vital aspects of world listening. $16.50. BK1184

*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop ● Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. $1.50 for the first book, $1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail $10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

ADVERTISERS

***Please contact these advertisers directly.**
To receive full information from our advertisers please complete the postage-paid card.

R. S. No.	Advertiser	Page
2	AEA/Advanced Electronic Applications	79, 88, 115, 126, 165
115	*A5 ATV Magazine*	173
164	A & W Productions	38
448	Advanced Communications International	79
124	Advanced Computer Controls	97
*	Alaska Microwave Labs	121
475	Albia Electronics	67
20	All Electronics Corp.	173
193	Alpha Delta Communications	41
*	Amateur Electronic Supply	55, 69
5	Amateur-Wholesale Electronics	19, 87, 165
334	Amidon Associates	121
71	Applied Invention	154
483	Applied Invention	143
*	Associated Radio	112
186	Atomtronics	121
130	Auto Connect	40
*	Autek Research	165
11	Barker & Williamson, Inc.	41
305	Barry Electronics Corp.	59
439	Ben Franklin Electronics	173
153	Bit "O" Byte	155
157	Boman Industries	61
12	BEC/Bullet Electronics	186
*	Butternut Electronics Corp.	121
187	Call Letter Hats	145
92	Ceco Communications, Inc.	38
102	Centurion International	4
89	Clutterfree Modular Consoles	81
163	Com-Rad Industries	120
150	Commtek	133
382	Communications Concepts, Inc.	157
*	Communications Design	41
15	Communications Specialists	83, 113
184	Contemporary Electronics Products	145
190	Control Products Unlimited	155
152	CQ Products	39
*	Crown Micro Products	77
21	Current Development Corp.	161
106	Cushcraft Corp.	157
346	Data Service Co.	120
482	DenTron Radio Co., Inc.	142
*	DGM Electronics, Inc.	38
477	DGM Electronics, Inc.	143
*	Digi Com Engineering, Inc.	123
144	Digatek Corp.	175
57	Discount Ham Radio	62
425	Doppler Systems	124
453	EGE, Inc.	27
447	Electronic Hobby Innovations	144
146	Electronic Rainbow Industries, Inc.	12
*	Electrovalue Industrial, Inc.	173
24	Encomm, Inc.	50
400	Engineering Consulting Service	175
85	Faxscan, Inc.	123
23	Flesher Corp.	34
323	Fox-Tango Corp.	162, 165
151	Francis Enterprises, Inc.	131
149	G & R Design, Inc.	131
178	Galaxy Electronics	173
479	Ghost Fighters	141
37	Gillaspie & Associates	30
489	Gillaspie & Associates	140
143	GLB Electronics	154
*	Global Specialties	142
417	Gotham Antenna	162
195	Goldsmith Scientific Corp.	30
352	Grove Enterprises, Inc.	146
487	Guild Radio Rack	141
86	H & R Communications	77
31	Hal-Tronix	54
345	Hal Communications	17, 98, 99, 154, 155, 162
*	Ham Radio Outlet	3
33	Hamtronics, NY	188, 189
491	Hamtronics, NY	141
129	Harvey	33
303	Heath Co	109
320	Hoosier Electronics	86
*	ICOM	Cov. II, 100, 142, 149
78	Independent Crystal Supply	175
445	Instant Software Amateur Radio Programs	114, 163, 167
165	Integrated Electronics Unlimited	152
*	iRL	9
38	Jameco Electronics	191
*	Japan Radio Co.	13
72	JDL Industries	161
490	JL Industries	143
*	JWL Electronics	164
*	Kantronics, Inc.	39, 89
81	KDK Distributing Comp., Inc.	147
*	Kenwood	Cov. IV, 7, 102-107
*	KLM Electronics	96
452	Lewis Construction Co.	161
77	M-Squared Engineering, Inc	124
44	Macrotronics, Inc.	53
46	Maggiore Electronics	135
134	Martin Engineering	161
139	Memphis Amateur Electronics	146
47	MFJ Enterprises	73, 77, 79, 81
48	MHz Electronics	176-185
49	Micro Control Specialties	95
50	Microcraft Corp.	126, 157
51	Microlog	70, 71
196	Microtek	173
*	Mor-Gain	123
318	National Comm. Group Co.	33, 168
492	National Comm. Group Co.	148
412	Nemal Electronics	138
*	*Orbit* Magazine	54
*	P. C. Electronics	97, 168
*	Palomar Engineers	4, 88, 140
182	Peterson Electronics	175
176	Polar Research, Inc.	21
199	Proham Electronics	49
*	Proham Electronics	142
191	Pro-Search Electronics	15
61	Radio Amateur *Callbook*, Inc.	89
454	Radiokit	154, 159
493	Radio Society of Great Britain	150
397	Radio World	42, 126
105	Radios Unlimited	157
62	Ramsey Electronics	187, 192
185	Ramsey Electronics	155
147	Randall Sherman	162
*	RCA Service Co.	115
156	RF Electronics	161
171	Ridge Systems Co., Inc.	119
485	Riehl Time Corporation	141
133	Rivendell Associates	120
*	R. L. Drake	5, 31, 111
418	Rolin Distributors	89
*	RQ Service Center	173
65	S-F Amateur Radio Services	119
500	*73*	
	Books	127-130, 133, 169, 171
	Dealer Ad	167
	Moving	167
	Subscriptions	125, 147, 164, 173
	University Microfilms	133
194	Semi Conductor Super Mart	123
*	Simple Simon Electronics Kits	23
112	Sintec Co.	49
367	Slep Electronics	186
476	Smith Kettlewell Eye Research Foundation	142
*	SMP	126
162	Space Electronics	175
*	Spectronics	40, 190
68	Spectrum Communications	35
436	Spectrum International, Inc.	120
198	Speedcall Corp.	22
69	Surplus Electronics	175
192	Synergistic Systems	175
183	Tayco Communications	175
316	Telex Communications	42, 43
*	Ten-Tec, Inc.	91
170	TET Antenna Systems	97
480	TET Antenna Systems	141
*	The Antenna Bank	131
118	The Blacksburg Group	145
449	The Ham Shack	63
57	The Tuned Antenna	159
481	Thermax Corp	140
76	Trac Electronics	124
104	Trionyx Industries	69
197	Twin Oaks & Associates	96
*	Universal Communications	146
155	Universal Distributors	164
*	Universal Electronics	62
189	Universal Software	123
488	Universal Software	140
179	Users International Radio Club	164
*	V-J Products, Inc.	159
484	Valor Enterprises	142
*	Van Gorden Engineering	34, 39, 81, 119
311	Vanguard Labs	173
90	VoCom Products	40, 152
*	W9INN Folded Uniroid Antennas	145
302	W-S Engineering	124, 159
79	Wacom Products	119
478	Wayne R & D	143
80	Western Radio Electronics	121
154	Westland Electronics	115
83	Yaesu Electronics Corp.	Cov. III, 93, 194
486	Yaesu Electronics Corp.	143
336	Z Associates	175

BOOKS, ETC.

To order, complete the postage-paid card, or itemize your order including detailed credit card information or check and mail to: 73 Magazine/Mail Order Dept./Peterborough NH 03458.

Catalog#	Item	Price
73300	73 BACK ISSUE—BEFORE JULY 1980	$ 3.00
73350	73 BACK ISSUE—JULY 1980 THRU OCT. 1981	$ 3.50
73350P	73 BACK ISSUE—NOV. 1981 TO PRESENT	$ 3.50
73005	73 BACK ISSUE—5 YOUR CHOICE	$10.75
	Add $1.00 per magazine for shipping	
73010	73 BACK ISSUE—10 YOUR CHOICE	$16.00
73025	73 BACK ISSUE—25 YOUR CHOICE	$27.00
73125	73 BACK ISSUE—25 OUR CHOICE	$14.00
	Add $7.50 per order for shipping	
BK1196	ALL ABOUT CUBICAL QUAD ANTENNAS	$ 5.95
BK7384	ANNOTATED BASIC, VOL. 1	$10.95
BK7385	ANNOTATED BASIC, VOL 2	$10.95
BK1197	BEAM ANTENNA HANDBOOK	$ 5.95
BK7307	BEHIND THE DIAL	$ 4.95
BK7309	CHALLENGE OF 160	$ 4.95
BK1011	CMOS COOKBOOK	$10.50
CT7305	CODE TAPE—5 WPM	$ 4.95
CT7306	CODE TAPE—6 + WPM	$ 4.95
CT7313	CODE TAPE—13 + WPM	$ 4.95
CT7320	CODE TAPE—20 + WPM	$ 4.95
CT7325	CODE TAPE—25 + WPM	$ 4.95
CT7394	CODE TAPES (ANY FOUR ABOVE)	$15.95
BK1241	THE COMPLETE SHORTWAVE LISTENER'S HANDBOOK	$ 9.95
BK7308	THE CONTEST COOKBOOK	$ 5.95
BK7381	40 COMPUTER GAMES	$ 7.95
BK1244	EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TV	$ 9.95
BK7321	A GUIDE TO HAM RADIO	$ 4.95
BK7322	HOBBY COMPUTERS ARE HERE	$ 2.47
BK1201	HOW TO DEFEND YOURSELF AGAINST RADAR	$ 6.95
BK1028	IC OP AMP COOKBOOK	$14.95
BK1230	INTERFERENCE HANDBOOK	$ 8.95
BK7386	KILOBAUD KLASSROOM	$14.95
BK7312	MAGIC OF HAM RADIO	$ 4.95
BK7340	THE NEW HOBBY COMPUTERS	$ 2.47
BK7383	THE NEW WEATHER SATELLITE HANDBOOK	$ 8.95
CT7300	NOVICE THEORY TAPES	$15.95
BK7310	OWNER REPAIR OF RADIO EQUIPMENT	$ 7.95
BK1185	THE PRACTICAL HANDBOOK OF FM REPEATERS	$12.95
BK7302	PROPAGATION WIZARD'S HANDBOOK	$ 6.95
QW0250	QSL CARDS—STYLE W—250	$ 8.95
QW0500	QSL CARDS—STYLE W—500	$13.95
QX0250	QSL CARDS—STYLE X—250	$ 8.95
QX0500	QSL CARDS—STYLE X—500	$13.95
QY0250	QSL CARDS—STYLE Y—250	$ 8.95
QY0500	QSL CARDS—STYLE Y—500	$13.95
BK1199	THE RADIO AMATEUR ANTENNA HANDBOOK	$ 6.95
BK1044	RF & DIGITAL TEST EQUIPMENT	$ 5.95
BK1016	73 DIPOLE & LONG WIRE ANTENNAS	$ 5.50
BX1000	SHELF BOX—1	$ 2.00
BX1001	SHELF BOXES—2-7	$1.50 each
BX1002	SHELF BOXES—8 AND UP	$1.25 each
BK1200	SIMPLE, LOW COST WIRE ANTENNAS FOR RADIO AMATEURS	$ 6.95
BK7311	SOME OF THE BEST FROM KILOBAUD	$10.95
BK7351	SSB THE MISUNDERSTOOD MODE	$ 5.50
SG7357	STUDY GUIDE—NOVICE CLASS	$ 4.95
SG7358	STUDY GUIDE—GENERAL CLASS	$ 6.95
BK1190	THE TEN METER FM HANDBOOK	$ 4.95
LB7360	TEST EQUIP LIB V2—AUDIO TESTERS	$ 4.95
LB7361	TEST EQUIP LIB V3—RADIO EQUIP	$ 4.95
LB7362	TEST EQUIP LIB V4—IC TEST EQ	$ 4.95
BK7387	TEXTEDIT—WORD PROCESSING KIT	$9.97
DS7387	TEXTEDIT—DISK	$19.97
BK7348	TOOLS & TECHNIQUES	$ 4.95
BK1063	TTL COOKBOOK	$ 9.50
BK1064	TVT COOKBOOK	$ 9.95
BK7382	UNDERSTANDING & PROGRAMMING MICROCOMPUTERS	$10.95
BK7368	VHF ANTENNA HANDBOOK	$ 5.95
BK1198	VHF HANDBOOK FOR RADIO AMATEURS	$ 6.95
BK1202	WORLD PRESS SERVICE FREQUENCIES	$ 7.95
BK1184	WORLD RADIO TV HANDBOOK	$16.50
BK7315	WORLD REPEATER ATLAS	$ 2.00

SHIPPING AND HANDLING CHARGES: $1.50 for the first book, $1 for each additional book for US delivery and foreign surface, $10 per book for foreign airmail.

READER SERVICE

A. My vote for the most interesting ad in this issue goes to____________ ____________(company) whose reader service number is____________.

B. During the past 12 months, I have spent the following amount on ham radio equipment:
- ☐1. $0-$50
- ☐2. $51-$100
- ☐3. $101-$250
- ☐4. $251-$500
- ☐5. $501-$1,000
- ☐6. Over $1,000

C. During the next 12 months, I anticipate spending the following on ham radio gear:
- ☐1. $0-$50
- ☐2. $51-$100
- ☐3. $101-$250
- ☐4. $251-$500
- ☐5. $501-$1,000
- ☐6. Over $1,000

D. I currently own/use the following:
- ☐1. Low-band transceiver
- ☐2. 2m FM mobile transceiver
- ☐3. Handie-talkie
- ☐4. 2m multi-mode transceiver
- ☐5. HF linear amplifier
- ☐6. 2m linear amplifier
- ☐7. Microcomputer
- ☐8. Printer
- ☐9. Antenna tuner
- ☐10. Oscilloscope
- ☐11. Digital Multimeter
- ☐12. RTTY T.U.
- ☐13. HF antenna
- ☐14. 2m mobile antenna
- ☐15. 2m fixed antenna
- ☐16. Keyer
- ☐17. CW keyboard
- ☐18. TVRO system
- ☐19. SSTV gear
- ☐20. OSCAR gear
- ☐21. Repeater
- ☐22. Tower
- ☐23. CB rig
- ☐24. Scanner
- ☐25. SWL receiver

During the next 12 months, I anticipate purchasing the following:
- ☐26. Low-band transceiver
- ☐27. 2m FM mobile transceiver
- ☐28. Handie-talkie
- ☐29. 2m multi-mode transceiver
- ☐30. HF linear amplifier
- ☐31. 2m linear amplifier
- ☐32. Microcomputer
- ☐33. Printer
- ☐34. Antenna tuner
- ☐35. Oscilloscope
- ☐36. Digital multimeter
- ☐37. RTTY T.U.
- ☐38. HF antenna
- ☐39. 2m mobile antenna
- ☐40. 2m fixed antenna
- ☐41. Keyer
- ☐42. CW keyboard
- ☐43. TVRO system
- ☐44. SSTV gear
- ☐45. OSCAR gear
- ☐46. Repeater
- ☐47. Tower
- ☐48. CB rig
- ☐49. Scanner
- ☐50. SWL receiver

E. During the past 12 months, I have dropped my subscription to:
- ☐1. *Ham Radio*
- ☐2. *CQ*
- ☐3. *QST*
- ☐4. *73*

F. I believe the technical content of *Ham Radio* is:
- ☐1. Too complex
- ☐2. Just right
- ☐3. Too simple
- ☐4. Don't know

G. I believe the technical content of *CQ* is:
- ☐1. Too complex
- ☐2. Just right
- ☐3. Too simple
- ☐4. Don't know

H. I believe the technical content of *QST* is:
- ☐1. Too complex
- ☐2. Just right
- ☐3. Too simple
- ☐4. Don't know

I. I believe the technical content of *73 Magazine* is:
- ☐1. Too complex
- ☐2. Just right
- ☐3. Too simple
- ☐4. Don't know

J. If you are not a subscriber, please circle 500.

Reader Service: Return this card to receive full information on the products advertised in this issue. Refer to the add. You will find numbers near the logo of each advertiser. Each represents the advertiser's individual Reader Service Number. Circle the corresponding numbers on the card on this page, include your name, address & zip, and drop in a mailbox. In 4-6 weeks you'll hear from the advertiser directly.

This card valid until January 31, 1982

1	6	11	16	21	126	131	136	141	146	251	256	261	266	271	376	381	386	391	396
2	7	12	17	22	127	132	137	142	147	252	257	262	267	272	377	382	387	392	397
3	8	13	18	23	128	133	138	143	148	253	258	263	268	273	378	383	388	393	398
4	9	14	19	24	129	134	139	144	149	254	259	264	269	274	379	384	389	394	399
5	10	15	20	25	130	135	140	145	150	255	260	265	270	275	380	385	390	395	400
26	31	36	41	46	151	156	161	166	171	276	281	286	291	296	401	406	411	416	421
27	32	37	42	47	152	157	162	167	172	277	282	287	292	297	402	407	412	417	422
28	33	38	43	48	153	158	163	168	173	278	283	288	293	298	403	408	413	418	423
29	34	39	44	49	154	159	164	169	174	279	284	289	294	299	404	409	414	419	424
30	35	40	45	50	155	160	165	170	175	280	285	290	295	300	405	410	415	420	425
51	56	61	66	71	176	181	186	191	196	301	306	311	316	321	426	431	436	441	446
52	57	62	67	72	177	182	187	192	197	302	307	312	317	322	427	432	437	442	447
53	58	63	68	73	178	183	188	193	198	303	308	313	318	323	428	433	438	443	448
54	59	64	69	74	179	184	189	194	199	304	309	314	319	324	429	434	439	444	449
55	60	65	70	75	180	185	190	195	200	305	310	315	320	325	430	435	440	445	450
76	81	86	91	96	201	206	211	216	221	326	331	336	341	346	451	456	461	466	471
77	82	87	92	97	202	207	212	217	222	327	332	337	342	347	452	457	462	467	472
78	83	88	93	98	203	208	213	218	223	328	333	338	343	348	453	458	463	468	473
79	84	89	94	99	204	209	214	219	224	329	334	339	344	349	454	459	464	469	474
80	85	90	95	100	205	210	215	220	225	330	335	340	345	350	455	460	465	470	475
101	106	111	116	121	226	231	236	241	246	351	356	361	366	371	476	481	486	491	496
102	107	112	117	122	227	232	237	242	247	352	357	362	367	372	477	482	487	492	497
103	108	113	118	123	228	233	238	243	248	353	358	363	368	373	478	483	488	493	498
104	109	114	119	124	229	234	239	244	249	354	359	364	369	374	479	484	489	494	499
105	110	115	120	125	230	235	240	245	250	355	360	365	370	375	480	485	490	495	500

Name____________________________________

Address____________________________________

City ____________________ State______ Zip______

73 Magazine • December 1982

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY MAIL

FIRST CLASS PERMIT #29 P. O. BOX 326 DALTON MA 01226

POSTAGE WILL BE PAID BY ADDRESSEE

73 MAGAZINE
P.O. Box 326
Dalton, MA 01226-0326

CUSHCRAFT

A3 3 Element Triband Beam	$167.00
A4 4 Element Triband Beam	$204.00
A743 7 & 10 MHz Add On for A3	$55.00
A744 7 & 10 MHz Add On for A4	$55.00
AV3 3 Band Vertical 10-20m	$41.00
AV4 4 Band Vertical 10-40m	$82.00
AV5 5 Band Vertical 10-80m	$88.00
R3 14,21,28 MHz Ringo	$204.00
32-19 Boomer 19 Element 2m	$75.00
214B Jr. Boomer 14 Element 2m	$61.00
A147-11 2m 11 Element Antenna	$34.00
A147-4 2M 4 Element Antenna	$23.00
ARX-2B 134-164 MHz Ringo Ranger II	$34.00
A144-10T 145 MHz 10 Element	$41.00
A432-20T 432 MHz 20 Element	$41.00
A14T-MB Twist Mounting Boom & Bracket	$21.00

Full Line Available on Sale.Call.

ROHN

20G 10 ft. Stacking Section	$32.00
25G 10 ft. Stacking Section	$39.50
45G 10 ft. Stacking Section	$87.50
25AG 2,3 or 4 Top Section	$52.50
HDBX 48 48 ft. Free Standing Tower	$320.00
HBX56 56 ft. Free Standing Tower	$340.00
FK2548 48 ft. 25G Foldover Tower	$725.00*
TB3 Thrust Bearing	$48.00
SB25G Short Base for 25G	$16.50
BPH25G Hinged Base Plate	$59.75
AS25G Accessory Shelf	$9.50
HB25AG 14" House Bracket	$14.50
BPC25G Cement Base Plate	$32.00
BAS25G Short top section w/acc. shelf	$36.00
M200 16 gauge, 10 ft. 2" O.D. Mast	$19.50
M200H 1/8" wall, 10 ft. 2" O.D. Mast	$36.00

Freight prepaid on Fold-over towers. Prices 10% higher west of Rocky Mts.

MINI-PRODUCTS

HQ-1 Mini-Quad 6/10/15/20m Antenna	$129.95
B-24 2 Element HF Mini-Beam 6/10/15/20m	$99.00
RK-3 3rd Element Add-on for B-24. Improves 10-20m	$67.00
C-4 Mini-Vertical 6/10/15/20m	$59.00

The Antenna Bank
(703) 569-1200

HUSTLER

4BTV 40-10 Mtr. Vertical		$79.00
5BTV 80-10 Mtr. Vertical		$100.00
M01/M02 HF Mobile Mast		$18.00
HF Mobile Resonators.	**Std. 400W**	**SUPER 2KW**
10 or 15m	**$9.00**	$13.00
20m	**$11.00**	$16.00
40m	**$13.00**	$18.00
75 or 80m	**$14.00**	$29.00
BM-1 Bumper mt. with S.S. Strap		$13.00
SSM-2 Commercial S.S. Ball		$14.00
SF-2 5/8 Wave, 2 Meter Antenna		$9.00
HOT Hustloff Mt. with Swivel ball		$14.00
G6-144B 2M Colinear, fixed Station, 6db		$68.00
G7-144 2M Colinear, fixed Station, 7db		$99.00

Full Line Available on Sale Call

VISA **ORDERS ONLY** master charge

800-336-8473

- Shipping charges not included
- Prices subject to change without notice
- Limited quantities
- No COD's

Van Gordon and B&W in stock at special prices.

HY-GAIN

TH3JRS Jr. Thunderbird, 750W PEP	$150.00
HQ-2S Hy-Quad, 2 Element	$235.00
TH5DXS Thunderbird, 5 Element	$215.00
TH3MK3S Thunderbird, 3 Element	$195.00
TH2MK3S Thunderbird, 2 Element	$128.00
TH7DX Thunderbird, 7 Element	$336.00
392S TH6DXX Conversion Kit to TH7DX	$135.00
105BAS 5 Element 10m "Long-John"	$114.00
155BAS 5 Element 15m "Long-John"	$161.00
205BAS 5 Element 20m "Long-John"	$269.00
14AVQ/WBS 10-40m Vertical	$49.95
18AVT/WBS 10-80m Vertical	$87.50
V-2S Colinear Gain Vertical 138-174 MHz	$33.75
BN-86 Ferrite Balun, 10-80 meters	$13.00
HDR-300 Deluxe Rotor, Digital Readout	$378.00

★ SUPER HY-GAIN PACKAGE ★

HG52SS 52' Self Sup. Crank-Up
TH7DX Thunderbird, 7 Element
HM IV Rotor
COA (3) Coax Arms
HG-10 Mast Mast 10

25% OFF Free Freight

$1377 SALE SAVE $449.90

HG50MT2 50 ft. side sup. Crank-up tower
TH3MK3S 3 Element Thunderbird
CD-45 Rotor
COA 3 Coax-Arms
HG-5 Mast

25% OFF Free Freight

$1005.00 SALE SAVE $303.45

Philly Stran Guy Cable in stock

NO SUBSTITUTIONS PLEASE

ROTORS & CABLES

CDE HAM IV Rotor	$175.00
CDE T2X Rotor	$244.00
CDE 45 Rotor	$92.00
Alliance HD-73 Rotor	$92.00
Alliance U100 Rotor	$42.00
RG-8/U Foam Coax 95% Shield	24¢/ft.
RG-213 Coax, Mil. Spec.	28¢/ft.
Mini-8 Coax 95% Shield	12¢/ft.
Rotor Wire 8 Conductor	16¢/ft.
4 Conductor	7.5¢/ft.

NEW FAST CHARGE For Your Battery Packs

RECHARGE YOUR HAND HELD RADIO BATTERY PACKS TO FULL CAPACITY IN AS LITTLE AS 45 min. EXAMPLE—Fully Charge ICOM BP3 in 30-45 Minutes.

SEPERATE FUSES PROVIDED INTERNALLY FOR A.C. AND D.C. OPERATION. —BUILT IN REVERSE POLARITY PROTECTION.

ONE UNIT DOES IT ALL

Charge, ICOM, YAESU, KENWOOD, TEMPO, SANTEC and Others Automatically in Your Home, Car, Boat, R.V. or Airplane with Built-in Heavy Duty Power Supply or 12 to 24 V. External D.C. Supply Such as Cigar Lighter in Your Car.

All Solid State
Precision Components Used Throughout, In A Unique Circuit Allows Fast Changing Without Any Perceptible Heating Of Cells. Charger Measures Remaining Charge In Cells Constantly And Turns Off Automatically When Battery Is Fully Charged. Battery Can Be Left Connected Indefinitely.

START
CHG
HIGH
LOW
CURRENT
VOLTAGE
G-R
ACCU-CHARGER PROGRAMMABLE-1
ICOM
IC-BP4

INCLUDES: Removable 6 Ft. Cord for A.C. Operation and 2 Mating Connectors for D.C. Input and Battery Leads.

FEATURES: High Quality, Custom Designed Heavy Gauge Aluminum Cabinet.

FULL 1 YR. WARRANTY ON PARTS AND WORKMANSHIP

ACCESSORY CONNECTOR TO FIT ICOM BATTERY PACKS, BP-2, BP3, BP4, BP5, $3
PRE-PAID ORDERS INCLUDE $3 SHIPPING & HANDLING

$79.00
CALIF. RESIDENTS INCLUDE 6% TAX

PHONE ORDERS—CALL [209] 586-7059

MAIL PRE-PAID ORDERS TO:

G&R DESIGN INC
P.O. BOX 4463 SONORA, CALIF. 95370

DEALER INQUIRIES INVITED

↙149

FRANCIS ENTERPRISES INCORPORATED
P.O. Box 906
Poplar Bluff, Mo.
314-989-3248
WE ARE LOCATED 11 MI. SO. ON 67 HWY.

We Build Quality Into Our Products

MANUFACTURERS | DISTRIBUTORS
GRAIN BINS · INDUSTRIAL · ELECTRICAL · IRRIGATION EQUIP.

Satellite Television

Whether you need 1 system or 100 we have the highest quality antenna to meet your utmost expectations and quality standards, at easy to live with prices.

Send:
$7.95 for Introduction to Satellite manual.

Pictured is our 11 ft Dish with our easy setting one man installation trailer.

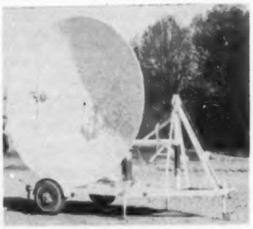

↙151

Write or call us for more information.

CIRCUITS

Do you have a technique, modification, or easy-to-duplicate circuit that your fellow readers might be interested in? If so, send us a concise description of it (under two pages, double-spaced) and include a clear diagram or schematic if needed.

In exchange for these technical gems, 73 offers you the choice of a book from the Radio Bookshop, to be sent upon publication. Submit your idea (and book choice) to: Circuits, Editorial Offices, 73 Magazine, Peterborough NH 03458. Submissions not selected for publication will be returned if an SASE is enclosed.

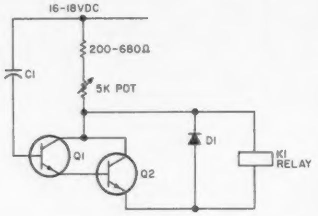
16-18VDC
200-680Ω
C1
5K POT
D1
K1
RELAY
Q1
Q2

Fig. 1.

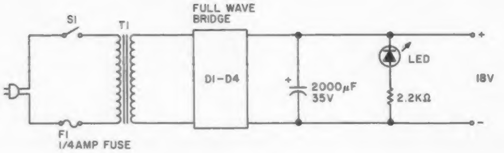
S1
T1
FULL WAVE
BRIDGE
D1-D4
2000µF
35V
LED
2.2KΩ
+
18V
-
F1
1/4AMP FUSE

Fig. 2.

THE KEYLESS KEYER: This circuit can be used to key a transmitter with just a touch. In Fig. 1, Q1 and Q2 are any NPN transistors. C1 can be any disc capacitor. Make sure the leads are long enough so that you can touch them. When the leads are shorted by your finger, the small signal from your body makes the relay drop from 5 volts to less than one volt. The relay toggles. The SPDT leads of the relay can be used to key a transmitter. No dangerous voltages pass through the capacitor. Diode D1 suppresses any high inductive kickback and thus protects the transistors. Use either two 9-volt batteries in series or build the power supply shown. The LED and 2.2-kilohm resistor serve to indicate when the supply is on and to bleed off any dangerous voltages from the 2000-uF capacitor.—Alan Weinberg KR7D, Tucson AZ.

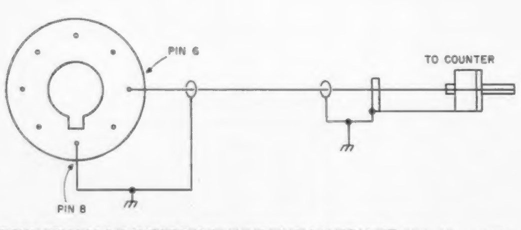
PIN 6
TO COUNTER
PIN 8

FREQUENCY ADJUSTMENT FOR THE YAESU FT-101: You can use an ordinary frequency counter to tell if your FT-101 is slightly off frequency. Pin 6 on the rig's accessory plug is connected to the vfo output, while pin 8 is ground. Connect a frequency counter to these two pins and check to see if the radio has the same frequency on transmit and receive. The counter will display the vfo frequency — between 8.7 and 9.2 MHz—not the frequency shown on the main dial. You can correct for any difference between the transmit and receive frequency by adjusting the control marked zero, located under the top cover.—Doc Hall W8ZJQ, Elyria OH.

SB-220 ORIGINAL ALC CKT

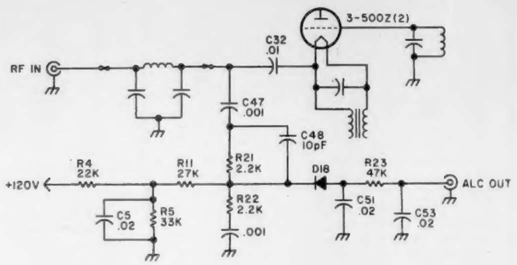
3-500Z(2)
C32
.01
RF IN
C47
.001
C48
10pF
R4
22K
R11
27K
R21
2.2K
D18
R23
47K
+120V
ALC OUT
C5
.02
R5
33K
R22
2.2K
C51
.02
C53
.02
.001

ALC THRESHOLD MOD

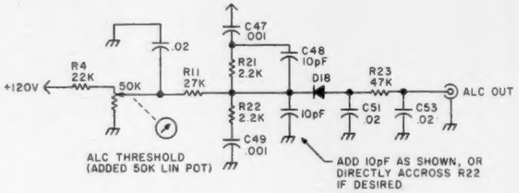
C47
.001
.02
C48
10pF
R4
22K
R11
27K
R21
2.2K
D18
R23
47K
+120V
50K
ALC OUT
R22
2.2K
10pF
C51
.02
C53
.02
C49
.001
ALC THRESHOLD
(ADDED 50K LIN POT)
ADD 10pF AS SHOWN, OR
DIRECTLY ACCROSS R22
IF DESIRED

ALTERNATE MOD

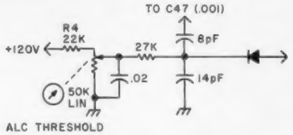
TO C47 (.001)
R4
22K
+120V
27K
8pF
.02
14pF
50K
LIN
ALC THRESHOLD

THIS ALTERNATE MODIFICATION REMOVES R21, R22, C49, C48 AND SUBSTITUTES THE 8pF AND 14pF SHOWN. THIS INVOLVES MORE WORK REMOVING COMPONENTS FROM THE TIE STRIP AND HAS NO ADVANTAGE OVER THE MODIFICATION SHOWN ABOVE.

RELATIVE POWER METER CIRCUIT MOD

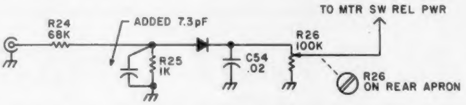
TO MTR SW REL PWR
R24
68K
ADDED 7.3pF
R25
1K
C54
.02
R26
100K
R26
ON REAR APRON

ALC MODIFICATION FOR THE HEATH SB-220: The ALC level in the Heath SB-220 is virtually unusable with the Collins 32S-3. This modification will provide an adjustable, stable ALC voltage for the SB-220. Install the ALC control in the front-panel position normally occupied by the Relative Power Sensitivity control. The RPS control is then installed on the left rear chassis apron about 4½ inches inboard from the left side. By adding a small capacitor across the R25, the response is made more uniform with respect to frequency. After modification, set the RPS to a reading of 270-280 measured on the grid milliameter.—E. A. Wingfield W5FD, Little Rock AR.

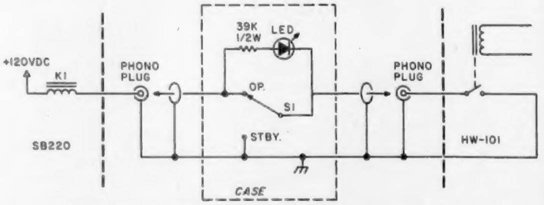
+120VDC
K1
PHONO
PLUG
SB220
39K
1/2W
LED
OP
S1
STBY.
CASE
PHONO
PLUG
HW-101

OPERATE-STANDBY SWITCH: This circuit is ideal for a linear amplifier, such as the SB-220, which does not have a standby switch. The circuit requires only three components and a miniature box in which to house them. When S1 is in the OP mode, the 39-kilohm resistor and LED are shorted. Thus, when K1 is energized, the linear is on the air. In the STBY mode, the LED cathode is grounded and energizes. Selection of the resistor is critical: If too low a value, the relay will close in the STBY mode. The exciter can be tuned for maximum power with the antenna connected through the linear's bypass relay. S1 is then switched to OP and the linear can be loaded into the antenna.—F. T. Marcellino W3BYM, Rockville MD.

HAM HELP

I would like to obtain schematics or manuals for the following:

- E. F. Johnson "Ultracom" 30-50-MHz FM transceiver
- Tempo One 80-10-meter transceiver (the black version)
- Unimetrics "Dura-Scan" 30-50-MHz scanner
- Lafayette "Micro" P-50 30-50-MHz tunable FM receiver
- J. C. Penney model 6237A citizens band transceiver
- Kris model XL-70 citizens band transceiver
- International Crystal "Executive" model 1500 citizens band transceiver
- Heath HP-20 power supply

If copies are sent, please specify if they are to be returned or are for me to keep.

Gary B. Trustie WB8SPV
424 Franklin Ave.
Waverly OH 45690

I am looking for:

- Someone who has modified a Heath HD-1410 keyer for use with a Hallicrafters HT-37 transmitter.
- Firms who sell Motorola MV1404 tuning diodes; MAN-1, MAN-64, and MAN-6680 LED displays; and .25% to 1% precision resistors with values of 243k Ω, ⅛ W, 11.2k Ω, ⅛ W, 2.43k Ω, ⅛ W, and 243 Ω, ⅛ W. Since the resistors are special items, the firms must be able to conduct business with an individual buying very small quantities.

Paul Kemp WB0CJB
1025 E. Loula
Olathe KS 66061

I would like to find manuals or schematics for the following:

- AMPEX model CC323 TV camera
- AIL model R1283/GRC receiver
- AIL model IP805/GRC display
- Tektronix model 1401A spectrum analyzer
- Dumont model 1062 oscilloscope
- model DM10-12A0-16-A04 video display

Fred Wolf N5ARO
1920 Ridgelawn Dr.
Gautier MS 39552

I am looking for the instruction manual, service manual, and any modifications for the Tennelec Memoryscan MS-2. I also need the service manual and paperwork for the Motorola LO3GB transceiver. I will pay for postage and copying costs.

Mark Kiziuk N2DMI
2623 E. 11th St.
Brooklyn NY 11235

I need an Eico or similar VFO for a local Novice study group.

G. Samkofsky N4ZB
1420 Mt. Vernon Dr.
Holiday FL 33590

Wanted: drive belts for an Aiwa TP708 4" reel-to-reel tape recorder, as well as schematics and info on how to build a good communications receiver.

Derek H. Rout
3-137 Champion St.
Christchurch, New Zealand

Wanted: an external vfo for the Sears 412.35730600 2-meter FM rig or a schematic of it. I will pay postage for the schematic.

SSG Gary E. Kohtala DA2XF
USAFS-A Box 1415
APO NY 09458

I am looking for a Hunter Bandit linear amplifier.

Ray Warner W7JU/K7JU
2200 Jamaica Cove
Riviera AZ 86442

SOCIAL EVENTS

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received at 73 Magazine by the first of the month, two months prior to the month in which the event takes place. Mail to Editorial Offices, 73 Magazine, Pine Street, Peterborough NH 03458.

FARIBAULT MN
DEC 4

The annual Handi-Ham Winter Hamfest will be held on Saturday, December 4, 1982, at the Eagles Club, Faribault MN. Registration will start at 9:00 am, followed by a Handi-Ham equipment auction, dinner at noon, and a program. Talk-in on .19/.79. For more information, contact Don Franz W0FIT, 1114 Frank Avenue, Albert Lea MN 56007.

HAZEL PARK MI
DEC 5

The 17th annual Hazel Park Amateur Radio Club Swap and Shop will be held Sunday, Dec. 5, at Hazel Park High School, Hazel Park MI. Hazel Park High School is located on Hughes Street at 9½ Mile Rd., 1 mile east of I-75. Tickets are $1.50 in advance or $2.00 at the door. Tables are $1.00 per foot. Doors open at 8:00 am. Plenty of food and parking will be available. Talk-in on 146.52. For tickets, table reservations, and information, send an SASE to Hazel Park Amateur Radio Club, PO Box 368, Hazel Park MI 48030 or telephone (313)-398-3189.

SOUTH BEND IN
JAN 2

A hamfest swap & shop will be held on Sunday, January 2, 1983, at Century Center, downtown on US 33 One Way North between the St. Joseph Bank building and the river, South Bend IN. Tables are $3.00 each in a carpeted, half-acre room. The Industrial History Museum is in the same building. Four-lane highways lead to the door from all directions. Talk-in on .52/.52, .99/.39, .93/.33, .78/.18, .69/.09, 145.43, and 145.29. For more information, contact Wayne Werts K9IXU, 1889 Riverside Drive, South Bend IN 46616, or phone (219)-233-5307.

RICHMOND VA
JAN 16

The Richmond Amateur Telecommunications Society will hold Richmond Frostfest '83, the annual winter ham radio and computer show, on Sunday, January 16, 1983, at the state fairgrounds, Richmond VA. General admission is $4.00. All flea-market and commercial exhibit spaces will be indoors in a 30,000-square-foot exhibit building.

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION (Required by 39 U.S.C. 3685). 1. Title of publication, *73: Amateur Radio's Technical Journal.* 2. Date of filing, Oct. 1, 1982. 3. Frequency of issue, Monthly. A. No. of issues published annually, 12. B. Annual subscription price, $25.00. 4. Location of known office of publication (Street, City, County, State and ZIP Code) (Not printers), 80 Pine Street, Peterborough, Hillsboro County, N.H. 03458. 5. Location of the headquarters or general business offices of the publishers (Not printers), 80 Pine Street, Peterborough, Hillsboro County, N.H. 03458. 6. Names and complete addresses of publisher, editor and managing editor. Publisher (Name and Address), Wayne Green, Peterborough, N.H. 03458. Editor (Name and Address), Wayne Green, Peterborough, N.H. 03458. Managing Editor (Name and Address), Jack Burnett, 12-C Granite St., Peterborough, N.H. 03458. 7. Owner (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given. If the publication is published by a nonprofit organization, its name and address must be stated.) Name, 73, Inc., Peterborough, N.H. 03458. Wayne Green, Peterborough, N.H. 03458. 8. Known bondholders, mortgagees and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities (if there are none, so state) Name, none. 9. For completion by nonprofit organizations authorized to mail at special rates (Section 411.3, DMM only). The purpose, function and nonprofit status of this organization and the exempt status for Federal income tax purposes (check one) Not applicable. 10. Extent and nature of circulation. (X) Average No. copies each issue during preceding 12 months. (Y) Actual No. copies of single issue published nearest to filing date. A. Total No. of copies printed (Net Press Run) (X) 69,828 (Y) 66,216. B. Paid circulation 1. Sales through dealers and carriers, street vendors and counters sales, (X) 11,858 (Y) 14,108. 2. Mail subscriptions (X) 47,906 (Y) 45,454. C. Total paid circulation (Sum of 10B1 and 10B2) (X) 59,764 (Y) 59,562. D. Free distribution by mail, carrier or other means, samples, complimentary, and other free copies (X) 446 (Y) 451. E. Total distribution (Sum of C and D) (X) 60,210 (Y) 60,013. F. Copies not distributed 1. Office use, left over, unaccounted, spoiled after printing (X) 6,355 (Y) 6,203. 2. Returns from news agents (X) 3,263 (Y) 0 G. Total (Sum of E, F1 and 2—should equal net press run shown in A) (X) 69,828 (Y) 66,216. 11. I certify that the statements made by me above are correct and complete. Signature and title of editor, publisher, business manager, or owner. Debra Wetherbee, Business Manager.

PRESERVE
73 MAGAZINE
BINDERS &
FILE CASES

Keep your issues of 73 Magazine together, handy and protected in handsome and durable library files or binders. Both styles bound in red leatherette with the magazine logo stamped in gold.
Files: Each file holds 12 issues, spines visible for easy reference, $5.95 each, 3 for $17.00, 6 for $30.00
Binders: Each binder holds 12 issues and opens flat for easy reading. $7.50 each, 3 for $21.75, 6 for $42.00
(Postage paid in USA. Foreign orders include $2.50 per item)
Please state years: 1977 to 1983
Send check or money order to:
JESSE JONES BOX CORP.
P.O. Box 5120
Philadelphia, PA 19141
Allow 4 to 6 weeks for delivery

this publication is available in microform

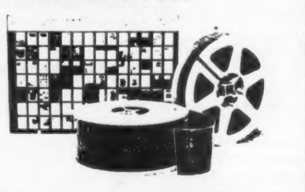

University Microfilms International

300 North Zeeb Road
Dept. P.R.
Ann Arbor, MI 48106
U.S.A.

18 Bedford Row
Dept. P.R.
London, WC1R 4EJ
England

CONTACT-80...

An ultra sophisticated yet simple to operate RTTY System for the demanding operator at an affordable price.

Features:
- Disk I/O; SAVE, LOAD, KILL & DIR...
- TRI-SPLIT screen, user defined...
- 10 CANNED MESSAGES
- DYNAMIC BUFFER ALLOCATION...
- Live HARDCOPY for parallel printers...
- Keyboard CONTROL of STATION...
- AUTO-ID; RTTY, CW (selectable ON/OFF)...
- CLOCKED OUTPUT rate...
- All BAUDOT speeds plus ASCII (110)...
- NAME, DATE, TIME from computer...
- On screen BIT PATTERN SCOPE...

Requires TRS-80, MOD-III with your CALL SIGN plus TU with 60ma loop.
DISK I/O; VERSION..................$279.00
CASSETTE I/O; VERSION............$229.00
Post Paid

CommTek

✓150

4493 Orleans Dr., Dunwoody, GA 30338
(404) 946-9314

✓See List of Advertisers on page 130

RTTY LOOP

Marc I. Leavey, M.D. WA3AJR
4006 Winlee Road
Randallstown MD 21133

For the past few days, I have been reading a book that has struck a responsive chord within me. Detailing some of the goings on behind the scenes of my favorite radio show, National Public Radio's "All Things Considered," the book describes how the show starts with the rudimentary outline first laid out in a morning conference, goes through edits and revisions, and then bursts upon the public at 5:00 pm sounding fresh and spontaneous.

The reason for the empathy I feel is the way RTTY Loop falls together each month. For the December issue, for example, I usually try to take a look at items which could be given as gifts to the ham involved in RTTY or computers, "'tis the season," and all that. Several rough outlines are penciled in over the months until now, when I try to assemble an exciting column.

Well, yes, Maryland (Virginia is a bit to my south), there is a Serendipity. For just as I was casting around, looking for something novel or unique, what comes in the mail but a packet from Tom Harrington of Universal Electronics, Inc.

Tom, you may recall, is the gentleman who produced the book *World Press Service Frequencies*, a tome reviewed in RTTY Loop back in August, 1981. For those who came in late, I shall explain. This publication, now in its third edition, covers the full specs on over 65 stations transmitting press information worldwide in English. Also covered is information on antennas, terminal units, and the like. Well, Tom has a few more goodies up his sleeve. A giant *List of Worldwide Radioteletype Stations in Frequency Order* contains 2198 frequencies of stations logged this year. The frequency, callsign, name of station, ITU country symbol, times of reception, and details are included. Over eighty press and news agencies are listed, along with weather, military, and other services using RTTY.

Not to stop there, Tom has another rather unusual offering. Did you know that there is a five-level code for Arabic, Cyrillic, Hebrew, Greek, and Korean—not to mention a six-level Japanese code? If we throw in Hebrew, Arabic, Cyrillic, Greek, and Japanese Morse codes and then top it all with over 500 identified Arabic words and station names in RTTY, would you be interested? Well, Tom's new work, *List of Special RTTY and CW Alphabets and Codes*, has all this, plus quite a bit more. Write to Tom at Universal Electronics, Inc., 1280 Aida Drive, Dept. L, Reynoldsburg OH 43068. Use order code "R" for the *Worldwide Stations* list, $12; order "P" for the *Press Service* list, $8; and "X" for the *RTTY and CW Code* booklet, $8. Be sure to mention RTTY Loop in the order, too, OK?

Before we leave Universal Electronics, and while we are on the subject of gifts, I think I have something for the high-powered RTTY types among you. Their Universal M-600 RTTY code receiver may be the ultimate demodulator on the market. This unit decodes signals using bit inversion, TOR, SITOR, and nonstandard shifts. Weather as well as standard format is supported with all speeds of ASCII, Morse, and Murray. Output is both standard video as well as ASCII or Murray printers, complete with a printer buffer of 2K. This brief description only summarizes the material I have in hand. I am sure that Universal would love to send you the full details if you drop them a note at the above address. At $799.95, this is quite a package.

If that's too much money for you, but you are looking for an object in the "sizable but not ridiculous" category, have you considered one of the new small microcomputers? For under $300, you can buy an Atari 400 (which has some of the finest graphics I have ever seen and can be expanded to a full system including disk), the TI99/4 (sold in many retail outlets), a Radio Shack Color Computer, or (pushing under the $100 mark), the Sinclair ZX-81, now marketed by Timex and widely discounted. These and other small computers can serve either as a first system or, as my Atari does, as an intriguing second computer for someone already afflicted with the computer bug.

Computers aside, and I will admit that it is becoming harder these days to put them there, there are quite a few products around that appeal to the RTTY buff. I don't know about your wife, but mine enjoys window-shopping during the holiday sale season. How do you window shop in a magazine? You look at the ads! Let's see what is available, right here in the pages of *73*. I must point out that information I have on some of these items is from literature or the advertisements themselves. If you want more details, write to the company, not to me. By the way, I recognize that many products covering a wide range are of interest to the amateur involved in RTTY, but let's look only at specific RTTY items. If you will follow me around the next corner . . .

I see that RCA is selling off old, used ASR-33 teleprinters. This is a usable terminal for ASCII circuits and would make a reasonable first start for the amateur interested in getting onto ASCII RTTY. We have covered the hookup of the ASR-33 in past RTTY Loops, and many hams have them on the air. Supporting uppercase ASCII only, these 110-baud machines include punched paper tape facilities. At $300, the price may be above what you would pay at a hamfest, but I presume the units are checked out and working. If you are interested, contact J. H. Bell at the RCA Service Company, Bldg. 204-2, Route 38, Cherry Hill NJ 08358.

Going from the earliest to one of the latest, Kantronics offers their "The Interface." For about $190, this box, plus software available separately, will put many popular microcomputers onto RTTY. Software for the Apple II computer is supplied on a diskette for about $30. Program boards, presumably containing ROMs, are available for the Atari 400/800 or VIC-20 for $50, or for the TRS-80C Color Computer for $60. Drop a line to Kantronics at 1202 E. 23rd Street, Lawrence KS 66044, for details.

Producing a fine stand-alone terminal, our old friend Microlog, located at 18713 Mooney Drive, Gaithersburg MD 20879 (just north of Washington DC), is still turning out their 6800-based systems. The ATR-6800, reviewed in this column some time back, is an expandable system which can be turned into a general purpose computer. Their newer ACT-1 (not to be confused with a simple computer terminal of the same name available a few years ago) is a dedicated RTTY/CW/SSTV computer. Both use the Motorola 6800 CPU, of which you all know I am quite fond, and appear to be very well engineered. The ACT-1 is a shade under $1000; I don't have a recent price on the ATR-6800. I'm sure the guys at MicrSolog would be happy to fill you in.

Another way to get onto computerized RTTY is with a package offered by Tufts Electronics, 61 Lowell Road, Hudson NH 03051. The experts up there will sell you the Kantronics interface detailed above, with a VIC-20 computer, cables, speaker, and instructions for the package price of $499, as of this writing. Sounds like it might be worth a peek.

Another advertised system is the MFJ Super Keyboard. This box operates on CW, Murray, ASCII, and as a memory keyer and Morse practice machine. Two versions are available. The MFJ-494 features a 50-character buffer, 30-character memory, and automatic messages, and sells for about $280. For another $60, the MFJ-496 increases the buffer and message memory to 256 characters each and adds serial numbering and a repeat message function. Options of AFSK keying, loop keying, and clock module are also available. Drop MFJ Enterprises, Inc., a letter at Box 494, Mississippi State MS 39762, if you would like further information.

We can't forget our old friends iRL, at 700 Taylor Road, Columbus OH 43230. Their two converters, the FSK-1000 and FSK-500 (reviewed in this column in the past), remain excellent products. They also tell me that they can interface their terminal units to many popular computer systems. Just ask them a question—they say they have the answer.

A common question in the mail has been whether there is an adapter made just for the TRS-80C Color Computer for RTTY. Well, Ridge Systems Co., Inc., is advertising their 4511 RTTY Interface. Selling for about $170, this ROM board supports Murray and ASCII, a split screen, and messages stored to cassette tape. Drop them a note at PO Box 772, Acton MA 01720, for more information.

Xitek, one of the first companies out with a single-board terminal, is still featuring their SCT-100 ASCII/Murray terminal. Listing at $229, it may be of interest to some of you. Their mailing address is PO Box 2952, Garland TX 75041.

Speaking of originals, Macrotronics, Inc., 1125 N. Golden State Blvd., Turlock CA 95380, was one of the first with interfacing to microcomputers. Their "TERMINALL" is a hardware/software system for the Apple II or TRS-80 (Model I or III) that combines terminal unit, computer interface, and bells and whistles into one neat package. For about $500, this is quite a system, supporting ASCII, Murray, or Morse.

Another computer interface, the ROM-116, is available from Crown MicroProducts, 606 State Street, PO Box 892-R, Marysville WA 98270. This package requires an external terminal unit and includes facilities to save text to disk along with other features similar to other systems. Write Crown for a brochure and pricing details.

The TRS-80 remains the most often supported computer for the RTTY interface, with another one offered by Commtek. Their Contact-80 is available for Model III disk or tape systems, selling for $279 or $229, respectively. With split screens, canned messages, date and time, and identifiers from the computer, this looks like a versatile package. Write them at 4493 Orleans Drive, Dunwoody GA 30338, if you are interested.

Another item we will look at in the window-shopping tour is a window in itself. AEA's MBA-RC reader/code converter. This decodes Morse, Murray, or ASCII and displays the data on a 32-character internal display. Not only that, but it can convert between codes, so that an old Murray machine could speak ASCII or Morse on the air. Looks quite interesting, and full details are available from the manufacturer, Advanced Electronic Applications, Inc., PO Box C-2160, Lynnwood WA 98036.

Last, but not least—by any means—is old standby Hal Communications, whose name is almost synonymous with RTTY. You have a complete choice of station accessories and options . . . enough to build a complete RTTY system or any part of it. For example, the HAL DS3100ASR and ST6000, when combined with the MS03100 Message Storage Option and a hard-copy printer, give you a top-notch station. If you're not prepared at this time to spend all your money on a complete layout, what about the RTTY tuning scope? HAL's RS2100 gives you an accurate display of the signal amplitude and phase of the received signal and a flock of other internal goodies. If you're a travelin' man, you'd like the HAL CWR-6850 Telereader . . . the smallest RTTY and CW terminal available, according to their specs, and complete with CRT display screen. Communicate with Hal Communications at PO Box 365, Urbana IL 61801.

You know, I often say to mention both *73* and RTTY Loop when you write an advertiser for information or to order something. Let me tell you why. This is not just to toot our own horns. Advertisers spend thousands of dollars putting their name and product before you in various media. They want to know which ones work, and where you hear of them, so that they can better direct future campaigns. The better directed the ads, the less "wasted" money, and the more that can go into better products for you and me. So, you see, telling them that you "saw it in *73*'s RTTY Loop column" is a wise move.

Still stumped for a gift? How about the one that comes a dozen times a year? Less than twenty bucks will get you a one-year subscription to *73*, the magazine that brings the active ham so much more of what you read magazines for. Besides, you wouldn't want to miss the next installment of RTTY Loop, would you?

HAM HELP

I am a wheelchair-bound amateur in need of equipment capable of working the MARS two- and six-meter bands. Please telephone me at (417)-561-4685 or write me.

Edward L. Maranville KA9COJ/AAT7GX
PO Box 512
Rockaway Beach MO 65740

I need a schematic and manual for a Hallicrafters CRX-2 (152-174 MHz) receiver. Any information will be sincerely appreciated. I will pay all costs involved, but please advise me of same first.

L. E. Taylor K9REB
Box 420
Mount Prospect IL 60056

FUN!

John Edwards KI2U
78-56 86th Street
Glendale NY 11385

HAM GEOGRAPHY

I'm always amazed at the average ham's grasp of geography. As if it weren't enough that most of us are already experts on electronic theory, radio propagation, and telegraphy, we can also claim a knowledge of virtually every square inch of this tired old planet's surface. Who else but a ham is intimately acquainted with such places as East and West Kiribati, Bajo Nuevo, Bouvet, and Chagos? When Great Britain and Argentina began fighting over a forsaken bit of territory known as the Falkland Islands, most of the world ran for an atlas. For hams, VP8-land was an old friend.

This month, Fun! tackles the field of ham geography. Think you know it all? Read on.

ELEMENT 1—CROSSWORD PUZZLE

(Illustration 1)

Across

1) G-land (2 words)
7) From
8) Eastern European land
11) Western state (abbr.)
12) New England state (abbr.)
13) Austria prefix
14) African country
16) To borrow
17) Agency involved in extreme DX (abbr.)
18) Arab country
21) Xmas in France
22) Type of power measurement (abbr.)
24) China (abbr.)
25) 49th state (abbr.)
26) This column
27) Vermont flow product
28) 0-land state (abbr.)
29) Green Mountain State (abbr.)
31) Soviet prefix
33) Midwest state (2 words)

Down

1) DL-land
2) Southern state (abbr.)
3) African country (abbr.)
4) Far East country (abbr.)
5) A ham radio commercial (abbr.)
6) Belonging to a group of northern states (2 words)
9) Face or type of cup
10) EP-land
13) Peru prefix
15) 6 down district number
19) EI-land
20) US York and Orleans
23) ___________New Guinea
26) ___________Lauderdale
29) India prefix
30) Chad prefix
32) Australia prefix

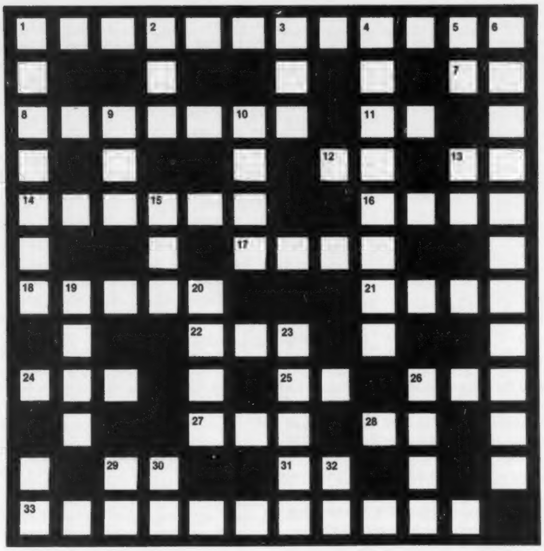

Illustration 1.

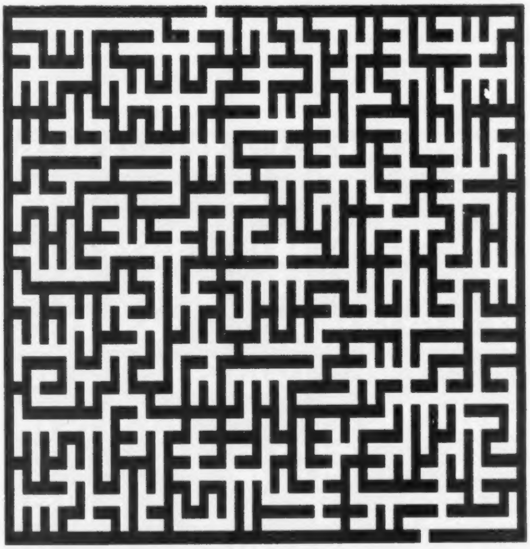

Illustration 2.

ELEMENT 2—MATCHING

Sure, you know all sorts of rare countries by prefix. But do you know their capital cities? Master this subject, and surprise your friend in Paraguay by asking him how things are doing in downtown Asuncion.

Column A	Column B
1) Malta	A) Bogota
2) Bulgaria	B) Reykjavik
3) Romania	C) Manila
4) Nepal	D) Tripoli
5) Maldives	E) Nicosia
6) Bhutan	F) Rangoon
7) Burma	G) Caracas
8) Philippines	H) Katmandu

Hi Pro LB-VHF-UHF REPEATERS
SOON TO BE FCC TYPE ACCEPTED

Hi Pro RECEIVER AND TRANSMITTER NOW USED IN ALL HI PRO REPEATERS

ASSEMBLED
SMALL SIZE
3 7/8 × 6 1/8"

HI PRO TRANSMITTER DESIGNED FOR REPEATER SERVICE WITH EXCELLENT AUDIO, STABILITY, HARMONIC REJECTION AND LOW SIDEBAND NOISE.

ADJUSTABLE POWER OUTPUT UP TO 5 WATTS FROM THE EXCITER BOARD COOL OPERATION

HI PRO RECEIVER THIS RECEIVER IS THE HEART OF THE REPEATER AND BOASTS SUPERIOR SQUELCH ACTION NEEDED FOR THIS TYPE OF SERVICE EXCELLENT SENSITIVITY, STABILITY AND SELECTIVITY

USE THIS RECEIVER TO REPLACE THAT TROUBLESOME RECEIVER IN YOUR PRESENT REPEATER

ASSEMBLED
SMALL SIZE
3 7/8 × 6 1/8"

ASK ABOUT OUR NEW COMPUTER CONTROL SYSTEM AND MICROCONTROL AUTO PATCH

Maggiore Electronic Laboratory ✓46
590 SNYDER AVE.
WEST CHESTER, PA. 19380
TELEX: 499-0741-MELCO
PHONE 215-436-6051

9) Indonesia
10) Australia
11) Algeria
12) Senegal
13) Nigeria
14) Libya
15) Sudan
16) Angola
17) Venezuela
18) Colombia
19) Cyprus
20) Turkey
21) Iceland
22) Iraq
23) Pakistan
24) Fiji
25) Surinam

I) Baghdad
J) Lagos
K) Luanda
L) Islamabad
M) Sofia
N) Suva
O) Paramaribo
P) Djakarta
Q) Khartoum
R) Valletta
S) Dakar
T) Algiers
U) Bucharest
V) Thimphu
W) Ankara
X) Canberra
Y) Male

ELEMENT 3—TRUE-FALSE

	True	False
1) In 1977, the president of the Comoros (D6) had every dog in his capital city of Moroni killed.	______	______
2) North Yemen (4W) used to be known as Aden.	______	______
3) The movie *The King and I* is banned in Thailand (HS).	______	______
4) In Tanzania (5H), wearing a wig is punishable by flogging.	______	______
5) When visiting Nepal (9N), one can stop in government-approved hashish stores.	______	______
6) Timbuktu is located in Mali (TZ).	______	______
7) Half of the population of Kenya (5Z), is less than 16 years old.	______	______
8) Paraguay (ZP) is the only country with two faces to its flag.	______	______
9) In South Africa (ZS), only whites may hold ham tickets.	______	______
10) Dueling is legal in Uruguay (CX).	______	______

ELEMENT 4—MAZE

(Illustration 2)

You know, ham radio is a lot like a maze. Thousands of frequencies, dozens of modes, hundreds of antenna types—it can all get very confusing. Here's a much simpler maze. All it requires is a pencil and some time. No money or physical effort is needed. Thanks go to my Radio Shack TRS-80 Model II for creating it.

THE ANSWERS

Element 1: See Illustration 1A.
Element 2: 1-R, 2-M, 3-U, 4-H, 5-Y, 6-V, 7-F, 8-C, 9-P, 10-X, 11-T, 12-S, 13-J, 14-D, 15-Q, 16-K, 17-G, 18-A, 19-E, 20-W, 21-B, 22-I, 23-L, 24-N, 25-O.
Element 3: 1—False At his witch doctor's request.
2—False No, that was South Yemen.
3—True They believe the film presents a false view of their history. No Yul.
4—True Yul.
5—True Mount Everest ain't the only thing high in Nepal.
6—True Once a great city, it's now a town of about 6,000.
7—True Thanks to a very high mortality rate.
8—True Boon to flag manufacturers.
9—False Not officially, but what's the difference?
10—True Great way to settle frequency disputes.
Element 4: See Illustration 2A.

SCORING

Element 1: Twenty-five points for the completed puzzle or one-half point for each question correctly answered.
Element 2: One point for each correct answer.
Element 3: Two and one-half points for each correct answer.
Element 4: Twenty-five points for the completed puzzle.

How worldly are you?

1-20 points—Hermit
21-40 points—Recluse
41-60 points—Know where your area repeater is located
61-80 points—Armchair traveler
81-100+ points—Man of the World

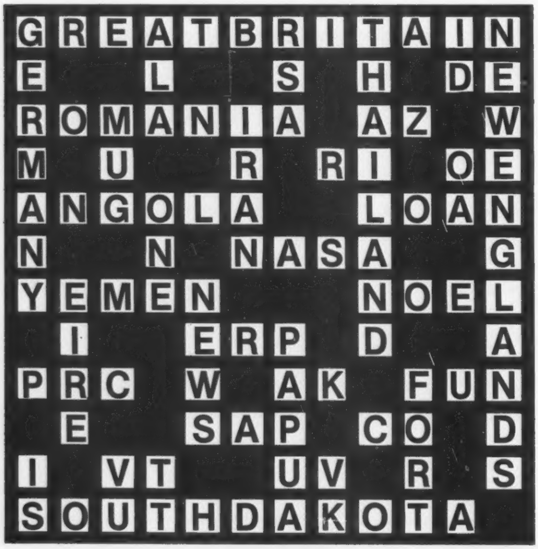

G	R	E	A	T	B	R	I	T	A	I	N
E			L			S		H		D	E
R	O	M	A	N	I	A		A	Z		W
M		U			R		R	I		O	E
A	N	G	O	L	A			L	O	A	N
N			N		N	A	S	A			G
Y	E	M	E	N				N	O	E	L
	I			E	R	P		D			A
P	R	C		W		A	K		F	U	N
	E			S	A	P		C	O		D
I		V	T			U	V		R		S
S	O	U	T	H	D	A	K	O	T	A	

Illustration 1A.

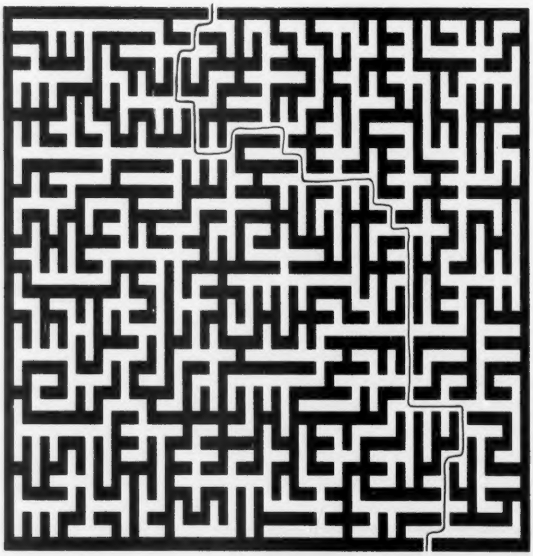

Illustration 2A.

LETTERS

TALK FAST

While reading your response to W6EOT's letter in the September issue, it dawned on me just why the "already-known techniques" for high-speed communication are not used in the ham bands.

You say we can communicate at 8,500 words per minute using these techniques. That would be great for traffic handlers (of which W6EOT is one) and maybe contesters if one could figure out how to program the system to be fast enough. One could conceivably work two or three thousand stations per minute!

However, you often expand on how nice good old rag chewing is. I can't understand how you propose to rag chew at 8500 wpm!

Some simple testing of my talking speed netted only 235 wpm. I sure can't talk coherently or even think at 1000 wpm, much less 8500 wpm!

Therefore, to communicate at 8500 wpm, I would have to preprogram some device at my own speed (say 200-400 wpm), contact another station, and punch the proper button to transmit my message at 8500 wpm. I could no doubt say everything on my mind at the time in less than thirty seconds, if I had 4000 words to say.

The other station's reply would then be transmitted to me at 8500 wpm, but I would have several minutes to wait while he programmed reply comments into his "super QRQ box." And, of course, he would have several minutes to wait for my next round of comments.

The fact that actual transmission time is very small and more stations can use the available spectrum is a nice idea but needs some human engineering, namely, a QRQ to QRS receive converter that would convert the high-speed transmission to normal talking speed with a voice synthesizer, either synced to the other station's voice tones or to a pleasing blonde (for OMs) or tall, dark, and handsome buck (for YLs).

The transmit converter would take a few dozen words spoken into the microphone and blip-transmit them at 8500 wpm, take a few dozen more and blip, and so on.

The receive converter takes the 8500-wpm transmission and begins "talking" to the receive operator at 200 or so wpm (adjustable of course).

And there you have a high-speed system compatible with us relatively slow humans.

Dennis Younker NE6I
Lancaster CA

So what's the difference if your transmitter is on the air, keeping anyone else from using a channel while you mumble inconsequentials at 200 words per minute? Why not have your processor save all that garbage up, put it into a compactor, and dump it at 8500 wpm? Then a bunch of other people could use the same channel. Dunno why we're talking about voice anyway . . . unless all of the code lovers have suddenly died. There are still a few old-time hams around, graduates of early American schools where reading and writing were taught. We could consider opening up classes in our ham clubs on the first two Rs so newcomers could cope with code and printed types of communications.—Wayne.

LETTER ACCELERATION

For some time I have been practicing CW just for the fun of it, as in the HK zone, code is required only for the first-class license.

When getting on the air I find many Novices eager to make the HK contact. They go at my speed when they are calling CQ, but surprise, surprise, once they get to their own callsign, their speed increases by several words per minute, so even if I know that they would immediately answer when they hear the HK coming back to their CQ call, I am not able to call them. Maybe you could write something about this in your magazine.

I usually try to answer CQ calls because when I call CQ with my HK there are just too many stations who come back on my call, even if I sign the HK only once.

I intend to keep you posted on my adventures in CW land.

Rudolf Aumann HK1ESU
Cartagena, Colombia

TOPFSHUTTLER?

My grandmother would say you are a Topfshuttler—a pot stirrer. Isn't that just what an editor is supposed to do? Make people think! You do that well. Obviously, you allow your writers the same freedom.

73's view from Olympus must be a heady one. However, the view is occasionally obscured. Could it be from too much looking down the nose at mortal hams?

A case in point is John Edwards' comment in his column in the July issue, page 123. Commenting on his question, "Do you own a microcomputer?" he stated, "I can't see how a technically-inclined person can be without one." That is editorial nailbuffing from a have to the have-nots and is anything but constructive.

Wayne, please tell the lesser gods at *73* that it ain't 'xactly necessary to have a microcomputer or the latest flamethrower from Japan in order to have fun (and fulfill our responsibilities under Part 97). Yes, *73* should tell us what is new and keep us up to date. But, too often, you promote the idea that the ham should be measured by his equipment when the equipment should be measured by the ham.

Robert F. Solon WD8LKI
Toledo OH

Never let it be said that I interfered with your inalienable right to be totally, thoroughly, ridiculously wrong.—Wayne.

WHAT'S THE FUSS?

You all wanted more teenagers in ham radio? Here I am! I'm 15 years old and just received my Tech ticket. I skipped the Novice test and was really surprised at how simple the FCC exam was. I finished my first year of electronics in high school, which provided all the theory I needed to know, but I had to learn Morse code on my own. I don't know what the big fuss is over learning Morse code. Anyone can do it. Even with the end of the school year approaching and final exams just around the corner, I was able to find time to study code. Everywhere I went I carried a set of phonetic flash cards with me. When I would finish an assignment in class, I would pull out my cards and study a group of letters. I even found time to study during my Spanish final exam! Nobody can use the excuse: "I just don't have the time to study code."

It took me two months before I was ready for the FCC code test. After I took the code test I continued to study Morse code. Within two days I was up to 13 wpm. It kind of made me wish I had held out one more week to take the General code test. I do plan to update to General or Advanced sometime in the near future.

I remember reading a letter in which someone said that the high price of ham gear was keeping kids out of the hobby. I say that is 100% untrue. I agree that prices these days are a little steep, but you do not have to own gear to be a ham. My ham shack consists of a DX-302 receiver and several dipole antennas. My school has a transmitter/receiver combination but we do not have a ham radio club, so I cannot use the equipment. I do plan on starting a club at school but that will take some time. In the meantime, I am asking any ham in the Springfield, Va., area to get in touch with me at 455-1490; I'm dying to get on the air.

I would like to thank the hams who work 3999 kHz at night. I never miss a night listening to this frequency. The more I listened to these fellows, the more I wanted to get my license. Unfortunately, I can't tell them this because I cannot work 75-meter phone. Oh well, this just gives me more incentive to update to Advanced.

Jim Jones N4HQC
Burke VA

STILL BUILDING

Having been involved in ham radio for half a century, I look back at what ham radio was and what it is today.

In the "Good Old Days," the talk during a QSO was largely technical, dealing with home-made projects. Traffic was handled in an era when telephones were considered a luxury. Parts for your favorite projects were always available at "downtown" distributors. A less affluent society made hams more ingenious in their needs.

Today's QSOs are far different! Each new contact allows the ham to list his Japanese-made appliances as if owning a $3,000 layout reflected on his technical ability. But let a transistor or IC go bad, and the appliance is quickly returned to a "repair depot."

The irony is also that, even for those few hams who can handle difficult repairs, manuals for said appliances lack sufficient information or cost fairly large amounts of money!

It is indeed fortunate for current hams that *73 Magazine* is alive and kicking today! For myself, now 65 and retired, the many construction articles have given me many enjoyable evenings. At the same time, local newcomers (age 12-80) likewise were able to discover the "joys of building" via *73*.

Perhaps many readers may disagree with my viewpoints, but I bet the old-timers who remember building a Bearcat receiver or a 47-46-46 push-pull transmitter will agree, the golden years of hamming are past.

Gerald Samkofsky N4ZB
Holiday FL

Oh, guano, Gerald. I started in 1938 and I visited every active ham I could find. They were a bunch of turkeys, just like today. Nothing has changed except your memory. Remember that the first ham contact with Europe was made by a pirate and we never found out who it was. If you've read any 30s ham magazines (or still survive those days) you know that QRM is no better today than it was fifty years ago. Yeah, the old-timers did build, but they didn't know what the hell they were doing and as often as not blew out the filaments by hooking them to the plate voltage. Gerald, I get on 20m and talk with DX that wasn't even imagined 50 years ago and I do it without a lot of trouble. I had a 20-minute contact this morning with a chap in Apia, Western Samoa . . . then a shorter one with a chap in Colombo, Ceylon . . . followed by a nice long chat with HS1ALV. We've never in the history of ham radio had it this good!—Wayne.

DESTINATED

After a few years of operating K1OIQ/R at the summit of Mount Washington, and then this recent summer of traveling about the countryside, I have the following observations and comments to make. This letter was originally a reply to one that I received after criticizing a fellow's operating habits. I would like to give this opinion wider coverage, as it is meant for the entire amateur community.

I apologize only for the way I sometimes come across; tact is one of the things I am still learning. Really, Bill, those of us here are not trying to impose "custom" on anyone's operating habits. Some of it is rather complex—some, kind of stupid I suppose; but I would like very much to get a cheery reply when I call CQ, CQ, rather than some jerk's admonishment: "That's not the way we do it on this repeater." No logic, no conversation, just "that's not the way . . ." Here, at least you get some logic, advice, and conversation as well.

I submit that most hams, like most of the public, are being Madison Aved into an abortion of the language. I am not opposed to such a word as "destinated" (though I hear from a lot who are). I don't know of a shorter, more to the point way of saying, "I'm at to where I'm goin'." The coining of such new words is how our language grows; some day Mr. Webster may even include it in his book. However, I do object to the misuse of language (words and grammar), the sometimes cliquish use of words and phrases, the double question to which one can always answer yes and/or no and still be right, and the long-winded, nonstop monolog method of two-meter operation when, as I think, it should be more like face to face (eyeball, hi hi) or telephone like. Not to mention the editorial we—and the sometimes never ending ID.

Now that I've got this started I shall continue (might even send this in to my friend Wayne Green, hi hi—I might even write a book).

Handel (?) . . . no, I think that's supposed to be handle . . . yes that's better; "handle" is bad enough . . . is for pots . . . is made of wood . . . the vandals stole my handles so I have to use my name (hope you don't mind) . . . Have you been asked for your "personal"? ". . . the personal here is . . ." "What's a personal?" said I in reply; and the new ham apologized for having been a CBer. "No apology expected nor required," I said. "Some of my best friends used to be CBers; a lot of us have taken that same promotion. No ham shack is complete if it doesn't have a working CB radio. But let us try speaking English here, not some silly dialect."

And then there is the editorial we. *We* did this and *We* did that and *We* are going and *We* are using . . . I was listening in one day (needless to say I've got LISTENERS NET LISTENING CERTIFICATE #1) when a friend of mine replied to one of those we-we-we monologs by saying how it was ". . . so wonderful that you and your wife can do everything together . . ." The we didn't even respond. What ever happened to I? Is it taboo or something to say "I did this . . ."?

And the never ending ID. Bad enough again, what with ID required only once every ten minutes, that two hams will ID back and forth after every speech . . .

". . . WWW this is ZXC and back to you before I time this thing out. Ya ZXC this is WWW fine business . . . blah blah and OK on this, that, and the other thing . . . ZXC this is WWW. OK WWW, ZXC right back . . ." and on it goes. But when there are four or five of 'em and each one has to say the calls, in proper turn mind you, they spend more time blowing all the horns than they do in any meaningful conversation.

SO! if one wants to "listen" or "monitor," calling out and announcing same once a day should be sufficient. Also, I feel it should be a "custom" that one who has previously announced that he is "listening" should announce "not listening" when not.

ABC signed on "listening." A minute or so later ZXC announced he was "listening." ABC "listened" again a short time later and before the tail dropped, ZXC "listened" a little louder. Finally, after a pregnant pause, ABC *called* ZXC and the usual ". . . fine business, nice to meet you, hope to see you further on down the log . . ." QSO followed. Now tell me Bill, was that a "customary initiation of QSO" or was that a "power struggle"?

If what one really wants is to QSO, then I respectfully submit that what one should do is call. Call, as in CQ, CQ. Or, if that is too straightforward and meaningful, then at least something like "Hullo radio! . . ."

In this arena I am not concerned with custom; I am not trying to promote any particular way over any other way; I merely want people to say what they mean, be concise, and not be afraid to say "I" once in a while so that when they say "we" you'll *know* there is more than one of them.

However, I'll turn right around and fall back on custom when it comes to badmouthing the shortcomings of the tourists. I know it is the tourist money that "helps keep New Hampshire green." But I also

NEMAL ELECTRONICS
COAXIAL CABLE SALE

This Month's Specials
Same Day Shipping

RG8U-20 ft., PL-259 ea. end	$4.95
RG214U dbl silver shield, 50 ohm	$1.35/ft.
100 ft. RG8U with PL-259 on each end	**$19.95**
BELDEN Coax in 100 ft. rolls	
RG58U #9201	**$11.95**
Grounding strap, heavy duty tubular braid	
3/16 in. tinned copper	**10¢/ft.**
3/8 in. tinned copper	**30¢/ft.**

POLYETHYLENE DIELECTRIC

RG213 noncontaminating 95% sheild mil spec	**36¢/ft.**
RG174/U mil spec. 96% shield	**10¢/ft.**
RG11U 96% shield, 75-ohm mil spec	**25¢/ft.**
RG8U 96% shield, mil spec	**$27.95/100 ft. or 31¢/ft.**
RG6A/U double shield, 75-ohm	**25¢/ft.**
RG58AU stranded mil spec	**12¢/ft.**
RG58 mil spec. 96% shield	**11¢/ft**

LOW LOSS FOAM DIELECTRIC

RG8X 95% shield (black, white or gray)	**$14.95/100 ft.** **17¢/ft.**
RG8U 80% shield	**18¢/ft.**
RG58U 80% shield	**07¢/ft.**
RG58U 95% shield	**10¢/ft.**
RG59U 100% foil shield, TV type	**$7/100 ft. 10¢/ft.**
RG8U 97% shield 11 ga. (equiv. Belden 8214)	**31¢/ft.**
Rotor Cable 8-con. 2-18 ga, 6-22 ga	**19¢/ft.**

CONNECTORS MADE IN USA

Amphenol Pl-259	**79¢**
PL-259 push-on adapter shell	**10/$3.89**
PL-259 & SO-239	**10/$5.89**
Double Male Connector	**$1.79**
PL-258 Double Female Connector	**98¢**
1 ft. patch cord w/RCA type plugs each end	**3/$1.00**
Reducer UG-175 or 176	**10/$1.99**
UG-255 (PL-259 to BNC)	**$3.50**
Elbow (M359)	**$1.79**
F59A (TV type)	**10/$2.15**
UG 21D/U Amphenol Type N Male for RG8	**$3.00**
BNC UG88C/U, male	**$1.25**
3/16 inch Mike Plug for Collins etc	**$1.25**
UG273 BNC to PL-259	$3.00

FREE CATALOG
COD add $1.50—FLA. Res. add 5% Sales Tax

Connectors—shipping 10% add'l, 2.50 minimum
412
Cable—shipping $3.00 1st 100 ft., $2.00 each add'l 100 ft.

1327 NE 119th Street, Dept. RLO, No. Miami, FL 33161 Call (305) 893-3924

know what it is to be a tourist . . . and hear all the speed demons from Massachusetts griping about being behind a slow-moving farmer.

I censor neither what nor who gets talked about on this repeater. I encourage and even incite lively debate. It seems to me that most of the folk on the receiving end of these barbs are so serious and uptight about their inanities that they fail to see the humor in a serious debate.

If only I could run the repeater on all this hot air.

Al Oxton K1OIQ
Mount Washington NH

Feel better now?—Wayne.

THE $1.98 LICENSE

I just finished reading the code vs. no-code gangfight letters in the October issue. Frankly, I felt like throwing up. Such lack of imagination; such lack of perception. What we need is negotiation. You know what negotiation is: that's where them what have agree to give all or part of it away in return for return of a hostage, or not getting their heads busted, etc.

In the spirit of negotiation, let me suggest that no one has tried to unite all the factions of this argument by proposing an amateur radio licensing program with something for everyone. Let me then address it from that standpoint.

First, we need to set a goal; hell, anyone familiar with success can tell you that you must establish a goal. The goal must be reasonable—one you can expect to be able to fulfill by a certain time.

Amateur radio's goal then should be to find the method by which everyone will be licensed within 3 years . . . Change that: everyone who wants to be a ham; we don't want anyone bitching about how we forced him or her to become a ham.

I hear it already: someone saying, "Where would we put them all?" We have literally millions of amateur radio frequencies which are relatively unused. No one said everybody had to be on 20 meters.

The reason for not proposing to include any life forms in other galaxies is twofold. First, it is unreasonable, and the goal must be kept reasonable to be feasible. Second, although the life form known as "slime" must be integrated into amateur radio if we are to meet our goal (a belief in the "inherent goodness of man" being implicit), we do not know whether or not we would want to share our frequencies with other life forms. Between slime and upright man, we should be able to bring enough hams into amateur radio to make it worthwhile for manufacturers and others with pecuniary interests, thereby assuring the future of our bands.

It thus being established that our goal should be to make available an amateur radio operator's license to anyone and everyone who desires one within 3 years, let's look at how to accomplish our goal.

First, the US should lead the way and show the rest of the world how it's done. Wayne Green has stated many times that the FCC has stifled the growth of amateur radio here. Anyone familiar with the doldrums which followed the incentive licensing system imposed back in the 60s should require no further proof. Anyone, though, who needs more proof as to whether or not the FCC should administer the amateur radio service, is reminded of the Citizens Band class-D service and the monumental FCC mismanagement there. Clearly, we do not need the FCC, and responsibility for amateur radio management should be moved to the private sector. More recommendations on that later.

The big hang-up seems to be inflexibility by all parties. I would remind you, if you admit you are inflexible, that when it became apparent Johnny could not read, rather than universities going out of business they provided new innovation. Their goal remained unchanged: to pass out the degrees. Only the requirements changed. Rather than being compelled to submit to remedial reading classes, colleges gave credits for music appreciation, penny pitching, ant watching, etc. This innovation, coupled with sports scholarships and the introduction of new specialties in the liberal arts, kept the degrees flowing. It didn't do a damn thing about Johnny's reading difficulty, nor technically staying ahead of the Russians, but the universities remained open.

US hams are accustomed now to the multiple-choice examination style. Our solution lies in going a step further. We should allow the amateur radio aspirant the greatest possible latitude in the entry requirements for our fraternity, within certain reasonable limits necessary to protect the integrity of amateur radio, lest someone succeed in obtaining a license for his dog, etc. There is enough bitching without that. An either-or testing format would allow the aspirant to choose only subjects they feel confident in.

As an example: Code is a requirement for the HF bands, but, as letter writer Roger E. Berube points out in the October *73*, code is our link to nostalgia. Machines can now send and receive code, usually faster and cleaner than humans. If an inability to learn code is the only obstacle keeping out an aspirant, then he should be allowed to demonstrate some other skill in lieu of sending and receiving code by hand. Perhaps he is a skilled typist, or could learn to type easier than he could learn to copy code. If so, he should be allowed to appear for testing with his computer keyboard and digital code readout under his arm. Provided he successfully operates his machinery and has ample reading skills, he should pass the code test without investing in the *73 Magazine* code tapes.

We could also simply fail to honor our commitment to ITU and drop the code requirement, as some countries do, upon demonstration that the aspirant has finely tuned his "money" skills. An aspirant with money should be permitted to substitute money for code skill. This would just be a liberalization of a policy popular in the Third World . . . or perhaps there is some other explanation why many of their phone (or phony) ops clutter up the bands which gentlemen have long reserved for CW only, ending each sentence with "Roger, QSL?" and refer to the CW underneath them as "portadoras" (carriers?). *Alguien nos esta poniendo una portadora* . . . Roger, QSL? (Someone is putting a carrier on us, Roger, QSL?)

The Roger, QSL? kind of operator, when allowed a reciprocal license to operate in the US, is the subject of considerable anguish at the FCC, which threatens to stop third-party traffic for all reciprocal licensees (if not all US hams). Further evidence that the FCC should not be involved in administering amateur radio! Our fraternity should be turned over to the private sector for administration and the second step after the abolishment of code should be to strike out the requirement that amateur radio communications be noncommercial. No other aspect of amateur radio is noncommercial; why shouldn't we allow tow-truck dispatchers to use it and foreign visitors to conduct their financial dealings via amateur radio? Nets could even be set up to allow hams to manage their stock transactions right on ham radio, since eventually our goal is to license everyone on Wall Street as well.

People are basically good; everyone will behave himself or herself. Remember that. If they won't, we can just legalize the offense.

Or, perhaps the trouble is not with the code at all, but with the theory, or the rules. We can be flexible here as well. If a person can copy 20 wpm, but can neither read nor write coherently and without moving his lips, he should not be denied access to an amateur radio license so he may participate in our fraternal brotherhood. In lieu of a theory or rules examination, he should be permitted to demonstrate some other skill, or possess money. Such substitute skills should of course be radio-related: wire splicing, tube replacement, etc.

Now the big question about who should replace the FCC in administering amateur radio. If the job were turned over to the ARRL, then *Ham Radio*, *73 Magazine*, and perhaps *CQ* (is there still a *CQ*?) would cry foul. I submit that the federal government should, as an expedient to our reaching our goal in 3 short years, sell the management of amateur radio to the highest bidder in the free enterprise market, to be operated as a concession.

Cereal companies have an inherent edge here, since they have the box-top and $1.98 marketing technique down to a science. Providing an aspirant can demonstrate the ability to properly fill out the coupon, locate the proof of purchase seal on the package, and has the requisite $1.98 or equal value in food stamps, nobody should have any difficulty in becoming a genuine radio amateur, state of the art.

A test frequency has been set aside where this is essentially the licensing technique. If you care to listen, it's 27.185 MHz.

Robert G. Wheaton W5XW
San Antonio TX

Thank you, you've been most helpful. Now, does anyone else have any more gasoline to throw on this here fire?—Wayne.

CIRCUITS

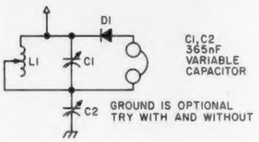
D1
L1
C1
C2
C1,C2 365nF VARIABLE CAPACITOR
GROUND IS OPTIONAL TRY WITH AND WITHOUT

AM BROADCAST RECEIVER: Here is a neat project for a first-time builder. The gimmick is the coil L1. By using an alligator clip at the various taps on the coil, stations are shifted to the lower frequencies on the capacitor. This enables you to separate the stations more easily. D1 is a 1N34A—don't use a cheap diode. C1 and C2 are both 365-pF variable capacitors. A good earth ground is required (the finger-stop on a dial telephone is ideal).—Jim Burtoft N3BQH, Washington PA.

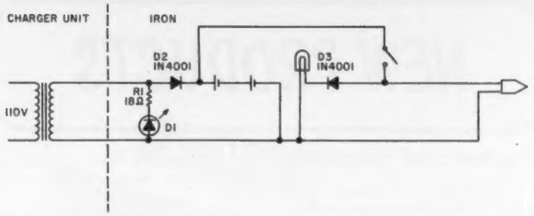
CHARGER UNIT
IRON
110V
R1 18Ω
D1
D2 1N4001
D3 1N4001

SOLDERING IRON MODIFICATION: To have a better rechargeable soldering iron, remove the diode from the charging unit and install it on the soldering iron. Because the nicads in the iron will now be isolated from the charging pins, it will be impossible to short out. By placing an LED with a current-limiting resistor into the iron, you will get a visual indication every time the battery is charging. Installing the circuit shown here will enable you to charge your battery from either ac or dc. By installing a power diode in the headlamp circuit, the lamp is protected against accidentally burning out when the battery is at full charge.—Richard J. Molby WB7NZG/DA1DB, APO NY.

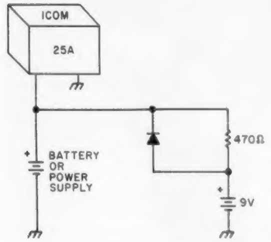
ICOM
25A
470Ω
BATTERY OR POWER SUPPLY
9V

IC-25A BATTERY BACKUP: Here is a simple but effective battery backup for retaining memory when the rig is temporarily removed from the power supply. In tests, the battery retained the memory over eight hours.—Francis J. Piraino WA3KKM, Pocono Summit PA.

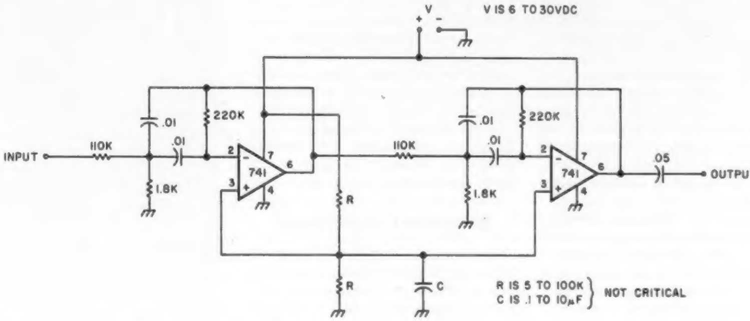
V
V IS 6 TO 30VDC
INPUT
110K
.01
.01
220K
1.8K
741
2
3
4
6
7
R
R
C
110K
.01
.01
220K
1.8K
741
.05
OUTPUT
R IS 5 TO 100K
C IS .1 TO 10μF
NOT CRITICAL

TWO-STAGE ACTIVE FILTER: This filter passes an 800-Hz signal. A single section has a bandwidth of about 150 Hz; the two-stage version's bandwidth is approximately 100 Hz. Gain is close to unity at the passband center. The circuit should be added in a low-drive-level section of the audio amplifier if a 12-volt power supply is used.—Penn Clower W1BG, Andover MA.

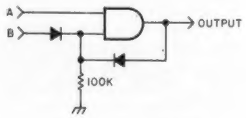
A
B
OUTPUT
100K

SIMPLE AND/OR LATCH: This circuit can be used to trip a repeater relay in a timer circuit. For example, if A is high and B is pulsed by a timer, the output will latch high until the input signal ceases. The high output can be used to disable the transmitter. This eliminates the necessity of having a timer which remains high until well after the desired count is reached. A brief pulse is all that is required. The resistor is needed to hold the B input low since the diodes isolate the input. An OR gate could be used in place of the diodes, but the diodes work well. The gate is a CMOS 4081 or a 4011 NOR gate coupled to an inverter at the output.—John Ackermann AG9V, Green Bay WI.

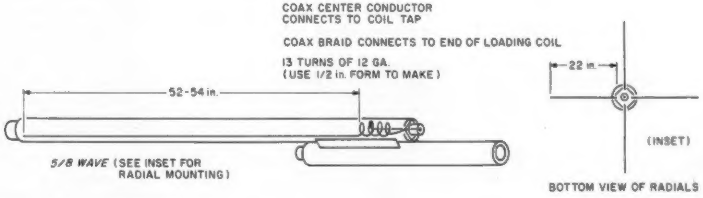
COAX CENTER CONDUCTOR CONNECTS TO COIL TAP
COAX BRAID CONNECTS TO END OF LOADING COIL
13 TURNS OF 12 GA. (USE 1/2 in. FORM TO MAKE)
52-54 in.
22 in.
(INSET)
BOTTOM VIEW OF RADIALS

5/8 WAVE (SEE INSET FOR RADIAL MOUNTING)

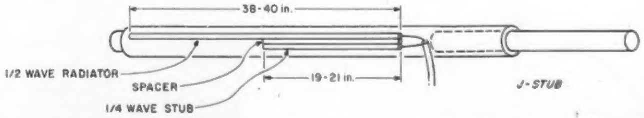
38-40 in.
19-21 in.
1/2 WAVE RADIATOR
SPACER
1/4 WAVE STUB

J-STUB

THE PVC PRINCIPLE VHF ANTENNA: Take one 6' and one 9' piece of 12-gauge copper wire and pull each piece until both are slightly longer. This serves to stiffen the copper. Wind the 6' piece 13 turns on a ½-inch form. Leave ½ inch unwound to make a connection. Remove the coil form and cut the "one piece" radiator as shown. Solder one end of a short length of 28-gauge copper wire to the center terminal of an SO-239 and the other to an alligator clip. Attach the clip to the coil about 2 turns from the radiator. Cut the 9' piece into four equal lengths (2¼') and attach them to the SO-239 as shown. Hang the antenna so that you can trim it for vswr adjustment. Vswr is adjusted by 1) coil tap position, 2) spacing of coil turns, 3) radiator length, and 4) length/angle of radials. After vswr is optimum, solder the coil tap in place. The trimmed antenna can be slid into PVC pipe and epoxied into place. To make the J-stub, take three pieces of RG-8 coax, two 19-21 inches and one 38-40 inches. Carefully remove the outer insulation and braid. Lay the three pieces on a flat table and tape them together temporarily. Solder the coax to the antenna, and connect it to the radiator and the braid to the stub. The radiator/stub assembly can be slid into a PVC pipe. Unsolder the coax, thread it through the hole, and solder it back. The end can be capped and coax putty applied.—Jack Sammarco KC2FS, Union NJ.

NEW PRODUCTS

16-DIGIT DTMF DECODER

Palomar Engineers has announced a new low-cost 16-digit decoder, model P-411. The decoder features high-input impedance so it does not load the line, crystal control for long-term stability and operation over a wide temperature range, dual bandpass filters ahead of the detector, and digital logic that makes it almost entirely free of false outputs. The P-411 operates from +12 volts dc and has a 16-line output as well as BCD code and strobe on 5 lines.

For further information, contact *Palomar Engineers, 1924F W. Mission Road, Escondido CA 92025; (714)-747-3343.*

PORTABLE EARTH STATION

The first completely portable, battery-powered Earth station for receiving satellite transmitted television has been introduced by Gillaspie and Associates, manufacturers of state-of-the-art satellite equipment. The system can be tossed into a station wagon or recreational vehicle and used by campers to watch up to 105 channels of TV. The product also has more serious applications because of its ability to provide visual and audio information and data to remote, communications-poor areas.

The system can provide nine to ten hours of television before the batteries have to be recharged, so it could be used to communicate in civil defense emergencies or natural disasters and in areas susceptible to power outages. The system consists of an 8- or 10-foot metalized-fabric dish antenna that collapses like an umbrella, and a battery-operated satellite receiver complete with a five-inch screen. It can be hooked up to a battery-powered television set if a larger picture is desired.

The portable unit, like the larger home systems, collects microwave beams sent from satellites circling 23,000 miles above. It electronically amplifies less than one Watt of power more than 10,000 times to produce clear, undistorted picture and sound.

Additional information may be obtained through *Diane McNutt, Donald J. Sherman & Associates, 4300 Stevens Creek Boulevard, San Jose CA 95129; (408)-247-7300.* Reader Service number 489.

LOW-COST WIND POWER

Thermax has announced a new wind generator design for small power systems. The TC25WG helius rotor kit was developed as a low-cost battery charger for remote sites and applications, including power for camping, boats, radio operation, RVs, cottages, experimentation, and emergency power. The patented helius design offers several advantages: It responds to winds from any direction and is self-starting. The TC25WG rotor operates at low rpm and avoids overspeed problems common in propeller designs. Virtually no maintenance is required, and the Lexan* vanes resist sun, snow, sleet, and extreme temperatures. Assembly is easy with regular hand tools.

A free information package and further information are available from *Thermax Corporation, One Mill Street, Burlington VT 05401.* Reader Service number 481.

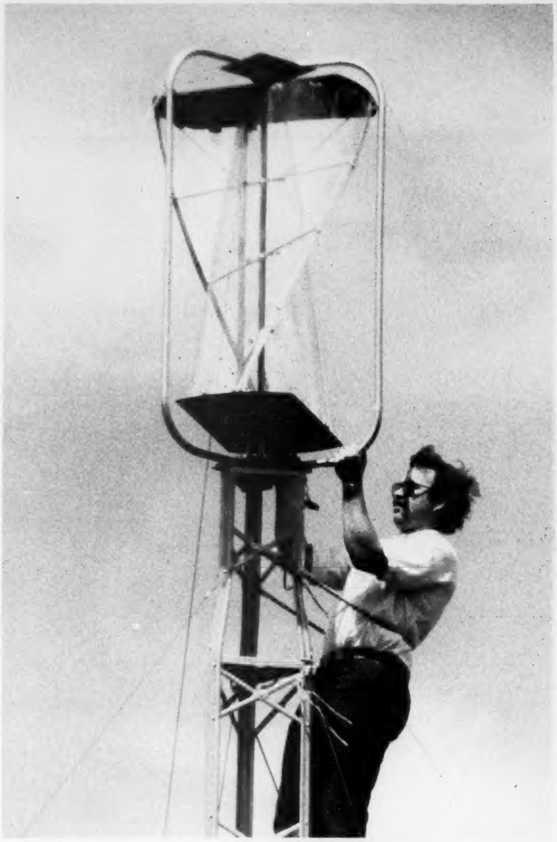

The helius rotor kit by Thermax for low-cost wind power.

SUPER-RATT SOFTWARE

With the Super-Ratt radioteletype and CW program for the Apple II, you can have your own RTTY RBBS station on line quickly and easily, according to Universal Software Systems. Super-Ratt is the lowest-priced RTTY/CW program which also contains a full radio bulletin board system.

The program will operate in ASCII as well as Baudot at any speed from 40 to 300 baud. CW speeds range from 5 to 100 wpm, with an automatic speed adjust on receive.

The program may be run in either manual or RBBS modes. Extensive use of disk files permits storage of "canned" material for manual operation. In the RBBS mode, the system automatically saves nearly one hundred user messages to the disk. There are thirty-five different commands on the RBBS. They are all simple English words—and quite memorable.

Almost any modern terminal unit or converter, such as iRL, Flesher, Kantronics, HAL, or others can be used with Super-Ratt as well as such devices as the "RADCOM" card by AF6W. The program is not protected against copying. The Basic portion may be listed and modified to suit your tastes. (The registered owner's call is installed in the machine code by the factory.)

A free one-year subscription to the user newsletter, *The Ratt's Nest*, is included in the purchase price of $59.95, which also covers shipping via UPS or first-class mail.

For a complete data sheet or other information, write or call *Universal Software Systems, Inc., 9 Shields Lane, Ridgefield CT 06877; (203)-438-3117.* Reader Service number 488.

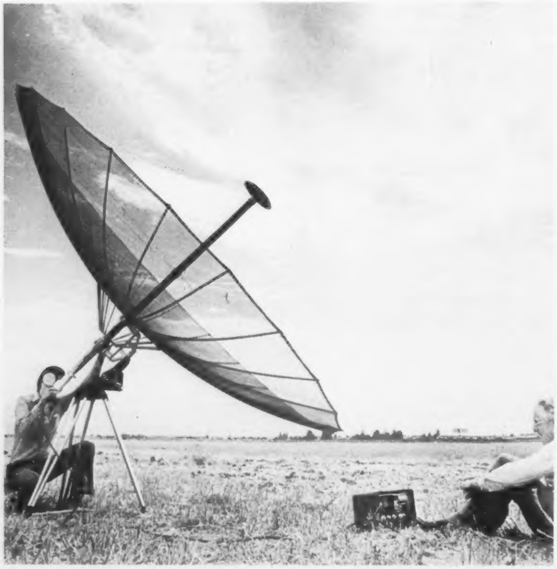

The portable Earth station—in operation.

The portable Earth station from Gillaspie and Associates—ready to put up.

The Synchronar 2100 solar watch.

SOLAR WATCH

Riehl Time Corporation has just announced a new technological breakthrough in wristwatches, the Synchronar 2100, powered by the sun and programmed to the year 2100 with no resetting required, even for daylight saving time or leap-year adjustments. Miniature silicon solar cells automatically gather and store energy from the sun, daylight, or even an ordinary lightbulb, and this energy is used to drive a complex integrated circuit. The solar cells also measure the ambient light and adjust the brightness of the readout so that it may be viewed under any lighting conditions ranging from full sunlight to total darkness. Synchronar's system totally eliminates the problem of battery replacements, and even if left in a drawer for months, it will continue to operate.

Synchronar 2100 has dual time zones and is available in either standard or international time modes or a combination of both. It is guaranteed accurate to within plus or minus four seconds per year. An exclusive self-calibration system enables the wearer to adjust the watch to run faster or slower, should environmental extremes require recalibration.

A discrete alarm system, or "polite" alert, is provided which, at a prescribed time, causes the display to flash on and off for a period of one minute. Synchronar 2100 features a patented, totally-sealed construction in which all electronic systems are encapsulated within a transparent Lexan* module which can withstand shocks up to 25,000 G and water depths up to 750 feet.

Light enters the top surface of the transparent module and charges the solar cells, and the lighted display shines out through the edge above the band, providing a naturally-positioned side view. Control switches are magnetically operated from outside the watch, meaning that the seal of the module is never broken.

For further information, contact *Riehl Time Corporation, 53 South Jefferson Road, Whippany NJ 07981*. Reader Service number 485.

RADIO RACK

The Guild Radio Rack comes in finished solid ash. No assembly is required. Guild's rack comfortably holds Kenwood's TS830S/VF0230/SP230 or TS820 series, or any similar rigs. Exact measurements are (overall) 16-7/8" W times 14-3/4" H times 14-1/2" D; (top compartments) 7-1/2" W times 6" H, and (bottom compartment) 15-5/8" W times 7" H. It is also fully vented.

For more information, contact *Guild Radio Rack, 225 West Grand St., Elizabeth NJ 07202; (201)-351-3002*. Reader Service number 487.

The Guild Radio Rack.

TRIBAND BEAM

TET Antenna Systems has announced that their top-of-the-line HB35T triband beam is now available. This is a 5-element dual-drive antenna for 20, 15, and 10 meters. With the dual drive concept, both the radiator and the reflector are driven with a phase difference that provides extra gain and improved front-to-back ratio.

The beam has only one pair of traps per element for simplicity and reliability. The trap capacitors are coaxial rods mounted inside the elements to give low losses and weatherproof operation.

The HB35T has a 25' boom, weighs 50 lbs., and provides excellent gain for DX work.

For further information, contact *TET Antenna Systems, 1924E W. Mission Road, Escondido CA 92025*. Reader Service number 480.

HAMTRONICS FM REPEATER

Hamtronics, Inc., has announced the availability of the REP-100 line of complete repeater packages, including all the hardware and controls.

The REP-100 is constructed on a 7-inch rack panel, with an uncluttered control arrangement. Electrical features include excellent sensitivity (0.15 uV at VHF and 0.2 uV on UHF), both 8-pole crystal filter and ceramic filter for ± 12 kHz at − 100 dB, afc and hysteresis squelch to lock onto drifting or fading signals, a clean, easy-to-tune transmitter, and up to 20 Watts output. A proportional-controlled crystal oven option provides 2 ppm frequency stability down as low as − 30° C (− 22° F), if needed.

The REP-100 repeater is available for the 6m, 2m, 220-MHz, and 440-MHz bands and adjacent frequencies. It is available also in configurations for remote linking and crossbanding, including 10 meters. The 2m and 220-MHz models employ a 3-section helical resonator in the receiver front end. The UHF version uses 6 tuned lines in the receiver. (That is important if you share a site with other transmitters.)

A complete catalog on the REP-100 repeater, and other information, is available from *Hamtronics, Inc., 65-F Moul Rd., Hilton NY 14468-9535; (716)-392-9430*. (For overseas mailing, please enclose $1.00 or 4 IRCs.) Reader Service number 491.

SATELLITE TV ANTENNA KIT

Ghost Fighters, television antenna specialists, has announced the Space Cowboy P-600 series of parabolic antenna kits.

The Space Cowboy P-610 is a 10-foot hexagonal parabolic microwave antenna specifically designed to receive signals from all the domestic satellites, with over 60 channels of video and audio programming to choose from. It tracks the satellite orbit belt on a polar mount and changes from satellite to satellite in seconds. This kit is for the home-video enthusiast who wants to save money and have the satisfaction of building.

The P-610 model, compared with most 10-foot fiberglass dishes, has a surface-intercept area 10% larger and a longer-than-average focal length. Surface accuracy is proofed-on-site and fully tunable over the entire surface on a point-by-point basis (patent pending) for maximum gain and good picture quality. The surface is heavy-duty galvanized steel screen. The P-610 is a true parabolic reflector with at-

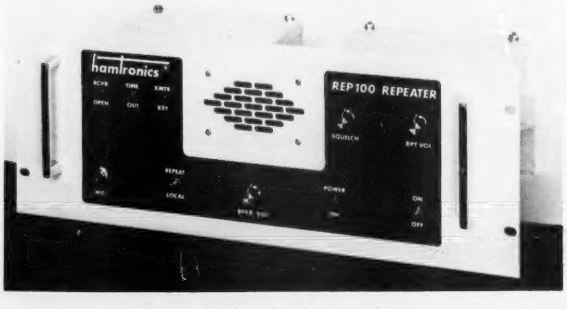

The Hamtronics REP-100 repeater.

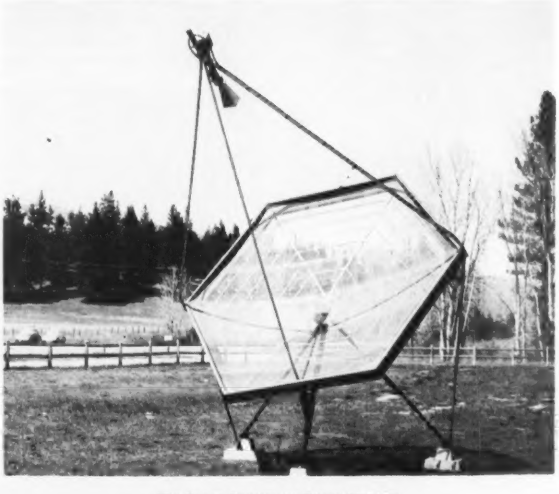

The Space Cowboy by Ghost Fighters.

DENTRON
MLX 20
AF GAIN
RIT
MIC
OFF
W

DenTron's MLX Mini transceiver.

tached feedhorn assembly and adjustable polar mount for easy selection of satellites.

The kit comes complete with all materials pre-cut and ready for assembly. Some portions of the assembly will require two persons. Assembly and installation of the antenna can be accomplished by the average homeowner in a weekend or two. The polar mount is set on three concrete footings requiring 4 to 6 bags of pre-mix concrete.

Other models in the P-600 series include the P-613 and P-616 (13- and 16-foot antennas respectively).

For further information, contact *Ghost Fighters, TV Antenna Specialists, Route 2, Box 136-B, Stevensville MT 59870; (406)-642-3405.* Reader Service number 479.

NEW MICRO SIDEBAND TRANSCEIVER

DenTron Radio Company has announced production of its new mini-sized, monoband transceiver. Titled the MLX Mini, it operates at 25-W PEP and 20-W CW with an LED frequency readout of ± 100 Hz accuracy. Available in models from 160-6 meters, the MLX Mini has selectivity of 2.1 Hz with sensitivity better than .35 uV for 10-dB signal-to-noise ratio. Receiver design is the single-conversion superheterodyne type with total power requirements of 12-14 V dc.

For more information contact *Tim Neill, Technical Sales Representative, DenTron Radio Company, Inc., 1605 Commerce Drive, Stow OH 44224; (216)-688-4973.* Reader Service number 482.

GLOBAL'S DIGITAL PULSER KIT

The DPK-1, a new digital pulser kit designed for use as a pulse injector in stimulus/response testing of digital circuitry, has been introduced by Global Specialties Corporation.

This pulse generator is a portable test instrument featuring multi-logic-family compatibility; it operates on both TTL and CMOS circuits. Its pulse width is 1.5 seconds ± 30% for TTL and 5-V CMOS and 3.0 seconds ± 30% for 15-V CMOS.

One touch of the pulse button and the DPK-1 attempts to inject a positive pulse, then a negative pulse. One of these pulses is ignored, depending on the logic state the DPK-1 output is biased at (determined from node under test). Keep the pulse button depressed and after one second the DPK-1 delivers a continuous pulse train of positive and negative pulses at a rate of 150 pulses per second. In the same manner as the single-shot event, one of these pulses will be ignored, leaving a positive- or negative-going pulse train at a 75-pulse-per-second rate.

An LED indicator flashes once to confirm single-pulse output and remains on for continuous pulse train confirmation.

Pulse voltage level is determined by the current requirements of the node under test. The DPK-1 output pulses are capable of sinking or sourcing up to 100 mA, which is sufficient drive to permit forcing most nodes to an opposite state without desoldering.

This digital-pulse generator offers short-circuit protection. High impedance output (minimum, 20-megohm) when not pulsing allows the DPK-1 to pulse into a short circuit continuously without damage.

The DPK-1 is circuit-powered at 5–18 V dc from Vcc of the circuit under test. A power cable, wired directly into the unit, terminates in two color-coded vinyl-jacketed alligator clips.

The DPK-1 digital pulser comes as a complete kit, including all parts, solder, wire, PCB, etc., and a comprehensive construction and operating manual. Kit construction and testing can usually be completed in one to three hours. Its dimensions are 5.8" × 1.0" × 0.7", and it weighs 3 oz.

For further information, contact *Global Specialties Corporation, 70 Fulton Terrace, PO Box 1942, New Haven CT 06509; (203)-624-3103.*

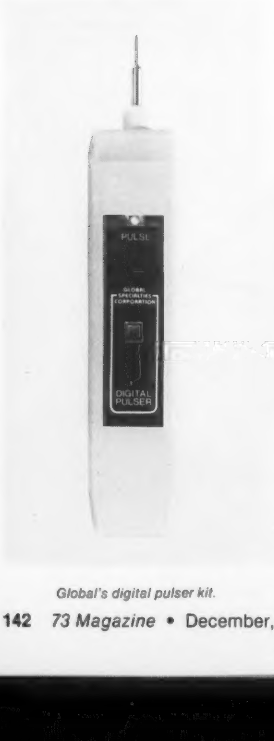

Global's digital pulser kit.

AIDS FOR THE BLIND AMATEUR

Although many textbooks have been translated into braille and onto recorded media, blind hams, technicians, and scientists are faced with the continual frustration of obtaining current and supplemental materials.

The Rehabilitation Engineering Center publishes a newsletter quarterly in braille, large print, and recorded form which will serve as a guide to the current technology as applied to the needs of the blind and persons with impaired vision. The newsletter, called *Technical File*, facilitates the pursuit of electronics interests among technically-oriented, visually-impaired persons by serving as a reference source, a teaching tool, and a hands-on guide for construction projects through lists of materials already transcribed, catalog abstracts, data on integrated circuits, manufacturers' applications notes, and construction details, to list just a few of the contents.

General interest, do-it-yourself descriptions of such processes as soldering, project layout on circuit boards, and the use of power tools focus directly on techniques used by the blind. The articles in *Technical File* are submitted by readers, training-facility personnel, and other interested professionals and non-professionals.

In the Winter, 1982, issue, for example, "Soldering, Part IV," "Singing Chips," "A Tactile Read-Out for Digital Instruments," "Earphones for the Blind Traveler," and "Vocational Aids Catalog" were among the features. Bill Gerrey's "Editor's Corner" and "Editor's Crystal Ball" are always popular.

For your subscription to the Braille Edition ($12 per year), the Large Print Edition ($12 per year), or the Talking Book Edition ($6 per year for half-track cassette, 15/16 IPS) contact *Bill Gerrey, Editor, Smith Kettlewell Eye Research Foundation, 2232 Webster Street, San Francisco CA 94115.* Reader Service number 476.

PROHAM'S FASTRAK ELECTRONIC KITS

Proham Electronics, Inc., has just introduced a new line of electronic kits dubbed the Fastrak* series, wherein each kit is a functional building block that can be assembled in less than one evening. Fastrak modules are for the novice and experienced home-brewer alike, providing not only versatility but complete documentation as well. Each module is built on a commercial-grade printed circuit board that conforms to the HAM (Hardware Application Module) Standard described in the May, 1982, issue of *QEX* magazine, and is uniform in size. Exact board dimensions are governed by the amount of space required to accomplish the intended electronic function, but connector arrangements, bus wiring, and PC-board form factor are uniform and constant for simplicity of assembly and interconnection between units.

Fastrak modules feature a top-down system design, making it easy to configure and assemble complete receivers, transmitters, controllers, and instruments from standard "family" members. Ten Fastrak modules are available, with another ten coming within six months. Functions performed range from basic voltage-regulator and audio-amplifier modules to a 2-chip DTMF decoder and a 1-chip TV.

Fastrak kits come with complete documentation and use readily available components. For more information, write *Proham Electronics, Inc., 34620 Lakeland Boulevard, Eastlake OH 44094.*

ICOM IC-45A SYNTHESIZED UHF MOBILE

Icom has announced availability of the IC-45A, providing FM mobile coverage of 440-450 MHz. Major features are its small size (2" H × 5½" W × 7" D), easy-to-read LEDs, 5 memories, priority channel, band and memory scan with automatic resume, memory backup provisions, 1-MHz upbutton for quick QSY, and variable duplex offsets. The touchtone™ microphone is included.

For more information, contact *Icom America, Inc., 2112 116th Ave. NE, Bellevue WA 98004; (206)-454-8155.*

The Icom IC-45A synthesized UHF mobile.

MOBILE ANTENNAS

Valor Enterprises, Inc., introduced a new series of mobile high-frequency antennas at the Chicago CES Show last June. These HF mobile antennas for the professional and amateur operator are approximately 8 feet in length, and are of a heavy-duty, slim line construction designed for HF amateur bands on 75, 40, 20, 15, and 10 meters. Heavy-gauge copper wire wound on ½" fiberglass with nickel-chrome brass fittings, and 17-7 taper ground stainless-steel whips ensure dependable mobile operation. The 4' stainless-steel whip is field-tuned for lowest vswr and double-locked with stainless-steel set screws. The antennas feature 3/8-24 ferrules to fit standard mobile mounts and are power-rated at 500 Watts PEP for top mobile performance.

For further details, contact *Valor Enterprises, Inc., 185 W. Hamilton St., West Milton OH 45383.* Reader Service number 484.

RETICON ACTIVE FILTER

Applied Invention is the source for the recently introduced Reticon R-5620 programmable active filter—a complex MOS integrated circuit. The R-5620 uses switched-capacitor technology to synthesize a two-pole pair active filter that requires no external components and operates over the range of 0.05 to 25 kHz.

The five basic filter types: low-pass, high-pass, bandpass, band reject, and all-pass can all be implemented by the R-5620, and a programmable sine-wave oscillator is also possible.

Switched-capacitor filters (SCFs) are analog filters in which fixed resistors are replaced by time-division-variable switched capacitors, resulting in very stable filters that can be tuned with a variable clock source.

The simple programmability of this new SCF makes it attractive for computer-controlled synthesizers and other analog/digital systems applications.

For additional information, contact *Applied Invention, RFD #2, Route 21, Hillsdale NY 12520.* Reader Service number 483.

YAESU'S ACTIVE ANTENNA

Yaesu Electronics Corporation recently announced the introduction of the FRA-7700 active antenna for the FRG-7700 deluxe HF receiver.

The FRA-7700 utilizes a four-foot (1.2-meter) whip in conjunction with a low-distortion MOSFET preamplifier, providing shortwave reception for receiver owners unable to erect an outdoor antenna. The FRA-7700 includes front-panel gain control, tuned-circuit peaking, and a preamplifier on/off switch for maximum versatility.

For details on the FRA-7700, contact *Yaesu Electronics Corp., PO Box 49, Paramount CA 90723.* Reader Service number 486.

RT-1100 MULTIMODE TERMINAL

DGM Electronics has just introduced the RT-1100 receive terminal for Baudot, ASCII, and Morse. The RT-1100 converts the audio from your receiver, decodes it, and displays the words on a video monitor or TV set (using rf modulator). The RT-1100 incorporates an active filter demodulator with scope-tuning outputs. It will copy 170-, 425-, and 850-Hz-shift RTTY signals at speeds of 60, 66, 75, and 100 wpm on Baudot and 110 baud on ASCII. The unit will copy 6-60 wpm Morse signals using automatic or manual speed tracking. The RT-1100 has a parallel ASCII printer output for hard copy. The video output provides 16 lines of 32 characters per line with 2 pages. The second page is stored in memory and can be recalled by using the page 1-2 switch on the front panel. The unit has a built-in 110-V-ac power supply and is housed in an attractive 3" × 10" × 10" case with brushed, anodized front and rear panels. The cover is a gray wrinkle finish. The unit comes with a one-year warranty on parts and labor.

For more information, contact *DGM Electronics, Inc., 787 Briar Lane, Beloit WI 53511; (608)-362-0410.* Reader Service number 477.

SPEED TRACKING
TUNING
INDICATOR
MODE
RTTY
MORSE
ASCII
SHIFT
CLEAR
SCREEN
PAGE 1
PAGE 2
ON
OFF
DGM ELECTRONICS
RT-1100

DGM Electronics' RT-1100 receive terminal.

MOBILE ANTENNA CONVERTER

JL Industries has just announced their new X-Panda-Five mobile antenna adapter, which enables the owner of a Hustler, Hy-Gain, or similar mobile antenna to convert his antenna to a five-bander by adding resonators.

The X-Panda-Five consists of a precision-machined aluminum hub fitted with five rustproof 3/8" by 24" studs made from high-tensile-strength carbon steel. The hub is attached to the antenna mast, and each of the five resonators screws onto the hub. One resonator is mounted vertically and four are mounted horizontally.

When the adapter is installed on your antenna, you can use either regular or super-size resonators and change bands without leaving the driver's seat. This assumes, of course, that you pre-tune each resonator to your favorite operating frequency in that band. No antenna tuner is required.

The X-Panda-Five also makes a good antenna for apartment houses and condominiums when fitted with the appropriate resonators and ground planes. It can be used to make a multiband antenna system for vans, campers, motor homes, and travel trailers.

For more information, contact *JL Industries, PO Box 030413, Fort Lauderdale FL 33303.* Reader Service number 490.

ANTENNA COUPLER

Wayne Research & Development has announced the availability of a new antenna coupler that replaces the center insulator of a balanced rf antenna system. The Wayne B-T-L antenna coupler contains an air balun, a tapped inductor, and a variable capacitor. The coupler is housed in an ABS plastic box with a removable lid for inspection and servicing. The strain insulator is made of Delrin® plastic.

With the aid of graphs in the instruction booklet (supplied) and an swr meter, the user can design a matching network to match the low impedance of his wire beam or the high impedance of his loop antennas. Using the network as a T or an L, the Wayne B-T-L antenna coupler will match impedances over a frequency range from 1.8 to 30 MHz.

The insertion loss is not more than −0.006 dB from 1.8 to 25 MHz, and minimal from 25 to 30 MHz. The introductory price is $49.95. For further information, contact *Wayne L. Jamison W5FJS, Wayne Research & Development, PO Box 75144, Houston TX 77234.* Reader Service number 478.

WAYNE
ANT.
ANT.
B-T-L
ANTENNA
COUPLER
BALUN
0
1
2
3
4
5
10
CAP.
GND.
COAX
MODEL

The Wayne B-T-L antenna coupler.

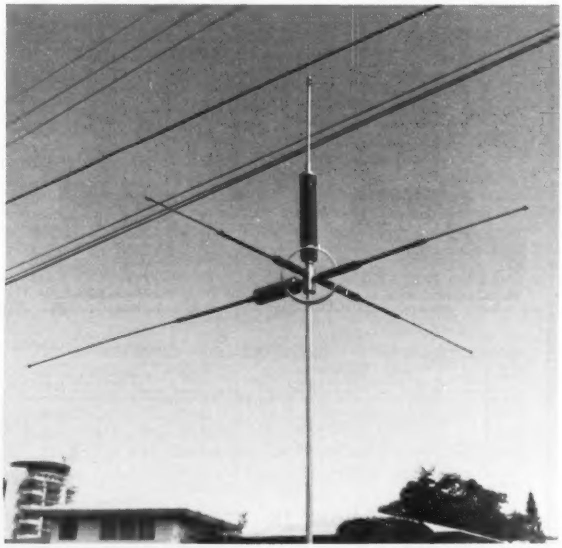

The X-Panda-Five mobile antenna adapter by J. L. Industries.

YAESU
PREAMP OUT
ON
OFF
GAIN
MIN
MAX
BAND
TUNING
FRA-7700

Yaesu's FRA-7700 active antenna.

AVANTEK
GPD SERIES AMPLIFIERS
GPD 401,402,403
12 - 14 DB GAIN

5-500 MHZ POWER 15 VDC TO5 MOUNTING
IDEAL FOR COUNTER AND TV PREAMPLIFIERS
COMPLETE WITH CIRCUIT BOARD FOR MOUNTING
$25.00 EA., SET OF THREE $65.00

AMATEUR
MICROWAVE DOWNCONVERTER
COMPLETE ASSEMBLED READY TO INSTALL NOT A KIT
SPECIAL $179.95
INCLUDING SHIPPING (U.P.S.) VISA AND MASTERCARD ACCEPTED

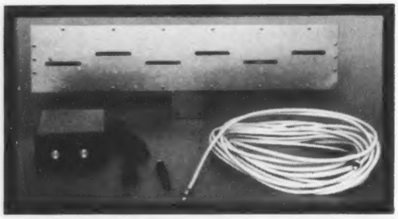

50+ dB SYSTEM GAIN
TUNES 2.1 Ghz. to 2.4 Ghz.
PREAMPLIFIER 20+ dB GAIN @2.5 dB NF
OUTPUT TUNES TV CHANNELS 2 TO 6

OUTPUT IMPEDANCE 75 OR 300 OHMS
FULL YEAR WARRANTY
PERFORMANCE GUARANTEED OR
YOUR MONEY REFUNDED

CALL (804) 489-2156 ✓447
ELECTRONIC HOBBY INNOVATIONS
7510 GRANBY STREET SUITE 207 NORFOLK, VIRGINIA 23505

FREQUENCY COUNTERS to 1.3 GHZ
By OPTOELECTRONICS inc Ft. Lauderdale, Florida

MODEL K-7000-AC 10 Hz to 550 MHz counter 50 Ohm & 1 Megohm inputs via BNC type connectors on rear panel This model is available in optional kit form

•K-7000-AC	counter assembled 115VAC 12VDC	$150.00
•K-7000-ACK	counter kit form	120.00
•Ni-Cad-70S	internal Ni-Cad battery pack	25.00

MODEL 7010-S 10 Hz to 600 MHz counter 50 Ohm & 1 megohm inputs via BNC type connectors on rear panel Precision TCXO or optional ±.01 PPM ovenized (OCXO) time base Both have 10 turn calibration adjustment accessible from rear panel Excellent UHF sensitivity with new amplifier circuitry Optional extended frequency range to 1 GHz

•7010-S	600 MHz counter 115VAC 12VDC	$199.00
•ER-1000	1 GHZ extended frequency range	95.00
•OCXO-70	Ovenized .01 PPM time base Osc	65.00
•Ni-Cad-76	Internal Ni-Cad Battery Pack	25.00

MODEL 8010-S Deluxe 10 Hz to 600 MHz counter External 10 MHz clock input output on rear panel display "HOLD" function display "TEST" function Optional 1 GHz extended range Excellent sensitivity Optional ultra precision ovenized oscillator with ±0.05 PPM stability 10-45° C

•8010-S	600 MHz counter 115VAC 12VDC	$295.00
•ER-1000	1 GHz extended frequency range	95.00
•OCXO-80	0.05 PPM oven time base	106.00
•Ni-CAD-86	internal Ni-Cad battery pack	60.00

MODEL 8013-S 10 Hz to 1.3 GHz frequency counter Has all features of model 8010-S plus standard range to 1.3 GHz Typical sensitivity at 1.3 GHz < 50 mV (-13 DBM)

•8013-S	1.3 GHz counter 115VAC 12VDC	$495.00
•OCXO-80	0.05 PPM oven time base	106.00
•Ni-Cad-86	Internal Ni-Cad battery pack	60.00

MODEL LFM-1110 Low frequency multiplier A frequency counter accessory enabling tone frequencies to be counted faster and more accurately Has low pass filter for off-the-air Tone-squelch measurements BNC input output

•LFM 1110	Low frequency multiplier 115VAC 12VDC	$125.00
•Ni-Cad-1110	internal Ni-Cad battery pack	25.00
•BNC-PC	3 ft 50 OHm BNC patch cable	8.95

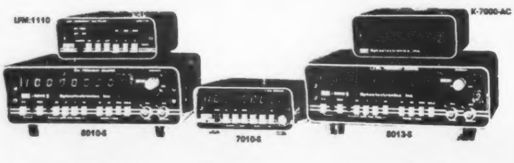

- ALL ALUMINUM CASES WITH MACHINE SCREWS
- 100% PARTS & LABOR GUARANTEE FOR FULL YEAR
- 115 VAC or 12 VDC OPERATION
- CERTIFIED NBS TRACEABLE CALIBRATION
- COMPACT SIZES 8010-S 8013-S 3 H x 7 W x 6 D 7010-S K-7000-AC 1 H x 4 W x 5 D

MODEL	RANGE (FROM 10 Hz)	TIME BASE		AVERAGE SENSITIVITY		GATE TIMES	MAX RESOLUTION			SENSITIVITY CONTROL	EXT CLOCK INPUT OUTPUT	METAL CASE
		FREQ	STABILITY DESIGN	BELOW 500 MHz	ABOVE 500 MHz		12 MHz	60 MHz	MAX FREQ			
K-7000-AC	550 MHz	5.24288 MHz	±1 PPM RTXO	15 mv 24 DBM	N/A	(2) .1 1 SEC	10 Hz	10 Hz	100 Hz	No	No	Yes
7010-S	600 MHz *1 GHz	10 MHz	±1 PPM TCXO *±.01 PPM OCXO	10 mv 27 DBM	20 mv 21 DBM	(3) .1 1 10 SEC	.1 Hz	1 Hz	10 Hz	Yes	No	Yes
8010-S	600 MHz *1 GHz	10 MHz	±1 PPM TCXO *±.005 PPM OCXO	10 mv 27 DBM	20 mv 21 DBM	(4) .01 .1 1 10 SEC	.1 Hz	1 Hz	10 Hz	Yes	Yes	Yes
8013-S	1.3 GHz	10 MHz	±1 PPM TCXO *±.005 PPM OCXO	10 mv 27 DBM	20 mv 21 DBM	(4) .01 .1 1 10 SEC	.1 Hz	1 Hz	10 Hz	Yes	Yes	Yes

*AVAILABLE OPTION

NOW IN STOCK

TERMS Orders to U.S. and Canada add 5% for shipping handling and insurance to a maximum of $10.00

CORRECTIONS

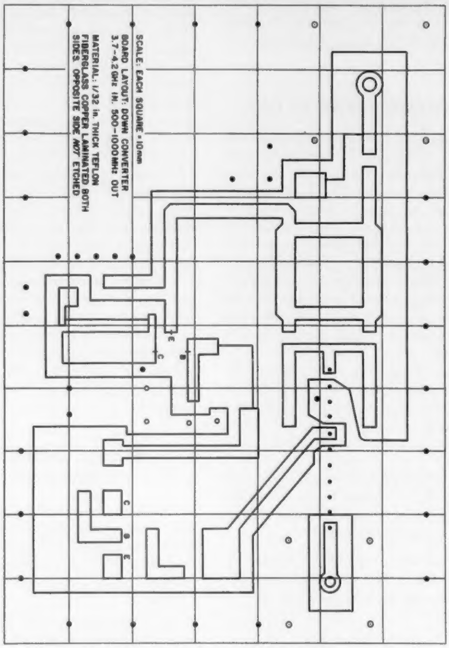
SCALE: EACH SQUARE = 10mm
BOARD LAYOUT: DOWN CONVERTER
3.7-4.2GHz IN. 500-1000MHz OUT
MATERIAL: 1/32 in. THICK TEFLON
FIBERGLASS COPPER LAMINATED BOTH
SIDES. OPPOSITE SIDE NOT ETCHED
E
C
B
C
B
E

G. W. Legel's (N6TO) article "Dissertation Upon Roast Pig" (October) offers an interesting and useful suggestion for transformer salvage, but ignores an extremely important personal caveat.

Old transformers were frequently filled with polychlorinated biphenyls (PCBs). This is a dangerous, toxic material that should be dealt with by trained professionals. Old, oil-cooled transformers must be presumed contaminated. Unless they bear a green certification sticker, they should not be handled by amateurs under any circumstances.

Tom Archer KC8MR
Huron OH

The $100 TVRO receiver is a real winner. I'm going to build one, except for one small detail. The August issue of *73* (on page 64) has the layout of the downconverter used in Rex's "Cheap Trick." The only problem is that in Fig. 4 the scale is 10mm per division. The printed version is 128mm long when it should be 100mm. I'm sure that was done for clarity, but it is hard to interpolate 128mm to 100mm. I'm also sure that you know the dimensions at the frequency are critical.

What I'm asking is if you have an actual-size drawing from Steve Gibson, could you print it in the next issue at 1:1? Please??

David Lawson WA1YMC/5
Dallas TX

Here you go.—Ed.

Fig. 1 in "The Vertical Deuce," on page 81 of the September issue, was drawn incorrectly. As drawn, closing the relay would put a short across the center conductor and braid of the feedline. Instead, the braid should be connected directly to ground and the center conductor should be hooked up to the coil at the opposite end from the antenna.

Avery Jenkins WB8JLG
73 Staff

HAM HELP

I need the manual and/or schematic for a Knight T150 transmitter. I am willing to pay a reasonable amount for any information.

J. W. Roberson W5RDI
745 Willow St.
Hurst TX 76053

Anyone out there have a schematic for an Ameco six-meter type CN VHF converter? Expenses will be reimbursed.

H. S. Robb AF0W
Box 17
Bird Island MN 55310

I would appreciate information on using the Interact computer in amateur radio applications.

George W. Moran W2DGZ
950 Erlen Drive
York PA 17402

I need a schematic for a Majestic Fairfax model 200 superhet broadcast receiver. I will pay copy/mail costs.

Dan Sindorf KS0C
11937 McCoy Drive
Omaha NE 68123

80M IN 24 FT!

Put a broad bandwidth 80M dipole in 24 ft with the SLINKY DIPOLE® antenna. Comparable low SWR, space savings and performance on ALL HF bands, including SWL and WARC. Complete kit: 2 special 4" coils, 50' RG-58/U coax, balun kit, mounting hardware and instructions. Great for apartments, condominiums, motels and vacation use. Easy set up and adjustment.

Ask for **FREE** antenna comparison sheet

Blacksburg Group
Box 242 Suite 500
Blacksburg, Virginia 24060
703/951-9030

49.95 postpaid (in U.S.A.)
Money Back Guarantee
Virginia residents
add 4% sales tax

✓118

MOBILE POWER
For Your H.T.
only **$21.95ppd**

The new MOBILE ENERGIZER will provide operating power for your H.T. from any 12 volt source, and charge it's nicads at the same time! Featuring a time-proven regulator circuit enclosed in a tough, rugged housing that plugs into the cigarette lighter jack of your car, it will work with any synthesized H.T. except Icom, Azden, and Tempo S-15. Specify H.T. model when ordering.

CONTEMPORARY ELECTRONIC PRODUCTS
P.O. BOX 570549
MIAMI, FL 33157

✓184

MULTI-BAND SLOPERS
160, 80, and 40 meters

Outstanding DX performance of slopers is well known. Now you can enjoy 2 or 3 band BIG-SIGNAL reports! Automatic bandswitching • Very low SWR • Coax feed • 2kw power • Compact • Ground or tower feed • Hang from any support 25 ft. high or higher • Easy to install • Very low profile • Complete instructions • Immediate shipment - Check ok

3 BAND SLOPER · 160, 80, & 40 Meters · 60 ft. long	$ 43.00 frt.ppd.
2 BAND SLOPER · 80 & 40 Meters · 41 ft. long	$ 30.00 frt.ppd.
3-BAND NO TRAP DIPOLE, 160, 80, & 40M · 113 ft. long	$ 66.00 frt.ppd.
2-BAND NO TRAP DIPOLE, 80, & 40M · 84 ft. long	$ 49.00 frt.ppd.
FOR ADDN'L INFO on these and other unique antennas:	send SASE

W9INN ANTENNAS
BOX 393-S MT. PROSPECT, IL 60056

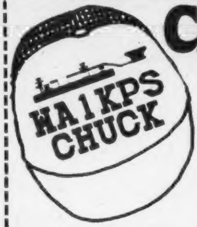

CALL LETTER HATS

ONLY
$5

✓187

101 Elm St Suite 4
Peterborough, NH 03458

Hats Are One Size Fits All w/Nylon Mesh Back

LINE 1 ☐ Morsekey ☐ My Own Logo

CIRCLE ONE
Green Blue Red Gold

LINE 2 ☐☐☐☐☐☐☐☐☐

LINE 3 ☐☐☐☐☐☐☐☐☐

Or ☐☐☐☐☐☐☐☐☐☐☐☐☐☐☐☐☐☐

WA1KPS
CHUCK

Introduced and the talk of the Dayton Hamfest these Attractive and Durable Call Letter Hats are just the thing for Hamfests, Field Day, contests and Club Activties. Messages are printed by computer and can be up to 6 lines of 18 small letters, 3 lines of 9 large letters or any cobination. The Morse Key or your logo takes one large line. Discounts for Club orders and Free logo with orders for 12 and up. Once your logo is on file with us it is free with any quantity, and remember every hat can have a different call or message.

CALL LETTER T SHIRTS

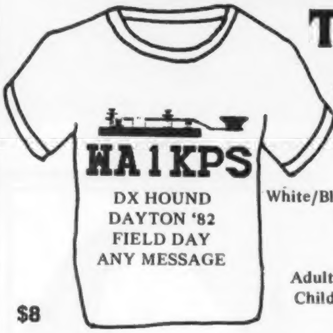

T-Shirts are Highest Quality
50/50 Cotton Polyester

COLOR
White/Blue Trim White/Red Trim
Light Blue Tan

SIZE

Adult	Sm	Med	Lrge	X-Lrge
Child	2-4	6-8	10-12	14-16

$8

LINE 1 ☐ Morsekey ☐ My Own Logo (Provide B & W Copy)

LINE 2 ☐☐☐☐☐☐☐☐☐☐

LINE 3 ☐☐☐☐☐☐☐☐☐☐

LINE 4 ☐☐☐☐☐☐☐☐☐☐

LINE 5 ☐☐☐☐☐☐☐☐☐☐

N2NSD/1
MOST STATES
10 GHZ

Our comfortable and durable T-Shirts are the finest quality available. Make up your own message, DXCC, WAS, WAC, Hams do it with higher frequency, DX Hound, DX-Peditions, Please QSL and any other message. Up to six lines of 10 large letters each or up to 12 lines of 20 small letters each. Discounts for Club orders and FREE logo with orders for 12 or more. FAST MAIL ORDER ! !

CALL LETTER HATS 101 Elm St. Suite 4, Peterborough, NH 03458

Name ______________________

Address ______________________

City ______________ **State** ____ **Zip** ________

Ck ☐ Money Order ☐ Charge Card ☐

Card ______________________ **Exp Date** ______

Signature ______________________

ORDER BLANK

Add $2 To Total For Shipping Charges

Season's Greetings

UNIVERSAL COMMUNICATIONS
P.O. BOX 339
ARLINGTON, TEXAS 76004-0339
(817) 860-1641

A DIVISION OF
INNOVATIVE LABS, INC.

KITS	
DOWN CONVERTER	$19.95
VARIABLE P/S	$19.95
CIGAR ANTENNA	$19.95
KIT SPECIAL	
(ORDER ALL THREE & SAVE)	$49.95
HIGH-GAIN TRANSISTOR	$6.95
DRIFT MODIFICATION	$1.25
KD 44 DISH ANTENNA	$47.95

ASSEMBLED	
ASSEMBLED DOWN CONVERTER	$39.95
ASSEMBLED POWER SUPPLY	$29.95
CIGAR ANTENNA	$19.95
ULTIMATE SPECIAL	
(ALL THREE ABOVE PRODUCTS)	$79.95
SUPERVERTER I—CRYSTAL *NOT* INCL. (ASSEMBLED ONLY)	$109.95
SELECTIVE PREAMP	$26.95

OUR PRODUCT MAY BE COPIED. . . BUT THE PERFORMANCE IS NEVER EQUALLED

MC—VISA WELCOME **8:30-5:30 MON-FRI**

HOW CAN I INTERCEPT SMUGGLERS? SECRET SATELLITES? RESCUE MISSIONS? SIGNALS FROM SPACE?

WHAT IS THE TRUTH ABOUT ANTENNAS? TUNERS? PREAMPLIFIERS?

HOW CAN I CHOOSE THE BEST RECEIVER? ANTENNA?

WHAT ARE THE LAWS REGARDING LISTENING IN?

UNCOVER LISTENING EXCITEMENT YOU NEVER THOUGHT POSSIBLE!

For your FREE COPY of MONITORING TIMES--

CALL NOW! Toll-free
1-800/438-8155
(cont. US except NC).
Others dial 1-704/837-2216
or write to
Grove Enterprises, Dept. D , 140 Dog Branch Road
Brasstown, NC 28902

✓352

CALL TOLL FREE
1-800-238-6168

In TN. call 901-683-9125

MEMPHIS AMATEUR ELECTRONICS
(Formerly-Germantown-Sere-Rose)

Authorized Dealer for: Kenwood, Icom, Drake, Mirage, AEA, Info-Tech, Ten-Tec, MFJ, and B&W.
Used Equipment

MON-FRI 9:00—5:00
SAT 9:00—12:00

✓139

Write: 1465 Wells Stat. Rd., Memphis, Tn. 38108

YES! I'd like to give 73 Magazine for the holidays. (12 issues—$19.97).

☐ Check enclosed

☐ MC ☐ VISA ☐ AE ☐ Bill me

Card#____________________Exp. date____________

Signature____________________Interbank#__________

Name______________________________

Address____________________________

City__________________State________Zip________

Please enter a one year gift subscription to:

Name______________________________

Address____________________________

City__________________State________Zip________

Canada & Mexico $22.97, 1 year only, U.S. Funds
Foreign $39.97, 1 year only, U.S. Funds Drawn on U.S. Bank

62DR6B

All Gift Subscriptions Begin with Jan. 1983 Issue.
73 Magazine•Box 931•Farmingdale, NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 73 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 Magazine
Box 931
Farmingdale, NY 11737

SAY

.... .— .——. .——. —.——

.... ——— .—.. .. —.. .— —.—— ...

with a subscription to
73 MAGAZINE

73 is a virtual encyclopedia for radio amateurs, covering everything from Amplifiers to Zepps, including

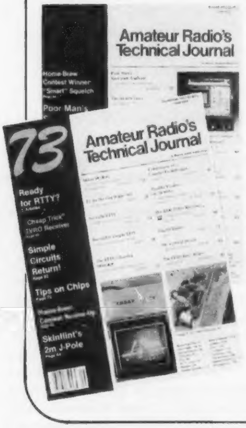

- *Digital communications
- *Hardware construction
- *Pioneering articles
- *Satellite TV

No other ham radio magazine covers the entire spectrum of amateur radio better than 73. Can you think of a nicer way to say Happy Holidays to your favorite ham than by sending them a subscription to 73 Magazine? After all, it is better to send than to receive.

YES!
I'd like to give 73 Magazine for the holidays. (12 issues—$19.97).

☐ Check enclosed
☐ MC ☐ VISA ☐ AE ☐ Bill me

Card# ____________
Exp. date ____________
Signature ____________
Interbank# ____________
Name ____________
Address ____________
City ____________
State ________ Zip ________

Please enter a one year gift subscription to:

Name ____________
Address ____________
City ____________
State ________ Zip ________

Canada & Mexico $22.97, 1 year only, U.S. Funds
Foreign $39.97, 1 year only, U.S. Funds Drawn on U.S. Bank
All Gift Subscriptions Begin With Jan. 1983 Issue.
73 Magazine•Box 931•Farmingdale, NY 11737 **62DR6**

It's Hard To Be Humble When You're Number One On 2 Meters!

KDK

The best selling and performing 2 meter FM rig in the USA, gives you more for your money. 25 watts, Touchtone® mike, 10 memories with built-in memory retention, scanning priority channel, sub-audible tone module built-in . . . and much, much more! Call or write for brochure.

ORDER NOW DIRECT
CALL TOLL FREE
800-251-4141
This number for ORDERS ONLY!
ORDER DIRECT or at your dealer!
DISTRIBUTED BY:

KDK

INCLUDES Tone Pad Microphone and all accessories.
Shipping: $5.00 Eastern U.S.A. $7.50 Western U.S.A.

FM2030
$309

Central & South American orders:
PHONE: (305) 592-7016

Mail Order – COD – Bank Cards

Company reserves the right to change specifications and prices without notice.

KDK DISTRIBUTING CO., INC. ✓81
762 S. GALLATIN RD. (MADISON SQUARE SHOPPING CTR.) – MADISON, TN 37115 – PHONE (615) 865-7949 –TLX56-8652

REVIEW

THE HF 10/160 SOLID-STATE PLL TRANSCEIVER

The voice at the other end of the telephone line belonged to Bruce Stwertnik, president of National Communications Group, Inc., importers of that nice little NCG 15-meter monoband rig which was reported on in the July, 1981, *73*. Now, it isn't unusual for Bruce to call and chat, but I sensed that he had something special up his sleeve this time. After the usual chit-chat, he dropped the other shoe: "Jim, I've just got a new rig in from Japan; how'd you like to put it through its paces?"

At the hint of something new and possibly different, my mind began racing with questions such as what kind of rig? For which bands? How much power? What does it look like? How does it play? What features? You know the kind of things I mean . . . but I barely managed to get a few of them across to Bruce as I quickly stammered a "Sure, I'd be delighted!"

Bruce hastened to explain that this rig would be a scoop for *73* since there are only two in the States at the moment, but a lot more on the way. I was to get the first one to test and Bruce was to keep the other for himself. As a matter of fact, the English-language manuals weren't quite ready yet, he said, so I could expect only a spec sheet and a brief translation of some of the features, operating hints, and comparisons with similar rigs currently on the market.

The NCG HF 10/160 transceiver is much as one would expect. It is definitely a new-generation transceiver, with solid-state circuitry and PLL frequency synthesis. And apparently, if one can judge from the pictures in *CQ-Ham Radio*, the Japanese amateur radio magazine, it has been in use in Japan for some time.

Physical Description

The transceiver is manufactured by Matsushita Electronic Industries Company Ltd., a parent company of Panasonic, among others. It measures approximately 13 inches wide by 5-1/2 inches high by 16 inches deep (if you count the massive rear-panel heat sink) and weighs just shy of 21 pounds . . . but wait a minute: that includes both ac and dc supplies—built in! No need for an external supply, whether you are mobile or fixed. The usual tilt bail on the bottom to raise the rig to a comfortable angle for viewing the front panel is provided, and there is the side carrying handle intended to make the rig conveniently portable. The case is dull black and has a vaguely military, i.e., functional, look. Perhaps the first thing you notice is the centrally-located spinner dial on the front panel, just below the large digital readout frequency display whose green alphanumerics are nearly one-half inch high and are easy to read. There are prefix letters ahead of the numbers when the rig is operated in its various modes: "C" for CW, "U" for upper sideband, and "L" for lower sideband.

The VOX sensitivity, VOX delay, and anti-VOX controls are on the left-hand side of the rig, and the VOX sensitivity control knob has a concentric switch for the 100-kHz frequency marker provided in addition to the synthesized readout, because this permits the on-board phase-locked-loop circuitry to be zeroed against WWV, for example.

The new bands are provided for as well, and the rig covers all amateur frequencies with generous overlap on the ends for MARS or other use. The S-meter dial is in the upper left-hand corner, and indicates relative power output or ALC (your choice) in the transmit mode and S-meter readings in the receive mode. As a matter of fact, I think you would be particularly pleased with the S-meter, as it doesn't seem to be particularly scotch or particularly generous. Somehow, I have the feeling that it is about right—and consistent—from band to band.

The power on-off switch is a toggle in the upper left-hand corner; below the meter is a row of switches that control receiver functions such as noise blanker, meter scale, fast-slow agc, and tuning rate. The tuning device is an optical chopper which permits simple dial lock to a desired frequency simply by disengaging the manual dial. There is a tuning-rate switch that permits you to tune each band in 25-Hz, 100-Hz, or 1-kHz increments. Right next to that manual selector is an auto-tuning switch that functions in the *up* or *down* modes, and changes frequency at the rate selected by the adjacent rate switch. I never thought I would need—or want—such a device, but it's handy and I use it a lot.

Below the switches just mentioned are the microphone connector (standard Japanese 4-pin) and the phone jack (standard 1/4-inch diameter) right next to it. Then comes the key jack, which uses the smaller-diameter plug of the size used to plug in speakers and the like (I believe it is .168" diameter). Fortunately, another rig I tested recently had this size key jack, so I was ready, but on the *front* panel? Why there of all places? The answer is simple—convenience; I realized that as I recalled the many times I have fumbled around the back of a rig in the dark trying to find the key jack.

The HF 10/160 has a built-in speaker placed on the bottom plate of the rig, and a jack for an external speaker should you wish to use one. I found the audio quality to be quite good, even with the small enclosed speaker . . . and that certainly is the way to go for portable/mobile . . . unless or until you wear headphones, of course. An external speaker is normally used in my shack, however, so I used that for the evaluation.

Next to the key jack is the mode-selector switch—permitting wide or narrow CW and upper or lower sideband . . . you have to choose which. On the dial escutcheon you will find two small push-buttons that activate the dial lock (left button) and the TX/RX REV switch. On the upper right-hand side of the panel you will find the Delta F switch and the RX offset switch (RIT).

The Delta F control corresponds to the receiver incremental tuning control (RIT) on the other rigs. By pushing the switch, a red LED comes on to show that the circuit is activated. Now, by varying the Delta F knob, you can adjust the receive frequency higher or lower than the dial-set frequency by about 1 kHz.

The TX/RX REV control permits further adjustment of the transmit or receive frequencies separately. When the switch is depressed, a red LED is illuminated to show that the circuit is active. Here's how it works. Suppose you want to leave your transmit frequency where it is but wish to change the receive frequency. Push in the TX/RX REV switch to lock the transmitter frequency on the existing dial setting. Now the receive frequency can be adjusted by the main tuning dial. This gives the effect of a dual vfo, and permits you to set the transmitter "up five," for example, when working DX on a split frequency, and then use the receiver and main dial to tune the DX station. If you wish to listen to *your* frequency momentarily, turn the TX/RX REV switch off, and presto, you're back on the transmit frequency with the receiver.

The memory-selection push-buttons are next, and require a separate discussion—so we'll come back to them later. You should know, however, that you can store up to four different frequencies and scan between any part of them at a variable rate, using "autowatch."

If you really want to get fancy about all this, you can use all these features in concert: TX/RX REV, Delta F, and memory select. I am sure that an accomplished dial twister and button pusher could really play a symphony on this rig after a few evenings of practice. Versatility is the name of the game with the HF 10/160 from NCG, and it's unlikely you will run out of permutations and combinations to try.

The main control knobs of the transceiver lie below the switches, and include in the top row: transmit frequency variation (Delta F), i-f tuning (± 1 kHz) and the audio/rf gain controls on concentric shafts for the receiver; and in the bottom row: the mike gain/CW carrier-control knob, the audio-compressor/speech-processor control, and finally the bandswitch covering 1.8-29.7 MHz.

I found that all controls fall more or less conveniently to hand, and that if you have used any of the modern solid-state rigs from Japan, you will find everything about where you expect it. I was impressed with the nice manual tuning feel and the utter simplicity of using the rig.

Electrical Description

The NCG HF 10/160 contains 30 integrated circuits, 6 FETs, and 124 diodes/transistors. Power consumption is nominally 50 Watts on receiving in the ac mode, and 0.6 Amperes current drain in the dc mode. Transmitting consumes 550 Watts in the ac mode, and 20 Amperes current drain in the dc mode. Nominal dc voltage requirements are 13.8 volts (negative ground) at 20 Amps—enough to require that you have a battery charger, if portable, or a good alternator system if mobile and operating at the full-power capability. Ac requirements are the usual 120 volts, 50 cycles.

Band Coverage

The HF 10/160 covers 1.8-2.0 MHz in the 160-meter band, 3.5-4.0 MHz in the 80-meter band, 7.0-7.3 MHz in the 40-meter band, 10.0-10.5 MHz in the 30-meter band (providing some general reception, too), 14.0-14.35 MHz in the 20-meter band, 18.068-18.168 MHz in the 17-meter band, 21-21.45 MHz in the 15-meter band, 24.89-24.99 MHz in the 12-meter band, and 29.0-29.7 MHz in the 10-meter band.

Stability is given as less than ± 200 Hz within one hour and less than ± 20 Hz after one hour. A comment about the extraordinary frequency stability was received from a ham on 40 meters who had been listening to me for a half an hour. He mentioned that my frequency as measured on his frequency meter had not changed one cycle during the entire time he had been monitoring! This means that both voltage and temperature stability is excellent. The comment, by the way, was unsolicited.

Transmitter Description

The final-stage input is 200 Watts (160-12 meters) and 100 Watts on 10 meters. Balanced-type modulation is used, and carrier suppression is more than 40 dB. Sideband suppression is more than 50 dB, and spurious radiation is at a level below − 40 dB. Microphone impedance is about anything you want, and a range of 600 to 50k Ohms is acceptable. The output connector for rf is the usual 50-Ohm UHF type SO-238.

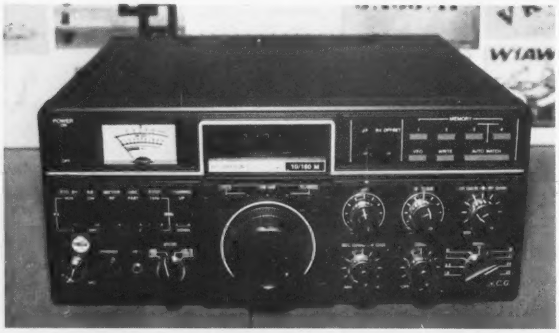

NCG's HF 10/160 transceiver.

SOME FEATURES COMPARED

Feature	NCG 10/160	TS-830	FT-101
Tuning	PLL-synthesized	Vfo (capacitor)	Vfo (capacitor)
Power Supply	Ac/dc built in	Ac	Ac (dc optional)
Weight	21 pounds	30 pounds	32 pounds
Dimensions (H × W × D)	5.2 × 2.68 × 12.44	5.24 × 13.11 × 13.11	6.18 × 13.58 × 12.83
Frequency memory	Yes	No	No
Autoscan	Yes	No	No
Dual vfo	Yes	No	No
Tuning rate	3-step	N/A	N/A
Passband tuning	No	Yes	Yes
I-f tune	Yes	Yes	No
Notch filter	No	Yes	Yes
CW/af	Yes	No	Yes
Tone Control	No	Yes	No
Drift-free tune	Yes	No	No
All solid state	Yes	No	No

Receiver Description

The receiver is a single-conversion superheterodyne of the type well known for its good sensitivity and lack of images, yielding a factory-measured sensitivity figure of less than − 12 dB (.25 V) at 10-dB S/N ratio. The i-f frequency is 9.0007 MHz on CW and 9.000 MHz on phone. Selectivity on SSB or wide CW is 2.2 kHz at − 6 dB, less than 3.0 kHz at − 20 dB, and less than 6 kHz at − 60 dB down, for a shape factor of about 2.7. On narrow CW, the figures are 400 Hz at − 6 dB, 1 kHz at − 20 dB, and 1.6 kHz at − 60 dB, respectively. This gives a shape factor of about 4:1 for narrow CW. The narrow CW option could not be observed at the time of testing because the sharp filter had not yet been received.

Spurious images are down more than 60 dB, i-f rejection is likewise more than 60 dB, and other spurious response is down more than 70 dB.

With the built-in speaker (nominal 8-Ohm impedance), the audio output power is 0.5 Watts (10% THD) and with an external speaker, the audio output power is 1 Watt (10% THD).

Using the Rig

This report is necessarily a preliminary and admittedly sketchy evaluation because the manual I have is in Japanese. The English versions should be available (along with the rigs) by the time you read this. In spite of, or perhaps because of, the lack of an English-language manual, I found that I paid more careful attention to the drawings and photos than usual. These are abundantly clear, and it would be almost impossible to set up the rig incorrectly if you have had any experience at all in putting a "transceiver-from-the-box" on the air.

Carefully unpacking the rig from the usual sanitary plastic bags and foam-sheltered security of the container, I found a separate bag containing the microphone and still another small box with the ac and dc power cords inside. Selecting the ac cord, I plugged it into the polarized multipin socket on the back. My ground wire was put on the terminal, underneath the usual washer and wing nut. The microphone plugged into the usual 4-pin front-panel connector.

One obtains a first impression of any rig as it comes from its cocoon, and this one was no exception. Its general appearance, weight, and feel lend the impression that it is functional and business-like, with its matte black finish and vaguely military look.

Being a CW man at heart, I wanted to try that mode first, so I plugged my electronic keyer into the rig, switched the operate switch to VOX, and set the sensitivity control and delay control for comfortable semi-automatic break-in. Keying the rig produced a fine sidetone—pleasant to the ear—and my power-output meter showed a power output of approximately 70 Watts on 40 meters. A quick twist of the Mic Gain/CW CAR control brought the output to 100 Watts. The stations I worked on 80, 40, 20, and 5 meters all reported fine keying and good solid signals with a nice CW note.

The only small objection I had was from an operator who claimed that on the initial make (when the relay came on) there was a slight frequency warble which disappeared once the relay held in. (This will be corrected in subsequent production rigs.) However, if you choose to set the VOX delay to a long duration, there will be only one little warble at the beginning of the first character. This would also be true, of course, in the manual mode, and thereafter you should hear no complaints. Not having heard this myself, I can only report what that one operator told me. Significantly, perhaps, no one else mentioned it.

I was somewhat bothered by the lack of a narrow-CW filter, but I found that I could operate in all but the worst of crowded conditions by using the i-f shift control to move the i-f window into a better location with respect to the carrier. This gave the impression of an improved selectivity by removing part of the bandpass through which extraneous signals could slide. All in all, I found CW operation very satisfactory, and was delighted to be able to work about anything I could hear. Although I did not find the sidetone pitch and volume controls which are internal, I must confess that I didn't search for them either. Once the English-language manual arrives, it will be a snap to adjust them to one's own special comfortable listening level and tone. With earphones on, I found everything to be exactly right, so I didn't bother trying to change them.

Single-sideband operation is where this rig really shines. I am not much of a phone operator, and because of this I was perhaps a bit overconcerned about the modulation and signal levels that I would be able to produce. I needn't have worried; each report was outstanding.

The first evening of sideband operation went somehting like this: "W1XU, this is W—; you are five by nine here. By the way, what rig are you running? The audio is outstanding!" (Mic Gain control positioned at 10 o'clock.)

"W—, this is W1XU right back. Thanks, OM, for the fine report. The rig is a new one undergoing test for *73*. I'm not at liberty to tell you the make and model just yet, but I can tell you it is nominally a 100-Watt-output rig, made offshore."

(Breaker)"W1XU, this is K—; what kind of rig did you say you were running? The audio is superb. Are you running a processor?"

"K—, thanks for the good report. I appreciate it. Can't tell you what the rig is, but you'll read about it in *73* one of these months."

(Breaker) "W1XU, this is W—. I just wanted to tell you that I have been listening to you for half an hour, and your frequency is rock steady. You haven't varied by one cycle since I started listening. I also wanted to tell you that your rig is super, whatever it is."

(Later that evening) "W1XU, this is WA—. Your audio certainly doesn't sound any better with that compressor in your circuit. In fact, it sounds better without it. Are you sure you don't have some audio processing? It's crystal-clear and has magnificent 'punch.' "

Rather than bore you with further reports of the same or similar content, I'll just mention that *every* report has been outstanding. I have been very careful about avoiding requests for an audio quality report, and each one was unsolicited. In spite of the fact that I consider myself a dyed-in-the-wool CW operator, this rig has gone a long way to turn me back to SSB. Maybe it will help to understand that when I admit that my voice is one of those mid-range voices that could be described as soft-spoken. It does not "talk up" a rig like many that you hear. In fact, I usually use a mike amplifier to help out . . . but with this rig it surely isn't necessary and probably is not desirable.

Of course, being solid-state, no tune-up is required, and full output is achieved into a matched antenna. I did not notice any swr shutdown protection at swr values up to about 1.5 to 1. Inadvertently, I once attempted to transmit with the antenna shorted to ground. Obediently, the finals shut down, and—fortunately—no damage was done. This was immediately obvious by the power output meter, which didn't even flicker. Not having any swr values in the 3:1 range, I can't be sure at what point shutdown began, but I would guess that 3:1 would result in a power output of about 50 Watts or less . . . in other words, a progressive protection. Nice.

The memory function had me a bit perplexed, but I got brave enough to finally give it a whirl. I dialed in two frequencies about 50 kHz apart and committed them to memory as follows: 14.007 on dial, punch the Write button, followed by button 1. 14.007 is now in memory 1 and also displayed on the screen. (Punch the vfo button and you are able to dial in another frequency.) This time, I dialed up 14.012, depressed Write and button 2, followed by vfo. 14.012 was now in the memory 2 location. Next, I wanted to put in two more frequencies in memories 3 and 4 . . . which I did, according to the previously described method. Now, by merely selecting any of the four memory buttons, I could instantly recall the frequency in memory. Nothing special, you'll agree —and about like any transceiver with memory.

Now, what about the autowatch function? Well, I pushed it—and guess what? The receiver goes into a scanning mode and scans between the two frequencies in memories 3 and 4! It scans very slowly—I would guess no faster than about 10 Hz/second. When it reaches the top frequency it returns to the lower one and begins scanning again. Although I don't have any particular need for that feature at the moment, I can visualize a few occasions when it might be very worthwhile to have. For example: Suppose you are looking for a friend on a particular frequency, "plus or minus QRM." Just set two frequencies above and below the intended frequency and punch autowatch! When your friend comes on, you'll hear him because the scan rate is slow enough to permit call identification before it moves on. Neat.

Frankly, I have not used audio compression except on some DX contacts, where the reports have indicated an improved readability—perhaps because of the higher average power output. There were no adverse comments as there had been on local contacts.

So far, I've not been able to find the time to install the rig in the car . . . but may do so in time to drive to a hamfest this coming weekend. It's a longish trip—about 400 miles each way—so that should provide ample opportunity to give the rig a real mobile shakedown. I have no reason to believe that it will perform other than spectacularly.

Is this rig for you? Well, of course, it depends upon what you are looking for. Certainly it has many nice features, including some that aren't available in the run-of-the-mill modern transceiver, and it is rugged and functional. The price is competitive, as it is squarely in the range of similar transceivers. I felt the dial was very satisfactory, and the knobs, switches, and controls equally so. The only picky-picky complaint I have (and this wouldn't bother anyone else, I'm sure) is that the small knobs have skirts that are decorated with a plastic trying to simulate metal . . . and it *looks* like plastic, not metal. If I were the manufacturer, I'd forget trying to dress it up with this charade. Leave 'em all black, and they'll be that much better for it.

You may find there is enough information available on the metering modes; all you get is rf output, S-meter, and ALC information. Upon further consideration, what more do you really need?

With this article is a handy comparison chart for you, between the HF 10/160 and two other contemporary rigs in the same price class. Look it over and decide for yourself whether you're interested. If you're like me, I think you will be . . . very much so!

For more information, contact *NCG Company, 1275 North Grove Street, Anaheim CA 92806*. Reader Service number 492.

Jim Gray W1XU
***73* Staff**

ICOM IC-290A/E ALL-MODE 2-METER TRANSCEIVER

The Icom IC-290A/E (A is the American version and E is the European model) is just what the doctor ordered if you are looking for an all-mode 2-meter rig. It has all the features a 2-meter op could want, and even a seasoned VHF operator would be pleased with the unit. The capabilities of the IC-290 are astounding for its small size. It operates USB, LSB, FM, and CW from 143.8 MHz to 148.2 MHz. In addition to two completely independent vfo's the 290 features five memories and a flexible band-scanning system. Yet, at 64 mm (H) × 170 mm (W) × 218 mm (D), it is smaller than many FM rigs.

On the Road

I had been wanting to try 2-meter SSB mobile for years, and finally had the chance the day the IC-290 arrived. So, I installed the radio and headed out on a business trip from Peterborough NH to New York. Before leaving, I programmed the memories for five of the repeaters I might encounter enroute and put vfo A on 144.200 MHz, the calling frequency for SSB. I set vfo B on 146.52 and set the scanner for memory scan. This allowed me to scan all seven frequencies.

Although SSB during the day is not as busy as FM, there is still a considerable amount of activity, with new stations on the air every day. I could leave the rig in FM scan, and when a station came on 144.200 MHz the squelch would open and all I had to do was switch to USB to see who was calling. This system worked very well. I worked several stations between New Hampshire and New York. The added range on 2 SSB and the lack of beepers, timers, and kerchunkers is truly a pleasure. My friends on "the low end" may be upset by my publicizing their secret, but there is plenty of room for everyone. It reminds me of a bumper sticker seen on a car up here in New Hampshire after a particularly large influx of "flatlanders." "Keep NH a Secret," it read. Well, it's hard to keep a secret about something so great, and 2-meter SSB is the same.

Technical Highlights

The rf amplifier and first mixer circuits of the IC-290 use MOSFETS which allow for a receiving system that is more sensitive than any other 2-meter multi-mode rig I have tried. Unlike other transceivers, the 290 does not need a preamplifier for successful operation. I took the rig with me on a trip to Boston and tried to work a repeater in NH while in the back yard of another that was 15 kHz away. Contrary to other receivers that I had put through the same test, the IC-290 came through with flying colors. The receiver features selectable agc in SSB and CW plus a noise blanker that worked very well in removing ignition noise that was being radiated by my auto and adjacent vehicles as well.

The Icom 290 has two continuous-tuning vfo's. What this means is that when you get to the end of the tuning range (i.e., 148.200) the vfo automatically switches to the bottom edge (143.800). This feature saves a lot of time if you are on 147.51 MHz and you want to QSY to 144.220 MHz. In the SSB and CW modes, quick tuning in 1-kHz steps is available or, with a push of the front panel tuning rate switch, fine tuning in 100-Hz steps. On FM, the tuning rates are 5 kHz and 1 kHz. The tuning knob has click stops which allow for eyes-on-the-road tuning. A priority switch allows you to sample any one of the memory channels every five seconds, regardless of whether the scanner is on or another frequency is being listened to. The S-Meter/Rf-Output indicator is of the currently-popular LED-bar type.

The transmitter in the IC-290 has a high output of 10 Watts. By pulling out on the squelch knob, you are in low power which comes through from the factory set at 1 Watt and is internally adjustable. Transmitted audio reports that I received were all favorable. The repeater offsets are controlled by two front panel switches. To the left of the main tuning knob is a three-position offset switch, selecting either up, down, or simplex. The offset frequency is selected by placing the mode switch in the Offset/Write position and dialing the main tuning knob to the desired offset frequency. Then you return the mode switch to the FM position and your offset is set until you change it. Internal transmitter controls include everything you should need from deviation-adjust in FM to CW sidetone-adjust.

Icom has provided an excellent operating manual. It includes inside photographs with all internal adjustments very well labeled. In fact, the manual is so good that Jeff DeTray WB8BTH used it to describe to me over the phone where the deviation pot was located. The manual with all its descriptive pictures was at his house and the rig was on my bench. He found the pot and described to me exactly where it was in just a matter of seconds. There is no need for an extra-cost service manual just to make adjustments.

With the IC-290A/E, Icom has once again demonstrated its ability to pack many features into an extraordinarily small package. And yet they've done it without sacrificing operator convenience. As the sunspot cycle declines and all-mode rigs proliferate, we can expect to see more and more SSB and CW activity on 2 meters. Radios like the IC-290 will bring lots of new blood to the low end of two.

For further information, contact *Icom America, Inc., 2112 116th Ave. NE, Bellevue WA 98004; (206)-454-8155.*

Bob Cunningham K1XR
***73* Staff**

HF ANTENNAS FOR ALL LOCATIONS

L. A. Moxon G6XN scarcely needs an introduction to at least two generations of antenna enthusiasts. His fascinating descriptions of antennas of all kinds, ranging from beams to vertical and from wire antennas to space-saving and "hidden" antennas, have inspired thousands of radio amateurs in this country and abroad to try their hand at just one more antenna. More often than not, the G6XN antenna will exactly fit the requirements and will perform at least as well as—and sometimes better than—whatever you may have tried before.

Les Moxon's articles, sketches, and ideas have appeared in the RSGB publications, in *QST*, and in collections and manuals everywhere. Now, at last, we have the man all by himself in a book that is bound to become a must for the bookshelf of every right-thinking antenna experimenter: *HF Antennas for All Locations*, published by the Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE, England ($12).

Here is a book you can really get your teeth into—one that you can use to answer questions you may have about a particular aspect of theory or to build a practical antenna from a concise sketch with exact dimensions for the frequency of your choice. Not only that, the English seem to have a unique way of making difficult subjects seem very simple, and Moxon's book is no exception. His explanations and drawings of the ionosphere, for example, are quite fascinating, and show a three-dimensional space in two dimensions by some very clever art work.

Let's for just a moment peek into the contents and see what's there that may interest you and have application to your particular situation. (I'm convinced that Les has something for every antenna taste and persuasion.) The book is divided into two basic parts. Part I is titled "How antennas work," and covers in ten chapters the following subjects: Taking a new look at HF antennas; Waves and fields; Gains and losses; Feeding the antenna; Close-spaced beams; Arrays, long wires, and ground reflections; Multiband antennas; Bandwidth; Antenna design for reception, and The antenna and its environment.

Part II covers "Theory into practice," and includes these chapters: Single-element antennas; Horizontal beams; Vertical beams; Large arrays; Invisible antennas; Mobile and portable antennas; What kind of antenna?; Making the antenna work, and Antenna construction and erection.

As you can see, there's enough material there to fuel your winter's needs for reading matter, and sufficient practical "how to" information to occupy several year's worth of summertime building frenzy.

Take the first chapter in Part I, for example, which invites the reader to take a *new* look at HF antennas. Just what does Les Moxon mean by a *new* look? Well, let him speak for himself.

"Amateurs have been using HF antennas for 60 years or more so that some slowing down in the rate of progress might be expected. As evidence of this, some of the best antennas in use today were designed 20 to 30 years ago yet, impelled by strong incentives, the search for the 'better' ones continues unabated. At times of slow progress it is not a bad idea to look at problems from new angles, and a possible first step is to erase from one's mind the picture of 'things as they are' and concentrate, for a few moments at least, on the way one would *like* them to be. Listing the reasons why they are not and challenging each in turn can be good fun; moreover, before accepting once again the status quo, one feels entitled to convincing evidence that there are no alternatives.

"In the following pages the reader will find few such proofs but instead several challenges to existing beliefs and practices, 'proof of impossibility' being reserved mainly for the antenna gain figures frequently claimed by authors and advertisers."

Les then goes on to explain that weight, size, and cost of beam antennas must be considered to be fair game for investigation and that a reduction in these values *without compromising performance* is a worthy goal. Another goal is minimizing interfering signals, and G6XN questions whether that goal is incompatible with the goal of increased gain. Today's thinking suggests that there is no answer, but Les points out a new and striking possibility: Why not change the antenna characteristics between transmitting and receiving?

In fact, the contents of the book suggest that the desired objectives can be met with *dipole* elements only, and that loops or other configurations are not necessary—provided that one doesn't think that a *straight* dipole is necessary!

Well, this is just a taste of what the book holds, and it goes into great detail explaining how new configurations can be achieved, what they might look like, and what may be possible.

In Part II, there are some concrete examples given on the construction of minimum-size antennas that more or less fulfill the promise of the earlier portion of the book. Whatever your antenna problem may be or however limited your space or budget, G6XN has something for you.

No one suggests or would dream of suggesting that *HF Antennas for All Locations* is a panacea for antenna problems, but it is interesting and requires some study. I'd be willing to bet that seventy-five percent of us could greatly improve our HF antenna installations by reading what Les Moxon has to say. Ask your book dealer today to get you a copy. Reader Service number 493.

Jim Gray W1XU
***73* Staff**

CONTESTS

Robert Baker WB2GFE
15 Windsor Dr.
Atco NJ 08004

CALENDAR

Dec 4-5	**ARRL 160-Meter Contest**
Dec 4-5	**Connecticut QSO Party**
Dec 11-12	**ARRL 10-Meter Contest**
Dec 19	**CARF Canada Contest**
Jan 8	***73 Magazine* 40-Meter World SSB Championship**
Jan 9	***73 Magazine* 80-Meter World SSB Championship**
Jan 15	**World Communication Year Amateur Radio Activity**
Jan 15-16	***73 Magazine* 160-Meter World SSB Championship**
Jan 15-16	**Hunting Lions in the Air Contest**
Jan 15-16	**QRP CW Contest**
Feb 19-20	**YL ISSB QSO Party—CW**
Feb 26	**RTTY World Championship Contest**
Mar 12-13	**YL ISSB QSO Party—Phone**

CONNECTICUT QSO PARTY

Starts: 1100 GMT December 4
Ends: 1100 GMT December 5

Sponsored by the Candlewood Amateur Radio Association (CARA). Phone and CW are considered to be the same contest. Stations may be worked once on each band and each mode.

EXCHANGE:

Send QSO number and ARRL section or Connecticut county.

SCORING:

Out-of-state stations multiply total QSOs by the number of Connecticut counties worked (8 maximum). Connecticut stations multiply total QSOs by the sum of ARRL sections and provinces. Additional DX contacts count for QSO points but only one DX multiplier overall is allowed. W1QI, the club station, will be operating CW on the odd and SSB on the even hours, and counts as 5 points on each band and mode. Novice contacts count as 2 points each and OSCAR contacts count 3 points each.

FREQUENCIES:

CW—40 kHz up from the bottom of each band.

SSB—3927, 7250, 14295, 21370, and 28540.

Novice—3725, 7125, 2119, and 28125.

ENTRIES & AWARDS:

A Worked All Connecticut Counties certificate will be awarded to each station working all the counties. Other awards given as usual, minimum of 5 QSO points! Logs must show category, date/time (GMT), stations, numbers, bands, QSO points, and claimed scores. Enclose a large SASE for results. Logs must be postmarked by January 2nd and sent to Steve Grouse KA1ECL, 3 Queens Court, Danbury CT 06810.

CANADA CONTEST

Starts: 0000 GMT December 19
Ends: 2400 GMT December 19

Sponsored by the Canadian Amateur Radio Federation (CARF), the contest is open to all amateurs and everybody works everybody. Entry classes include single-operator allband, single-operator single band, and multi-operator single-transmitter allband. There are separate single-operator QRP (5 W dc, 10 W PEP out) and single-operator non-Advanced amateur classes.

Use all bands from 160 to 2 meters on CW and phone combined. All contacts with amateur stations are valid. Stations may be worked twice on each band, once on CW and once on phone. No crossmode contacts, and no CW contacts in the phone bands are allowed.

EXCHANGE:

Signal report and consecutive serial number starting with 001; VE1 stations also should send their province (NS, NB, PEI).

SCORING:

Score 10 points for each contact with Canada, 1 point for contacts with others. VE0 counts as Canada. Score 10 points for each contact with any CARF official news station using the suffix TCA or VCA. Multipliers are the number of Canadian provinces/territories worked on each band, on each mode (12 provinces/territories × 8 bands × 2 modes for a maximum of 192 possible multipliers). Contacts with sta-

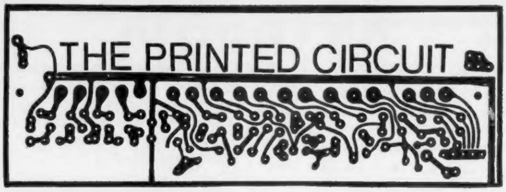

NEWSLETTER OF THE MONTH

This month's winning newsletter is the *Printed Circuit*, published by the Lubbock Amateur Radio Club in Lubbock, Texas.

As well as its unique masthead, the *Printed Circuit* offers a variety of features not found in most newsletters. For example, one issue features a full-page profile of a local old-timer, which was followed by a column on personal computers.

Not leaving out other areas of interest, the editors of the *Printed Circuit* included a story on amateur participation in a recent disaster drill and devoted another full page to DX news and propagation predictions.

And that's not all—There is also a regular technical column, public service announcements, repeater update, puzzles, and a monthly activity calendar.

One sure way of divining the success of a publication is by the activity of its letters section, and the *Printed Circuit* is not lacking in that area, either. Many newsletter editors must dream of getting the number of letters received by the *Printed Circuit*.

To top it all off, the *Printed Circuit* publishes a Q & A session with "The Old Ham." The Old Ham addresses timely and pertinent subjects, such as what to do in a Toronado warning and how to tell a Toronado from a Chevy.

Hats off to Becky Swann WD5KBO and her staff for putting out a newsletter with more stuffed into it than a five-flavor banana split.

73 encourages clubs to send in their club newsletters. Just address them to *73*, Pine Street, Peterborough NH 03458. Keep us up to date with what is happening in your area, and maybe even win the Newsletter of the Month contest.

tions outside Canada count for points but not multipliers.

FREQUENCIES:

Phone—1820, 3770, 3900, 7070, 7230, 14150, 14300, 21200, 21400, 28500, 50.1, and 146.52.

CW—1810, 3525, 7025, 14025, 21025, 28025, 50.1, and 144.1.

Suggest phone on the even hours (GMT), CW on the odd hours (GMT). Since this is a Canadian-sponsored contest, remember to stay within the legal frequencies for your country!

AWARDS:

A plaque will be awarded to the highest score single-operator, allband entry. Certificates will be awarded to the highest score in each category in each province/territory, US call area, and DX country.

ENTRIES:

A valid entry must contain log sheets, dupe sheets, a cover sheet showing claimed QSO points, a list of multipliers, and a calculation of final claimed score. Cover sheets and multiplier check lists are available. Entries should be mailed within one month of the contest, with your comments, to: CARF, PO Box 2172, Stn. D, Ottawa, Ontario K1P5W4, Canada.

Results will be published in *TCA*, the Canadian amateur magazine. Non-subscribers may include an SASE for a copy of the results.

RESULTS

1982 A5 *MAGAZINE* WORLDWIDE DX SSTV CONTEST

1st DX	FM7CD	1622 pts.
1st US	KE1Y	810
2nd	VE4ADG	453
3rd	KB6WP	410
4th	VE3JW	368
5th	WD9IPX	331

(63 entries total were received)
Next SSTV contest is the WAS SSTV in January.

2ND ANNUAL 40-METER WORLD SSB CHAMPIONSHIP

Starts: 0000Z January 8
Ends: 2400Z January 8

SPONSOR:

73, Peterborough, New Hampshire 03458.

MISCELLANEOUS RULES:

Work as many stations as possible on 40-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All the multi-operator stations may operate the entire 24-hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

EXCHANGE:

Stations within the continental 48 US states and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RS report and DX country.

POINTS:

1 QSO point is earned for each station worked in the continental 48 US states and Canada or within your own country. All other contacts are two points each. List points for each contact on your logsheet.

MULTIPLIERS:

1 multiplier point is earned for each US state (48 maximum), each Canadian province or territory (13 maximum), or DX country worked.

FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include a contest log, a contest summary, and multiplier checklist. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1983.

DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification.

AWARDS:

Contest awards will be issued in each operator class in each of the continental 48 US states, Canadian provinces and territories, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to be eligible for contest awards.

CONTEST ADDRESS:

To obtain entry forms or to submit an entry, forward an SASE to: 40-Meter Contest, Billy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.

2ND ANNUAL 80-METER WORLD SSB CHAMPIONSHIP

Starts: 0000Z January 9
Ends: 2400Z January 9

SPONSOR:

73, Peterborough, New Hampshire 03458.

MISCELLANEOUS RULES:

Work as many stations as possible on 80-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All the multi-operator stations may operate the entire 24-hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

EXCHANGE:

Stations within the continental 48 US states and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RS report and DX country.

POINTS:

1 QSO point is earned for each station worked in the continental 48 US states and Canada or within your own country. All other contacts are two points each. List points for each contact on your logsheet.

MULTIPLIERS:

1 multiplier point is earned for each US state (48 maximum), each Canadian province or territory (13 maximum), or DX country worked.

FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include a contest log, a contest summary, and multiplier checklist. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1983.

DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification.

AWARDS:

Contest awards will be issued in each operator class in each of the continental 48 US states, Canadian provinces and territories, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to be eligible for contest awards.

CONTEST ADDRESS:

To obtain entry forms or to submit an entry, forward an SASE to: 80-Meter Contest, Billy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.

2ND ANNUAL 160-METER WORLD SSB CHAMPIONSHIP

Starts: 0000Z January 15
Ends: 2400Z January 16

SPONSOR:

73, Peterborough, New Hampshire 03458.

OBJECT:

To work as many stations as possible on 160-meter phone in a maximum of 30 hours allowable contest time. Multi-operator stations may work the entire 48-hour contest period. Stations may be worked only once.

ENTRY CATEGORIES:

(1) Single operator, single transmitter, phone only. (2) Multi-operator, single transmitter, phone only.

EXCHANGE:

Stations within the continental US and Canada transmit an RS report and state, province, or territory. All other stations, transmit RS report and DX country.

POINTS:

All valid two-way contacts score five (5) QSO points each.

MULTIPLIERS:

1 multiplier point is earned for each US state (48 maximum), each Canadian province or territory (13 maximum), and DX country outside the continental 48 US states and Canada.

FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include logsheets, dupesheet for 100 or more contacts, a contest summary sheet, and a multiplier checksheet.

ENTRY DEADLINE:

Each entry must be *postmarked* no later than February 19, 1983.

DX WINDOW:

Stations are expected to observe the DX window from 1.825-1.830 MHz as mutually agreed by top band operators. Stations in the US and Canada are asked not to transmit in this 5-kHz segment of the band. During the contest all stations are requested to utilize those frequencies from 1.808-1.825 and 1.830-1.900 MHz.

DISQUALIFICATIONS:

Operator omits a required entry form, operates in excess of legal power authorized for his/her given area, manipulates operating times to achieve a score advantage, or fails to omit duplicate contacts which reduce the overall score more than 2%.

AWARDS:

Contest awards will be issued in each entry category in each of the continental US states, each Canadian province and territory, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to qualify.

CONTEST ADDRESS:

To obtain entry forms or to submit a contest entry, forward an SASE to : 160-Meter Contest, Billy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.

2ND ANNUAL RTTY WORLD CHAMPIONSHIP CONTEST

Starts: 0000Z February 26
Ends: 2400Z February 26

SPONSORS:

73 and *The RTTY Journal.*

MISCELLANEOUS RULES:

The same station may be worked once on each band. Crossmode contacts do not count. Single-operator stations may work 18 hours maximum, while the multi-operator stations may operate the entire 24-hour period. Off periods are no less than 30 minutes each and must be noted in your log(s).

OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

ENTRY CATEGORIES:

(A) Single band. (B) Allband, 10-80 meters.

EXCHANGE:

Stations within the continental 48 US states and Canada must transmit an RST report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RST report and consecutive contact number.

QSO POINTS:

1 QSO point is earned for each valid contact.

MULTIPLIER POINTS:

1 multiplier point is awarded for each of the 48 continental US states, Canadian provinces or territories, and DX countries worked on each band.

FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Entries must include a separate log for each band, a dupesheet, a summary sheet, a multiplier checklist, and a list of equipment used. Contestants are asked to send an SASE to the contest address for official forms.

ENTRY DEADLINE:

All entries must be postmarked no later than March 26, 1983.

DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification.

AWARDS:

Contest awards will be issued in each entry category and operator class in each of the US call districts and Canadian provinces and territories, as well as in each DX country represented. Other awards may be issued at the discretion of the awards committee. A minimum of 5 hours and 25 QSOs must be worked to be eligible for awards.

CONTEST ADDRESS:

Send an SASE to RTTY World Championship Contest, c/o *The RTTY Journal*, PO Box RY, Cardiff CA 92007.

WORLD COMMUNICATION YEAR

Next month's World Communication Year amateur radio activity will be using the 75 ITU zones for scoring multipliers. Be sure you use the correct ITU zones and not the ARRL zones for this contest. Copies of a world map and prefix list showing the ITU zones can be obtained from the contest sponsors, the Potomac Valley Radio Club, by sending an SASE or an IRC to: PVRC, PO Box 337, Cromsville MD 21032. Complete rules will appear here in my January column.

Introducing the POWER PACKET™ from VoCom

An innovative new product that you can combine with your VoCom Power Amplifier to obtain the functions of the famous VoCom Power Pocket™ *using any handheld radio.*

AF POWER — 2 to 3 watts of road-noise-overcoming audio to your vehicle speaker or to external Packet Speaker™ (optional).

EASY HOOK-UP — Packet Bracket™ at bottom of Power Packet, provides place to clip almost any make or model handheld. Connects to handheld through pin jacks. Hooded light on Power Packet illuminates portable's front panel.

CHARGE POWER — 35 mA charge on receive, 400 mA when mic is keyed. Unless your handheld draws more than 400 mA, you can talk as long as you wish and the batteries will be at least as charged as when you started.

MIC PREAMP — adjustable; tie in your handheld directly without changing its mic input. Also makes Power Packet compatible with most standard mobile mics. Optional Packet Mic™ available.

Suggested retail $84.95. See your favorite amateur radio dealer.

VoCom
PRODUCTS CORPORATION
65 E. Palatine Rd., Prospect Heights, IL 60070
(312) 459-3680 ✓90

Power Pocket, Power Packet, Packet Bracket, Packet Mic, Packet Speaker and VoCom are trademarks of VoCom Products Corp.

MICROWAVE AND SATELLITE TELEVISION

The standard RP downconverter package shown below gives you a proven 2150 Mhz downconverter mounted in a weathertight antenna that features low wind loading and easy installation.

All downconverters use microstrip construction for long and reliable operation. A low noise microwave preamplifier is used for pulling in weak signals. The downconverters also include a broad-band output amplifier matched to 75 ohms. The RP model is recommended for up to 15 miles. Over the range of 15 to 25 miles the RP+ which has a lower noise and higher gain RF amplifier stage, provides better television reception. For installations over 25 miles, an RPC unit which uses a separate antenna is available. All models are transient voltage protected by surge protection on both the power supply and the converter inputs. All models are warranted for one year.

The DCI 466 is a completely self-contained **IMAGE REJECTION DOWN CONVERTER** that is used for TVRO downconversion at the Satellite antenna where optimum signal to noise ratio can be obtained. The DCI 466 converts the TVRO band to 70 Mhz. The unit's DC power and a 17 to 25 volt local oscillator tuning voltage are superimposed on a single RG 59 line for easy installation. The unit has an on board IF amplifier matched to 75 ohms that gives plenty of drive for long cable runs. The overall conversion gain is 25db. Image rejection is a minimum of 14db. $300 in singles.

Write for details on our low priced model VCO 40 voltage controlled oscillators in the four pin TO-8 package that cover the TVRO band. Also check our 120 degree low noise amplifier for low cost satellite ground stations.

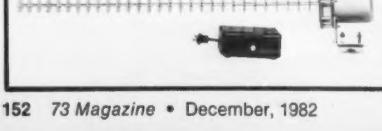

INTEGRATED ELECTRONICS
PO BOX 204
CARLISLE MA 01741
617-369-0536 ✓165

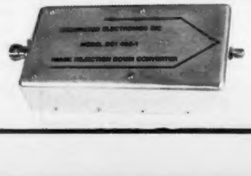

CIRCUITS

Do you have a technique, modification, or easy-to-duplicate circuit that your fellow readers might be interested in? If so, send us a concise description of it (under two pages, double-spaced) and include a clear diagram or schematic if needed.

In exchange for these technical gems, 73 offers you the choice of a book from the Radio Bookshop, *to be sent upon publication. Submit your idea (and book choice) to: Circuits, Editorial Offices, 73* Magazine, *Peterborough NH 03458. Submissions not selected for publication will be returned if an SASE is enclosed.*

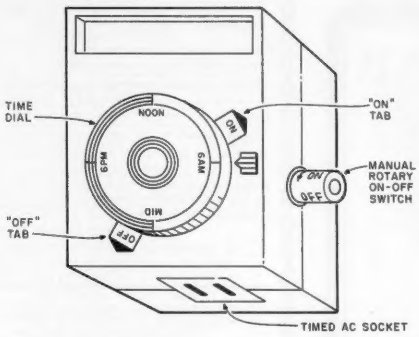
TIME DIAL
"ON" TAB
NOON
ON
6AM
6PM
MID
OFF
MANUAL ROTARY ON-OFF SWITCH
ON
OFF
"OFF" TAB
TIMED AC SOCKET

OVERTIME PROTECTION FOR NICADS: Nicad batteries are prone to damage if the batteries are charged for more than 12 to 16 hours. Unfortunately, most timers don't have a timer. To protect your batteries from possible overcharge and venting, you can add an outboard timer and thus protect your batteries. 24-hour appliance timers are available for less than $10. The timers have sliding "on" and "off" tabs which trip a switch when the dial rotates. There is also a rotary-type override switch on the back or side of the unit. To use this timer for your nicad charger, first disassemble the timer. Remove the tab from the "on" switch. To use the modified timer, set the dial to noon and set the "off" switch to a time 16 hours later. This would be 4:00 am. Plug in the charger to the timer, and turn the timer on with the manual override switch. If you have to interrupt the charging cycle and move the unit into another location, your unit will have a "memory" and the charging cycle will resume at the same time when you reconnect the unit.—John F. Sehring WB2EQG, Oradell NJ.

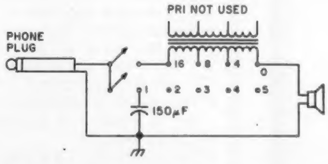
PRI NOT USED
PHONE PLUG
16
8
4
0
1
2
3
4
5
150μF

SIMPLE FILTER SPEAKER: There is nothing magical about this circuit. It consists of a universal output transformer which is secondary-tapped at 4, 8, and 16 Ohms, a 150-uF paper capacitor, and a two-deck five-position rotary switch to select combinations as shown. The clockwise position goes straight through to the speaker and each step to the left cuts more high frequencies in the manner of a typical tone control on a broadcast receiver. There is some attenuation of the overall signal (chiefly above the male voice range), so you can reduce the heterodynes from Radio Moscow and the adjacent channel sideband QRM to a tolerable level. You could use a transformer with more taps or more than one capacitor if that is what your junk box offers.—W. B. Cameron WA4UZM, Tampa FL.

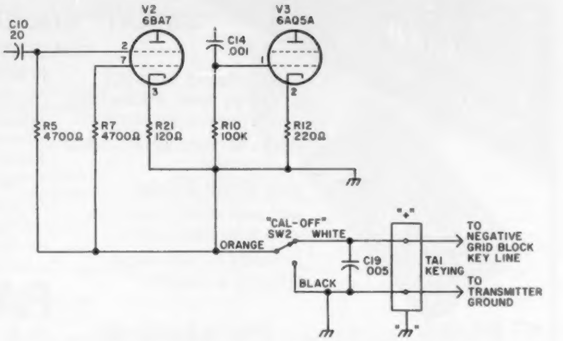
C10 20
V2 6BA7
2
7
3
C14 .001
V3 6AQ5A
1
2
R5 4700Ω
R7 4700Ω
R21 120Ω
R10 100K
R12 220Ω
"CAL-OFF" SW2
ORANGE
WHITE
BLACK
C19 .005
"+"
TA1 KEYING
TO NEGATIVE GRID BLOCK KEY LINE
TO TRANSMITTER GROUND

HALLICRAFTERS HA-5 GRID-BLOCK KEYING CONVERSION: The Hallicrafters HA-5 vfo is cathode-keyed. This conversion will enable the rig to be grid-block-keyed with a minimum of surgery to the unit. Begin by disconnecting cathode resistors R12 and R21 from the orange lead of the "Cal-Off" switch, grounding them to chassis. Open R22 at the TA1 keying terminal strip. Disconnect R5, R7, and R10 from chassis, and connect their junction to the orange lead of the "Cal-Off" switch. To reconvert to cathode keying, disconnect the ungrounded ends of R5, R7, R10, and R22, leaving them bent out, while installing new R5, R7, and R10 resistors whose long leads will more readily reach to the orange "Cal-Off" switch lead. The grid-block transmitter lead (negative) then connects to the terminal marked "+", and the transmitter ground connects to the terminal marked "ground" on the vfo keying terminal strip.—Tuckerman S. Jalet AA1C, Stamford CT.

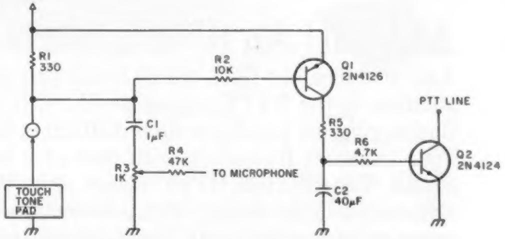
+13V
R1 330
R2 10K
Q1 2N4126
C1 1μF
R5 330
PTT LINE
R6 4.7K
Q2 2N4124
R4 47K
R3 1K
TO MICROPHONE
TOUCH TONE PAD
C2 40μF

TOUCHTONE™ TECHNIQUES: This circuit allows for one-hand operation of any surplus-type touchtone pad. Q1 and Q2 form a high-low switching circuit controlled by R1. When any key is depressed, Q1 will conduct, applying 12 volts to the pad. Then Q2 conducts, keying the transmitter. After you have completed dialing, the keying circuit returns to the "rest" mode and the transmitter must be keyed by the PTT. Delay time is controlled through selection of C2 and R6. Component values are not critical.—Joseph A. Taylor W9JO, Green Bay WI and Hugh Kelley WB9NON, Rhinelander WI.

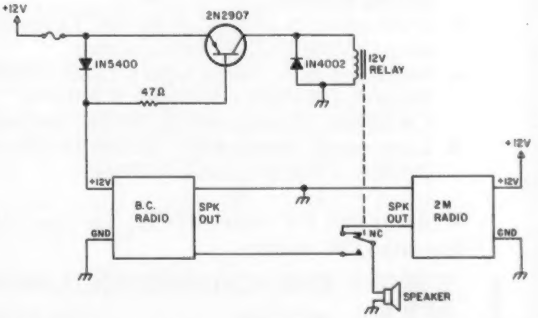
+12V
2N2907
1N5400
1N4002
12V RELAY
47Ω
+12V
+12V
B.C. RADIO
SPK OUT
GND
SPK OUT
2M RADIO
+12V
GND
NC
SPEAKER

SUPER AUTOMATIC SPEAKER SWITCH: This circuit will switch a speaker between your broadcast radio and your two-meter rig, depending on which radio is turned on at the time.—Haim Sandel KB2IV, Flanders NJ.

Homebrew Headquarters

"SMART" SQUELCH FOR SSB

73 MAGAZINE 8/82

- Detects human voice but ignores noise, steady tones and Russian woodpecker
- Works for voice signals below noise level
- Ideal for net activities
- Audio operated — no receiver modification
- Connects between audio output and speaker

KIT $49.95
Plus $2.50 Shipping & Handling

Other Kits:
- R-X Noise Bridge (hr 2/77)
- General Coverage Reception Drake R-4C Receiver (QST 5/81)
- 2 Meter Converter (73 4/82)
- 40 Meter QRP Transceiver (hr 1/81)
- Fun-Mitter (73 2/81) Fun-Ceiver (73 7/81)
- Fun-Oscillator (73 2/82) Fun-Amp (73 5/82) and others

1982 CATALOG 50¢

RADIOKIT
Box 411S, Greenville, NH 03048
(603) 878-1033

RTTY SCOPE

NEW!
HAL
RS2100
LOOP
OFF ON
RTTY SCOPE

At Last! An RTTY Tuning Scope!

And who else but HAL would bring you such a practical solution to the RTTY tuning problem. If all you have is flashing lights, you know how difficult it can be to match your transmit frequency with that of a received RTTY signal. The RS2100 RTTY Scope ends these problems with an accurate display of the received signal (both signal amplitude and phase). The RS2100 is a matching companion for the CT2100 Communications Terminal and may be used with most HAL and other manufacturers' RTTY equipment. An internal loop supply is included.

- **X-Y tuning scope indication**
- **1" diameter green phosphor CRT**
- **Front panel focus, intensity, and position controls**
- **Internal 200 VDC, 60 ma loop supply**
- **Two loop keying circuits (high voltage or optical isolator)**
- **3-1/2" × 8-1/4" × 10-3/16", 9 lbs net, 12 lbs shipping 120/240 VAC, 50/60 Hz power**
- **Scope indicator works with CT2100, DS2050, DS2000, CWR685, CWR6850, CWR670, CWR6700, ST5000, ST-6K, ST-5K, and more**
- **Loop supply works with CT2100, DS2050, DS2000, CWR685, and CWR6850**

Write or call for more details. See the RS2100 at your favorite HAL dealer.

HAL COMMUNICATIONS CORP.
BOX 365
URBANA, ILLINOIS 61801 **217-367-7373**
✓345

APPLIED INVENTION

THE **SOURCE** FOR SOLID STATE / STATE-OF-THE-ART

GaAs FETS by MITSUBISHI

2M — K Band. Very low noise and medium power.
BEST BUY: MGF1402 1.1dBNF (13dBG) @ 4GHz $15.00/
MGF1412 GUARANTEED 0.8 $50.25 — 0.9 or 1.0 dBNF @ 4GHz
MGF1403 GUARANTEED 0.7 dBNF @ 4GHz
Also: MGF1200, MGF1400, MGF1801 and MORE

Microwave Modules

MITSUBISHI X BAND Hybrid Integrated Circuits with Dielectric Resonator (0.12MHz/°C) GaAs FET Oscillators

FO-1010X 10.4 GHz, 15mw out, UER100 Flange	$37.50
FO-1210Y 11.5 or 12.0 GHz, UER120 Flange	$37.50
* **FO-UP11KF** Complete Heterodyne Rx, 10.468 GHz LO	$34.50
Use with 2 GHz IF for 12 GHz Satellite TVRO	
* **FO-DP13KF** Doppler Module 10.525 GHz UER100 Flange	$41.00
Modules mechanically tune ± 0.15 GHz, voltage tune ± 4 MHz	
* **X-Band** 15 dBG die cast horn antenna (UER100)	$17.00
* **GaAs FET Preamp** 1.7-2.1 GHz or 2.0-2.35 GHz, 2dBNF	$48.00

Active and Passive Components

OPTOELECTRONICS from **MITSUBISHI** and **SIEMENS**

* **LASER DIODES** 3 mw single mode CW. ML3101 830nM	$100.00
ML4101 780nM	$146.00
IR LED · High efficiency 16 mW @ 100 mA LD271	$ 0.75
PIN PHOTODIODE · Large area, fast detector BPW34	$ 3.00
UNIVERSAL PROGRAMMABLE SWITCHED CAPACITOR AUDIO ACTIVE FILTER. No external R or C. 16 pin DIP. RETICON R5620 $7.50/ Ap. Notes	$ 2.00
MRF 901 Substitute. 2SC2876, FT = 7GHz, 2.2dBNF @ 1GHz	$ 1.50
LEADLESS DISK CAPS 100, 220, 470, 680, 1000 pF 10 for	$ 2.50
MICROWAVE CHIP CAPS · Very low loss VITRAMON P7800 series G08(0.7-1.4 GHz) G04(1.3-2.6 GHz) G01(2.6-4.2GHz)	$ 1.00
STRIPLINE SHUTTLE TRIMMERS (VOLTRONICS) 0.1-2.5, 0.5-9.0pF	$ 3.19
HI-Q SEALED CERAMIC PISTON TRIMMERS (VOLTRONICS) 0.6-9.0pF	$ 3.41
* **THERMOELECTRIC HEAT PUMPS:** 19 Watt, 30x30mm, 8.6 volts	$ 21.00
1.6 Watt 4.6x4.6mm, 1.5 volts	$ 30.00

WE ALSO STOCK: SMA Connectors, Teflon/Glass PC board, negative voltage convertors for GaAs Fet bias, ferrite beads and torroids for preamps, GaAs Fet circuit designs, and more.

PROMPT SERVICE. SEND FOR CATALOG
MINIMUM ORDER $5.00 ADD POSTAGE AND HANDLING
* ITEMS (UPS) $3.75 · ALL OTHER ITEMS $2.50 (FIRST CLASS)
NY STATE RESIDENTS ADD 6% SALES TAX

R.D.2 ROUTE 21 HILLSDALE, NY 12529
518-325-3911
✓71

GLB

HIGH PERFORMANCE PRESELECTORS

MODEL P50 to P500

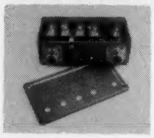

- **50 - 500 MHz**
- **Ultimate rejection over 80 dB**
- **Five large helical resonators**
- **Low noise**
- **High overload resistance**
- **Typical rejection figures:**
  - **±600 kHz at 144 MHz: −30 dB**
  - **±1.6 MHz at 220 MHz: −40 dB**
  - **±5 MHz at 450 MHz: −45 dB**
- **The solution to interference, intermod and desens problems on repeaters**
- **12V DC operation**
- **Dimensions only 1.6 x 2.6 x 4.75 excluding connectors**
- **Custom tuned to your frequency**
- **Low cost — only $69.95**
- **Allow $2.00 for shipping and handling**

We have a complete line of transmitter and receiver strips and synthesizers for Amateur and commercial use. Write or call for our free catalog.

We welcome MasterCard or VISA

GLB ELECTRONICS
1952 Clinton St., Buffalo, N. Y. 14206
1-(716) 824-7936, 9 to 4
✓143

≥≥ BIT "O" BYTE ≤≤

All Prices Include Shipping and Tax in the U.S.A. ALL DISK are WARRANTED against material defects for 90 days from date of purchase.

- 5 1/4 inch Diskettes (soft sectored), Center Reinforcing Ring, Jacket and plastic box-stand. = $27 for box of 10 to 20. 20 to 100 is $25 per box.
- SYMTEC HIGH RES LIGHT PEN—With software = **$185.00**
- 16K RAM CARD for the APPLE II or II + BARE BOARD = **30.00**
- PADDLE-ADAPPLE only = **$27.50**
- MAGIC KEYBOARD only = **$86.00**
- MICROBUFFER II For most printers 32K = **$250.00**
  Epson Parallel 16K = **$135.00**
  Epson Serial 8K = **$135.00**
- ECHO II Speech Synthesizer with Software on 3.3 disk and Speaker = **$170.00**
- THUNDERCLOCK PLUS with software = **$125.00**
  BSR X-10 INTERFACE OPTION = **$45.00**
  DOS-DATER DISK = **$20.00**
  PASCAL SOFTWARE DISK = **$20.00**
- RAMDISK-320 = **$1225.00**
  Advertised in SoftTalk.
- I will carry other items in the future. If you don't see what you need let me know. Coming soon VISA charging and computer ordering.

Most products carry a 90 day warranty.
The prices may change without notice.
Please send ORDERS with payment
and inquiries to:

✓153

BIT "O" BYTE
P.O. Box 60972
Sunnyvale, CA 94088

SATELLITE TV KIT

Sat-Tec
SATELLITE TV RECEIVER

THE POPULAR SAT-TEC RECEIVER IN KIT-FORM!

Featured in a Radio Electronics magazine cover story (May 82), the reliable R2B Sat-tec TV receiver is now operating in thousands of locations. The R2B is easy to build; pre-etched, plated boards with screened component layout assures accurate component placement and the critical IF section and local oscillator are pre-assembled and aligned! All parts are included for the R2B; attractive case, power supply, descriptive operating manual as well as complete assembly instructions. Features of the receiver include; dual conversion design for best image rejection, fully tunable audio to recover 'hidden' subcarriers, divide by two PLL demodulator for excellent threshold performance, tight tracking AFC to assure drift free reception, and of course, full 24 channel tunable coverage.

Build your satellite TV system around the R2B, close to ten thousand others already have and now it's available in kit form at a new low price. Order yours today.

A complete Satellite TV System requires a dish antenna, LNA (low noise amplifier), Receiver and Modulator.

R2B Receiver Kit	$359.00
R2B Receiver, Wired and Tested	$595.00
120° K Avantek LNA	$495.00
RM3 RF Modulator	$49.95

Prices include domestic UPS shipping and insurance.

RAMSEY ELECTRONICS INC.
2575 BAIRD RD.
PENFIELD, NY 14526
716-586-3950

✓185

VISA master charge

ORDER TOLL-FREE
1-800-828-6286

NICAD MEMORY ERASE – WHAT??

- Complete automatic operation
- Erases + Charges + Checks
- Rapid charges in 35 min. (typically)
- Automatically repairs shorted cells
- No dangerous heat build up
- Front panel selects up to 3 different packs
- Unlimited battery combinations with program modules (user programable)
- LED status indicators
- Supplied with universal EZ hook wire leads

Specify Voltage of Battery Pack(s) with order.

$79.95 plus $3.00 Shipping
(PA Residents add 6% sales tax)

Coming Soon – Multiple pack memory erase charger for municiple commercial applications - write for information or send requirements.

CONTROL PRODUCTS UNLIMITED

The GMS 401 is a complete automatic NICAD conditioner and rapid charger. Never before has this been offered anywhere at any price and it's so good it's being patented. NICAD memory characteristics must be dealt with otherwise your battery pack is not delivering all it could. The GMS 401 will automatically erase and rapid charge any type NICAD pack from 1 to 10 cells automatically.

CONTROL PRODUCTS UNLIMITED, INC.
P.O. Box 10, Downingtown, PA 19335
215-383-6395

✓190

HAVE RTTY—WILL TRAVEL

HAL TELEREADER

Yes, now you can take it with you! The new **HAL CWR-6850 Telereader** is the smallest RTTY and CW terminal available, complete with CRT display screen. Stay active with your RTTY and CW friends even while traveling. Some of the outstanding features of the CWR-6850 are:

- **Send and receive ASCII, Baudot, and Morse code**
- **RTTY and Morse demodulators are built-in**
- **RTTY speeds of 45, 50, 57, 74, 110, and 300 baud**
- **High or Low RTTY tones**
- **Send and receive CW at 3 to 40 wpm**
- **Built-in 5 inch green CRT display**
- **Four page video screen display**
- **Six programmable HERE IS messages**
- **Pretype up to 15 lines of text**
- **External keyboard included**
- **Runs on +12 VDC @ 1.7 Amperes**
- **Small size (12.75" × 5" × 11.5")**

Write or call for more details. See the CWR-6850 at your favorite HAL dealer.

✓345

HAL COMMUNICATIONS CORP.
BOX 365
URBANA, ILLINOIS 61801 **217-367-7373**

1982 INDEX

AMPLIFIERS

Egad! A 9-Tube Linear	Amplifier Design	W7CSD	Jan	12
The Fun-Amp	20-Watt CW	WA0RBR	May	32
Taming the 2-M Linear	Construction	VE3LMP	Dec	28

ANTENNAS

The Great Compromiser	Wideband Doublet	W5JJ	Jan	104
Those Amazing Bobtails	Why They Work	W1XU	Feb	30
Top-Notch for Top Band	Antennas for 160	N3BEK	May	26
The CCD Ant. Revisited	CCD Design for 40-M	W4ANL	May	40
Americanizing the German Quad	Horizontal Quad	WA3GWY	May	76
Zepp and Sons	End-Fed	W1GV	May	96
The Vertical Deuce	40 and 75 Meters	W9CRC	Sep	80
The J-Pole Love Affair	2-Meters and Mobile	WB5AOX	Sep	84
Pleasures and Perils of Crankup Towers	Tower Tips	K4TWJ	Oct	40
The Incredible Antenna Mark 2	Space-Saving	KL7ISA	Oct	44
The Multiband Vertical	20, 15, 10 Meters	W1GV	Oct	54
The Campbell J	2M Soup Can	W4YVY	Oct	60
The Coax Matcher	Tuner	W9PFJ	Oct	84
A Tuner for Antenna Fanatics	Save Your Finals	Staff	Nov	42
The Hangman's 2-Meter Collinear	6-Element Array	W1GV	Dec	10
Build Yourself A Paralyzed Beam	2M Array	WB2WIK	Dec	24

ATV AND SSTV

ATV's Stripper	ATV Converter	VE3CYC	Mar	20

CB CONVERSIONS

Peaking and Tweaking Surplus CB Boards	Hy-Gain Boards	WB0NPN	Mar	38
CB to CW?	Hy-Gain Boards	W1BG	Jul	18
Maximum Modulation for CB Conversions	Audio Preamp	AJ0P	Dec	122

CONSTRUCTION

Building for Beginners	Soldering, Etc.	N1II	Jun	42
Coping With PC Boards	Make Your Own	KC7M	Jun	48

CORRECTIONS

"Lab Quality...Supply"	Mar-Apr '80		Jan	146
"New Freqs. for IC-2"	Oct '81		Jan	146
"ATV's Stripper"	Mar '82		Mar	104
AEA Code Reader Review	Jan '82		Mar	104
"TVRO Signal Source"	Jan '82		Mar	104
"ATV's Stripper"	Mar '82		Apr	145
"The Hesitator..."	Jan '82		Apr	145
"The Masher"	Mar '82		May	145
"VHF Converter"	Apr '82		Jun	64
CES Microdialer Review	May '82		Jul	121
"Watching the Weather"	Apr '82		Jul	121
"VHF Converter"	Apr '82		Aug	135
"Coherent CW for VHF"	Jul '82		Sep	141
"The...Best CW Filter"	Jul '82		Sep	141
"Counter Evolutionary"	Aug-Sep '82		Oct	142
"Double Trouble..."	Sep '82		Oct	142
"Dissertation On...Pig"	Oct '82		Dec	144
"The $100 TVRO Rcvr"	Aug '82		Dec	144
"The Vertical Deuce"	Sep '82		Dec	144

CW

Hands Across the Water	CW on Cape Cod	KA1D	Jul	38
A Three-Piece CPO	Quick and Simple	WB5WAF	Jul	46
Coherent CW for VHF	Matched Filtering	W3QVC	Jul	48
The Very, Very Best CW Filter	Low-Cost Filter	WB4TYL	Jul	56
The True-Blue Keyer	Keyer With Display	W3BYM	Jul	60
Touch-Type CW	TRS-80 Program	K8TT	Jul	64
CW-The Air Force Way	How They Teach It	Metzler	Jul	72
CW and the Apple II	Morse Program	N5MR	Nov	84
Keyer on a Shoestring	Cheap	WB5PPV	Nov	104

EQUIPMENT MODIFICATIONS

Police Freqs for the TR-2400	HT Modification	N9AK	Feb	26
CQ Mars de IC-2A	Mars/CAP Capability	WD8JLW	Feb	46
Polishing Kenwood's R-1000	Several Easy Mods	K9EUI	Mar	34
Scanning With the IC-280	Drill No Holes	N7AAD	Apr	36
A Split Personality for the KDK FM2015R	Split Frequency	K0BV	Jun	40
F1 for the HW-101	True FSK	K0JH	Sep	20
Fine-Tune Your IC-280	5 kHz-Step Tuning	K4SB	Oct	68
A Gem of an RIT	For the SB-104	KK5R	Oct	70
Remote-Control Your IC-701	Several Functions	N2GW	Nov	14
The Sound of Silence	TS-180 Modification	HB9BLU	Nov	70
Tempo MARSer	MARS Capability	WB6IQN	Nov	76
Speed Demon	WPM for H-1410	K4ZHM	Nov	102

GADGETS

The Simplex Autopatch	Repeaterless Patch	WA7VZR	Jan	26
The Cheapskate	Diode Checker	K9QLL	Jan	30
The Hesitator: A Wiper Control	Rainy Day Project	N4UH	Jan	40
Touch-Tune With Thumbwheels	Feel the Frequency	ZL4LM	Jan	110
The Masher	Speech Processor	W5VSR	Mar	76
Line Voltage at a Glance	Voltage Monitor	W4RNL	Aug	84
The Splattometer	Overmod Warning	W1BG	Oct	10
Dissertation Upon Roast Pig	Surplus Transformers	N6TO	Oct	28
Automatic Beam Aimer	Set and Forget	K9AZG	Nov	22
Dial-A-Frequency	Remote Control	K1WGN	Dec	44
Red-Hot and Ready To Go	Cordless Solder Gun	W7XRV	Dec	101

HISTORY

Messages from Station Charlie	Spy Communications	Phenix	Jan	88
The Father of FM	E.H. Armstrong	Hammond	Feb	50
The AC4YN Story	Tibet, 1936-1937	G5YN	Aug	32
The Bunesti Caper	Ham Builds Spy Rig	W9PJF	Dec	56

I/O

Micro-Programmed Controllers	Control Concepts	K2OAW	Jan	68
CW Interface	Construction	W9JD	Feb	104
Compugrams Are Here	Message Handling	WA6ZZL	Apr	76
Got an Apple? Want RTTY?	Apple Interface	WB6FBN	Oct	34
Amazing Beam Header	PET BASIC Program	WA4NAG	Oct	46
Award-Winning Program	Contest PET Program	WB2GFE	Nov	94
The Program That Knows It All	BASIC for TRS-80	W8XW	Dec	72
Berserk Direction Finding	TRS-80 BASIC	WD8CBE	Dec	76

MISCELLANEOUS

Drama on Mt. McKinley	High Altitude Hams	W7KUF	Jan	18
Indian Hams Rejoice	Restrictions Lifted	Rama	Mar	64
Licensing for Americans Overseas	DX Licensing	KA3B	Mar	68
Innovation or Consternation	Radio Patents	AK0Q	Mar	78
Let's Go Shopping	Used Gear	WD4SKH	Mar	88
The Sinkhole That Ate Winter Park	Hams vs. Hole	KA4RUL	Apr	18
Detect Killer Tornadoes	Use a TV	K2VJ	Apr	50
Flash and Crash 101	Weather the Storm	K1NYK	Apr	94
Pacific Odyssey	DXpedition	KB7NW	May	12
Antenna Raising: the Good Neighbor Policy	Ham PR	AK5Q	May	42
Surviving the Unthinkable	After the Bomb-Pt. I	AK0Q	May	110
Surviving the Unthinkable	Part II	AK0Q	Jun	30
Crime-Stopper's Text	Rules of Thumb	Diefenbach	Jun	84
Electric Health Via Negative Ions	Ion Generation	W0OGX	Jul	52
All Tied Up in Knots?	Knot-Tying	KC7M	Oct	78
Shack from Scratch	Planning Ahead	W2XQ	Dec	84

MOBILE AND PORTABLE

Life-Support System for HTs	Charger and Box	WB6BHI	Nov	26
Frugal Floppy Bazooka	HT Antenna	N7BGZ	Dec	32

NEVER SAY DIE

Power Struggle	ARRL Board War		Jan	6
Dannals New Manager	ARRL Politics		Jan	6
Club 'Em	Ham Clubs		Jan	8
Greedy Green?	Personal History		Jan	148
Fruit Basket Leaks	Hussein in L.A.		Jan	148
Bunk in 73	CW vs. Phone		Jan	148
Synergism	Computers		Jan	148
Articles Needed	Call for Articles		Jan	150
More Detectors	Radar Detectors		Jan	150
Now, The Good News	New Legislation		Feb	6
Friendly Clubs	Advice for Clubs		Feb	131
Deregulation	FCC Paper		Feb	131
Ham Watch Repair	Replacing Batteries		Feb	133
Getting Rich	Work and Money		Feb	133
Morse and the Demised Plain Language Rules	Emergency Operation		Mar	6
Code Courses the Pits	Modern Methods		Mar	118
It's Up To Us!	Alien Radio Messages		Mar	120
We've Been Bashed	Critique		Apr	6
The CD Debacle	Civil Defense		Apr	6
Killing the Woodpecker	Self-Defense		Apr	8
ARRL Attacked	Ham Radio Magazine		Apr	44
Building	Call for Articles		Apr	44
The Dannals Deal	ARRL Director		Apr	44
Favors	FCC Shenanigans		Apr	45
Smith Charts	World Tour		Apr	45
Good ARRL News	Contest Rules Change		Apr	45
Reader Responses	Survey Results		Apr	46

THE LAST WORD IN READERS

MORSE BAUDOT ASCII READER
mba READER
MORSE · BAUDOT · ASCII READER

THE NEW
AEA
MBA-RO

FEATURES:

- 32 CHARACTERS FOR EASY HIGH SPEED COPY OF MORSE
- ASCII and BAUDOT RTTY
- NO RECEIVER MODIFICATION NECESSARY
- INSTANT SPEED TRACKING FOR MORSE CODE OVER WIDE SPEED RANGE FROM 2 TO 99 WPM
- OPERATES FROM 12 V.D.C.

For AEA Readers or other AEA Products, call or visit:

AEA
Brings you the Breakthrough!

Radios Unlimited
1760 Easton Avenue
Somerset, N.J. 08873
(201) 469-4599
(800) 526-0903 ✓105

Take your favorite H.T. out for a drive tonight.

VISA or MASTERCARD for same day shipment.

For $69.95 you get the most efficient, dependable, fully guaranteed 35W 2 meter amp kit for your handy talkie money can buy.
Now you can save your batteries by operating your H.T. on low power and still get out like a mobile rig. The model 335A produces 35 watts out with an input of 3 watts, and 15 watts out with only 1 watt in. Compatible with IC-2AT, TR-2400, Yaesu, Wilson & Tempo! Other 2 meter models are available with outputs of 25W and 75W, in addition to a 100W amplifier kit for 430MHZ.

✓382

Communication Concepts Inc. 2648 N. Aragon Ave., Dayton, OH 45420
(513) 296-1411

CODE★STAR--NEW LOW PRICE!

- ★ Ideal for Novices, SWL's and seasoned amateurs
- ★ Built-in code practice oscillator & speaker
- ★ 12 VDC Operation or 120 VAC with adapter provided
- ★ Optional serial/parallel ASCII output port

CODE ★ STAR
Microcraft

- ★ Copies Morse, Baudot & ASCII codes
- ★ Two optimized Morse ranges
- ★ Digital & Analog filtering with 16 db AGC
- ★ Automatic speed tracking 3 – 70 WPM

More Features Per Dollar Than Anything Else! Call or write for brochure or order direct.

CODE★STAR™Kit	CS-K $159.95
CODE★STAR Wired	CSF $219.95
Optional ASCII Output Port Kit	CS-IK $ 59.95
Optional ASCII Output Port Kit Wired (Specify 110 or 300 Baud and 20mA or TTL level)	CSIF $ 79.95

Send check or money order. Use your VISA or MasterCard. Add $5.00 shipping and handling for continental U.S. Wisconsin residents add 5% Wisconsin State Sales Tax.

Microcraft Corporation Telephone: (414) 241-8144
P. O. Box 513G, Thiensville, Wisconsin 53092

✓50

BASE

RINGO RANGER II

7dB GAIN
HIGHEST GAIN 2 METER OMNI
OUTPERFORMS CONE AND DOUBLE ZEPP
WORK MORE STATIONS
ELIMINATE NOISE
LIGHTNING PROTECTED
ACCESS MORE REPEATERS
ASSEMBLE EASILY
INSTALL QUICKLY
A COMPLETE ANTENNA ALL PARTS INCLUDED
600,000 HAPPY USERS BECOME ONE TODAY
ARX-2B 134-164MHz
ARX-220B 220-225MHz
ARX-450B 435-450MHz

TERRIFIC 2 METER RANGERS

MOBILE RANGERS

MORE RANGE
3 dB GAIN
5/8 λ STAINLESS WHIP
GRIP TIGHT 90LB MAGNET
CHROME PLATED BASE
NEAT APPEARANCE
THUMB LOCK ADJUSTMENT
NO WHIP CUTTING
LOW PRICE
MAGNETIC MOUNTS
AMS-147 146-148 MHz
AMS-220 220-225 MHz
TRUNK LIP MOUNTS
ATS-147 146-148 MHz
ATS-220 220-225 MHz

MOBILE

BUY FROM YOUR DEALER

cushcraft CORPORATION
THE ANTENNA COMPANY
48 Perimeter Road, P.O. Box 4680
Manchester, NH 03108
Telex - 953050 ✓106

Walkman Talkman	New Product	Apr 46
Energizer...or Nicad?	Battery Costs	May 6
A Word for DX Ops	Education	May 6
Blitz Code Learning	New Approach	May 117
Foreign Aid	DX Ragchewing	May 118
Fighting Back	Non-Smoker's Rights	May 118
Hooked	Becoming a Ham	Jun 6
Coping With Emergencies	Organization Plans	Jun 121
The Next Step	Future Strategies	Jun 123
Harry Thrown Out!	ARRL Politics	Jun 123
National Policy	Hams and CD	Jun 123
What's That Cloud?	Cigarette Sales	Jun 124
No News vs. Good News	Daily News Days	Jun 124
Harry, Where Are You?	ARRL History	Jul 6
Instant Licenses	FCC Test Sales	Jul 6
Dayton '82	Hamvention Success	Jul 6
We Need Kids	Mercenary Teaching	Jul 8
Navassa Time	DXpedition	Jul 8
China!	Travel	Jul 118
An ARRL Responsibility	Fighting Back	Jul 120
General Notes	Magazine Policy	Jul 121
Articles	Call for Articles	Jul 121
The Phone	Getting Through	Jul 121
The World's Fair--Knoxville	Fair Station	Aug 6
Saddle Stitching	73 Changes	Aug 139
A New Cover...Again?	73 Changes	Aug 139
Rochester	Hamfest Review	Aug 139
Travel	Home and Abroad	Sep 6
Radioaficionados	Finding Foreign Hams	Sep 128
Success	Teaching Values	Sep 130
Ionized	Ion Generators	Sep 130
Emergencies	Communications	Sep 130
Ham Publications	Magazines Decline	Sep 132
The Old Man	Reminiscences	Oct 6
The Non-DXpedition	CE0X Story	Oct 8
Someone Needs Help!	Repeater Alarms	Oct 100
Untold Wealth	Entrepreneurship	Oct 100
S-9 Gone, Too	Publishing Business	Oct 101
Circuits, Circuits	Call for Circuits	Nov 6
Where's the Solder?	Construction	Nov 6
CQ Fails Code Test	Misspelled Ad	Nov 8
No Second Languages	Immigrants	Nov 140
Bunch Gets Bashed	FCC Exam Changed	Nov 140
Should DXCC Be Prohibited?	PY0SB Dxpedition	Dec 6
Hamfest Catastrophe	Mail-Order Lotteries	Dec 172
The Great American Ham Club...Disaster	Making Clubs Succeed	Dec 174

NEW PRODUCTS

Advanced Analog Systems	Compandor Kit	May 124
Advanced Computer Cont.	Repeater Controller	May 123
Advanced Electronic	Keyer Update	May 124
Advanced Electronic	Reader/Converter	Jul 107
Alpha Delta	Control Console	Nov 136
Alpha Delta	Surge Protectors	Apr 133
Aluma Tower	Tower Trailer	Feb 136
Applied Invention	Active Filter	Dec 143
Arco Solar	Solar Module	Aug 127
Arunta Engineering	TVRO Receiver	May 125
AutoConnect	Autopatch	Sep 118
Benjamin Michael	24-Hour Wall Clock	Jun 119
Bilal Co.	Compact Antenna	Jun 119
Blacksburg Group	Straight-Key Keyer	Jul 104
Centurion International	Flexible UHF Antenna	May 123
CES	Phone Interconnect	Jul 104
CES	Microdialer	Oct 118
Channel Master	Earth Stations	Oct 116
Channel Master	Earth Station Rcvr	Nov 138
Com-Rad Industries	2M DDRR Antenna	May 124
Com-Rad Industries	Antennas	Oct 121
Commsoft Inc.	Apple SSTV	Aug 127
Contest Software	Logging Program	Jun 120
CQ Products	Operator's Desk	Jul 104
Current Development	Mobile Connection	Oct 118
Cushcraft	No-Radial Vertical	May 122
Cushcraft	Base Station Antenna	Sep 118
Daiwa	Speech Processor	Jan 153
Daiwa	Electronic Keyer	Jun 120
DenTron	Linear Amplifier	Aug 126
DenTron	5-Band Transceiver	Nov 134
DenTron	Monoband Transceiver	Dec 142
Desco Industries	Flashlight/mirror	Jan 154
Electronic Specialists	Power Line	Apr 133
Electronic Specialists	Phone Interconnect	Jul 104
Electronic Specialists	Microdialer	Oct 118
Encomm Inc.	Transceiver	Jun 119
Encon Corp.	Photovoltaic Catalog	Nov 136
Fox Tango Corp.	TS-830 Filter Kit	Nov 138
Frontier Enterprises	CW Instruction Pgm.	Feb 136
G&T Service Co	Callsign Display	Sep 118
Ghost Fighters	Satellite TV Ant.	Dec 141
Gillaspie and Assoc.	Portable Earth Stn.	Dec 140
Global Specialties	Breadboard	Sep 119
Global Specialties	'Scope Multiplexer	Oct 116
Global Specialties	Digital Pulser Kit	Dec 142
Gould Inc.	Standby Power System	May 123
Grove Enterprises	Antenna Tuner	Mar 110
Grove Enterprises	Wideband Antenna	May 125
Grove Enterprises	Scanner Converter	Oct 120
Guild Radio Rack	Shack Furniture	Dec 141
HAL Communications	RTTY/CW Terminal	Feb 136
HAL Communications	Telereader Terminal	May 123
Hamtronics	VHF Kits	Jul 104
Hamtronics	FM Repeater	Dec 141
Heath	Oscilloscope	May 125
Heil, Ltd.	Mike Equalizer	Apr 132
Henry Radio	Marine Portable	May 123
Hustler	1:1 Balun	Aug 127
Hustler	6-Meter Antenna	Oct 116
Hy-Gain	7-Element Tribander	Apr 132
Icom	6-Meter Multimode	Aug 126
Icom	IC-740 Transceiver	Sep 118
Icom	IC-45A UHF Mobile	Dec 142
IIX Equipment	Ginpole	Jun 119
Imac Products	Weather Station	Jul 106
International Crystal	Satellite Receiver	Aug 127
International Satellite	3.3 Meter Dish	Mar 110
JL Industries	Antenna Converter	Dec 143
Jon Presley	DX Prefix List	Mar 110
Kalglo Electronics	Surge Suppressors	Oct 118
Kantronics	CW to RTTY Converter	Apr 133
Kenwood	R-600 Receiver	Jan 152
Kenwood	TR-2500	Jan 152
Kenwood	4-Band Transceiver	Mar 110
Kenwood	TS-930S Transceiver	May 122
Kettlewell Eye Research	Aids for Blind Hams	Dec 142
Lance Johnson Eng.	Ground Plane Buss	Jun 119
Larsen Antennas	Mobile Radio Mount	Jun 120
Larsen Antennas	Quarter-Wave Ant.	Oct 120
Leader Instruments	Digital Multimeter	Jan 152
LNR Communications	TVRO Downconverter	Feb 135
Lunar Electronics	VHF/UHF Amplifiers	Nov 134
Macrotronics	Comm. Terminal	Aug 126
Martin Engineering	Tower Aid	Jun 120
MFJ Enterprises	Antenna Tuner	Jan 153
MFJ Enterprises	Keyers	Feb 135
MFJ Enterprises	SWR/Wattmeter	Mar 111
MFJ Enterprises	Inductive Modem	Apr 132
MFJ Enterprises	Active Antenna	Sep 119
MFJ Enterprises	Police Converter	Nov 138
Micro-Control	Repeater Power Amp	Jun 120
Microcraft	CW Reader	Jan 153
Microwave Filter Co.	Interference Trap	Aug 127
Mirage Communications	220 MHz Amplifier	May 122
MLM Associates	Heath Programs	Apr 132
MORTTY	Comm. Software	Nov 136
Non-Linear Systems	Circuit Analyzer	Sep 119
Palomar Engineers	Antenna Baluns	Apr 133
Palomar Engineers	VLF Converters	Apr 134
Palomar Engineers	Auto SWR Meter	Jun 119
Palomar Engineers	Antenna Tuner	Jul 106
Palomar Engineers	Electronic Keyer	Sep 118
Palomar Engineers	DTMF Decoder	Dec 140
Pegasus Electronics	Diversity Reception	Nov 136
Power Gain Systems	Coax Antenna	Mar 110
Proham Electronics	Modular Kits	Dec 142
R.L. Drake	Surge Shunt	Jan 153
R.L. Drake	Transceiver and Rcvr	Apr 132
Ridge Systems	RTTY Interface	Oct 118
Riehl Time	Solar Watch	Dec 141
Rivendell Associates	20 MHz Scope	Jun 120
Snyder Antenna Corp.	Compensating Dipole	Aug 126
Stellmaker Enterprises	Etching system	Jan 152
Telecom Industries	TVRO Receiver	Mar 111
Telecom Industries	Earth Station	Oct 118
Ten-Tec	Antenna Tuner	Feb 135
Ten-Tec	Satellite Station	Jul 106
TET Antenna Systems	Triband Beam	Dec 141
Thermax	Low-Cost Wind Power	Dec 140
Tuned Antenna Co.	HT Antenna	Mar 111
Twin Oaks Associates	CW Teaching Systems	Oct 120
Universal Software	CW and RTTY Program	Dec 140
Valor Enterprises	Mobile HT Charger	Feb 136
Valor Enterprises	Mike Stand	Apr 133
Valor Enterprises	Pro-Ham Antennas	May 122
Valor Enterprises	Mobile HF Antennas	Dec 142
VHF Communications	Novice Course	Aug 127
VoCom Products Corp.	Amplifier/Power Pack	Nov 138
W-S Engineering	Porta-Peater M-100	Nov 134
W-S Engineering	Simplex Link	Nov 134
W.H. Nail Co.	RTTY Program	May 123
Wahl Clipper	Soldering Station	Jul 104
Wayne Research	Antenna Coupler	Dec 143
Yaesu	Portable Transceiver	Jul 107
Yaesu	FT-102 Transceiver	Nov 134
Yaesu	Active Antenna	Dec 143

OPERATING

The Art of Listening	Speakers, etc.	W8FX	Feb 64
Operation Skywarn	Tracking Tornadoes	WB5ZAM	Apr 24
Tune In the World's Tinderbox	Mideast SWL'ing	Peterson	Jun 66
The Colorado Queen	Raft Transmissions	K3PUR	Jul 12
I Got My Ticket! Now What?	Advice	N1II	Nov 106

POWER SUPPLIES

Constant Current from A Voltage Regulator	Solid Supply	WA4WDL	Jan 39
The Ultimate Fuse	Overload Protection	W2OLU	Aug 52
Avoid an Electrical Nightmare	Ground Faults	N4UH	Oct 64
Protect Your Pass Transistors	Keep Them Cool	K8JL	Oct 76
The Money-Maker Power Supply	12V Low-Cost	WA6TTY	Nov 56
Build the Re-Fuser	Reusable Fuse	K5CN	Nov 72
No Smoking in the Ham Shack	Overvoltage Reg.	N7JJ	Nov 74

RECEIVING

Stormy Weather	Weather Broadcasts	W9CGI	Apr 102
"Smart" Squelch for SSB	Voice-Only Squelch	W9MKV	Aug 44
Another Audio Filter Project	A QRM-Crusher	W4MLE	Nov 32
The Tube Returns	1-Tube Receiver	W1BG	Dec 64

V-J POWER UP

2 METER 90 WATT OUTPUT AMPLIFIER WITH 18 DB GAIN PREAMP

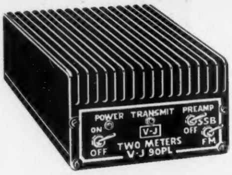

Model 90PL FOR ONLY **$139.95***

FACTORY DIRECT PLUS SHIPPING

- **FREQUENCY** range 144 - 148 MHz
- **OPERATION FM or SSB** (completely linear) Class AB1
- **RF DRIVE** 1 to 30 watts
- **KEYING RF** activated with high quality relays
- **SSB** operation built in delay
- **POWER REQUIREMENTS** typical 10 watts drive, 13 amps at 13.8 VDC
- **IDLE** current 20 mills
- **MOBILE** or **FIXED** operation
- **PREAMP** 18DB gain minimum
- **NOISE FIGURE** less than 1.5 DB
- **PREAMP KEYING** independent — separately RF activated relays
- **CONSTRUCTION** wrap around aluminum heat sink 2 pieces 360 degrees cooling
- **SIZE** 7"(w) x 6"(d) x 3"(h) — **WEIGHT** 3 lbs. 9 ozs.
- **IMMEDIATE SHIPMENT**

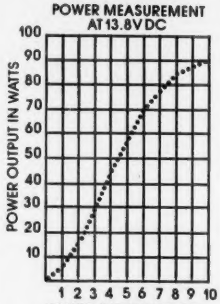

POWER CHART

SPECIAL OFFER

Matching Power Supply **$99.95*** PLUS SHIPPING

15 AMP SUPPLY wt. 13 lbs. size 8"(w) x 5"(h) x 6"(d)
IMMEDIATE SHIPMENT
ALL PARTS AND LABOR WARRANTED ONE FULL YEAR

VJ90PL Amplifier $139.95 plus $3.00 shipping
VJ15 POWER Supply $99.95 plus $7.00 shipping
*Prices USA only

VISA, MASTER CHARGE, M.O. or C.O.D. • PHONE (713) 477-0134

V-J PRODUCTS, INC. 505 East Shaw, Pasadena, Texas 77506
SERVING THE ELECTRONICS INDUSTRY SINCE 1965

PORTAPEATER™

M100 A INSTANT REPEATER

ANY BAND ANY MODE

$179.00 assembled unit

$99.00 assembled board

- *4Channel PROM CW I Der
- *VOX or COR operation
- *250 volt switching capability
- *An Instant Repeater
- *Works with any type radios
- *Complete Timer Functions
- *Built In Test Functions
- *20 Page Technical Manual

RECEIVER AUDIO INPUT
LOCAL MICROPHONE
PTT OUTPUT
TRANSMIT ON
ID TEST
DC POWER
PORTABLE EMERGENCY REPEATER SYSTEM
PORTA PEATER
W-S ENGINEERING

(Fully tested, programmed, assembled) ↙302

W-S ENGINEERING P.O. BOX 58, PINE HILL, N.J. 08021
(201-852-0269)

Homebrew Headquarters

"SMART" SQUELCH FOR SSB

73 MAGAZINE 8/82

Detects human voice but ignores noise, steady tones and Russian woodpecker
Works for voice signals below noise level
Ideal for net activities
Audio operated — no receiver modification
Connects between audio output and speaker

Other Kits:

- R-X Noise Bridge (hr 2/77)
- General Coverage Reception Drake R-4C Receiver (QST 5/81)
- 2 Meter Converter (73 4/82)
- 40 Meter QRP Transceiver (hr 1/81)
- Fun-Mitter (73 2/81) Fun-Ceiver (73 7/81)
- Fun-Oscillator (73 2/82) Fun-Amp (73 5/82) and others

KIT $49.95
Plus $2.50 Shipping & Handling

1982 CATALOG 50¢

RADIOKIT
Box 411S, Greenville, NH 03048
(603) 878-1033

↙454

HT-Power!

Super Stick II & III

+9db 5/8 wave + 3 db 1/4 wave

Plus a 2 Meter or 220 mhz Duck For Under A Buck

$19.99 + 1¢ FOR THE DUCK

THE WORD IS OUT!

The SSII 2 meter & SSIII 220 mhz 5/8 wave ants. exhibit 9db gain over a short rubber duck when fully extended and 3db when collapsed to a quarter wave. The SSII or SSIII is the solution to many of those fringe area problems that plague every repeater system. With the Tuned Antenna's exclusive modular construction you can replace or exchange any of the 15 types of base connectors, plus the telescopic section may be replaced for only $5.00. The tuned loading coil/spring is soldered to the machined end caps not swedged...And there are no ticky tacked capacitors or leads in the SSII or SSIII's loading coil to break.

There are no short cuts in designing and building quality ants. The Super Stick ants. are the only 5/8 wave ants. that spec gain in db at a 1/4 wave and 5/8 wave over a rubber duck. These gain figures were obtained from extensive field testing on HT's. Now you know why the word is out. The SSII & SSIII ants. give your HT more effective power. Call one of our 112 dealers today.

RD25 Stubby
MODULAR CONSTRUCTION FEATURES
REPLACEABLE TELESCOPIC SECTION
TUNED COIL/SPRING

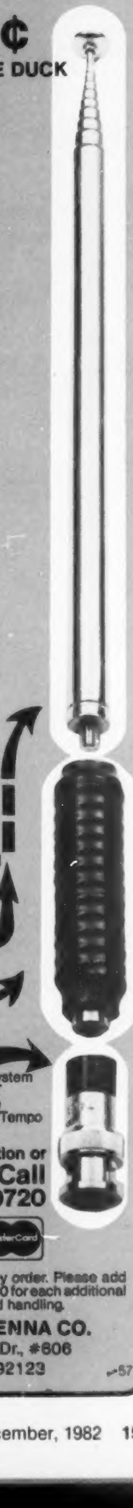

This Multi-Based System available for any HT BNC, TNC, "F" Type PL-259, or Motorola/Tempo

For Dealer Location or To Order Call (714) 268-0720

VISA MasterCard

Terms: C.O.D., check or money order. Please add $2.00 for first antenna and $1.00 for each additional antenna to cover shipping and handling.

THE TUNED ANTENNA CO.
9520 Chesapeake Dr., #606
San Diego, CA 92123

↙57

REPEATERS

Put Talking Time on Your Repeater	Talking Clock	WA4VYR	Jan	116
The Porta-Peater--the Instant Communicator	Controls 2 Rigs	WA2BHB	Mar	12
Death for Squelch Tails	Audio Delay	WA2NYE	Dec	14
Taking It Higher	Antenna Height	W4MLE	Dec	36
Improving God's IDer	K2OAW Modifications	K9XI	Dec	51

REVIEWS

AEA	Morse/RTTY Reader	KA1LR	Jan	119
Astron	RS-7A Power Supply	AB1Z	Aug	131
CES	Microdialer	KA1LR	May	138
Com-Rad Industries	CR2A Antenna	W1XU	Oct	111
Com-Rad Industries	"Mobile Ear" Ant.	W1XU	Nov	140
Curtis	K-5 Keyer	KA1LR	Mar	144
Cushcraft	R-3 Vertical	W1XU	Oct	107
Daiwa	DK-210 Keyer	W1XU	Sep	109
Debco	Charger	N8RK	Jan	125
DFD Systems	RTTY System	K0DG	Feb	119
Digital Electronics	Comm. Terminal	N4DDS	Aug	99
Electric Motion Co.	Grounding Braid	KA1LR	Apr	122
Flesher Corp.	Terminal Unit	WB6CRD	Aug	106
Heath	SA-2060 Tuner	AG9V	May	139
Heath	SA-5010 Keyer	KA1LR	Jun	117
Heath	VL-1180 VHF Amp	WB8BTH	Jul	136
Heil	Mike Equalizer	KA1LR	Aug	130
Icom	IC-720A	AE1K	May	136
Icom	IC-4A Hand-Held	N8BSG	Jul	133
Icom	IC-25A Mobile Rig	KA1D	Jul	135
Icom	IC-730	KA1LR	Oct	101
Icom	290A/E 2-M Xcvr	K1XR	Dec	149
Indiana Quick Charge	Charger	N8RK	Jan	125
KB1T Radio	Contest Calendar	WB8BTH	May	137
KDK	FM-2025 Xcvr	N8RK	Feb	118
Kem-Tron Industries	KTI-20 Power Supply	AG9V	Oct	109
Kenwood	TR-2500 HT	WB5GCX	Jun	115
MFJ Enterprises	J-312 VHF Converter	KA1LR	Apr	120
MFJ Enterprises	Computer Interface	Hall	Aug	130
Microlog	ACT-1 Terminal	KA1LR	Apr	121
Microwave Modules	Morse Trainer	AG9V	Jun	118
Multiband Antennas	Spider Antenna	W1XU	Oct	106
NCG	QRP Transceiver	KA1HY	Jun	116
NCG	HF 10/160 Xcvr	W1XU	Dec	148
Palomar Engineering	SWR/Power Meter	W1XU	Oct	111
Radio Publications	Interference Book	N8RK	Feb	119
Radio Society of G.B.	HF Antenna Book	W1XU	Dec	150
Rivendell Associates	Oscilloscope	N8RK	Aug	132
Rogo Computer Products	CW Software	KC0CE	Oct	110
Silicon Systems	DTMF Decoder	AG9V	Aug	131
Spectrum International	The Morse Talker	AG9V/1	Jan	125
Standard Communications	Portable Xcvr	WB8BTH	Apr	123
Tab Books	Packet Radio Book	KA1LR	May	138
Teltone	Tone Decoder Board	WA4TEM	Jan	121
Vani-Plate Co.	License Plate Holder	W1XU	Oct	104
Yaesu	FT-290 Transceiver	KA1LR	Jan	120
Yaesu	FT-680R	KA1LR	Mar	142

RTTY

Micro Modem	TU for Computers	WA4GKO	Sep	10
No-Frills RTTY	Surplus	WA4STO	Sep	24
Incredibly Simple RTTY	TRS-80 Interface	W0XI	Sep	28
RTTY/Tribander Marriage	Full Duty Cycle	K0ARG	Sep	32

SATELLITES

Shoot the Moon!	Visual Tracking	W9CGI	Feb	34
OSCAR Pathfinder	Apple II Program	WB6NQK	Mar	46
Watching the Weather	FAX Reception	KA9DGL	Apr	10

TECHNICAL AND THEORY

Fighting Air Pollution	Tuner Theory	W2AET	May	68
Digital Basics	Part I	K4IPV	Sep	72
Digital Basics	Part II	K4IPV	Oct	20
Digital Basics	Part III	K4IPV	Nov	46
Winning the Coax War	Feedline Theory	W9RTF	Dec	90

TEST GEAR

Build This Antennalyzer	Antenna Tester	W1BG	Feb	16
Measure Ohms with Your Calculator?	For High Ohms	Johnson	Apr	28
Poor Man's Spectrum Analyzer	Scope Add-On	WB5IPM	Aug	10
Multi-Purpose Peak Adapter	Read Meter Peaks	K9EUI	Aug	54
VUM:Volume Units Meter	Easy dB Meter	W4MLE	Aug	72
Analog Isn't Dead	Use of Meters	WB6AFN	Aug	76
Confessions of a Counter Evolutionary	Deluxe Counter	WA2FPT	Aug	100
Confessions of a Counter Evolutionary	Part II	WA2FPT	Sep	38
A Perfect "10"	10 Function Meter	WA2BHB	Nov	10
Everyman's Audio Amp.	1-Chip Amplifier	W3KBM	Nov	90
Cutting Current to Size	Current Measurement	W7CRY	Dec	108
All-American Audio Signal Generator	Variable Frequency	WA2SUT	Dec	116

TRANSMITTING

The Fun-Oscillator	QRP Vfo	WA0RBR	Feb	12
Build This Digital Vfo	Microprocessor	WA5VQK	Jun	12
Double Trouble on 50 MHz	DSB QRP	KL7GLK	Sep	58

TVRO

TVRO Signal Source	Test Gear	N1BEP	Jan	46
Satellite TV Glossary	Part II	Reed Pub.	Jan	54
Going Bird Hunting?	Sat. Central Pt. III	Gibson	Jan	60
A Dish Antenna Anyone Can Build	Parabolic	W8DJY	Feb	88
Job's Own LNA	Low Noise Amplifier	WA4CVP	Feb	92
Microwave Master	Wave Behavior	WB4APC	Feb	96
Which TVRO Antenna Is Best?	Sat. Central Pt. IV	Gibson	Mar	52
Home-Brew a TVRO Downconverter	Construction	WA4CVP	Mar	58
TVRO Q&A	Part I	WB0POP	Mar	62
TVRO Dish Selection Tactics	Sat. Central Pt. V	Gibson	Apr	54
Taylor Howard: TVRO Trailblazer	Profile	N8RK	Apr	60
TVRO Q&A	Part II	WB0POP	Apr	62
'Lite Receiver IV	Part I	WA4CVP	May	48
TVRO Sound Decoders	Sat. Central Pt. VI	Gibson	May	58
'Lite Receiver IV	Part II	WA4CVP	Jun	52
TVRO Transducer	Antenna to LNA	WA4CVP	Jun	58
The MTV Music Box	Sat. Central Pt. VII	Gibson	Jun	60
TVRO: Georgia Style	Antenna From Junk	N8RK	Jul	96
The $100 TVRO Rcvr	Sat. Cent. Pt. VIII	Gibson	Aug	60
The $100 TVRO Rcvr	Sat. Central Pt. IX	Gibson	Sep	60
TVRO Q&A	Part III	WB0POP	Nov	64

VHF AND UP

VHF Converter	2M Receiving	Edwards	Apr	68
Omni-Gain: A Collinear For 70 and 23 Cm	For ATV and FM	WA6SVT	May	64
Are You Ready For 900 MHz?	Using Microwaves	WB4LNM	Jun	74
Try the GHz Getter	Antenna	WA4WDL	Oct	50

HAM HELP

I need a manual or a copy of it for the Globe Scout model 680-A. I will gladly pay all costs.

Dennis Cornell
7835 Captain St.
Millington TN 38053

I am looking for the following: MK 731/ARC-51X, H-157/AIC, H-158/AIC, ME-57/U, USM 281E, ME-11/U, URM-120, URM-127, O-1131/GRC, URM-103, AN/AIC-25, PRC-49, PRC-90, URC-10, ARA-50, SRD-7, URD-4, OA-3633/ORC, R442/VRC, RT524/VRC, PRC-74B, RT-662/GRC, R1051/VRR, 61BT, ARC-159. I also need modules for the following: ARC-58, SG-179A, AM1528B/URC, CV465C/URC, RE-284/URC, 0-655/URC, MC-286B/URC, KY-305/URC, CV-466A/URC, CV-987/GRC-110A, AM1525/URC, AM-476C/AIC-10 unpotted, CU786/TRC-75, CU749/TRC-75, C2848/TRC-75, URM-124, MK-500/U, 878L-3, GRM-21, GRM-10, CU-523/ARC-58, C-1939/ARC-58, R1149/ARC-58(v), C-1940/ARC-58, R-1283/GRC, R484/APR-14, APR-13, URT-23(v), AM-1780/VRC, H-250/U, RT834/GRC, R1123/ARC-73, C-4074/RC-73, C-3940/ARC-94, URM-205, VRM-1, and USM-223. I am also seeking any documentation on the ARC-58, TRC-75, and ARC-159, and I would like to hear from anyone using the TRC-75.

Leroy Ritta
PO Box 102
St. Marys 5042
South Australia
Australia

I need the 20-meter heterodyne oscillator coil (part no. 40-771) for my Heath SB-301 receiver.

George Savino KV2V
368 N. Monroe Ave.
Lindenhurst NY 11757

I would like a schematic for an Allied Star Roamer receiver, number 22-3993-710042-713.

Joe Hustak WA5ZNO
6821 NW 27th St.
Bethany OK 73008

I am in need of videotapes (VHS format) of Novice- and General-class theory material. I also need good audio tapes for mastering Morse Code.

Robert M. Gallery
9214 Weathervane Place
Gaithersburg MD 20879

I need a 3CV1500 tube for my Alpha Vapor amplifier.

David Ornee KA9JKQ
4615 Howard Ave.
Western Springs IL 60558

I need help correcting a severe drift problem in the lmo/vfo of my Heath SB-102. Anyone with information on this problem or who can fix it, please write.

Harold Wright K4MFN
Rt. 1 Box 259
Chancellor AL 36316

I am trying to find a 3-inch picture tube, type C6407, for a Symphonic model TPS-30 television. I would also be interested in buying the entire set if the picture tube is good.

Al Duester
179 Woods Hole Rd.
Falmouth MA 02540

I am badly in need of the manual or schematic for Navy surplus receiver R808/GRC-14, a unit of radio set AN/GRC14.

Lee A. Grunewald K5JGZ
1020 K St. NW
Miami OK 74354

I need the construction manual and schematic for a Dycomm 2-meter linear amplifier. I will pay for the original or copying costs and postage.

Marvin Rosen N3BQA
20 W. Madison St.
Baltimore MD 21201

Wanted: 40-kV, 0-200-pF vacuum variable capacitor.

Cliff Young WA2TGY
PO Box 790
Parker CO 80134

SATURN V

STATE-OF-THE-ART

The Saturn V is a deep fringe microwave receiver for homeowners that are outside of the service area of local pay TV stations (i.e., HBO, Showtime). It is normally used within line of sight of a transmitting tower in a 50 mile range and is simply attached to your TV antenna mast. This unit is completely ready to install including all cable and mounting hardware. It is designed to be installed by the homeowner.

We accept MasterCharge & Visa.

Microwave and Satelite Systems

JDL Industries T.M.

1-3	$165.00
4-11	$120.00
12-49	$105.00
50-99	$ 95.00
100-149	$ 85.00
150-up	$ 80.00

4558 Auburn Blvd., Suite 208
Sacramento, California 95841 (916) 454-2190 ✓72

TUSA

A WHOLE NEW WORLD OF TV VIEWING WITH TUSA'S NEW MODEL CVU-40, 40 CHANNEL CABLE TV CONVERTER

Receive all the EXTRA CABLE TV "MIDBAND" & SUPERBAND CHANNELS on your UHF DIAL.

Eliminates the need for renting or leasing. This stable and reliable system converts extra cable TV channels so they can be received on the UHF tuner of your TV set.

Use of this unit may be subject to rules by your local cable TV Co.

A MUST FOR VIDEO-TAPING FROM CABLE TV!

The system allows you to program both pay (pay TV decoder required) and standard cable channels for taping on any VCR — while you are watching a different channel on your TV.

Now $28.95 ea. PLUS POSTAGE

Simple to install and operate on any make of TV with UHF.

NOW AVAILABLE
NEW TUNEABLE DELUX MODEL CVU-1000 $34.95 ea.

POPULAR IC's

TOP QUALITY NO SECONDS

TYPE	DESCRIPTION	1 - 9	10 - UP
LM-380N	2 watt Audio Power Amp	$1.49	$1.29
LM-386N-3	Low Voltage Audio Amp .500W/9V	1.59	1.29
NE-564N	Digital Phase Locked Loop	3.50	3.15
LM-565N	Phase Locked Loop	1.49	1.29
LM-733N	Video Amp	1.89	1.44
MC-1330	Video Detector	2.49	1.89
MC-1349	Video If Amp	2.06	1.85
MC-1350	Video If Amp	1.75	1.56
MC-1352	Video If Amp AGC	2.69	2.09
MC-1358	Audio If Amp	1.95	1.79
MC-1374P	R.F. Modulator	3.19	2.87
MC-1458	Dual Comp. Op Amp	.99	.79
MC-1496N	Balanced Mod/Demodulator	1.79	1.59
MC-5121	Hybrid Amplifier	13.72	Call
LM-1800	PLL Stereo Decoder	4.49	3.95
LM-1889	Video Modulator	2.95	2.49
	LINEAR VOLTAGE REGULATORS		
LM-7805	5 Volt Positive Volt. Reg.	1.39	1.25
LM-7808	8 Volt Positive Volt. Reg.	1.39	1.25
LM-7812	12 Volt Positive Volt. Reg.	1.39	1.25
LM-7815	15 Volt Positive Volt. Reg.	1.39	1.25
LM-7818	18 Volt Positive Volt. Reg.	1.39	1.25
LM-7824	24 Volt Positive Volt. Reg.	1.39	1.25

WINEGARD 75 OHM UHF YAGI ANTENNAS

12 db GAIN
CHANNELS 44 - 52
$8.95 EA.
6 OR MORE
$6.95 EA.

OPTIONAL
Winegard UHF Antenna Preamp
18db Gain
$39.95 ea.

BRAND NEW UHF VARACTOR TUNERS

Sanyo 45 MHz Output — YOUR CHOICE $24.95 ea. — Mitsumi 45 MHz Output

Call for Quantity Prices

POPULAR MICROWAVE PARTS

MRF-901	$2.75
9 - Up	2.19
MRF-911	3.46
9 - Up	3.12
MBD-101	.88
CHIP CAPS - .001 mfd	.50
28 - Up	.30
2N6603 (formerly MRF-902)	11.98

MV-2109
33pf Tuning Diode
1 - 9 .... $1.20 ea.
10 - Up ..... .98 ea.

5% MICA CAPS 5%

10pf	.42¢ ea.	560pf	.68¢ ea.
43pf	.36¢ ea.	1200pf	.89¢ ea.
110pf	.36¢ ea.	3000pf	1.39 ea.

Radial Lead Caps

10 mfd@35V	1 - 11	$.25 ea.
	12 or more	.16 ea.
1 mfd@35V	1 - 11	.25 ea.
	12 or more	.16 ea.
470 mfd@35V	1 - 11	.59 ea.
	12 or more	.49 ea.
1000 mfd@35V	1 - 11	.89 ea.
	12 or more	.69 ea.
2200 mfd@35V	1 - 11	1.29 ea.
	12 or more	1.09 ea.
2200 mfd@50V	1 - 11	1.69 ea.
	12 or more	1.39 ea.

Axial Lead Caps

1000 mfd@50V	1 - 11	$.98 ea.
	12 or more	.79 ea.
2200 mfd@35V	1 - 11	1.39 ea.
	12 or more	1.19 ea.
2200 mfd@50V	1 - 11	1.89 ea.
	12 or more	1.59 ea.
3300 mfd@35V	1 - 11	1.98 ea.
	12 or more	1.79 ea.

Call us for CERAMIC DISCS

CABLE CONNECTOR

F-59 Male connector for RG-59/U cable. Complete with ferrule. Mates with female "F" connectors.

25¢ ea.
100 for $14.70

TUSA MAX-2 LOW LOSS MATCHING TRANSFORMERS

Indoor 75 - 300	$1.29
10 - Up	.98
Outdoor 75 - 300	1.60
10 - Up	1.49

PROJECT BOXES
Woodgrain

This box is 11¾"W - 4½"H - 6½"D with a removable aluminum U-shaped chassis 11"W - 3½"H - 6"D inside.

$12.50 ea.
4 or more $10.95 ea.

UHF - VHF - FM SPLITTER
40-900 MHz
TUSA MAX-3

Low Loss 3.5-4 db, Low VSWR
Waterproof Housing $2.49 ea.

SURPLUS AUDIO & VIDEO RF MODULATORS

Hook up sheet included
Now $5.49 ea.

DELUXE A-B SWITCH

For CATV - MATV - VCR
75 ohm - 90 db Isolation
While They Last $6.95 ea.

SURPLUS SYLVANIA VHF VARACTOR TUNERS

45 MHz output. Channels 2 through 13 as well as the midband channels. Schematic included.

WHILE THEY LAST!
$13.95 ea.

POPULAR MISCELLANEOUS PARTS

10K Volume Control with DPDT switch	$1.49
10 - Up	1.19
¼ w 10K Thumbwheel pots	
1 - 12	.39
13 - 50	.35
Toroids - T30-12	.46
20 - Up	.25
Toroids - T37-2	.38
20 - Up	.25

ORDER NOW
TOLL FREE
800-854-4655
OUTSIDE CALIFORNIA
714-635-5090
INSIDE CALIFORNIA

R.F. ELECTRONICS
1056 N. STATE COLLEGE BLVD., DEPT. G
ANAHEIM, CALIFORNIA 92806

✓156

OPEN
TUES - FRI
10 - 6
SAT 10 - 5
CLOSED
SUN & MON

Call or Write for FREE Mail Order Catalog

MAIL ORDERS WELCOME - PLEASE INCLUDE POSTAGE - SHIPPED SAME DAY RECEIVED - NO MINIMUM ORDER

SATELLITE TV SYSTEMS

"COMPARE OUR QUALITY, PRICES AND SERVICE!"

WE MANUFACTURE:

PARABOLIC DISHES
POLAR MOUNTS
DEMO TRAILERS
CUSTOM PARTS
MOTORIZATION SYSTEMS
LNA HOLDERS
ALUMINUM HORNS

WE STOCK:

WASHBURN
KLM
AVANTEK
GARDINER
GILLASPIE
DRAKE
LOWRANCE
ALLIANCE
ATV
CABLE & CONNECTORS
SWITCHES & HARDWARE

CALL, WRITE OR ✓ FOR OUR LATEST BROCHURE AND PRICES.

AUSTIN C. LEWIS
K4GGC
901-784-2191

LEWIS CONSTRUCTION CO.
P.O. BOX 100
HUMBOLDT, TN. 38343

"IN BUSINESS AT THIS LOCATION SINCE 1964" ✓452

COMPARE the HAZER™ with foldover + telescoping towers

- Antenna systems mount on Hazer-Hazer follows parallel to outside of tower - Raise to tower top or lower completely to ground level.
- Safety lock system on Hazer operates while raising-lowering & in normal position. Never can fall.
- Weight transferred directly to tower. Winch cable used only for raising & lowering.
- Will support most antenna arrays up to 20 sq. ft.
- High quality materials & workmanship
- Safety - speed - convenience - smooth travel
- Ease to install and use
- For Rohn 20 & 25 tower — Other towers on request

Complete with winch, 100 ft. of cable, hardware and instructions.

HAZER II Heavy alum. $279.95 + $17.00 UPS
HAZER III Standard alum. $199.95 + $13.00 UPS
HAZER IV Heavy gal. steel $249.95 + $28.00 UPS

Specify mast diameter when ordering.

MARTIN ENGINEERING P.O. BOX 253 BOONVILLE, MO 65233

✓134 **816-882-2734**

Introducing our Latest Model — NOVAX II

SIMPLEX / DUPLEX AUTOPATCH

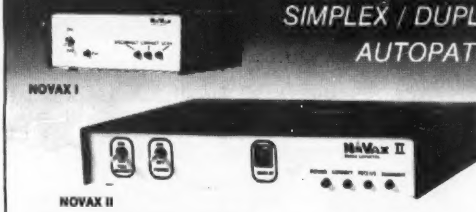

NOW TWO MODELS TO SERVE YOU BETTER

YOUR OWN PRIVATE AUTOPATCH

NOVAX MOBILE CONNECTION

NOVAX interfaces your standard 2 meter; 220; 450; etc. Base station and telephone, using a high speed scan switching technique so thct you can direct dial from your automobile or with your HT from the backyard or poolside — Automatically ... Easy installation transceivers, featuring solid state switching, offer best results ... Available interfaced with an ICOM 22U.

FEATURES	NOVAX I	NOVAX II
• 3 min. Call duration timer	YES	YES
• Up to 45 sec. activity timer	YES	YES
• Single digit Access Control	YES	NO
• DTMF (Touch Tone)* phone connection	YES	YES
• 4 digit Access Control	NO	YES
• Toll Restrict	NO	YES
• LED Digital Display	NO	YES
• Vinyl covered alum. case size	5" x 6" x 2"	10" x 8" x 1¾"
• Directly Interfaces with Repeater	NO	YES
• Rotary Dial System (incl. Last digit dial)	NO	YES—"Option"—$49.95
• Ring Back (reverse autopatch) "Option"	YES—$39.95; Kit $29.95	YES—Wired—$39.95
• Price	Kit;$169.95/wired $219.95	Wired only $279.95
N.Y.S. Res. add appro. Sales Tax	SHIPPING ADD $3.50 in U.S.A.	

* Trademark ITT

To order, send check, money order to:
MASTER CHARGE AND VISA ACCEPTED

Current Development Corporation
(formerly R.W.D. Inc.)

Box 162 - Tudman Rd.
Westmoreland, N.Y. 13490
or Phone 315-829-2785 ✓21

✓See List of Advertisers on page 130

DX-Notes Have Gained Wide Acceptance *In the Amateur Media
*At DAYTON Hamvention *All across the USA *With DX TOO

5B DXCC PLUS
*SEVEN Wide W/C Columns
*Log Entire DX Callsign
*YOU Choose Modes/Bands
PLUS *Buro *3rd Party *More
*Enter YOUR Atlas Page #
*CQ Zone *IARU Continent
*Unique "Rareness" Guide
*Latitude *Longitude
PLUS Info Computed for YOUR QTH:
*Time Zone Difference
*EXACT Beam Heading
*Miles *Kilometers

DX-Notes Invites Comparison
*Compare Accuracy
*Compare Efficiency
*Compare Useability
*Compare Convenience
*Compare Completeness!
PLUS PREFIX Cross Reference
1200+ Current, Commemorative
Special Event & Historic
Prefixes Indexed
PLUS COUNTRY Cross Reference
500+ Possessions, Islands,
Deleted, ETC Names Listed

JARL Awards Kit
*Highly Acclaimed Worksheets
*AJD 10 Call Areas
*WAJA 47 Prefectures
JCC 647 Cities
*JCG 569 Guns
Complete with JARL Information
*Logical Organization
*Efficiency Engineered
Alphabetical Cross Reference
*Determine the JARL Code #
*Available ONLY from KH6MD
*1400 Entries Listed
PLUS FREE Bonus
**3075 US Counties Listing

PLUS FREE Bonus **5B WAZ Kit : BUY DX-Notes Just $12.95PPd ! JARL Awards Kit Just $7.95PPd

Send Call, Name, Address, Latitude, Longitude, Time Zone AND Check or Money Order TO:
KH6MD Randall Sherman POB 158 Kahului, Maui, HAWAII 96732

147

PRINT THE WORLD

See What You've Been Missing!

Stay in touch with world events, monitor weather, ship traffic, and radio amateurs. Connect to your receiver and display shortwave radio teleprinter and Morse code transmissions with the new receive-only **HAL CWR-6700 Telereader.**

- **Receive ASCII or Baudot RTTY**
- **Six standard RTTY speeds**
- **3 RTTY shifts for low or high tones**
- **Adjustable space for fine tuning**
- **Receive Morse code — 4 to 50 wpm**
- **16 lines by 36 or 72 character display**
- **Two page video display**
- **Parallel ASCII printer output**
- **Requires ±12 VDC and external TV monitor**
- **One year limited warranty**
- **Small size (8" × 3" × 12.75")**

Write or call for more details. See the CWR-6700 at your favorite HAL dealer.

HAL COMMUNICATIONS CORP.
BOX 365
URBANA, ILLINOIS 61801 217-367-7373

345

GOTHAM ANTENNAS
(305) 294-2033

SMALL LOT TRAP DIPOLES 417

MODEL	BANDS	LGTH	PRICE
TSL 8040	80.40	78'	$49.95
TSL 4020	40.20.15	40'	$47.95

SMALL LOT SHORTENED DIPOLES

SL-8010	80.40.20. 15.10	75'	$59.95
SL-160	160	130'	$38.95
SL-80	80	63'	$37.95
SL-40	40.15	33'	$36.95

FULL SIZE PARALLEL DIPOLES

FPD-8010	80.40.20. 15.10	130'	$49.95
FPD-4010	40.20.15.10	63'	$44.95

NEW! PORTABLE VERTICAL! IDEAL FOR APARTMENTS, CAMPING, TRAILERS!

Folds to 5' Package. No Radials. Required. Fully Assembled Full Legal Limit. 1:1 VSWR

MODEL	BANDS	HGHT	PRICE
PV-8010	80.10	13'	$59.95

PROVEN DESIGN GOTHAM ALL BAND VERTICALS

V-160	160.80.40.20. 15.10.6	23'	$44.95
V-80	80.40.20 15.10.6	23'	$42.95
V-40	40.20.15.10.6	23'	$40.95

FAMOUS GOTHAM QUADS
2 Elements—3 Bands Complete $149.95
CHAMPIONSHIP GOTHAM BEAMS
Full Size Complete from $99.95
DEALER INQUIRIES INVITED

CALL OR SEND **LARGE** SASE FOR CATALOG. Shipping: Dipoles & Verticals $2.50 USA: $7.00 Canada: $5.00 FPO, APO Beams & Quads Shipped UPS or Freight Collect Fla. Add 5% Sales Tax

1415 First St. • Key West, FL 33040

FILTER CASCADING

The most cost-effective way to improve the selectivity of any receiver – old or new – is to improve its IF filtering. A Fox-Tango Cascading Kit puts a high-quality steep-sided 8-pole filter in series with your present filter(s), both SSB and CW. The result is narrower Bandwidth and better Shape Factor, both of which dramatically reduce adjacent channel QRM – a necessity in today's crowded bands.

CONSIDER THESE KIT FEATURES

- Easy installation - 30 minute average.
- No drilling, switching, alignment.
- 16 poles of filtering yield:
  Filter Shape Factor as high as 1.19.
  Ultimate Rejection better than 100dB.
  Works wonders on SSB; improves CW.
- Compensates for Filter insertion loss.
- Complete instructions, clear diagrams.
- No RX audio impairment, TX unaffected.
- Includes Filter and all needed parts.
- Fits all models of Series - any letter.
- All Filters 8-pole – Guaranteed One Year.

SPECIFY KIT WANTED WHEN ORDERING

YAESU FT101 $75; FT101ZD $70; FT107 $75; FT901/2 $65; FR101 $55 (filter only). KENWOOD TS520/R599 $70; TS820 $70; TS830/RB20 $150 (Two Filters). HEATH SB104A $60.

Shipping $3 (Air $5). FL Sales Tax 5%

In addition to the above, FOX-TANGO stocks a wide line of $55 SSB, CW, and AM 8-pole filters for Yaesu, Kenwood, Drake R4C and 7-line, and Heathkit. Also, special filters made to order. Send specs for quote.

F T

GO FOX-TANGO – TO BE *SURE!*
Order by Mail or Telephone.
AUTHORIZED EUROPEAN AGENTS
Scandinavia: MICROTEC (Norway)
Other: INGOIMPEX (West Germany)

FOX TANGO CORPORATION
Box 15944S, W. Palm Beach, FL 33406
Phone: (305) 683-9587

323

FREE!
Brand New Catalog With Over 150 Programs

Best
Software
Under The
Sun

Instant Software's new catalog is free and it offers 150 of the finest programs you can find. At reasonable prices...and a variety you've never seen before in one catalog. And they're all contained in the new 16 page 1983 Instant Software catalog. You'll find:

ASSEM/ZSIM—2 great utilities in one super package. Assembly language programmers, this package solves all your programming problems from ASSEM to ZSIM.

Super Utility Plus—the most powerful program of its kind. A must for every serious TRS-80* disk installation.

Geography Explorer Series—the exciting, attention-holding series that teaches your children essential geographical facts.

Phaser Blast—phaser-armed robots, enemy Hovertanks...prepare for a journey into the war of the future.

Space Shuttle—experience the ultimate flight as you pilot America's Columbia through launch, orbit, re-entry and landing.

Plus dozens of other practical, mind-boggling or spine-tingling programs.

And now you can get the new 1983 Instant Software Catalog absolutely free. You don't even have to pay for the phone call. Just dial toll free:

1-800-258-5473

and ask for your free copy of Instant Software's 1983 Catalog.
It could be the smartest call you'll make all year.

Instant Software. The best software under the sun.

SPACE SHUTTLE
SPACE SHUTTLE
BUSINESS ANALYSIS
Instant Software
JET FIGHTER PILOT
GEOGRAPHY EXPLORER: USA
Instant Software

Instant Software™

(a subsidiary of Wayne Green Inc.) Route 101 & Elm St. Peterborough, NH 03458

*TRS-80 is a registered trademark of the Radio Shack division of Tandy Corp.

Yes, I want a free catalog!
Please send my free copy to:

Name ____________________

Address ____________________

City ________ State ______ Zip ______

I have a ____________ computer

Instant Software™
Peterborough, N.H. 03458 USA A subsidiary of Wayne Green Inc.

The best software under the sun.

1273NC

ANTENNAS FOR HF, VHF, UHF

Two Meter

"The Big John"* 13 Element Quad 22' Boom 16.5dBd gain F/B 30 dB Mast Size Up to 2" Bandwidth 144-145 MHz **$129.95**

"The Little John"** 11 Element Quad 18' Boom 15.5 dBd gain F/B 30db Mast Size 2" Bandwidth 144-145 MHz **109.95**

"PTG Special"*** 9 Element Quad 13' Boom 14.8 DBd F/B 30 dB Bandwidth 144-146 MHz **$89.95**

Featuring The Wondermatch Driven Element

Six Meter

"6-PTG-4" 4 Element Yagi 13' Boom 12 dBi Mast Size 2" Longest Element 115" 50-51 MHz **$79.95**

You've Heard About Us On The Air, So Call Collect Between 8AM-10PM Or Write For Details

*Measured at JWL Laboratories

**First Place Winner at Baton Rouge Gain Measuring Contest (7/31/82).

***Second Place Winner at Baton Rouge Gain Measuring Contest (7/31/82).

COPYRIGHT 1982

(713) 464-7720 Dick-WB5JWL
Gordy-KD5NQ

JWL ELECTRONICS
9138 Western Drive
Houston, TX 77080

YOU MISSED IT!

73 MAGAZINE FOR RADIO AMATEURS
73
Amateur Radio's Technical Journal
Poor Man's Spectrum Analyzer
The Ultimate Fuse
Trek to Tibet
$100 TVRO Receiver
Confessions of a Counter Evolutionary
Positive Ions: Invisible Menace?
Ready for RTTY?
Simple Circuits Return!
Tips on Chips
Home-Brew Contest Runner-Up
Skinflint's 2m J-Pole

But you still need that issue of *73 Magazine.*
Well, it's not too late to get it.
Send for your free Back Issue Catalog.
A complete listing, including editorial highlights.

You still need it.
And we've still got it.

YES, I want my free Back Issue Catalog for *73 Magazine.*

Name ______________________

Address ______________________

City______________ State______ Zip_______

73 Magazine, Mail Order, 80 Pine St., Peterborough, NH 03458

REGENCY SCANNERS				BEARCAT SCANNERS	
T720 Air	169.00	D810	270.00	BC350	369.00
D 100	159.00	M 100	205.00	BC300	339.00
D 300	209.00	M 400	245.00	BC200	CALL

All Bundy low profile IC Sockets just 1¢ per pin
Example: 8 pin—8¢; 40 pin—40¢
Ham IV Rotor—$165.00
Columbia 8 Con (2#18/6#22)—17¢/ft.
Columbia RG 59v 100 foil shield TV type—7¢/ft.
Berk Tek Grey 96% RG 8X—14¢/ft.
US made PL 259—10/$5.50
Call for Quantity Quotes

UG 176 Reducer—10/$1.99
SO 239—10/$5.89
3 amp fuse—20/$1.50
Sanyo 3V Lithium—$5.95
Gould 1.2v 500 mAh AA Nicad
10/$14.50 100/$125.00
1000/$1100.00
GSC Reg. Power Supply
35 Amp Rack Mt. List $227.00
SALE $149.00

VISA
master charge

Universal Dist.
RAYMOND RICHARD
RT. 1, BOX 25E
CLERMONT, FL 32711

(904) 394-2511
(313) 278-8217

✓155

ATTENTION: ICOM & KENWOOD OWNERS!!

IF YOU ARE NOT RECEIVING OUR MONTHLY NEWSLETTERS, YOU ARE NOT TUNED INTO A WEALTH OF INFORMATION!!!

VISA
MasterCard

USERS INTERNATIONAL RADIO CLUB

Subscription Cost for 10-ICOM or Kenwood Newsletters: USA $9.00 Annual (Bulk Rate); $12.00 First Class, Canada & Mexico $10.00 - elsewhere (Air Mail) $12.00 **SPECIAL PRICE FOR BOTH NEWSLETTERS (20 issues) $2.00 OFF INDIVIDUAL PRICES.** We honor Master Charge and VISA. Telephone orders accepted. "We are an information exchange for ICOM and Trio/Kenwood Users". Please send a S.A.S.E. for our informational brochure and list of ICOM & Kenwood Kits. Send to:

USERS INTERNATIONAL RADIO CLUB
364 Kilpatrick Ave., Port St. Lucie, Fl 33452
USA - Phone 305/878-7296

✓179

THE AUTEK "QRM ELIMINATOR"

Autek Research
QF-1A SSB/CW/AM FILTER
AC ON
OFF (BY PASS)
AUX. NOTCH FREQ.
11000 HZ
NOTCH
PEAK
LOWPASS
HP
SELECTIVITY
NOTCH
(MAX.)
FREQUENCY
2500 HZ

Model QF-1A
For SSB & CW
$69.00 (+$4)

115 VAC supply built-in. Filter by-passed when off.

Auxiliary Notch rejects 80 to 11,000 Hz! Covers signals other notches can't touch.

Four main filter modes for any QRM situation.

Continuously variable main selectivity (to an incredible 20 Hz!)

Continuously variable main frequency. (250 to 2500 Hz)

AUTEK pioneered the ACTIVE AUDIO FILTER back in 1972. Today, we're still the engineering leader. Our new QF-1A is the latest example. It's INFINITELY VARIABLE. You vary selectivity 100:1 and frequency over the entire usable audio range. This lets you reject whistles with dual notches (to 70 dB), or reject SSB hiss and splatter with a fully adjustable lowpass plus aux. notch. Imagine what the NARROWEST CW FILTER MADE will due to QRM! HP rejects low frequencies. Skirts exceed 80 dB. 1 watt speaker amp. Built-in 115 VAC supply. 6½x5x2½. Two-tone grey styling.

Even latest rigs include only a fraction of the QF-1A selectivity. Yet it hooks up in minutes to ANY rig--Yaesu, Kenwood, Drake, Swan, Atlas, Tempo, Heath, Collins, Ten-Tec, etc. Just plug it into your phone jack and connect spkr. or phones to the output. Join the thousands of owners who now hear stations they couldn't copy without a QF-1A! It really works!

WORLDS RECORD KEYER. OVER 4000 DX QSO'S IN 2 DAYS!

SPEED
MEMORY
OPERATING
Autek Research
REPEAT
COMBINE C/S
RECORD
PLAY
TUNE
VOLUME
RESET
A
B
C
D
OFF

$100.50 (+$4)

Model MK-1 Keyer

Probably the most popular "professional" contest keyer in use, yet most owners are casual CW operators or novices. After a few minutes, you'll see how memory revolutionizes your CW operation! Just start sending and record your CQ, name, QTH, etc. in seconds. 1024 bits stores about 100 characters (letters, numbers). Playback at any speed. Dot/dash memories, triggered clock, repeat, combine, 5 to 50+ WPM, built-in monitor and 115 VAC supply. Works with any paddle. Sit back and relax while your MK-1 calls CQ and handles standard exchanges!

Optional memory expander (ME-1) expands any MK-1 to 400 characters. ME-1 factory installed $35. Owner installed, only $21 (+$4). Add more memory now or later!

Autek Research
BOX 302 DEPT. S
ODESSA, FLORIDA 33556 • (813) 920-4349

NO LONG DELAYS. WE SHIP 95% OF ORDERS FROM STOCK

We sell only factory direct. No dealer markup in our price. Order with check, M.O., VISA, MC. Add $4 postage and handling in 48 states. ($7 for UPS air). Add $7 to Canada, Hi., Ak. Add $22 elsewhere (shipped air). Add 5% tax in Fla.

AZDEN®

PHASE II
TWIN ANTENNA

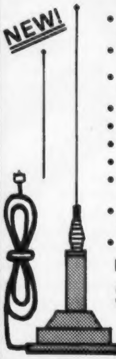

- SUPER 80-POUND, 100-MPH GRAY MAGNETIC MOUNT WITH MYLAR BASE
- 5/8 WAVE FOR **PHASE II** SIGNAL
  * AND *
- 1/4 WAVE FOR CLOSE-IN AND RESTRICTED HEIGHT AREAS
- INSTANT CHANGE-OVER
- SUPERIOR PERFORMANCE
- STAINLESS STEEL SPRING AND WHIP
- CHROME ON BRASS BASE-COMPARE!
- BOTH ANTENNAS ARE FREQUENCY ADJUSTABLE
- COMPLETE WITH 17 FEET OF FOAM COAX AND PL-259 CONNECTOR
- MADE IN U.S.A.

INTRODUCTORY PRICE:

$29.95

COMPARE!!

TWO ANTENNAS FOR THE PRICE OF ONE!

AMATEUR-WHOLESALE ELECTRONICS
8817 S.W. 129th Terrace, Miami, Florida 33176
Telephone (305) 233-3631 - Telex: 80-3356
HOURS: 9 - 5 Monday thru Friday
• U.S. DISTRIBUTOR • DEALER INQUIRIES INVITED

VISA® master charge ✓5

ORDER NOW TOLL FREE

800-327-3102

NEW TS830S for $150?

Yes indeed! Just add a Matched Pair of top-quality 2.1KHz BW (bandwidth) Fox Tango Filters. Here are a few quotes from users:

". . . Makes a new rig out of my old TS830S! . . ."
"...VBT now works the way I dreamed it should..."
"...Spectacular improvement in SSB selectivity..."
"...Completely eliminates my need for a CW filter..."
"...Simple installation - excellent instructions..."

The Fox Tango filters are notably superior to both original 2.7KHz BW units but especially the modest ceramic 2nd IF; our substitutes are 8-pole discrete-crystal construction. The comparative FT vs Kenwood results? VBT OFF — RX BW: 2.0 vs 2.4; Shape Factor: 1.19 vs 1.34; 80dB BW: 2.48 vs 3.41; Ultimate Rejection: 110dB vs 80. VBT SET FOR CW at 300Hz BW — SF 2.9 vs 3.33; Insertion Loss: 1dB vs 10dB.

OPTIONAL CONNECTIONS

Fox Tango filters for RX and TX; Fox Tango for RX - Kenwood for TX; FT for RX – switch-select FT or K for TX; switch-select FT or K for RX/TX.

INTRODUCTORY PRICE: (Complete Kit)...$150
Includes Matched Pair of Fox Tango Filters,
all needed cables and parts, detailed
instructions.
Shipping $3 (Air $5). FL Sales Tax 5%

ONE YEAR WARRANTY
GO FOX-TANGO – TO BE *SURE!*
Order by Mail or Telephone.
AUTHORIZED EUROPEAN AGENTS
Scandinavia MICROTEC (Norway)
Other: INGOIMPEX (West Germany)

FOX TANGO CORPORATION
Box 15944S, W. Palm Beach, FL 33406
Phone: (305) 683-9587 ✓323

Don't Be Left Out in the Cold
with the Russian Woodpecker

GET A MOSCOW MUFFLER™

Another first from AEA. The Woodpecker Blanker, WB-1 really works. This unit effectively blanks the pulsing interference of the Russian Woodpecker. Two versions are available, the WB-1 for use with communication receivers and WB-1C for use with all popular transceivers.

AEA ADVANCED ELECTRONIC APPLICATIONS, INC.
WIDTH
SYNC
PWR
GAIN
BLANKER
RATE
ON
OFF
MOSCOW MUFFLER
WOODPECKER BLANKER WB-1

This extremely useful accessory is designed for direct insertion between your receiver (or transceiver) and the antenna. It is both MORE EFFECTIVE than I.F. type blankers and requires NO MODIFICATIONS to your receiver! The unit operates from a 13 VDC ± 2 VDC power source at less than 575 mA. (AEA AC wall unit AC-1 will operate the blanker.)

The blanker works well on both CW and SSB modes that are being interfered with by a woodpecker. Controls on the front panel include; four push button switches, a synchronize control and a width control The WB-1 also features a low-noise untuned broadbanded 6 db gain pre-amp which can be selected with or without the blanker enabled. The WB-1C uses the same circuitry but includes a carrier operated relay (COR). This provides protection to the receiver section during transmissions from the attached transceiver.

For more details, write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation.

ADVANCED ELECTRONIC APPLICATIONS, INC.
P.O. Box C-2160,
Lynnwood, WA 98036
(206) 775-7373
Telex: 152571 AEA INTL

✓2

AEA **Brings you the Breakthrough!**

AWARDS

Bill Gosney KE7C
Micro-80, Inc.
2665 North Busby Road
Oak Harbor WA 98277

LMRE AWARDS

Here are the details of an awards program recently instituted by the Liga Mexicana de Radioexperimentadores (LMRE) and open to all amateurs anywhere; there are currently four awards offered.

6Z6 Award

Available for confirmed contact with any 6 Mexican stations after January 1, 1980.

American Award

Requires confirmed contact with 40 countries in the Western hemisphere (ARRL DXCC list) plus 10 contacts with XE stations.

Mexico Award

Requires confirmed contacts with 20 stations in Mexico.

Worked All XE (WAXE)

Requires 25 confirmed contacts, 15 with XE1, 5 with XE2, and 5 with XE3 stations.

Awards cost US $3.00 or 10 IRCs each and require that either the QSL cards or a list certified by the awards secretary of the local league be submitted to the LMRE of Mexico City. If QSL cards are submitted, be sure to include sufficient funds for return of same via international registered air mail. The address for applications is: LMRE Awards Manager, c/o Manuel De Lera, PO Box 907, Mexico 1, DF, Mexico.

JOLIET AMATEUR RADIO SOCIETY

The Joliet Amateur Radio Society is sponsoring the JARS award. Illinois stations must contact 10 JARS members. Continental US stations must contact 5 JARS members. No repeater contacts. An updated membership list is available on request for an SASE or 2 IRCs. Send list of log information and $1.00 (DX station may send 3 IRCs) for the award to: Paula Franke WB9TBU, Certificate Chairman, PO Box 873, Beecher IL 60401.

THE IOWA AWARD

An award will be issued to any amateur who has worked 19 Iowa counties. Cost will be $1.00. Each additional 20 counties will earn a new award. QSLs not required. Send usual log information and statement by two other amateurs or one club officer to the Mississippi Valley Radio Club, 3518 Columbia, Davenport IA 52804.

THE PLANET EARTH AWARD

The South West Ohio Repeater Club (SWORC) takes great pleasure in presenting the Planet Earth Award. To qualify, applicants must submit proof of QSOs with 10 different stations on the planet Earth. There are no restrictions, but QRP operations will be noted. Send your list of contacts along with the award fee of $4.00 or 12 IRCs with an SASE to the Awards Chairman, South West Ohio Repeater Club, PO Box 18005, Cincinnati OH 45218.

WORKED ALL MORTON AWARD

The Morton Amateur Radio Club has announced its new award program. The Worked All Morton award is issued to those hams who have had QSOs with five members of the Morton Amateur Radio Club, or hams living in Morton, Illinois. Only contacts made on or after January 1, 1981, will count. To receive the award, applicants should send log information listing at least five Morton contacts along with a large SASE to Morton Amateur Radio Club, 701 Columbus Avenue, Morton IL 61550.

The club operated a special events station, W9EEB, during the Annual Morton Pumpkin Festival. An attractive certificate for the Pumpkin Award will be sent to all who QSL. The operation was held September 16 through 18, 1981, on 7.280, 14.280, 21.380, and 28.680 MHz. The award will be issued on receipt of QSL and a large SASE by W9EEB, 701 Columbus Avenue, Morton IL 61550.

In an effort to restore good operating practices to the amateur bands, a group of Morton Amateur Radio Club members have undertaken the sponsorship of the All American Alligator Award. This probably least-coveted certificate will be issued to those stations which exhibit acts inconsistent with the spirit or laws of amateur radio. We hope the award will be received in the same spirit with which it is being issued.

TEN-METER FM AWARDS

Sponsored by the North Whidbey Island Repeater Association (NWIRA), all contacts must be made on or after January 1, 1981. Crossmode contacts do not count. Contacts must be two-way ten-meter FM. Special endorsements include All-Mobile, All-Simplex, Single-Frequency accomplishments, and contacts made within a single day, week, month, or year. *Do not* send QSL cards; forward your list of contacts showing the date, time, and frequency of each QSO and provide a brief station description. Send with the fee of US $4.00 for each award to the attention of: Ten-Meter FM Awards Program, 2665 North Busby Road, Oak Harbor WA 98277.

Worked All Districts

To qualify, applicants must work one ten-meter FM station in each of the ten US call districts.

Worked All States

Applicants must work a minimum of 50 US states on ten-meter FM.

Centurion

This award requires the applicant to work a minimum of 100 stations on ten-meter FM.

DX Decade

Applicants must work a minimum of ten DX stations outside the fifty US states and Canada on ten-meter FM.

North American

To qualify, applicants must work all ten US call districts, a minimum of six Canadian provinces and/or territories, and at least four DX countries within the North American continent (other than the US and Canada) on ten-meter FM.

OTHER AWARDS

3rd Call District Maryland

Worked all Bowie ARC in two classes. First figure US stations, second, DX stations: class 1 = 4/2; class 2 = 2/1. Log data, SASE. No charge. To: John Rouse KA3DBN, PO Box Drawer M, Bowie MD 20715.

4th Call District Florida

Florida Skip Certificate of Merit issued on recommendation of two other amateurs for outstanding service. $1.00. Send to: Florida Skip, Box 501, Miami FL 33166.

XYL Award by Florida Skip

Only requirement is to render aid and comfort to your husband in and out of the shack. $1.00 or 4 IRCs to: Elizabeth Clark W4GGQ, 41 Lenape Drive, Miami FL 33166.

Three Thousand DX Award

North Florida ARS. Work three or more stations 3,000 miles or more distant, ragchew-type QSOs only. Two certificates will be awarded, one to you and one to the DX stations. $2.00 to: Dale Mann N4AWI, 5433 Glorianne Circle North, Jacksonville FL 32207.

Worked Broward County Cities

Broward ARC. Stations in the Florida counties of Broward, Colliers, Dade, Glades, Henry, Lee, Martin, Monroe, or Palm Beach must work all 29 cities; others, 15. Work mobiles in Broward county. No awards for your mobile. GCR, US $1.00; DX, 10 IRCs, to: WD4RAF, 1921 NW 41st Street, Oakland Park FL 33309.

6th Call District

CHC Worked All Counties California. Issued in five classes: Class D = 20 to 28; class C = 30 to 38; class B = 40 to 48; class A = 48 to 57; class AA = 58; GCR, SWL, $3.00 endorsements. $1.00 to: Scott Douglas KB7SB, PO Box 46032, Los Angeles CA 90046.

7th Call District

CHC awards, to: Scott Douglas KB7SB, PO Box 46032, Los Angeles CA 90046.

Washington State Counties Award. Issued in five classes: Class D = 10 to 15 counties; class C = 15 to 20; class B = 20 to 30; class A = 30 to 43; class AA = 44.

Oregon State Counties Award. Issued in four classes: Class C = 10 to 15 counties; class B = 20 to 25; class A = 30 to 35; class AA = 36.

Nevada State Counties Award. Issued in three classes: Class C = 8 to 10 counties; class B = 10 to 15; class A = 15 to 17.

Utah State Counties Award. Issued in three classes: Class C = 7 to 10 counties; class B = 18 to 24; class A = 22 to 29.

Wyoming State Counties Award. Issued in three classes: Class C = 7 to 10 counties; class B = 15 to 20; class A = 20 to 23.

Idaho State Counties Award. Issued in four classes: Class C = 15 to 20 counties; class B = 20 to 30; class A = 30 to 43; class AA = 44.

Montana State Award. Issued in five classes: Class D = 15 to 20 counties; class C = 20 to 30; class B = 30 to 40; class A = 40 to 55; class AA = 56.

GCR, SWL, $3.00; endorsement, $1.00.

Morocco

CN8 Award by AREM. Work 15 CN8 stations on 1 band, 12 stations on 2 bands, or 8 stations on 3 bands. GCR and 3 IRCs to AREM, PO Box 2060, Casablanca, Morocco.

Diploma De La Ville Rabat by Assoc. Royale Des Radio Amateurs De Maroc, c/o CN8OB, PO Box 299, Rabat, Morocco. Work 10 stations in Rabat after January 1, 1968. All others, 5. SWL 10 IRCs, list.

India

Worked Republic of India, by ARSI, Box 534, New Delhi, India. Contact 50 different VU stations after January 16, 1950. QSLs, list, 12 IRCs.

The Gateway of India Award, by ARS of India, Western Zone. Work VUs in the Western Zone after November 9, 1957. Asia stations work 10; others, 5. GCR, 6 IRCs. To: Dady Major VU2MD, 85 Sleater Road, Petit Mansion, Bombay 7, India.

Lebanon

By Lebanese RAA, PO Box 1217, Beirut, Lebanon. Work 10 stations after July 1, 1958; with endorsement seals additional 10. No charge, GCR.

Spain

Spanish Diploma, by URE, Apartado De Correos, Num 220, Madrid, Spain. QSLs from 125 Spanish stations on CW with 60 on 3.5 or 7 MHz, 10 on 28, 15 on 21, and 10 on 14 MHz. After January 1, 1952. Send 40 QSLs, list, and return postage.

125 EA Award: By URE, Hortaleza 2, Apartado 220, Madrid, Spain. Work 125 EA stations after January 1, 1952, including all Spanish call areas. At least three contacts must be made with each (EA1 through EA0) counting EA9 and EA0 as one area. QSLs, list, and return postage.

Romania

"YO-AD" All Districts Award. Work YO districts as follows: First figure is the number of districts to be worked, second is the number of QSOs per district. Applicants in zones 15, 16, 20: class I = 8/10; class II = 6/6; class III = 3/3. Applicants in zones 14, 17, 21, 33, 34: class I = 8/6; class II = 6/4; class III = 3/2. Applicants in all other zones: class I = 8/3; class II = 6/2; class III = 3/1. 144 MHz: class I = 4/1; class II = 3/1; class III = 2/1. There are 8 YO districts in all.

Canary Island

Work EA8 stations after April 4, 1971. QSLs, SWL, 10 IRCs to: URE, PO Box 860, Las Palmas, Canary Islands, Spain. EA and LX stations work 30, rest of EU, Central and South America work 20, North America and Africa work 10. Asia, Oceania, VHF and UHF, work 5.

Austria

WAOE Diploma. Work OE districts all CW, all phone, or mixed after January 4, 1954. Austria and adjoining countries work three stations each in OE districts 1 through 9 (with OE4 and OE9 counting as one district) using at least two different bands. At least one contact per OE district must have been made on 40 or 80 meters. Rest of EU stations: Same as above but without 40- or 80-meter requirements. GCR stations outside EU. Work one OE station station in each OE district on any band (8 QSLs). GCR. Same station may be worked on all bands. WAOE SWLs for 8 districts. Send list and 10 IRCs.

Colombia

100 HK3 Award: by LCRA. Third HK zone. Coordinator for contacts with 100 HK stations after January 1, 1960. SWLs, no charge, GCR, list in alphabetical order and send full log data to: HK3VV, AP 584, Bogota, Colombia.

Double Call Award: Work HK stations with double- or triple-letter calls. Three

KITCHEN SINK

Beat The Price Increase!

Instant Software's prices are going up.

Instant Software's prices are going up. Stop waiting for the right time to buy! Stock up now on all the programs you want, and SAVE. Shop early and save $$$$$$ on your Christmas shopping also.

Remember, this is the last chance to buy Instant Software's products at the old 1982 prices. Effective November 15, 1982* Instant Software will be raising its prices on most of its products.

Order today so that you too can beat the Instant Software price increase. Just call toll free:

1-800-258-5473

*Old prices will not be accepted after this date.

Master Reversi
Cosmic Patrol
Instant Software

Instant Software™

(a subsidiary of Wayne Green Inc.)

Route 101 & Elm St. Peterborough, NH 03458
603/924-9471

Dealers . . . SELL

Selling *73 Magazine* will make money for you. Consider the facts:

Fact #1: Selling *73 Magazine* increases store traffic—our dealers tell us that *73 Magazine* is the hottest-selling amateur radio magazine on the newsstands.

Fact #2: There is a direct correlation between store traffic and sales—increase the number of people coming through your door and you'll increase sales.

Fact #3: Fact #1 + Fact #2 = INCREASED ALE, which means more money for you. And that's a fact.

For information on selling *73 Magazine*, call 800-343-0728 and speak with Ginnie Boudrieau, our bulk sales manager. Or write to her at *73 Magazine*, 80 Pine St., Peterborough, NH 03458.

73 MAGAZINE
80 Pine Street Peterborough, NH 03458
800-343-0728

MOVING?

Let us know 8 weeks in advance so that you won't miss a single issue of 73 Magazine. Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

73 magazine
Subscription Department
P.O. Box 931
Farmingdale NY 11737

☐ Extend my subscription one additional year for only $19.97
☐ Payment enclosed ☐ Bill me

Canada and mexico $22.97, US funds, Foreign Surface $39.97, US funds, drawn on US banks

If you have no label handy print OLD address here.

AFFIX LABEL

Name __________ Call ______
Address __________
City ______ State ______ Zip ______

print NEW address here:

Name __________ Call ______
Address __________
City ______ State ______ Zip ______

32DR6M

classes: Class C = 10, class B = 20, class A = all 26 double calls (AA to ZZ); AAA counts in lieu of AA, BBB for BB, etc. Contacts after January 1, 1960. No charge, GCR, log data to: HK3VV, AP 584, Bogota, Colombia.

CHK Award: by LCRA. Work HK stations. HK stations work 100 other HK stations, stations in Americas work 50, others work 25. HKs send QSLs, others send certified list authenticated by club official. QSLs must have been sent and received. To: LCRA, AP 584, Bogota, Colombia.

ZHK Award: by LCRA. Confirmed contacts with HK zones. HKs send QSLs from all 10 zones. Americas work 9, rest of the world work 8. All except HKs send list certified by club official. To: LCRA, AP 584, Bogota, Colombia.

(No charges given for any of the LCRA awards.)

HK7 Award: by RC Santander, PO Box 222, Bucaramanga, Colombia. Work 7 HK stations, either all CW or all phone, after January 1, 1962.

10 HK1 Award: by RC Del Atlantico, Apartado Nacional 184, Barranquilla, Colombia. Work 10 HK1 stations post World War II. GRC—certified by club officer. (No costs given.)

HK5 Award: by LCRA. Work HK5 stations after January 1, 1957. American countries work 12, Colombian stations work 20, rest of the world work 8. GCR list to: Box 6149, Cali, Colombia.

US Navy Award

Work 5 US Navy ships. To: Office of Naval Communications, Director, Navy MARS (OP945N), The Pentagon, Washington 25 DC 20301.

Radioman Submarine Award: Work 2 amateur radio stations on board submarines of Submarine Squadron Twelve plus club station W4YVS or any station on board the *Bushnell*. After January 1, 1961. Notarized log information with statement that the information is true and accurate to: Radio Amateur Club, Submarine Squadron 12, Naval Station, Key West FL 33040.

ARGONNE ARC

The Argonne Amatuer Radio Club plans to operate the club's memorial station, W9QVE, to commemorate the 40th anniversary of the first controlled nuclear chain reaction experiment conducted at the Alonzo Stagg field on the University of Chicago campus. Two stations will operate from 1500 GMT December 4 through 2400 GMT December 5.

Frequencies: phone and CW—20 kHz up from lower edges of the General portions of the 80-10m bands; Novice—40 kHz up; 2m—145.19/144.59, 146.52, and 147.42; RTTY—14.090 and 146.70. Send a business-type SASE or $1.00 for an 8" × 11" unfolded certificate to AARC, PO Box 275, Argonne IL 60439.

BETHLEHEM WV EXPEDITION

The Triple States Radio Amateur Club will operate daily from Bethlehem, West Virginia, December 9 through December 12, from 1400 to 2300 UTC. Operating frequencies for WD8DDL/8 will be 7.275, 14.325, 21.425, and 28.550 MHz on SSB, and 7.110, 14.075, 21.110, and 28.110 MHz on CW. A special holiday certificate will be sent to all those contacted who send an SASE to TSRAC, 26 Maple Lane, Bethlehem, Wheeling WV 26003.

CHRISTMAS VILLAGE

The K1BCI C/Q Radio Club will operate a special event station honoring the 35th anniversary of the Christmas Village located in Torrington, Connecticut. The club will operate from the Christmas Village from December 11 through 19, 1982, on 10, 15, 20, 40, and 80 meters. Certificates of this event will be issued for contacts made. For further information, contact Jim WA1YZA or Nellie WB1DVC.

SANTA CLAUS

The Pike County Amateur Radio Club of Winslow, Indiana, will operate a special events station from Santa Claus, Indiana, from 1700Z December 18 through 1700Z December 19, 1982. The callsign will be W9CZH. Operating frequencies will be (plus or minus QRM) 21.395, 14.305, 7.265, 3.925 phone, 7.133 CW, 14.093 RTTY, and 146.52 FM. Certificate for QSL and SASE to Santa Claus, PO Box 111, Ireland IN 47545.

CHESTER GREENWOOD DAY

The Sandy River ARC will operate KA1CNG on Saturday, December 18th, 1500Z, to Sunday, December 19th, 2100Z, in celebration of Chester Greenwood (inventor of the earmuff) Day. We will also operate mobile from the Chester Greenwood Day Parade and related activities on Tuesday, December 21st, 1400Z to 2100Z. Frequencies: 5 to 10 kHz from bottom of General band edges and 3940 kHz. Certificate for your QSL card and two first-class stamps (no envelopes please) to KA1CNG, 5 Franklin Ave., Farmington ME 04938.

HONG KONG ACTIVITY

The Hong Kong Amateur Radio Transmitting Society (HARTS) is pleased to announce that once again there will be a VS6 activity day between 0001G Saturday, April 2, 1983, and 2359G Sunday, April 3, 1983. As in previous years, many VS6 stations will be active on all bands/modes.

1983 is World Communications Year (WCY), and during 1983 the special callsign VS6WCY will be in use by the HARTS club station. Special QSL cards will be issued for QSOs with VS6WCY. QSLs for WCY station should be sent to the Hong Kong QSL Bureau Manager, PO Box 541, Hong Kong.

WORKED ALL NORTH POLE

The Borealis ARC will present, upon receipt of the request with the callsigns and dates worked of a minimum of three BARC members and $2.00, a Worked All North Pole certificate. Operating time will be from approximately 0400-0900Z, 30 kHz up from the lower edge of the Novice and General bands, plus or minus QRM. The club member whose callsign appears on the largest number of certificate requests during the month of December will win a prize. Certificate requests should be sent to: Borealis ARC, c/o Wendall Keller, SR Box 80343, Fairbanks AK 99701.

ALL NEW H.F. 10/160 METER
SOLID STATE P.L.L. TRANSCEIVER

USB-LSB
4 Memories
3 Way Auto-Scan
Includes New Bands
3-Step Tuning Speed
IF Tune ± 1 KHZ
Built-in Dual VFO

CW-W CW-N
200 W. PEP (160M-12M)
100 W. PEP (10M)
Built-in Power Supply
AC-120 VAC
DC-13.8 V -Ground
External ALC
13.5 VDC Relay

N.C.G. CO.
NCG

JUST SLIGHTLY AHEAD

1275 N. GROVE ST.
ANAHEIM, CA 92806

TO ORDER OR
DLR INFO. CALL
(714) 630-4541

✓318

NOTE: Price, Specifications subject to change without notice and obligation

FAST
SCAN
$399

Have you tried it yet?
ATV TRANSMITTER/CONVERTER

TC—1

*10 Watts Output
*Standard Frequencies Available
*Broadcast Standard Sound
*High-resolution & color video
*Regulated AC Supply Built In
*Tuneable Downconverter & Preamp

Connect to the antenna terminals of any TV set, add a good 450 MHz antenna, a camera and there you are...Show the shack, home movies, computer games, video tapes, etc.

ATV DOWNCONVERTER

For those who want to see the ATV action before they commit to a complete station, the TVC-4 is for you. Great for public service setups, demos, and getting a buddy interested. Just add an antenna and a TV set tuned to CH. 2, 3, or 4 and plug in to 117 volts a.c. $89.00

TVC-4

TVC-4L extra low-noise version...$105 delivered in USA

HOMEBREWERS: ASK FOR OUR BASIC FOUR-MODULE PACKAGE

CALL OR WRITE FOR OUR COMPLETE LIST OF SPECIFICATIONS, station setup diagrams, and optional accessories which include antennas, modulators, detectors, test generators, cameras, etc. WE ARE A FULL-LINE SUPPLIER OF ALL YOUR ATV NEEDS.

TERMS: VISA or MASTER CARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Allow three weeks after order for delivery.

P.C. ELECTRONICS
Tom W6ORG Maryann WB6YSS
(213) 447-4565
2522 Paxson Lane,
Arcadia, California 91006

WAYNE GREEN BOOKS

KILOBAUD KLASSROOM

by George Young and Peter Stark

Makes learning electronics fun and easy. First published as a series in *Kilobaud Microcomputing*, the book combines the learning of essential theory with practical, hands-on experience. The course begins with basic electronic projects and culminates in the construction of your own programmable microcomputer. The direct instructional methods of authors Young & Stark make KILOBAUD KLASSROOM a simple way for you to acquire a solid background in digital electronics.

BK7386 (419 pages)..$14.95

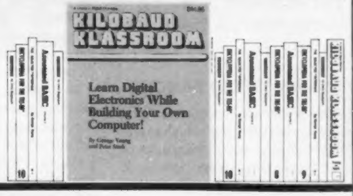

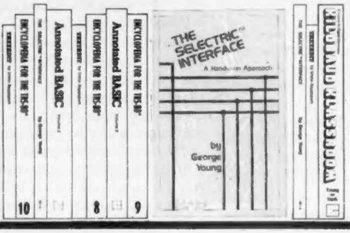

SELECTRIC INTERFACE by George Young

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. SELECTRIC™ INTERFACE, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Kilobaud Microcomputing* magazine's popular "Kilobaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer. SELECTRIC INTERFACE includes: step-by-step instructions, tips on purchasing a used Selectric, information on various Selectric models, including the 2740, 2980, and Dura 1041, driver software for Z80, 8080, and 6502 chips, tips on interfacing techniques. With SELECTRIC INTERFACE and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.

BK7388 (125 pages)..$12.97

GENERAL LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-and-answer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world.

SG7358 (87 pages)..$6.95

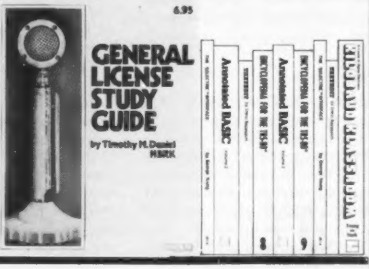

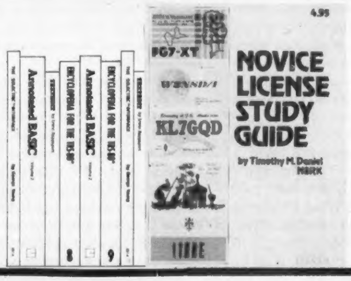

NOVICE LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

Here is the most up-to-date novice guide available. It is complete with information about learning Morse code, has the latest FCC amateur regulations and the current FCC application forms. This guide is *not* a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price.

SG7357 (98 pages)..$4.95

THE NEW WEATHER SATELLITE HANDBOOK by Dr. Ralph E. Taggart WB8DQT

Here is the completely updated and revised edition of the best-selling *Weather Satellite Handbook*—containing all the information on the most sophisticated and effective spacecraft now in orbit. Dr. Taggart has written this book to serve both the experienced amateur satellite enthusiast and the newcomer. The book is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Not just ideas, but solid hardware designs and all the instruction necessary to operate the equipment are included. For the thousands of experimenters who are operating stations, the book details all procedures necessary to modify their equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment.

BK7383 (132 pages)..$8.95

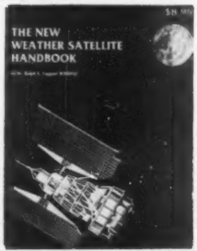

FOR TOLL-FREE ORDERING CALL 1-800-258-5473

WAYNE GREEN BOOKS•PETERBOROUGH NH 03458

Itemize your order on a separate piece of paper and mail to Wayne Green Books, Att: Sales, Peterborough, NH 03458. Be sure to include check or detailed credit card information. (Visa, MC or AMEX accepted.) No C.O.D. orders accepted. All orders add $1.50 for the first book, postage and handling; $1.00 each additional book; $10.00 per book foreign air mail. Please allow 4-6 weeks after publication for delivery. Questions regarding your order? Please write to Customer Service at the above address.

DX

Chod Harris VP2ML
Box 4881
Santa Rosa CA 95402

THE TEN-METER BAND

Many DXers abandon the 10-meter band as sunspot numbers fall. But 10 meters provides DX excitement even at the bottom of the sunspot cycle. Not as much, to be sure, as when 10 is wide open to three continents at once, but, still, there is plenty of action. Because 10 meters lies at the dividing line between HF and VHF, it displays some of the propagation features of each part of the spectrum. By learning to recognize the different modes of propagation and practicing the operating patterns unique to each propagation mode, the DXer can quickly improve his success on 10 meters. The second weekend of the month of December provides a fine opportunity to practice this skill, in the ARRL 10-Meter Contest.

Let's look at the various ways DX signals get from here to there, and how the DXer should modify his operating techniques to take full advantage of each propagation mode.

HF Spectrum

Most DX contacts are made via the F2 ionization layer of the ionosphere. The F2 layer is ionized by radiation from the sun and tends to be strongest near the middle of the day. Thus, 10 meters will open up to the east in the morning. As the Earth turns, the band opens farther south, and then it swings around to the west in the late afternoon. The DXer can recognize F2 propagation because it is so widespread, with signals from a large part of the world coming in all at once. This propagation mode is quite steady, building rather slowly and fading gradually. Normal DXing techniques will be successful: Aim your beam at the station and make your call.

Ten meters is not always "open" via F2 propagation. So some DXers will quickly tune across the band with the beam aimed east, hear nothing, and drop to 15 meters. However, even when the ionization is not strong enough to provide east-west propagation, it often is strong enough for north-south contacts. The equatorial region receives more solar radiation than latitudes farther north and often gets enough radiation to open the 10-meter band. Instead of the normal sequence of the band opening up in the east and swinging around to the west, around midday or a little later the band opens up just to the south.

WA1KID used to take advantage of this phenomenon during contests with a 4-element 10-meter beam fixed south. He could switch quickly to that antenna to watch for the trans-equatorial openings and nab the CEs, LUs, and other South Americans. The only trick to working DX via trans-equatorial propagation is to know when and where to look; if your beam is aimed east, for example, you might never hear the South Americans.

This same ionization over the equatorial regions provides one of the more interesting propagation modes on 10 meters: back scatter. Strong signals aimed south can reflect off the ionization layer over the equator and bounce down to earth, and some small portion of the signal then bounces back along the same path. Not much of a signal gets through, to be sure, since most of the energy is lost or absorbed in the multiple bounces, but directional signals will be scattered enough by the ground at the other end of the hop to send some energy back north.

This means that it is possible to work other stations north of the equator by pointing your beam almost due south! Backscatter signals are very weak, so both stations must point their beams toward the ionization to the south. If you hear a European signal while your beam is aimed south but the signal fades as you swing your beam up to the northeast, you are probably receiving back- or side-scatter signals. You can recognize these signals because they are weak and peak to the south, no matter in what direction the station is located.

If you hear a scatter signal, resist the temptation to swing your beam according to the beam-heading chart; the signal will disappear. (If it gets louder, you're not hearing a scatter signal!) Instead, swing your beam across the south, listening for the loudest direction, the direction of the most intense ionization, and, therefore, the most scatter. Note that both stations must be beaming south. If the DX station hears your signal and swings his beam up to the west to work you, the contact is lost.

Explaining this under the weak signal strengths of scatter contacts can be frustrating. I remember spending 20 minutes once trying to convince a station that we could make contact only if *both* of us pointed our beams south and not at each other! Whenever this W4 heard my call from New England, he would swing his beam north and lose it.

Side scatter is very similar to back scatter. The radio waves reflect off the side of the ionization region, not the underside. Again, you swing your 10-meter beam back and forth, listening for the loudest signal without regard to the direction of the other station. If you can convince the DX station to do the same thing, you can have a satisfying DX contact.

VHF Spectrum

Since the 10-meter band is near the VHF region it exhibits some of the exciting propagation modes of VHF bands, including meteor scatter and E-skip. These short-range propagation modes don't often provide much DX, but it helps to learn how to recognize and operate under each mode.

Meteor scatter is radio propagation off the ionized trails left after a meteor rips through our upper atmosphere. Since the Ten-Meter Contest coincides with a major meteor shower, you might well hear such signals then. Meteor-scatter signals last only a few seconds because the ionization region quickly dissipates. Your contact must be very short; giving your call three times probably will use up the entire opening! Listen for randomly-occuring, quite loud signals which appear and disappear very quickly. If you start a contact on one meteor burst, you may well be able to complete the contact on another burst a minute of two later if you stay on the same frequency and beam heading. Don't expect to exchange much more than a signal report, however, as meteor-scatter QSOs are extremely short.

E-skip enlivens the 10-meter band quite often. The E ionization layer is much lower than the F layer, and the maximum communication distance on a single hop is about 1200 miles, compared to twice that with F2 propagation. But multiple-hop E-skip can provide some DX contacts, thus injecting some life into a "dead" band.

Because the ionization regions in the E layer are much smaller than those in the F layer, the E-skip propagation is much more restricted in area. You might hear only one or two states or countries at a time, for example. E-skip signals can be very loud as well as very directional, but often you can work stations around the fringes. Say you work a few G stations but don't hear anything else. Try a call for EI, GM, GD, etc. People are always listening, and a direct call can pull them out of the woodwork. E-skip propagation is notoriously fickle, appearing and disappearing rapidly. Don't be surprised if your contact fades away in midsentence.

QSL Card Errors

However your signal gets from here to there, you will probably want a QSL card to confirm the QSO. And you had better fill your card out properly if you expect a return QSL. Almost 25% of all QSLs I have received are not filled out properly, yet there are only a half-dozen pieces of information that need to be entered. And any QSL which is improperly filled out can delay the return QSL or even end up in the circular file! Let's look at the common mistakes and how to avoid them.

The callsign. A surprising number of QSLs arrive without the DX station's call in the appropriate place. If the callsign is anywhere but in the "confirming QSO with" or "radio station" box, the QSL is invalid for awards. Don't confuse the QSL manger's call with that of the DX station.

The date. Almost every country in the world except the United States uses the sequence day/month/year for the date. 12/2/82 is February 12, not December 2. To remove all ambiguity from the date, use Roman numerals for the month, or English abbreviations: 12II82 or 12 Feb. 82. Make sure you changed the date at 2400 UTC, which occurs in the middle of the evening before, local US time. I can't tell you how many cards arrive with the date one day off.

The time. There is no excuse for using anything but UTC on DX QSLs. Local time is for local QSOs only. And if you try to convert your local-time log to UTC for the QSL card, sooner or later you will make a mistake. Keep your log in UTC and keep a UTC clock in the shack. And keep your clock accurately set to WWV. A DX station or DXpedition operating "contest style" might fill a 50-entry log page in less than 10 minutes. If the time on your QSL is off by more than 5 minutes, the QSLer might have to search through several pages of logs for your contact.

Frequency. Be careful not to put the *band* in this box—"Frequency 20," for example. If you change bands often (during a contest, for example), watch your log. It is very easy to change bands to work a station and forget to log the band change. Then the card has the wrong band. I always prefer to receive a card with the *exact* frequency, such as, 14205. Since I log my exact transmitting frequency, this can help to find a QSO with the wrong date or time.

Mode. If your QSL has this box labeled "2X," just write in the mode. If the box is labeled "mode," write "2X CW" or "2X SSB."

RST. Honest signal reports in DX are as rare as Albanian contacts. I always prefer honest reports, but usually get 59 even if the other station can barely hear me.

QSL. Always *ask for* the QSL if you want it. I get thousands of cards which I may assume are requests for my card, but nowhere does the station specifically request my card. If things get a little behind, I may assume these cards are answers to cards I sent, and I don't answer them. And if you need a card for a particular reason, say so: "Need 3 more cards for my DXCC, please QSL," or "Please QSL for 5BDXCC."

Other things to remember: If you work a DX station during a contest with consecutive numbers as part of the exchange, write the *other station's* QSO number on the card: "your number 1024." Don't put your own number on the card, as the DX station could care less. His consecutive number will locate your contact quickly in a long log.

Speaking of contests, be sure to mention that the contact was made during a contest, if it was. Many stations keep separate logs for contest and non-contest operations because of the special logs that contests require. So include "CQ WW SSB contest," as appropriate.

Always send a card for *each* QSO. Although it is tempting to put all your contest QSOs with a single DX station on one card, it often will slow up your response. The DX station might QSL one band at a time or, as in the case of major DXpeditions, have separate managers for each band. Splurge, and send separate cards.

Finally, write legibly and accurately. Numerous QSLs have the information so badly written that it is almost impossible to read. Or the information is mis-copied from the log. These QSLs end up in the "do tomorrow" file or the circular one. And I still have cards from five years ago in my "do tomorrow" file. . .

And now a special treat for you loyal readers of this DX column. Send me your QSL card by the end of the year and I'll put them all in a hat and draw out three cards. The lucky winners will receive: a 1983 DX Callbook, a one-year subscription to *The DX Bulletin*, the most prestigious of the DX bulletins, or a one-year subscription to the W6GO QSL List, a list of more than 5000 QSL managers which is updated every two weeks (more about this prize next month)!

So send in your cards to the address at the head of this column, right away. No cost, no obligation; just mail me your QSL card and I'll notify the lucky winners immediately. Include a slide or black-and-white photo of your shack, and I'll use the best shots. Thanks for being such devoted readers of this column.

HAM HELP

Do you need help in getting your Atari computer on RTTY or ASCII? Drop me a line, and I'll be more than happy to get you started.

Bob Holsti K7ZJD/KH2
PO Box 4426 AAFB BR
Yigo, Guam 96912

I would appreciate a copy of a schematic for an RCA #WA 504-A sine/square wave audio generator. I will be glad to pay postage and the cost of copying.

A. B. Wells WA5COH
PO Box 50
Tunica LA 70782

SATELLITES

Ariane Takes a Dive

The amateur radio space program suffered another setback on September 10. On that date, a European Space Agency (ESA) Ariane rocket fell into the Atlantic Ocean instead of achieving orbit as planned. It was the second failure in five launches for Ariane, the vehicle which was scheduled to carry the Phase IIIB amateur satellite aloft in early 1983.

This time, the Ariane carried no amateur birds, but two multi-million-dollar communications satellites on board were lost. Apparently, the rocket dove into the ocean when a third-stage fuel pump failed. If the problem turns out to be specific to the unit that failed and not a design flaw, the Phase III launch schedule may be only slightly affected and the amateur satellite could still be launched sometime this spring. Amateur satellite enthusiasts can only wait patiently for ESA to work out bugs.

Incidentally, the Ariane failure is a serious blow to ESA, which is in head-to-head competition with NASA and the Space Shuttle in the satellite launching business. With Ariane's success rate running only 60%, some ESA customers are getting edgy and may take another look at what the Shuttle has to offer.

MARECS: 0 for 2

One of the satellites lost in the ill-fated September launch was MARECS B, the second Maritime European Communications Satellite. What makes the loss particularly devastating is that the first bird in the series, MARECS A, failed in orbit without ever becoming operational. The bottom line is $250,000,000 spent without a single positive result for MARECS backers. Space flight remains an expensive business.

Thanks to *AMSAT Satellite Report.*—Jeff DeTray WB8BTH, *73* Staff.

Amateur Satellite Reference Orbits

	OSCAR 8		RS-5		RS-6		RS-7		RS-8		
Date	UTC	EQX	UTC	EQX	UTC	EQX	UTC	EQX	UTC	EQX	Date
Dec 1	0041	87	0127	2	0011	346	0010	343	0009	342	1
2	0045	88	0122	2	0154	14	0000	343	0006	342	2
3	0050	89	0116	2	0138	11	0150	12	0003	343	3
4	0054	90	0111	3	0123	9	0140	11	0000	344	4
5	0059	92	0106	3	0108	7	0130	10	0157	15	5
6	0103	93	0100	3	0052	5	0121	9	0154	16	6
7	0108	94	0055	3	0037	2	0111	8	0152	17	7
8	0112	95	0050	4	0021	0	0101	8	0149	17	8
9	0116	96	0044	4	0006	358	0052	7	0146	18	9
10	0121	97	0039	4	0149	25	0042	6	0143	19	10
11	0125	98	0034	5	0134	23	0032	5	0140	20	11
12	0130	99	0028	5	0119	21	0023	4	0137	21	12
13	0134	100	0023	5	0103	18	0013	3	0135	22	13
14	0138	101	0018	5	0048	16	0004	2	0132	23	14
15	0000	76	0012	6	0032	14	0153	32	0129	23	15
16	0004	77	0007	6	0017	12	0143	31	0126	24	16
17	0009	78	0002	6	0002	9	0134	30	0123	25	17
18	0013	80	0156	37	0145	37	0124	29	0120	26	18
19	0017	81	0150	37	0129	35	0114	28	0118	27	19
20	0022	82	0145	37	0114	32	0105	27	0115	28	20
21	0026	83	0140	37	0059	30	0055	27	0112	28	21
22	0031	84	0134	38	0043	28	0046	26	0109	29	22
23	0035	85	0129	38	0028	25	0036	25	0106	30	23
24	0039	86	0124	38	0012	23	0026	24	0104	31	24
25	0044	87	0118	38	0156	51	0017	23	0101	32	25
26	0048	88	0113	39	0140	48	0007	22	0058	33	26
27	0053	89	0108	39	0125	46	0156	51	0055	33	27
28	0057	90	0102	39	0110	44	0147	51	0052	34	28
29	0102	91	0057	40	0054	42	0137	50	0049	35	29
30	0106	92	0052	40	0039	39	0128	49	0047	36	30
31	0110	93	0046	40	0023	37	0118	48	0044	37	31
Jan											
1	0115	94	0041	40	0008	35	0108	47	0041	38	1
2	0119	95	0036	41	0151	62	0059	46	0038	38	2
3	0124	96	0030	41	0136	60	0049	46	0035	39	3
4	0128	98	0025	41	0121	58	0039	45	0032	40	4
5	0132	99	0020	42	0105	55	0030	44	0030	41	5
6	0137	100	0014	42	0050	53	0020	43	0027	42	6
7	0141	101	0009	42	0034	51	0010	42	0024	43	7
8	0002	76	0004	42	0019	49	0001	41	0021	44	8
9	0007	77	0158	73	0004	46	0150	70	0018	44	9
10	0011	78	0153	73	0147	74	0141	7?	0016	45	10
11	0016	79	0147	73	0131	72	0131	69	0013	46	11
12	0020	80	0142	73	0116	69	0121	68	0010	47	12
13	0025	81	0137	74	0101	67	0112	67	0007	48	13
14	0029	82	0131	74	0045	65	0102	66	0004	49	14

HAM HELP

Wanted: a relay for the Heathkit HW-12 monoband transceiver. Please send price info on how I can get one. Thank you very much.

Rick Dill WA0EDH
3007 S. 44th St.
Lincoln NE 68506

I'm looking for a 40m QRP SSB transceiver for mobile use. If anyone has a 40m QRP rig or info on converting a CB to 40, I would appreciate it if they would contact me.

Roosevelt Hamilton WD4PSW
1112 Lownde Ave.
Pensacola FL 32507

THE SELECTRIC™ INTERFACE
A Hands on Approach
by George Young

THE SELECTRIC™ INTERFACE

Daisy wheel quality without daisy wheel expense.

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. *Selectric™ Interface*, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Microcomputing* magazine's popular "Kilobaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer.

Selectric Interface includes:

- step-by-step instructions
- tips on purchasing a used Selectric
- information on various Selectric models, including the 2740, 2980, and Dura 1041
- driver software for Z80, 8080, and 6502 chips
- tips on interfacing techniques

With *Selectric Interface* and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.

Credit card orders call TOLL-FREE 1-800-258-5473. Or mail your order with payment plus $1.50 shipping and handling to: Wayne Green Inc. Attn: Retail Book Sales, Peterborough, NH 03458.
Dealer inquiries invited.

ISBN 0-88006-051-4 128 pages **$12.97**

☐ Yes, I want **Selectric Interface** (BK7388). Enclosed is $12.97 per copy plus $1.50 for shipping and handling.

☐ MASTER ☐ VISA ☐ AMEX

Card # ____________ Expires ____________
Signature ____________
Name ____________
Address ____________
City ____________
State and Zip ____________

All orders shipped UPS if complete street address is given. **SS12**

W2NSD/1
NEVER SAY DIE
editorial by Wayne Green

from page 8

But this pursuit is a totally selfish one. There are no benefits to the hobby...to society. The world is not inched ahead one whit by these chaps. The League has let loose a monster on the world of amateur radio with their Honor Roll.

My own solution to this problem was to work hard and have fun as I worked toward 300 countries. Once I got to that level, I stopped counting. Today, when I hear a new one, I'll take a few minutes to get him in the log...preferring to talk with him if at all possible. If things are too frantic, I have better uses of my time...a lot better. I haven't the vaguest idea of how many countries I've worked and I don't intend to try to count 'em up. Perhaps, if the League would let newcomers to DXing get credit for countries worked up to 300...with no further listings after that...we might be able to put a stop to this thing.

Remember that working DX and getting up on the Honor Roll requires mainly that one be able to spend enormous amounts of time at it. This is not time spent in learning anything or in developing a skill of use to the world. Once you have a decent station, you can make a contact anywhere in the world, so it's just a question of sticking around, being there at the right time, and then bludgeoning your way through.

One of the supposed purposes of amateur radio is to help develop world friendships. Show me a hint that DX pileups and the badgering of ops in rare countries for instant contacts and a QSL generates anything but a disdain. Much of this is aimed at Americans, who are by far the worst in this regard, though at times I find the Germans pushing us hard for bad manners awards. Oddly enough, those hundreds of thousands of no-code Japanese hams are about the best-mannered operators in the whole world...and they have almost one million licensed amateurs today!

Those no-code hams, trained by their local ham clubs, often make *us* look like the CBers. They put most Americans to shame when it comes to real operating skills. And I don't think we can excuse our behavior on the air by explaining that learning the code made us crazy. I know that a lot of hams use the Morse Code as an excuse for being such terrible operators, but I don't believe that something that simple could explain what happens when a PY0 comes on the air.

And I don't think we can shrug our shoulders and put the whole thing down to basic cultural differences. The Japanese may bow when they meet, but they knock you around in the subways and in stores just as hard as you get bumped in America. No, the difference is, I believe, in basic ham training...in their club-trained hams. That's where they get across the concept of pride in being a ham and the responsibility of being a good operator.

Or, as old and good friend Bob Sullivan used to say, "I may not be wrong, but I'm not far from it."

SMALL HAMFEST CATASTROPHE

Some years ago, a disgruntled ham almost got the New England ARRL Convention closed down. The problem hinged around the breaking of federal laws having to do with the advertising of lotteries through the mail. You can't, yet most hamfests and conventions continue to do this, ignoring the federal laws they are breaking.

Please note that it is presently against the law for any hamfest or convention to send a brochure through the mail which promises prize drawings if there is a charge for attendance...and there always is. Further, it is illegal for any magazine or other publication which uses the mails to mention that prizes will be given where there is a charge for attendance.

If you want to give prizes, fine ...but it is illegal for you to mention that in anything which is going to be sent through the mails. You cannot send flyers or posters with this information on them through the mail. Got it?

No one has ever determined just how much prizes build up attendance at hamfests. As far as I know, every hamfest gives prizes, so no one *could* yet have tested the concept. With the veil of secrecy on prizes being lowered by the post office (*we* have heard from them in no uncertain terms), it may get a whole lot more difficult to get cooperation from manufacturers in the way of donated equipment.

Before the "incentive licensing" debacle of '63, it was much easier to get prizes. The ham industry was growing rapidly, meeting the needs for the then-new sideband equipment, so they were happy to donate nice prizes for our hamfests. Today, with only a handful of American firms left, most of the hamfest prizes have had to be bought, so the munificence has not been awesome. If hamfest committees decide to spend less on prizes, this would leave them

UNCLE WAYNE WANTS YOU!

When was the last time you wrote an article for *73*? Never??!! Then it is time you got started.

We are going to make 1983 the best year ever for fun, exciting articles in *73*. To do this, we'll need articles on many different topics. That's where you come in. Even if you've never written an article for us before, we want to hear from you.

What Do I Write About?

Ham radio is really about two dozen hobbies all rolled into one, so there is no shortage of interesting topics. Here are just a few:

- Antennas. Almost every ham experiments with antennas. Whether you've built a 2-meter yagi, an 80-meter quad, a helix for Phase III, or a multiband dipole, other hams can't wait to try your design. Tell 'em all about it in *73*.
- DX. Been on a DXpedition? We all enjoy reading about exotic people and places. Here's a chance to recount your adventure.
- Special Events. Hams get involved in some wacky and wonderful activities. Like Field Day from a floating raft or operating from hot air balloons. If it's worth a story, let us here from you.
- Reviews. New ham gear is released every week, so how does anyone know what to buy? You can help by writing reviews of your new equipment for other hams to read. Check with us first though; we don't want you to duplicate the efforts of someone else.
- Accessories and Gadgets. Home-brewing small projects is an amateur radio tradition. If your latest preamp, digital clock, or electronic sock warmer is a good performer, the rest of us want to hear about it.
- Major Projects. The design and construction of a transmitter, receiver, or power amplifier is a task requiring knowledge and skill. We want to publish the details so that other hams can enjoy the satisfaction of building a big project.
- Test Gear. Hams love to save money. That's why they'll be interested in your homemade test equipment. We'll have room for lots of transistor checkers, capacitance meters, logic probes, diode testers, and the like during 1983.
- Satellites. Whether it's OSCAR, RS, or TVRO, hams want to know more about building their own satellite gear. Downconverters, antennas—you name it and our fellow amateurs are eager for plans and information.
- Digital Communications. Microcomputers make RTTY neat and simple, but we can do so much more. If you are experimenting with higher baud rates, packet radio, new TU designs, coherent CW, or any of a host of other possibilities, you can tell the amateur world about it by writing articles for *73*.
- Computers. Microcomputers are fast becoming a fixture in many shacks. What are you doing with yours?

Those are just a few of the many ideas for articles. You'll think of more if you work at it.

What's In It for Me?

Cash. Unlike some ham magazines, *73* pays for the articles we publish. It may not buy you a new tower, but it might get you that new beam.

Prestige. Just imagine how impressed your friends and relatives (not to mention your boss) will be when they see your article published in an international magazine!

Enthusiasm. When you write for *73*, you help to generate the excitement that makes ham radio so much fun. Both simple and complex articles find an eager audience.

What to Do Next

For a full description of the nuts and bolts of article preparation, send for the *73* Author's Guide. If you can't wait that long, double space your manuscript, leave generous margins, carefully organize your diagrams and photos, and send the whole package to us. Our address is: *73*, Peterborough NH 03458.

Now, don't just sit there—*start writing*!

SALE SALE SALE

GOING-OUT-OF-BUSINESS SALE

Last Day-Dec 31ST
1982
CALL US!

If we have what you want in stock we will beat ANYONE'S price and ship it FREE!

No charge cards . . .
cash or cashier's check

Ben Franklin Electronics
115½ N. Main Hillsboro KS 67063
316-947-2269

✓ 439

FREE! FREE! FREE! FREE! FREE

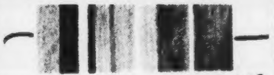

SEND FOR OUR NEW 1982/1983 PARTS CATALOG

THOUSANDS OF SURPLUS ELECTRONIC PARTS, SUPPLIES AND DEVICES.

ALL ELECTRONICS CORP
905 S. Vermont Ave.
P.O. Box 20406
Los Angeles, Cal. 90006

✓ 20

FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE! FREE!

PACKET RADIO TREASURE TROVE

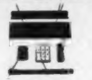

MODEM BOARD
SINGLE BOARD COMPUTER
POWER SUPPLY
AND MORE!

SURPLUS FINANCIAL TERMINAL CONTAINING:

- **202 TYPE MODEM BOARD:** 0-1800 baud, separate 600 ohm audio xfmrs, TTL digital I/0, 5 x 5.5"
- **8080A CPU BOARD:** With sockets for 4ea 2708s. Also in sockets; 8251 Programmable Communications Interface (USART), 8253 Triple Programmable Interval Timer, 8228 System Controller/3-state Bus Driver, 256 bytes RAM. 29 other support ICs, xtal, clock IC. 7.5 x 10"
- **ENCLOSED POWER SUPPLY:** With pwr cord & switch. +5V @ 2.5A, +12V @ 350ma, −5V @ 250ma, plus 2 unregulated voltages for display. 3 x 4 x 8"
- **DOCUMENTATION PACKAGE:** Includes schematics & Technically Oriented User Manual.
- **MISC.:** 20 Key Decimal & Function Keyboard, 16 Digit Fluorescent Display, Mag Stripe Credit Card Reader, Speaker and MORE.

Units are removed from service and in good working condition. High quality modern construction throughout. Each is given a full off-line test before shipment. Large quantity in stock. You'd have to buy a lot of turkeys before finding another gem like this.

PRICE, SURFACE UPS INCLUED $55
DOCUMENTATION PACKAGE $5

ELECTROVALUE INDUSTRIAL INC.
P.O. BOX 157-W
MORRIS PLAINS, NJ 07950
Formerly Electrovalue Industrial

Phone orders and questions [illegible]
201/267-1117

Subscription Problem?

73 Magazine does not keep subscription records on the premises, therefore calling us only adds time and doesn't solve the problem.

Please send a description of the problem and your most recent address label to:

73 Magazine
Subscription Dept.
PO Box 931
Farmingdale, NY 11737

Thank you and enjoy your subscription.

SYNTHESIZED
SIGNAL GENERATOR

MADE IN USA

MODEL SG1000
$349.95
plus shipping

• Covers 100 to 185 MHz in 1 kHz steps with thumbwheel dial • Accuracy 1 part per 10 million at all frequencies • Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate • Spurs and noise at least 60 dB below carrier • RF output adjustable from 5-500 mV at 50 ohms • Operates on 12 Vdc @ 1/2 Amp • Available for immediate delivery • $349.95 plus shipping • Add-on Accessories available to extend freq. range, add infinite resolution, voice and sub-audible tones, AM, precision 120 dB calibrated attenuator • Call for details • Dealers wanted worldwide.

VANGUARD LABS ✓311
196-23 Jamaica Ave., Hollis, NY 11423
Phone: (212) 468-2720

sample issue only $2.50 PPD

OUR 16TH YEAR!

AMATEUR TELEVISION MAGAZINE ✓ 115

"FOR THE SPECIALIZED COMMUNICATION RADIO AMATEUR"

	Surface U.S./Canada Mexico	Surface All Foreign	Airmail Central S. America	Airmail All Other Foreign
½ year	$ 10.00	$ 13.00	$ 20.00	$ 23.00
1 year	$ 20.00	$ 26.00	$ 40.00	$ 46.00
2 year	$ 38.00	$ 50.00	$ 78.00	$ 90.00
3 year	$ 56.00	$ 74.00	$116.00	$134.00

ATV-SSTV-FAX-RTTY-Satellites-EME
Microwave and Computers.

Published 12 times per year by Mike Stone WB0QCD
P.O. Box H, Lowden, Iowa 52255 0408

RIG TROUBLES
GOT YOU DOWN?

- YOU COULD SHIP YOUR RIG TO THE FACTORY FOR REPAIR.
- YOU COULD SHIP IT TO RQ SERVICE CENTER FOR REPAIR.
- BUT YOU STAND A GOOD CHANCE OF FIXING IT YOURSELF WITH HELP FROM YOUR OWN COPY OF "OWNER REPAIR OF RADIO EQUIPMENT"
- THIS BOOK WILL BE SHIPPED POSTPAID FROM K6RQ FOR $8.95

RQ SERVICE CENTER
14910 LG Blvd.
Los Gatos, CA 95030

QUALITY MICROWAVE TV SYSTEMS

1.9 to 2.5 GHz Antennas

Complete System (Rod Style as pictured)	$124.95
Complete System (Reflector Style as pictured)	$149.95
Down Converter, Assembled & Tested	$64.95
Power Supply (12 to 18v)	$49.95

Also Dish Style Antennas In Stock.

Galaxy Electronics ✓ 178
6007 N. 61st Ave.
Glendale, Az.
85301
(602) 247-1151

COD's
Quantity Pricing

MasterCard VISA

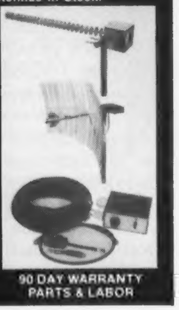

90 DAY WARRANTY PARTS & LABOR

Microwave Field Disturbance Motion Detector Kit

- Range 100′ unobstructed
- Safe low power 10mW output
- Detects motion from 0.1 to 20 MPH

Unlike ultrasonic motion detectors, the Microwave Field Disturbance Motion Detector, can see thru nonmetallic walls. Output is N.O. or N.C. relay contacts which can operate alarms, lights, or electric doors. Output can be programmed from seconds to hours and will reset automatically.

Kit contains: 10.525 GHz transceiver module, 10 db diecast horn antenna, all components, PC board, and instructions. Requires 10-14 VDC, 70mA standby, 110mA activated.

Model MT2 $89.95 PPD in U.S. COD add $2. N.J. residents add 5% sales tax.

MicroTek ☎ (201) 548-4321
35 West Francis St.,
Iselin, New Jersey 08830

✓ 196

with some cash to invest in better speakers.

It's been my observation that hams will drive for hundreds of miles to hear someone interesting talk about their favorite subject. I don't know of anyone crazy enough to drive a couple hundred miles for 1/10,000th chance at an HT. You know, *you* can help. Hamfest committees really don't know who to ask to come talk at their shows. If you'd take the time to write a short review of any interesting talks you've attended at hamfests, this might get the word around.

The fact is that we do have a number of hams who get to fascinating DX spots and go through all kinds of remarkable hell in the process. Some of these chaps are most interesting, if we could only hear about it. Please take the time to pass the word to us here at *73* ... and we'll get your material into the letters column as guidance to other hamfests.

The opposite side of the coin is that a few of our best known DXers are turkeys. It is most incredible how someone can go through some of the adventures these chaps have and be able to make it sound so incredibly dull to hear about. I once fell asleep at the dinner table trying to get anything of even the slightest interest out of two very well-known DXpeditioners.

There are plenty of interesting people around our hobby. Why not get one of our well-known ham publishers to tell about how he got his ham ticket in the '60s without knowing diddly squat about either the theory or the code? I'll bet we'd love to hear about his trip to northern Maine to get a "Conditional" license and his later trials with the FCC when they found out.

Then there is Jean Shepard K2ORS, with two successful PBS films to his credit and a third in production. Jean is by far the best humorist we have in the hobby and our hamfests should grab him when they can. I understand his latest film, "The Great American Fourth of July . . . and Other Disasters," is up for an award. If you do get him to speak, be sure to tape it and send me a copy. Shep isn't inexpensive to get, but he will pull 'em in . . . and be worth every dollar you spend.

No one really interesting is going to be cheap to get. That's the law of supply and demand. And, as Shep found out long ago, few people really appreciate anything they get for nothing.

My own experience has been that when I speak for free I often find a lack of support by the hamfest committee which results in two or three dozen in attendance. If I cost $1,000 plus all travel expenses (first class), you can bet they will be doing everything they can to get people to listen to me. Then I find myself facing two to three thousand in the audience instead of dozens. Between my already-made show commitments and trying to run my steadily-growing publishing firm while keeping up with two fast-growing industries, I'm not fishing for more work. If I do have extra time, it goes for writing, consulting, and even a touch of hamming. Most hamfests are on weekends, which is prime writing time.

In addition to getting interesting speakers for hamfests, with the no-longer-useful prize money, committees might look into putting on some really good demonstrations of new ham communications modes. I suspect that many amateurs would love to see some good slow-scan demonstrations. They'd also like to see fast-scan television. Then there is a growing interest in packet communications. But, for heaven's sake, watch out for some of the super turkey "experts" who flaunt their *doctor* titles. Several of these birds are crashing bores. Hamfest committees might, if they don't have personal recommendations on the "experts," ask for an audio tape preview and judge it as they might a radio audition.

If you have some hamfest committee members who are enthusiastic about the Morse code, why not try to inspire hams to accept code as a fun activity instead of merely something the government forces them to learn . . . and run code-copying contests, with certificates for the winners to display in their shacks. You can help bring some pride to knowing the code, something sadly lacking today. How can one have pride in something which is mandated by the government? Some of the prize money can go for awards for code skills. There's no lottery aspect to *that*.

You might get some of your more fanatic DXers to bring in their rare cards for a display . . . and for a talk on how to get the darned things. That is an art in itself. A big board for attendees to pin up their cards, with a QSL contest (also not a lottery, obviously), won't hurt.

I realize that bribery and greed are time-honored movers of people, but let's try to cope with the post office laws and find alternate ways of getting hams to come to hamfests.

THE GREAT AMERICAN HAM CLUB . . . DISASTER

When I see the Japanese ham magazine each month, with a whole section devoted to club activities . . . often with 70 or more pages of news about the clubs and pictures of their activities . . . I think of how little our clubs are doing . . . and reporting. I don't think we could generate that much news in a year, much less every month.

Even the best of our ham clubs seem to have their ups and downs. One thing that might help would be an updated series of articles on how to run a ham club. I did run such a series nearly twenty years ago and it was very well received. It's about time for an updated series, eh?

Running a ham club is show business, which many of us seem to forget. Many club presidents gather weak people around them to help make the club go. They do little to organize exciting meetings and often let business intrude on the fun . . . only to find that in a few months they have little left of the club.

I'd like to see some articles on how to make ham clubs succeed. I believe that the real strength of amateur radio lies in the strength of the clubs, not in a small group of professionals who are, for the most part, working for their own benefit first and ours second. How about some pictures of club groups and reports on club activities?

With amateur radio being a keystone, to my way of thinking, as far as providing our country with emergency communications, we're talking about club organization, not just individuals. Clubs can help get amateur radio set up so that it will be able to keep going after any kind of disaster. This means cooperative efforts to have both personal and mobile portable equipment, emergency repeaters, automated relaying, low-band interlinks, and—above all—experience. The duty is there, we already have the technology, and the work will be both fun and of help to tie us together, strengthening our clubs and our own value to our communities and country.

Then there is the responsibility of clubs to help amateur radio grow. This means devising schemes to interest teenagers in the hobby through talks at high schools, demonstrations at shopping malls, service for local groups, and participation in things like the March of Dimes. It means making sure that club activities are properly exploited with the local media. When there is a Field Day exercise, the local newspapers and television stations should get the word and be offered cooperation on the story.

Just getting the interest of teenagers isn't enough. Clubs should try to work with school officials to see that there is a radio club in the school which meets at least weekly. Schools have a serious problem about this which clubs can help solve. Any school activity has to have an adult advisor on hand. Since few schools have the budget to pay a teacher for this after-school work, the result has been a serious cutting down of after-school clubs. By providing the needed adult advisor, the local ham club could encourage the development of the school radio club.

Then there is the growing need for license classes to be put on by clubs. One of the really sad results of the Bash cheat-book approach to getting a ham ticket has been the lack of ham club members with even the small technical background it takes to teach the rudiments of theory required for the Novice exam. In some clubs, it is a case of those with scant information trying to teach newcomers, spreading confusion.

All of these problems have been solved by many clubs, so I'd like to see some letters and articles on these subjects for possible publication.

FROM TAYCO...
MAGNAVOX FV 25 – 26 CHANNEL
CABLE TV CONVERTER
and REMOTE CONTROL

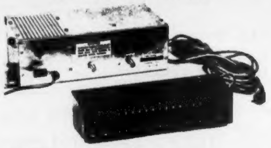

Get The Most From Cable TV
VHF-MIDBAND-SUPERBAND
- Select any channel with easy pushbutton tuning from up to 25' away
- Perfect for the bedroom TV
- Saves wear on TV tuner - avoid costly repairs
- Ideal for the handicapped
- Easy 5 minute installation
- Receives those EXTRA channels your TV can't get
- Works with any TV
- 90 Day Guarantee

only ~~$59.95~~
Mail Order SPECIAL
$49.95
+4.25 Shipping Handling

2-way Splitter 2.19
"F" Fittings .23ea - 10/1.80
Belden RG/59 .11/ft.

24 Hour Order Line
(607) 962-7313
NYS Add Tax
Buy 2 - We Pay Shipping
Order Direct From
C.O.D.'s - $1.50 extra
TAYCO COMMUNICATIONS
R3 - 146A Narrows Ck. Rd. - Corning N.Y. 14830
– DEALERS WANTED –
✓183

C.B. SPECIAL
(Repeat of a sell out)
CONVERT THESE TO 10 METER FM

New Hy-Gain 40 channel printed circuit boards assembly (Squelch pot, volume control and channel switch not included) Boards sold as is. Dimension 6"X6"

1-9 pcs $7.50 ea.
10-49 pcs $6.50 ea.
(While quantities last)

REMOTE 40 CHANNEL C.B.
Remotes have a metal frame. Speaker, plastic case, and control mic not included. Sold as is. **$14.95 ea**

C.B. BARGAIN
C.B. boards missing parts or damaged. Can be used for spare parts. Buy several!!
$3.50 ea

Order information: Please add $4.00 for S/H via UFS. COD's accepted for orders totaling $50.00 or more. Florida residents add 4% sales tax. Minimum order $15.00. Foreign orders US funds only add 20% for S/H. MASTER CARD and VISA accepted.

Surplus Electronics Corp.
7294 NW 54th St.
Miami FL 33166
P.H.# 305-887-8228
✓69

THE **LITTLE GIANT BRAKE**

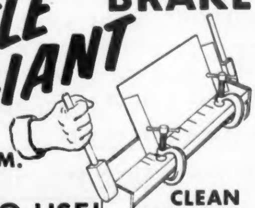

BEND
& FORM
.060 ALUM.
& STEEL!

EASY TO USE!
CLEAN SMOOTH BENDS TO 90°
BUILD CUSTOM CABINETS YOU'LL BE PROUD OF! COMMERCIAL QUALITY at 1/10 THE COST!!
GUARANTEED!
clamps not incl.

NO COD OR CREDIT CARDS.
ALL ORDERS IN US FUNDS.
ALL FOREIGN ORDERS ADD $5.50 SHIPPING IN ADDITION TO P&H.

$22.95
+ 2.50
P&H

Z ASSOCIATES
P O BOX 757
3050 NE 55 TH AVE.
SILVER SPRINGS, FLA. 32688
✓336

RELIABLE MICROWAVE TV ANTENNAS
2.1 to 2.6 GHz Frequency Range
34db System Gain (or Greater)

Complete System (as pictured)	$149.95
Down Converter Probe Style (Assembled and Tested)	$ 64.95
Power Supply (12V to 16V DC+) (Assembled and Tested)	$ 59.95

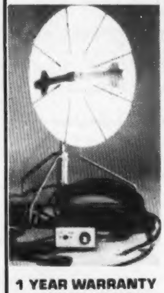

PETERSON ELECTRONICS
4558 Auburn Blvd.
Sacramento, CA 95841
(916) 486-9071
✓182

C.O.D.'s
SPECIAL QUANTITY PRICING
Dealers Wanted

1 YEAR WARRANTY PARTS & LABOR
MasterCard VISA

SAVE 90%

YES you can save up to 90% on a computer system of your own.

$150.00 buys a 4MHz Z80A with 64KB & a real Front Panel

$200.00 buys a Full Function 24x80 CRT with Keyboard

You can have your own computer and be running Fortran, Basic, Pascal, etc. If you get our

FREE BROCHURE
TODAY

DIGATEK CORP.
Suite 50A
2723 W. Butler Dr.
Phoenix AZ 85021

ROLL-YOUR-OWN TECHNOLOGY AND SAVE A BUNDLE
✓144

WANTED FOR CASH
Your Military Surplus Electronic Material: Airforce, Navy or Army Equipment, Modules, Tubes, or Parts. It costs nothing to get our highest offer.
Call Collect NOW
201-440-8787
35 Ruta Court
South Hackensack, N.J. 07606
SPACE ELECTRONICS Co.
Our 22nd Year
✓162

DELUXE CB MODULES FOR
10 METER CONVERSION
NAME BRAND 40 CHANNEL CB MODULES WITH BLUE/GREEN VF CHANNEL READOUT, LED BAR GRAPH S/POWER LEVEL INDICATOR, NOISE BLANKER, ANL, SQUELCH AND AUXILIARY SWITCHES, FULLY ENCLOSED IN METAL CASE, INCORPORATED INTO THOUSANDS OF BIG THREE AUTO COMPANY RADIO/CB UNITS.
- **Easily converted to 10 meter AM, FM, CW or FSK - Repeater or Simplex.**
- **AM & FM conversion information included**
- **Synthesizer similar to PLL 02A**
- **High performance circuit – 42 transistors & 7 IC's**
- **Low cost — $19.50 each**
- **Converted and tested units available**

SYNERGISTIC SYSTEMS
No. 1 Lumac Drive
P.O. Box 1258
Clanton, AL 35045
205-755-0174
✓192

YAESU FT-207R OWNERS
AUTO SCAN MODULE AND BATTERY SAVER KIT
WRITE FOR CLUB DISCOUNTS

15 minutes to install; scan restarts when carrier drops off; busy switch controls automatic scan on-off; includes module and instructions.
Model AS-1. $25.00

new
FT-207R BATTERY SAVER KIT MODEL BS-1 $14.95
- No more dead batteries due to memory back-up
- 30% less power drain when squelched
- Simple to install; step-by-step instructions and parts included
- 4 mA memory backup reduced to 500 μA.
- 45 mA receiver drain reduced to 30 mA.
- Improved audio fidelity and loudness

ENGINEERING CONSULTING
P.O. Box 3966
ANAHEIM, CALIFORNIA 92803
✓400

CB TO TEN METER CONVERSION KITS

10 METER FM—Limiter discriminator board with specific instructions to fit over 80 different AM & SSB chassis
SSB-AM KITS—Now in stock kits for most CB models—23 or 40 channels
NEW & USED—FM—SSB—AM converted C.B.'s in stock
ANEXTER MARK ANTENNAS—You saw them at Dayton. Now in stock the HW-3 three band helewhip that covers 10—15—20 meters with no traps
FREE CATALOG—Write or call today

INDEPENDENT CRYSTAL SUPPLY COMPANY
141 Rt. 6A, Box 183
Sandwich, Ma. 02563-0183
(617) 888-4302
✓78

FACIT 4555 SERIAL PAGE PRINTER

The Facit 4555 alphanumerical serial printer is complete. Equipped with RS232C Interface, printing mechanism, control electronics, drive electronics, power supply and character generator. The adaptation electronics can be modified in four versions:Bit-parallel data transfer, CCITT (EIA, RS232C) for bit-serial data transfer and the current loop (TTY) interface also for bit serial data transfer. The Facit 4555 prints on ordinary paper and is adjustable for different paper widths and formats, 9.5" paper width with 66 lines per page or DIN A4 with 70 lines per page.

SPECIFICATIONS

Print speed	up to 60ch.s.	Char. spacing	2.54mm/1/10" 80ch/line 1.55mm/0.06" 132ch/line
Printing mode	Incremental.		
Max. # of ch/line	80 alt. 132.	Char. Code	ECMA-6 7-bit coded char. set
Matrix	7 X 5 dot matrix.	Char. Set	63 Char. various national versions.
Char. Size Height	2.7mm/1/8"		
Char. Size Width	1.3mm/0.05" 132ch/line 2.1mm/0.083" 80ch/line	Feed mechanism	Sprocket feed.

THESE UNITS WERE PULLED OUT OF SERVICE IN GOOD WORKING CONDITION. WE CHECK EACH UNIT ON A RADIO SHACK TRS-80 COLOR COMPUTER.

PRINTER ONLY $129.99

Printer with linecord, box of paper, inter-connect cable for TRS-80 COLOR COMPUTER.
$149.99

GENEVA CALCULATOR WATCH

This attractive watch has the following modes:
Normal Time Setting,
Calendar Setting,
Daily Alarm Time Setting,
Weekly Alarm Time Setting,
Chronograph,
Calculator.

Featured in Black Plastic $24.99 or Featured in Stainless Steel $29.99

SILICON DIODES

MR751	100vdc	6Amps	10/$5.00	100/$38.00
MR510	1000vdc	3Amps	10/$3.75	100/$24.00
HEP170	1000vdc	2Amps	20/$2.00	100/$15.00
1N3209	100vdc	15Amps	$2.00	10/ $15.00
BYX21/200	200vdc	25Amps	$2.00	10/ $15.00
1N2138A	600vdc	60Amps	$5.00	10/ $40.00
DS85-04C	400vdc	80Amps	$10.00	10/ $80.00
1N3269	600vdc	160Amps	$15.00	10/$120.00
275Z41	300vdc	250Amps	$20.00	10/$175.00
7-5754	300vdc	400Amps	$30.00	10/$250.00
RCD-15	15KVDC	20ma.	$3.00	10/ $20.00
SMFR20K	20KVDC	20ma.	$4.00	10/ $30.00
1N4148	signal		30/$1.00	100/ $3.00

FEED THRU SOLDER RF CAPACITORS

470pf +-20%

5/$1.00 or 100/$15.00 or 1000/$100.00

1000pf/.001uf +-10%

4/$1.00 or 100/$20.00 or 1000/$150.00

E PROMS

2708	1024x1	$2.00 each
2716	2048x8	$4.00 each
27L32/25L32		$10.00 each

FAIRCHILD 4116 16K DYNAMIC RAMS 200ns. Part # 16K75

25 For $25.00 or 100 For $90.00 or 1000 For $750.00

HEWLETT PACKARD MICROWAVE DIODES

1N5711	(5082-2800)	Schottky Barrier Diodes	$1.00 or 10 for $ 8.50
1N5712	(5082-2810)	" " "	$1.50 or 10 for $10.00
1N6263	(HSCH-1001)	" " "	$ .75 or 10 for $ 5.00
5082-2835		" " "	$1.50 or 10 for $10.00
5082-2805	Quad Matched	" " " per set	$5.00 or 10 for $40.00

Toll Free Number
800-528-0180
(For orders only)

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"MIXERS"

WATKINS JOHNSON WJ-M6 Double Balanced Mixer

LO and RF 0.2 to 300MHz	IF DC to 300MHz	$21.00
Conversion Loss (SSB)	6.5dB Max. 1 to 50MHz 8.5dB Max. .2 to 300MHz	WITH DATA SHEET
Noise Figure (SSB)	same as above 8.5dB Max. 50 to 300MHz	
Conversion Compression	.3dB Typ.	

NEC (NIPPON ELECTRIC CO. LTD. NE57835/2SC2150 Microwave Transistor

NF Min	F=2GHz	dB 2.4 Typ.	MAG	F=2GHz	dB 12 Typ.	$5.30
	F=3GHz	dB 3.4 Typ.		F=3GHz	dB 9 Typ.	
	F=4GHz	dB 4.3 Typ.		F=4GHz	dB 6.5 Typ.	

Ft Gain Bandwidth Product at Vce=8v, Ic=10ma. GHz 4 Min. 6 Typ.
Vcbo 25v Vceo 11v Vebo 3v Ic 50ma. Pt. 250mw

UNELCO RF Power and Linear Amplifier Capacitors

These are the famous capacitors used by all the RF Power and Linear Amplifier manufacturers, and described in the RF Data Book.

5pf	10pf	18pf	30pf	43pf	100pf	200pf	1 to 10pcs.	$1.00 ea
5.1pf	12pf	22pf	32pf	51pf	110pf	220pf	11 to 50pcs.	$ .90 ea
6.8pf	13pf	25pf	33pf	60pf	120pf	470pf	51 up pcs.	$ .80 ea
7pf	14pf	27pf	34pf	80pf	130pf	500pf		
8.2pf	15pf	27.5pf	40pf	82pf	140pf	1000pf		

NIPPON ELECTRIC COMPANY TUNNEL DIODES

$7.50

		MODEL 1S2199	1S2200
Peak Pt. Current ma.	Ip	9min. 10Typ. 11max.	9min. 10Typ. 11max.
Valley Pt. Current ma.	Iv	1.2Typ. 1.5max.	1.2Typ. 1.5max.
Peak Pt. Voltage mv.	Vp	95Typ. 120max.	75Typ. 90max.
Projected Peak Pt. Voltage mv.	Vpp Vf=Ip	480min. 550Typ. 630max.	440min. 520Typ. 600max.
Series Res. Ohms	rS	2.5Typ. 4max.	2Typ. 3max.
Terminal Cap. pf.	Ct	1.7Typ. 2max.	5Typ. 8max.
Valley Pt. Voltage mv.	VV	370Typ.	350Typ.

FAIRCHILD / DUMONT Oscilloscope Probes Model 4290B

Input Impedance 10 meg., Input Capacity 6.5 to 12pf., Division Ration (Volts/Div Factor) 10:1, Cable Length 4Ft. , Frequency Range Over 100MHz.
These Probes will work on all Tektronix, Hewlett Packard, and other Oscilloscopes.

PRICE $45.00

MOTOROLA RF DATA BOOK

Listsall Motorola RF Transistors / RF Power Amplifiers, Varactor Diodes and much much more.

PRICE $7.50

Toll Free Number
800-528-0180
(For orders only)

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

RF TRANSISTORS, MICROWAVE DIODES

PART	PRICE
1S2199	$ 7.50
1S2200	7.50
2N1561	25.00
2N1562	25.00
2N2857	1.55
2N2857JAN	2.55
2N2876	11.00
2N2947	18.35
2N2948	15.50
2N2949	3.90
2N2950	4.60
2N3375	8.00
2N3553	1.57
2N3632	13.80
2N3818	5.00
2N3866	1.30
2N3924	3.35
2N3927	17.75
2N3950	25.00
2N4072	1.80
2N4127	21.00
2N4427	1.30
2N4428	1.85
2N4957	3.45
2N4958	2.90
2N4959	2.30
2N5090	13.90
2N5108	4.00
2N5109	1.70
2N5160	3.45
2N5177	21.62
2N5179	1.00
2N5583	4.00
2N5589	8.65
2N5590	10.35
2N5591	13.80
2N5635	10.95
2N5637	15.50
2N5641	9.20
2N5642	10.95
2N5643	15.50
2N5645	13.80
2N5646	20.70
2N5691	18.00
2N5764	27.00
2N5836	5.45
2N5842	8.00
2N5849	20.00
2N5913	3.25
2N5922	10.00
2N5923	25.00
2N5941	23.00
2N5942	40.00
2N5944	9.20
2N5945	11.50
2N5946	19.00
2N6080	9.20
2N6081	10.35
2N6082	11.50
2N6083	$ 13.25
2N6084	15.00
2N6094 /M9622	11.00
2N6095 /M9623	12.00
2N6096 /M9624	15.50
2N6097	17.25
2N6136	21.85
2N6166	40.25
2N6201	50.00
2N6459	18.00
2N6603	12.00
2N6680	80.00
2SC756A	7.50
2SC781	2.80
2SC1018	1.00
2SC1042	12.00
2SC1070	2.50
2SC1239	2.50
2SC1251	12.00
2SC1306	2.90
2SC1307	5.50
2SC1760	1.50
2SC1970	2.50
2SC2166	5.50
8B1087 (M.A.)	25.00
A50-12	20.00
A283B	5.00
ALD4200N (AVANTEK)	395.00
AM123	97.35
AM688	100.00
BB105B	.52
BD4/4JFBD4 (G.E.)	10.00
BFQ85	1.50
BFR90	1.30
BFR91	1.65
BFW92	1.50
BFX89	1.00
BFY90	1.00
BGY54	25.00
BGY55	25.00
BGY74	25.00
BGY75	25.00
BL161	10.00
BLX67	11.00
BLY568CF	25.00
BLY87	13.00
BLY88	14.00
BLY89	15.00
BLY90	20.00
BLY351	10.00
C4005	20.00
CA402 (TRW)	25.00
CA405 (TRW)	25.00
CA612B (TRW)	25.00
CA2100 (TRW)	25.00
CA2113 (TRW)	25.00
CA2200 (TRW)	25.00
CA2213 (TRW)	25.00
CA2418 (TRW)	25.00
CA2612 (TRW)	$ 25.00
CA2674 (TRW)	25.00
CA2881-1(TRW)	25.00
CA4101 (TRW)	25.00
CA4201 (TRW)	25.00
CA4600 (TRW)	25.00
CD1889	20.00
CD2545	20.00
CMD514AB	20.00
D4959	10.00
D4987M	20.00
D5147D	10.00
D5506	10.00
D5827AM	20.00
DMD6022	30.00
DMS-2A-250	40.00
HEP76	4.95
HEPS3002	11.30
HEPS3003	30.00
HEPS3005	10.00
HEPS3006	19.90
HEPS3007	25.00
HEPS3010	11.34
HTEF2204 H.P.	112.00
5082-0112 H.P.	14.20
5082-0253 H.P.	105.00
5082-0320 H.P.	58.00
5082-0386 H.P.	POR
5082-0401 H.P.	POR
5082-0438 H.P.	POR
5082-1028 H.P.	POR
5082-2711 H.P.	23.15
5082-3080 H.P.	2.00
5082-3188 H.P.	1.00
5082-6459 H.P.	POR
5082-8323 H.P.	POR
35826E H.P.	POR
35831E H.P.	29.99
35853E H.P.	71.50
35854E H.P.	75.00
HPA0241 H.P.	75.60
HXTR3101 H.P.	7.00
HXTR3102 H.P.	8.75
HXTR6101/2N6617 H.P.	55.00
HXTR6104 H.P.	68.00
HXTR6105 H.P.	31.00
HXTR6106 H.P.	33.00
QSCH1995 H.P.	POR
J02000 TRW	10.00
J02001 TRW	25.00
J04045 TRW	25.00
K3A	10.00
MA450A	10.00
MA41487	POR
MA41765	POR
MA43589	POR
MA43636	POR
MA47044	POR
MA47651	25.50

Toll Free Number
800-528-0180
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

MHz electronics

GaAs, TUNNEL DIODES, ETC.

PART	PRICE	PART	PRICE	PART	PRICE
MA47100	$ 3.05	MRF503	$ 6.00	PT4186B	$ POR
MA47202	30.80	MRF504	7.00	PT4209	POR
MA47771	POR	MRF509	5.00	PT4209C	POR
MA47852	POR	MRF511	8.65	PT4566	POR
MA49558	POR	MRF605	20.00	PT4570	POR
MB4021	POR	MRF629	3.47	PT4571	POR
MBD101	1.00	MRF644	23.00	PT4571A	POR
MD0513	POR	MRF816	15.00	PT4577	POR
MHW1171	42.50	MRF823	20.00	PT4590	POR
MHW1182	48.60	MRF901	3.00	PT4612	POR
MHW4171	49.35	MRF8004	2.10	PT4628	POR
MHW4172	51.90	MS261F	POR	PT4640	POR
MHW4342	68.75	MT4150 Fair.	POR	PT4642	POR
MLP102	25.00	MT5126 Fair.	POR	PT5632	POR
MM1500	32.32	MT5481 Fair.	POR	PT5749	POR
MM1550	POR	MT5482 Fair.	POR	PT6612	POR
MM1552	50.00	MT5483 Fair.	POR	PT6626	POR
MM1553	50.00	MT5596 Fair.	POR	PT6709	POR
MM1614	10.00	MT5764 Fair.	POR	PT6720	POR
MM2608	5.00	MT8762 Fair.	POR	PT8510	POR
MM3375A	11.50	MV109	.77	PT8524	POR
MM4429	10.00	MV1401	8.75	PT8609	POR
MM8000	1.15	MV1624	1.42	PT8633	POR
MM8006	2.30	MV1805	15.00	PT8639	POR
MO277L	POR	MV1808	10.00	PT8659	POR
MO283L	POR	MV1817B	10.00	PT8679	POR
MO3757	POR	MV1863B	10.00	PT8708	POR
MP102	POR	MV1864A	10.00	PT8709	POR
MPN3202	10.00	MV1864B	10.00	PT8727	POR
MPN3401	.52	MV1864D	10.00	PT8731	POR
MPN3412	1.00	MV1868D	10.00	PT8742	POR
MPSU31	1.01	MV2101	.90	PT8787	POR
MRA2023-1.5 TRW	42.50	MV2111	.90	PT9790	41.70
MRF212/208	16.10	MV2115	1.55	PT31962	POR
MRF223	13.25	MV2201	.53	PT31963	POR
MRF224	15.50	MV2203	.53	PT31983	POR
MRF237	3.15	MV2209	2.00	PTX6680	POR
MRF238	12.65	MV2215	2.00	RAY-3	24.99
MRF243	25.00	MWA110	7.45	40081	POR
MRF245	34.50	MWA120	7.80	40281	POR
MRF247	34.50	MWA130	8.25	40282	POR
MRF304	43.45	MWA210	7.80	40290	POR
MRF315	23.00	MWA220	8.25	RF110	25.00
MRF420	20.00	MWA230	8.65	SCA3522	POR
MRF421	36.80	MWA310	8.25	SCA3523	POR
MRF422	41.40	MWA320	8.65	SD1065	POR
MRF427	16.10	MWA330	9.50	SS43	POR
MRF428	46.00	NEC57835	5.30	TP1014	POR
MRF450/A	13.80	ON382	5.00	TP1028	POR
MRF453/A	17.25	PPT515-20-3	POR	TRW-3	POR
MRF454/A	19.90	PRT8637	POR	UTO504 Avantek	70.00
MRF455/A	16.00	PSCQ2-160	POR	UTO511 Avantek	75.00
MRF458	19.90	PT3190	POR	V15	4.00
MRF463	25.00	PT3194	POR	V33B	4.00
MRF472	1.00	PT3195	POR	V100B	4.00
MRF475	2.90	PT3537	POR	VAB801EC	25.00
MRF477	11.50	PT4166E	POR	VAB804EC	25.00
MRF502	1.04	PT4176D	POR	VAS21AN20	25.00

Toll Free Number
800-528-0180
(For orders only)

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

COAXIAL RELAY SWITCHES SPDT

Electronic Specialty Co./Raven Electronics FSN 5985-556-9683 $49.00
Part # 25N28 Part # SU-01
26Vdc Type N Connector, DC to 1 GHz.

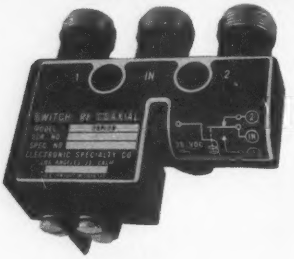
1
IN
2
SWITCH RF COAXIAL
ELECTRONIC SPECIALTY CO
26 VDC

NC
COM
NO
SWITCH COAXIAL FSN 5985 556 9683
630345
MFR RAVEN ELECTRONICS

Amphenol
Part # 316-10102-8
115Vac Type BNC DC to 3 GHz.

$29.99

FXR
Part # 300-11182
120Vac Type BNC DC to 4 GHz.
FSN 5985-543-1225

$39.99

FXR
Part # 300-11173
120Vac Type BNC Same
FSN 5985-543-1850

$39.99

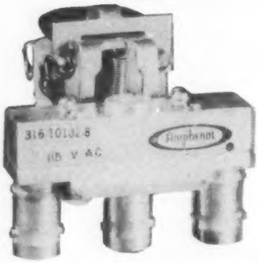
316 10102 8
115 V AC
Amphenol

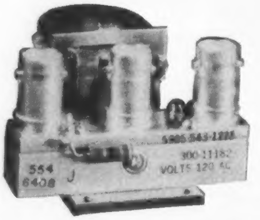
5985-543-1225
300-11182
VOLTS 120 AC
554
6408
J

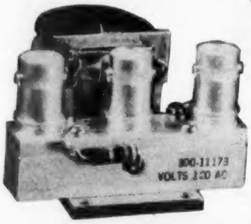
300-11173
VOLTS 120 AC

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

$7.99 or 2 For $13.99 or 10 For $50.00 $8.99 or 2 For $15.99 or 10 For $60.00

SOLID STATE RELAYS

P&B Model ECT1DB72 PRICE EACH $5.00	5vdc turn on	120vac contact at 7amps or 20amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.
Digisig, Inc. Model ECS-215 PRICE EACH $7.50	5vdc turn on	240vac contact 14amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.
Grigsby/Barton Model GB7400 PRICE EACH $7.50	5vdc turn on	240vac contact at 15amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

NOTE: *** Items may be substituted with other brands or equivalent model numbers. ***

MHz electronics

Toll Free Number
800-528-0180
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

RECALL PHONE MEMORY TELEPHONE WITH 24 NUMBER AUTO DIALER

The Recall Phone Telephone employs the latest state of art communications technology. It is a combination telephone and automatic dialer that uses premium-quality, solid-state circuitry to assure high-reliability performance in personal or business applications. $49.99

REAR VIEW
FRONT VIEW

ARON ALPHA RAPID BONDING GLUE

Super Glue #CE-486 high strength rapid bonding adhesive. Alpha Cyanoacrylate. Set-Time 20 to 40 sec., 0.7fl.oz. (20gm.)
$2.00

TOUCH TONE PAD

This pad contains all the electronics to produce standard touch-tone tones. New with data.

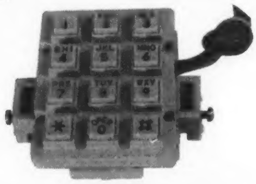

$9.99 or 10/$89.99

MITSUMI UHF/VHF VARACTOR TUNER MODEL UVE1A

Perfect for those unscrambler projects. New with data.

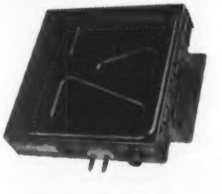

$19.99 or 10/$149.99

INTEGRATED CIRCUIT.

		1 to 10	11up
MC1372P	Color TV Video Modulator Circuit.	$ 4.42	$2.95
MC1358P	IF Amp., Limiter, FM Detector, Audio Driver, Electronic Attenuator.	5.00	4.00
MC1350P	IF Amplifier	1.50	1.25
MC1330A1P	Low Level Video Detector	1.50	1.15
MC1310P	FM Stereo Demodulator	4.29	3.30
MC1496P	Balanced Modulator/Demodulator	1.50	1.25
LM565N	Phase Locked Loop	2.50	2.00
LM380N14	2Watt Audio Power Amplifier	1.56	1.25
LM1889N	TV Video Modulator	5.00	4.00
NE564N	Phase Locked Loop	10.00	8.00
NE561N	Phase Locked Loop	10.00	8.00

FERRANTI ELECTRONICS AM RADIO RECEIVER MODEL ZN414 INTEGRATED CIRCUIT.

Features:

1.2 to 1.6 volt operating range., Less than 0.5ma current consumption. 150KHz to 3MHz Frequency range., Easy to assemble, no alignment necessary. Effective and variable AGC action., Will drive an earphone direct. Excellent audio quality., Typical power gain of 72dB., TO-18 package. With data. $2.99 or 10 For $24.99

NI CAD RECHARGEABLE BATTERIES

AA Battery Pack of 6 These are Factory New.	$5.00
SUB C Pack of 10 2.5Amp/Hr.	$10.00
Gates Rechargeable Battery Packs	
12vdc at 2.5Amp/Hr.	$11.99
12vdc at 5Amp/Hr.	$15.99

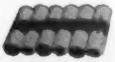

holiday greetings!

MHz electronics

Toll Free Number
800-528-0180
(For orders only)
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"SOCKETS AND CHIMNEYS"

EIMAC TUBE SOCKETS AND CHIMNEYS

SK110	Socket	$POR
SK300A	Socket For 4CX5000A,R,J, 4CX10,000D, 4CX15,000A,J	$520.00
SK400	Socket For 4-125A,250A,400A,400C,4PR125A,400A,4-500A,5-500A	260.00
SK406	Chimney For 4-250A,400A,400C,4PR400A	74.00
SK416	Chimney For 3-400Z	36.00
SK500	Socket For 4-1000A/4PR1000A/B	390.00
SK600	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	51.00
SK602	Socket For 4CX250B,BC,FG,R,4CX350A,F,FJ	73.00
SK606	Chimney For 4CX250B,BC,FG,R,4CX350A,F,FJ	11.00
SK607	Socket For 4CX600J,JA	60.00
SK610	Socket For 4CX600J,JA	60.00
SK620	Socket For 4CX600J,JA	66.00
SK626	Chimney For 4CX600J,JA	10.00
SK630	Socket For 4CX600J,JA	66.00
SK636B	Chimney For 4CX600J,JA	34.00
SK640	Socket For 4CX600J,JA	36.00
SK646	Chimney For 4CX600J,JA	71.00
SK700	Socket For 4CX300A,Y,4CX125C,F	225.00
SK711A	Socket For 4CX300A,Y,4CX125C,F	225.00
SK740	Socket For 4CX300A,Y,4CX125C,F	86.00
SK770	Socket For 4CX300A,Y,4CX125C,F	86.00
SK800A	Socket For 4CX1000A,4CX1500B	225.00
SK806	Chimney For 4CX1000A,4CX1500B	40.00
SK810	Socket For 4CX1000A,4CX1500B	225.00
SK900	Socket For 4X500A	300.00
SK906	Chimney For 4X500A	57.00
SK1420	Socket For 5CX3000A	650.00
SK1490	Socket For 4CV8000A	585.00

JOHNSON TUBE SOCKETS AND CHIMNEYS

124-111/SK606	Chimney For 4CX250B,BC,FG,R, 4CX350A,F,FJ	$ 10.00
122-0275-001	Socket For 3-500Z, 4-125A, 250A, 400A, 4-500A, 5-500A	(pair)15.00
124-0113-00	Capacitor Ring	15.00
124-116/SK630A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
124-115-2/SK620A	Socket For 4CX250B,BC,FG,R, /4CX350A,F,FJ	55.00
	813 Tube Socket	20.00

TUBE CAPS (Plate)

HR1, 4	$11.00
HR2,3, 6 & 7	13.00
HR5, 8	14.00
HR9	17.00
HR10	20.00

CHIP CAPACITORS

.8pf
1pf
1.1pf
1.4pf
1.5pf
1.8pf
2.2pf
2.7pf
3.3pf
3.6pf
3.9pf
4.7pf
5.6pf
6.8pf
8.2pf
10pf
12pf
15pf
18pf
20pf
22pf
24pf
27pf
33pf
39pf
47pf
51pf
56pf
68pf
82pf
100pf*
110pf
120pf
130pf
150pf
160pf
180pf
200pf
220pf*
240pf
270pf
300pf
330pf
360pf
390pf
430pf
470pf
510pf
560pf
620pf
680pf
820pf
1000pf/.001uf*
1800pf/.0018uf
2700pf/.0027uf
10,000pf/.01uf
12,000pf/.012uf
15,000pf/.015uf
18,000pf/.018uf

PRICES: 1 to 10 - .99¢ 101 to 1000 .60¢ * IS A SPECIAL PRICE: 10 for $7.50
11 to 50 - .90¢ 1001 & UP .35¢ 100 for $65.00
51 to 100 - .80¢ 1000 for $350.00

WATKINS JOHNSON WJ-V907: Voltage Controlled Microwave Oscillator $110.00

Frequency range 3.6 to 4.2GHz, Power ouput, Min. 10dBm typical, 8dBm Guaranteed. Spurious output suppression Harmonic (nf_0), min. 20dB typical, In-Band Non-Harmonic, min. 60dB typical, Residual FM, pk to pk, Max. 5KHz, pushing factor, Max. 8KHz/V, Pulling figure (1.5:1 VSWR), Max. 60MHz, Tuning voltage range +1 to +15volts, Tuning current, Max. -0.1mA, modulation sensitivity range, Max. 120 to 30MHz/V, Input capacitance, Max. 100pf, Oscillator Bias +15 +-0.05 volts @ 55mA, Max.

Toll Free Number
800-528-0180
(For orders only)

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2E26	$ 5.69	KT88	$ 20.00	6562/6974A	$ 50.00
2K28	100.00	DX362	50.00	6832	22.00
2X1000A	300.00	DX415	50.00	6883/8032A/8552	7.00
3B22	19.75	572B/T160L	49.00	6897	110.00
3B28/866A	7.50	592/3-200A3	144.00	6907A	75.00
3-500Z	102.00	807	7.50	6939	15.00
3-1000Z	400.00	811	10.00	7094	125.00
3CX1000A/8283	428.00	811A	15.00	7117	17.00
3CX1500A7/887	533.00	812A	35.00	7211	60.00
3X2500A3	200.00	813	50.00	7289/3CX100A5	34.00
3CX3000A7	490.00	829B	38.00	7360	11.00
4-65A/8165	45.00	832A	28.00	7377	67.00
4-125A/4D21	58.00	4624	310.00	7408	4.00
4-250A/5D22	75.00	4662	80.00	7650	250.00
4-400A/8432	90.00	4665	585.00	7695	8.00
4-400C/6775	95.00	5675/A	25.00	7843	58.00
4-1000A/8166	300.00	5721	200.00	7854	83.00
4B32	22.00	5768	85.00	7868	5.00
4E27A/5-125B	155.00	5836	100.00	7894	12.00
4CS250R	146.00	5837	100.00	8072	65.00
4X150A/7034	30.00	5861/EC55	110.00	8117A	130.00
4X150D/7035	40.00	5876A	25.00	8121	60.00
4X150G/8172	100.00	5881/6L6W	6.00	8122	100.00
4X250B	30.00	5893	45.00	8236	30.00
4CX250B/7203	45.00	5894/A	50.00	8295/PL172	506.00
4CX250F/G/8621	55.00	5894/B	60.00	8462	100.00
4CX250K/8245	100.00	5946	258.00	8505A	73.50
4CX250R/7580W	69.00	6080	10.00	8533W	92.00
4CX300A/8167	140.00	6083/AX9909	89.00	8560/A	65.00
4CX350A/8321	83.00	6098/6AK6	14.00	8560AS	90.00
4CX350F/J/8904	95.00	6115/A	110.00	8608	34.00
4X500A	282.00	6146	7.00	8637	38.00
4CX600J/8809	607.00	6146A	7.50	8643	100.00
4CW800F	625.00	6146B/8298A	8.50	8647	123.00
4CX1000A/8168	340.00	6146W	14.00	8737/5894B	60.00
4CX1500B/8660	397.00	6156	66.00	8873	260.00
4CX5000A/8170	932.00	6159	15.00	8874	260.00
4CX10000D/8171	990.00	6161	233.00	8875	260.00
4CX15000A/8281	1260.00	6291	125.00	8877	533.00
4PR60A	100.00	6293	12.00	8908	12.00
4PR60B/8252	175.00	6360	5.00	8930/651Z	71.00
4PR400A/8188	192.00	6524	53.00	8950	12.00
5CX1500A	569.00	6550	10.00		
6BK4C	6.00	6JM6	6.00	6LQ6 (Sylvania)	7.50
6DQ5	5.00	6JN6	6.00	6LU8	6.00
6FW5	6.00	6JS6B	6.00	6LX6	6.00
6GE5	6.00	6KG6/EL505	6.00	6ME6	6.00
6GJ5	6.00	6KM6	6.00	12BY7A	4.00
6HS5	6.00	6KN6	6.00	12JB6A	6.00
6JB5/6HE5	6.00	6LF6	6.00	6KD6	6.00
6JB6A	6.00	6LQ6 (GE)	6.00	6JT6A	6.00
				6KD6	6.00

NOTICE ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE !!!
TUBES MAY EITHER BE NEW OR SURPLUS CONDITION !!

Toll Free Number
800-528-0180
(For orders only)

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"TVRO BOARD LIST"

70 MHZ IF BOARD: This circuit provides about 43dB gain with 50 ohm input and output impedance. It is designed to drive the Demodulator. The on-board bypass filter can be tuned to bandwidths between 20 and 35 MHz with a passband ripple of less than ½ dB. Hybrid IC's are used for the gain stages.

SINGLE AUDIO BOARD: This circuit recovers the audio signals from the 6.8 MHz frequency. The Miller 9051 coils are tuned to pass the 6.8MHz subcarrier and the 9052 coil tunes for recovery of the audio.

DUAL AUDIO BOARD: Duplicate of the single audio but also covers the 6.2 range.

DC CONTROL BOARD: No description.

DUAL AUDIO BOARD		PRICE EACH
	Printed Circuit Board	$ 25.00
2	3pf sm	1.00
2	12pf sm	1.00
2	50pf sm	1.00
2	68pf sm	1.00
4	91pf sm	1.00
5	.001mfd	.35
6	.01mfd	.35
2	.047mfd	.35
1	.47mfd 25vdc	.35
2	1mfd 10vdc	.59
4	4.7mfd 35vdc	.59
1	470mfd 25vdc	1.29
2	220K 1/4w	.15
2	150K 1/4w	.15
2	6.8K 1/4w	.15
2	3.3K 1/4w	.15
2	2.2K 1/4w	.15
4	1K 1/4w	.15
2	10 ohm 1/4w	.15
2	50K pots	1.00
1	5K pot	1.00
2	CA3065	2.16
1	LM380	1.56
1	7812 Voltage Reg.	1.17
5	2N2222	.50
4	Miller 9051	5.99
2	Miller 9052	5.99
	TOTAL KIT PRICE	97.62

DC CONTROL BOARD		
	Printed Circuit Board	15.00
2	470mfd 25vdc	1.29
2	4.7mfd 25vdc	.59
1	1meg 1/4w	.15
3	10K 1/4w	.15
1	3.3K 1/4w	.15
3	2.2K 1/4w	.15
1	1K 1/4w	.15
2	5K 10 turn trimpot	1.00
4	10K 10 turn trimpot	1.00
1	10K 10 turn with dial	10.00
1	7815 Voltage Reg.	1.17
1	LM324	2.50
1	5 pole rotary switch	2.50
1	SPDT switch	1.00
1	DPDT swich	1.00
1	0-1ma meter	5.00
1	18 to 24vdc at 1 amp power supply	24.99
	TOTAL KIT PRICE	74.27

DEMODULATOR BOARD		PRICE EACH
	Printed Circuit Board	$ 40.00
1	1mfd 35vdc	.59
13	.01mfd 50vdc disc	.35
1	470mfd 25vdc	1.29
2	100mfd 16vdc	.69
2	22mfd 35vdc	.59
3	4.7mfd 35vdc	.59
1	4300pf sm	2.00
1	330pf sm	1.00
1	100pf sm	1.00
1	91pf sm	1.00
2	3pf sm	1.00
1	2 to 8pf ceramic trimmer	1.00
1	100uh choke	1.50
1	4.7uh choke	1.50
1	2.7uh choke	1.50
4	100K 1/4w	.15
1	51 ohm 1/4w	.15
1	27K 1/4w	.15
5	10K 1/4w	.15
1	8.2K 1/4w	.15
2	4.7K 1/4w	.15
1	2.2K 1/4w	.15
1	1.2K 1/4w	.15
3	1K 1/4w	.15
3	560 ohm 1/4w	.15
1	470 ohm 1/4w	.15
1	390 ohm 1/4w	.15
1	300 ohm 1/4w	.15
1	270 ohm 1/4w	.15
1	150 ohm 1/4w	.15
1	41 ohm 1/4w	.15
1	10K pot	1.00
1	NE592/LM733N	2.50
1	NE564	5.00
1	MWA120 (Motorola)	7.80
1	7812 Voltage Reg.	1.17
1	7815 Voltage Reg.	1.17
3	2N2222	.50
2	1N34/38	.50
1	HP5082-2800	2.20
1	5 to 7 volt Zenner	1.00
	TOTAL KIT PRICE	92.25

COMPLETE KIT WITH DUAL AUDIO	$923.23
COMPLETE KIT WITH SINGLE AUDIO	880.77

LESS 10% ON ALL COMPLETE KIT ORDERS

BOARDS AND PARTS MAY BE PURCHASED SEPERATELY AT THE PRICES LISTED ABOVE.

ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!

TVRO BOARD DESCRIPTION AND PARTS LIST

DUAL CONVERSION BOARD: This board provides conversion from the 3.7-4.2 band first to 900 MHz where gain and bandpass filtering are provided and, second, to 70 MHz. The board contains both local oscillators, one fixed and the other variable, and the second mixer. Construction is greatly simplified by the use of Hybrid IC amplifiers for the gain stages.

DEMODULATOR BOARD: This circuit takes the 70 MHz center frequency satellite TV signal in the 10 to 200 millivolt range, detects them using a phase lock loop, de-emphasizes and filters the result to produce standard NTSC video. Other outputs include the audio subcarrier, a DC voltage proportional to the strength of the 70 MHz signal, and AFC voltage centered at about 2 volts DC.

DUAL CONVERSION BOARD		PRICE EACH
	Printed Circuit Board	$ 25.00
6	47pf chip caps	1.00
2	4.7mfd 35vdc	.59
2	.01mfd 50vdc disc cap	.35
4	1.5 to 8pf piston trimmer cap	5.99
2	470 ohm 1/4w	.15
2	MWA320 (Motorola)	8.65
1	7815 Voltage Reg.	1.17
1	VTO8090	150.00
1	VTO8240	156.25
2	1N4005	.39
1	DBM500/1100 (Varil)	125.00
1	MLP102 (Engleman)	25.00
8	SMA Male Connector	5.00
	TOTAL KIT PRICE	572.64

70 MHZ IF BOARD		
	Printed Circuit Board	25.00
3	MWA120	7.80
7	.01mfd 50vdc	.35
2	4.7mfd 35vdc	.59
1	10pf sm	1.00
5	22pf sm	1.00
1	18pf sm	1.00
1	33pf sm	1.00
2	330 ohm 1/4w	.15
5	J.W. Miller 4500-4	4.99
1	7815 Voltage Reg.	1.17
	TOTAL KIT PRICE	86.45

SINGLE AUDIO BOARD		PRICE EACH
	Printed Circuit Board	$ 15.00
1	3pf sm	1.00
1	12pf sm	1.00
1	50pf sm	1.00
1	68pf sm	1.00
2	91pf sm	1.00
3	.001mfd	.35
3	.01mfd	.35
1	.047mfd	.35
1	.47mfd	.35
1	1mfd 10vdc	.59
3	4.7mfd 35vdc	.59
1	470mfd 25vdc	1.29
1	220K 1/4w	.15
1	150K 1/4w	.15
1	6.8K 1/4w	.15
1	3.3K 1/4w	.15
1	2.2K 1/4w	.15
3	1K 1/4w	.15
1	10 ohm 1/4w	.15
1	50K pot	1.00
1	5K pot	1.00
1	CA3065/MC1358P	2.16
1	LM380	1.56
1	7812 Voltage Reg.	1.17
3	2N2222	.50
2	Miller 9051	5.99
1	Miller 9052	5.99
	TOTAL KIT PRICE	55.16

Toll Free Number
800-528-0180
(For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

MHz electronics

"CHIPS"

FAIRCHILD VHF AND UHF PRESCALER CHIPS		PRICE
95H90DC	350MC Prescaler divide by 10/11	$ 8.50
95H91DC	350MC Prescaler divide by 5/6	8.50
11C90DC	650MC Prescaler divide by 10/11	15.50
11C91DC	650MC Prescaler divide by 5/6	15.50
11C06DC	UHF Prescaler 750MC D Type Flip Flop	12.30
11C05DC	1GHz Counter Divide by 4 (Regular price $75.00)	50.00
11C01FC	High Speed Dual 5/4 Input NO/NOR Gate	15.40
82S90	Presettable High Speed Decade/Binary Counter used with the 11C90/91 or the 95H90/91 Prescaler can divide by 100. (Signetics)	5.00
11C24DC	This chip is the same as a Motorola MC4024/4324 Dual TTL Voltage Control Multivibrator.	3.37
11C44DC	This chip is the same as a Motorola MC4044/4344 Phase Frequency Detector.	3.37

GENERAL ELECTRIC CO. GUNN DIODE MODEL Y-2167
Freq. Gap (GHZ) 12 to 18, Output (Min.) 100mW, Duty (%) CW, Typ. Bias (Vdc) 8.0, Type. Oper. (MAdc) 550, Max. Thres. (mAdc) 1000, Max. Bias (Vdc) 10.0. **$39.99**

VARIAN GALLIUM ARSENIDE GUNN DIODES MODEL VSX-9201S5
Freq. Coverage 8 to 12.4GHz, Output (Min.) 100mW, Bias Voltage (Max.) 14vdc, Bias current (mAdc) Operating 550 Typ. 750 Max., Threshold 850 Tup. 1000 Max. **$39.99**

VARI-L Co. Inc. MODEL SS-43 AM MODULATOR
Freq. Range 60 10 150MC, Insertion Loss 13dB Nominal, Signal Port Imp. 50ohms Nominal, Signal Port RF Power +10dBm Max., Modulation Port BW DC to 1KHZ, Modulation Port Bias 1ma. Nominal. **$24.99**

AVANTEK CASCADABLE MODULAR AMPLIFIERS	Model UTO-504	UTC-511
Frequency Range	5 to 500 MHz	5 to 500 MHz
Gain	6dB	15dB
Noise Figure	11dB	2.3dB to 3dB
Power Output	+17dB	−2dB to −3dB
Gain Flatness	1dB	1dB
Input Power Vdc	+24	+15
mA	100	10
PRICE	$70.00	$75.00

HEWLETT PACKARD MIXERS MODELS	10514A	10514B
Frequency Range	2MHz to 500MC	2MHz to 500MC
Input/Output Frequency L & R	200KHz to 500MC	200KHz to 500MC
X	DC to 500MC	DC to 500MC
Mixer Conversion Loss (A)	7dB	7dB
(B)	9dB	9dB
Noise Performance (SSB) (A)	7dB	7dB
(B)	9dB	9dB
PRICE	$49.99	$39.99

FREQUENCY SOURCES, INC MODEL MS-74X MICROWAVE SIGNAL SOURCE
MS-74X: Mechanically Tunable Frequency Range (MHz) 10630 to 11230 (10.63 to 11.23GHz) Minimum Output Power (mW) 10, Overall Multiplier Ratio 108, Internal Crystal Oscillator Frequency Range (MHz) 98.4 to 104.0, Maximum Input Current (mA) 400.

The signal source are designed for applications where high stability and low noise are of prime concern. these sources utilize fundamental transistor oscillators with high Q coaxial cavities, followed by broadband stable step recovery diode multipliers. This design allows single screw mechanical adjustment of frequency over standard communications bands. Broadband sampling circuits are used to phase lock the oscillator to a high stability reference which may be either an internal self-contained crystal oscillator, external primary standard or VHF synthesizer. This unique technique allows for optimization of both FM noise and long term stability. List Price is $1158.00 (THESE ARE NEW) **Our Price—$289.**

HEWLETT PACKARD 1N5712 MICROWAVE DIODE
This diode will replace the MBD101, 1N5711, 5082-2800, 5082-2835 ect. This will work like a champ in all those Down Converter projects. **$1.50 or 10/$10.00**

MOTOROLA MHW1172R LOW DISTORTION WIDEBAND AMPLIFIER MODULE.
Frequency Range: 40 to 300 MHz., Power Gain at 50MHz 16.6min. to 17.4max., Gain Flatness ±0.1 Typ. ±0.2 Max. dB., DC Supply Voltage −28vdc, RF Voltage Input +70dBmV **PRICE $29.99**

GENERAL ELECTRIC AA NICADS
Model #41B905HD11-G1
Pack of 6 for $5.00 or 60 Cells, 10 Packs for $45.00
These may be broken down to individual cells.

ORDERING INSTRUCTIONS

DEFECTIVE MATERIAL: All claims for defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed properly or it will void all warranties.

DELIVERY: Orders are normally shipped within 48 hours after receipf of customer's order. If a part has to be backordered the customer is notified. Our normal shipping method is via First Class Mail or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point.

FOREIGN ORDERS: All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.D. is not available to foreign countries and Letters of Credit are not an acceptable form of payment either. Further information is available on request.

HOURS: Monday thru Saturday: 8:30 a.m. to 5:00 p.m.

INSURANCE: Please include 25¢ for each additional $100.00 over $100.00, United Parcel only.

ORDER FORMS: New order forms are included with each order for your convenience. Additional forms are available on request.

POSTAGE: Minimum shipping and handling in the US, Canada, and Mexico is $2.50 all other countries is $5.00. On foreign orders include 20% shipping and handling.

PREPAID ORDERS: Order must be accompanied by a check.

PRICES: Prices are subject to change without notice.

RESTOCK CHARGE: If parts are returned to MHZ Electronics due to customer error, customer will be held responsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returns must have approval.

SALES TAX: Arizona must add 5% sales tax, unless a signed Arizona resale tax card is currently on file with MHZ Electronics. All orders placed by persons outside of Arizona, but delivered to persons in Arizona are subject to the 5% sales tax.

SHORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY
NO INFORMATION WILL BE GIVEN. 1-800-528-0180.

TERMS: DOMESTIC: Prepaid, C.O.D. or Credit Card
FOREIGN: Prepaid only, U.S. Funds—money order or cashier's check only.

C.O.D.: Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's check. We are sorry but we cannot accept personal checks for C.O.D.'s.

CONFIRMING ORDERS: We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, customers will be held responsible for any charges incurred, plus a 15% restock charge on returned parts.

CREDIT CARDS: WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.

DATA SHEETS: When we have data sheets in stock on devices we do supply them with the order.

master charge VISA

MHz electronics

✓48

(602) 242-3037
(602) 242-8916
2111 W. CAMELBACK ROAD
PHOENIX, ARIZONA 85015

Toll Free Number
800-528-0180
(For orders only)

SLEP ELECTRONICS

GIVES TOP TRADE on your used **ATLAS, COLLINS, DRAKE, ICOM, KENWOOD, TEN-TEC** amateur gear . . . plus we accept your used solid state **TEKTRONIX** and **HEWLETT-PACKARD** test equipment, used **AVIONIC** equipment, and military surplus avionic and ground electronic equipment.

WE OFFER new factory-boxed latest models of: **COLLINS, CUBIC/SWAN, DENTRON, DRAKE, ETO, HENRY, ICOM, TEN-TEC**, plus all major antenna and accessory lines.

Tell us what you want and what you have to trade. We'll do the rest.

Write or phone Bill Slep (704) 524-7519

Electronic Distributors

Slep Electronics Company
P. O. BOX 100, HWY 441, DEPT. 73
OTTO, NORTH CAROLINA 28763

✓367

HAM HELP

We are happy to provide Ham Help listings free, on a space-available basis. We are not happy when we have to take time from other duties to decipher cryptic notes scrawled illegibly on dog-eared post cards and odd-sized scraps of paper. Please type or print your request (neatly!), double spaced, on an 8½" × 11" sheet of paper and use upper- and lowercase letters where appropriate. Also, please make a "1" look like a "1," not an "l," which could be an "el" or an "eye," and so on. Hard as it may be to believe, we are not familiar with every piece of equipment manufactured on Earth for the last 50 years! Thanks for your cooperation.

Does anyone have information on RTTY software for a TRS-80 Model I Level II?

Gary Hansen KA0JUM
Route 1 Box 103
Deerwood MN 56444

I am looking for hams with RTTY equipment who would like to help deaf students attending school in Washington DC communicate with their families back home.

Jeffrey A. Meyer N8AHA
26366 Greythorne Trail
Farmington Hills MI 48018

I am looking for a used LCR bridge such as the Leader LCR 740.

Jim Buckwalter WA6FGM
3212 Millcreek
Visalia CA 93291

I need a service manual and schematic diagram for a Hy-Gain Galaxy GT-550-A SSB transceiver. I will pay reasonable copying costs or copy and return.

Jose Sanabrais
Av. Hidalgo No. 99
Queretaro, Qro.
76000 Mexico

I would like to buy the following WWII surplus receivers, in at least good used condition (they need not include power supply, dynamotor, etc.): ARB, RBB (0.5 to 4.0 MHz), and BC-946 (broadcast band ARC-5 receiver).

Meyer Gottesman W6GIV
3377 Solano Avenue, #312
Napa CA 94558

I am blind and bedridden and searching for someone to donate a Kenwood 600 receiver or any other shortwave receiver.

Richard Jastrow
Long Beach General Hospital
2597 Redondo Ave.
Long Beach CA 90806

My club's 5-page Novice-class study guide is offered in exchange for your club's Novice- and/or General-class handouts. Ours is a brief description of the items listed in the current FCC syllabus and has a 95% pass rate in our classes.

Jim Koski KT6W
1714 Austin Avenue
Los Altos CA 94022

* **BEC** * **Bullet Electronics Corp. P.O. Box 401244E Garland, TX. 75040 (214) 278-3553**

✓12

THE PRESIDENT SAYS: "HOGWASH!!"

After taking one look at the TRIPUT POWER SUPPLY our engineer declared that the units were worth several hundred dollars each. He pointed out the engineering, high quality construction and state-of-the-art integrated design in support of his position. The President of **BEC** more pragmatically pointed out the already full warehouse and the two trailer truck loads of power supplies waiting in the parking lot, and set the price to move them **QUICKLY!** We have a large quantity, but the supply won't last long. The only thing we ask is *please* read the ordering rules.

13.6V @ 20A MODIFICATION

By changing a few parts on the board the Triput Power Supply will do **11 - 14V** (adjustable) at up to **20A.** Perfect for that 2 meter linear amp! We send step by step instructions and necessary parts. **Modification per instructions will not void the 30 day warranty.**

QUALITY DOUBLE SIDED GLASS BOARD

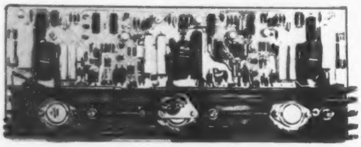

REGULATOR ASSEMBLY
(part of unit)

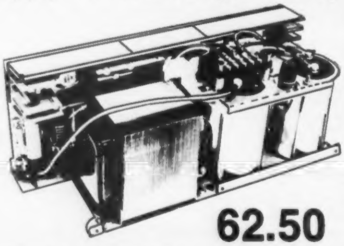

COMPLETE UNIT
(as you receive it)

62.50
Plus Freight
21 lbs.
6 x 5¼ x 12

+12V @ 7A; +5V @ 10A; -12V @ 5A
- UNIT IS COMPLETELY ASSEMBLED!
- Fused primary and DC sections
- HUGE SHIELDED TRANSFORMER
- 2% Load & Line Regulation
- Low Ripple (<100mv)
- Short Circuit Protection
- Overvoltage Protection on all three outputs
- 25A Bridge Rectifier
- Over 60,000 mfd of filters
- High Efficiency **Switching Regulator** reduces heatsink area
- Schematics and service guide included
- Thermal Shutdown
- Statis LED's (3)

ORDERS SHIPPED WITHIN CONTINENTAL U.S. ONLY!

ORDERING RULES

1. Mail check or MO for $62.50 + $5.00 for shipping or phone (214) 278-3553 to charge VISA/MC or COD order. (UPS COD only, add $2.50 COD fee)
2. Texas residents include 5% sales tax.
3. Orders for this unit will be shipped within **48 HOURS** or we pay the freight! (weekends or holidays excluded)
4. **ONE TIME OFFER! LIMIT TWO (2) SUPPLIES PER CUSTOMER.**

ramsey the first name in Counters !

9 DIGITS 600 MHz $129.95 WIRED

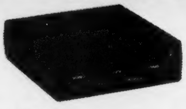

PRICES

CT-90 wired, 1 year warranty	$129.95
CT-90 Kit, 90 day parts warranty	109.95
AC-1 AC adapter	3.95
BP-1 Nicad pack +AC Adapter/Charger	12.95
OV-1, Micro-power Oven time base	49.95
External time base input	14.95

The CT-90 is the most versatile, feature packed counter available for less than $300.00! Advanced design features include; three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally; an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 10 MV to 150 MHz Less than 50 MV to 500 MHz
Resolution:	0.1 Hz (10 MHz range) 1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	9 digits 0.4" LED
Time base:	Standard-10.000 mHz, 1.0 ppm 20-40°C. Optional Micro-power oven-0.1 ppm 20-40°C
Power:	8-15 VAC @ 250 ma

7 DIGITS 525 MHz $99.95 WIRED

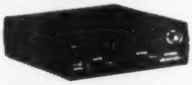

SPECIFICATIONS:

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz Less than 150 MV to 500 MHz
Resolution:	1.0 Hz (5 MHz range) 10.0 Hz (50 MHz range) 100.0 Hz (500 MHz range)
Display:	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power:	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as; three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

PRICES:

CT-70 wired, 1 year warranty	$99.95
CT-70 Kit, 90 day parts warranty	84.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC adapter/charger	12.95

7 DIGITS 500 MHz $79.95 WIRED

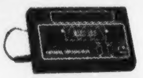

PRICES:

MINI-100 wired, 1 year warranty	$79.95
AC-Z Ac adapter for MINI-100	3.95
BP-Z Nicad pack and AC adapter/charger	12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

SPECIFICATIONS:

Range:	1 MHz to 500 MHz
Sensitivity:	Less than 25 MV
Resolution:	100 Hz (slow gate) 1.0 KHz (fast gate)
Display:	7 digits, 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	5 VDC @ 200 ma

8 DIGITS 600 MHz $159.95 WIRED

NEW READ RECEIVER FREQUENCY

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 25 mv to 150 MHz Less than 150 mv to 600 MHz
Resolution:	1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	8 digits 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:

CT-50 wired, 1 year warranty	$159.95
CT-50 Kit, 90 day parts warranty	119.95
RA-1, receiver adapter kit	14.95
RA-1 wired and pre-programmed (send copy of receiver schematic)	29.95

DIGITAL MULTIMETER $99.95 WIRED

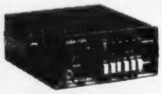

PRICES:

DM-700 wired, 1 year warranty	$99.95
DM-700 Kit, 90 day parts warranty	79.95
AC-1, AC adaptor	3.95
BP-3, Nicad pack +AC adapter/charger	19.95
MP-1, Probe kit	2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include; 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3½ digit, ½ inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts:	100uV to 1 KV, 5 ranges
DC/AC current:	0.1uA to 2.0 Amps, 5 ranges
Resistance:	0.1 ohms to 20 Megohms, 6 ranges
Input impedance:	10 Megohms, DC/AC volts
Accuracy:	0.1% basic DC volts
Power:	4 'C' cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

$29.95 Kit $39.95 Wired

ACCESSORIES

Telescopic whip antenna - BNC plug	$ 7.95
High impedance probe, light loading	15.95
Low pass probe, for audio measurements	15.95
Direct probe, general purpose usage	12.95
Tilt bail, for CT 70, 90, MINI-100	3.95
Color burst calibration unit, calibrates counter against color TV signal	14.95

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
- BNC Connectors
- Great for sniffing RF with pick-up loop

$34.95 Kit $44.95 Wired

ramsey electronic's, inc. VISA

2575 Baird Rd, Penfield, NY 14526 ✓62

PHONE ORDERS
CALL 716-586-3950

TERMS Satisfaction guaranteed examine for 10 days if not pleased return in original form for refund. Add 5% for shipping insurance to a maximum of $10. Overseas add 15%. COD add $7. Orders under $10 add $1.50. NY residents add 7% tax.

NEW LOW-NOISE PREAMPS

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.

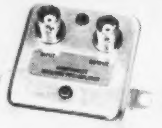

Models LNA( ), P30, and P432 shown

Model	Tunable Freq Range	Noise Figure	Gain	Price
LNA 28	20-40	0.9 dB	20 dB	$39.95
LNA 50	40-70	0.9 dB	20 dB	$39.95
LNA 144	120-180	1.0 dB	18 dB	$39.95
LNA 220	180-250	1.0 dB	17 dB	$39.95
LNA 432	380-470	1.0 dB	18 dB	$44.95

ECONOMY PREAMPS

Our traditional preamps, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freq. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

P30K, VHF Kit less case	$14.95
P30C, VHF Kit with case	$20.95
P30W, VHF Wired/Tested	$29.95
P432K, UHF Kit less case	$18.95
P432C, UHF Kit with case	$24.95
P432W, UHF Wired/Tested	$33.95

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

HELICAL RESONATOR PREAMPS

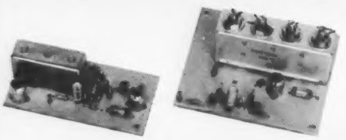

Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	$49.95
HRA-220	213-233 MHz	$49.95
HRA-432	420-450 MHz	$59.95

RECEIVING CONVERTERS

hamtronics RECEIVING CONVERTER
RCVR
PWR
ANT

Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	Antenna Input Range	Receiver Output
VHF MODELS	28-32	144-148
Kit $44.95	50-52	28-30
Less Case $39.95	50-54	144-148
Wired $59.95	144-146	28-30
	145-147	28-30
	144-144.4	27-27.4
	146-148	28-30
	144-148	50-54
	220-222	28-30
	220-224	144-148
	222-226	144-148
	220-224	50-54
	222-224	28-30
UHF MODELS	432-434	28-30
Kit $54.95	435-437	28-30
Less Case $49.95	432-436	144-148
Wired $74.95	432-436	50-54
	439.25	61.25

SCANNER CONVERTERS Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only $79.95.

SPECIAL FREQUENCY CONVERTERS made to custom order $119.95. Call for details.

SAVE A BUNDLE ON VHF FM TRANSCEIVERS!

FM-5 PC Board Kit – **ONLY $159.95**
complete with controls, heatsink, etc.
10 Watts, 5 Channels, for 6M, 2M, or 220

hamtronics
FM-5 TRANSCEIVER

Cabinet Kit, complete with speaker, knobs, connectors, hardware. Only $59.95

REPEAT OF A SELLOUT!

While supply lasts, get $59.95 cabinet kit free when you buy an FM-5 Transceiver kit. Where else can you get a complete transceiver for only $159.95?

TRANSMIT CONVERTERS

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 watts output.

	Exciter Input Range	Antenna Output
For VHF,	28-30	144-146
Model XV2	28-29	145-146
Kit $79.95	28-30	50-52
Wired $119.95	27-27.4	144-144.4
(Specify band)	28-30	220-222
	50-54	220-224
	144-146	50-52
	50-54	144-148
	144-146	28-30
For UHF,	28-30	432-434
Model XV4	28-30	435-437
Kit $99.95	50-54	432-436
Wired $149.95	61.25	439.25
	144-148	432-436*

*Add $35 for 2M input

FREE OFFER

For limited time, buy a transmit converter above with 40-45W PA ($129.95) and get $39.95 cabinet FREE.

hamtronics TRANSMITTING CONVERTER
PWR
RF IN
RF OUT

LOOK AT THESE ATTRACTIVE CURVES!

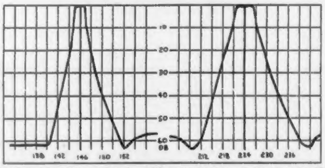

R144 & R220 Front Ends, HRA 144/220, & HRF-144/220

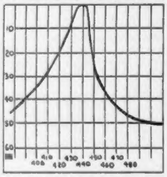

R451 Receiver Front End

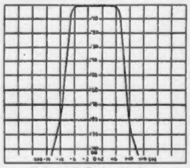

Rcvr I-F Selectivity

Typical Selectivity Curves of Receivers and Helical Resonators.

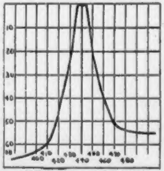

HRA-432, HRF-432

- Call or Write for FREE CATALOG
  (Send $1.00 or 4 IRC'c for overseas mailing)
- Order by phone or mail ● Add $2 S & H per order
  (Electronic answering service evenings & weekends)
  Use VISA, MASTERCARD, Check, or UPS COD.

hamtronics, inc.

65-W MOUL RD. • HILTON NY 14468
Phone: 716-392-9430

Hamtronics® is a registered trademark 33

AT LAST — A REPEATER YOU CAN AFFORD!

For years, Hamtronics ® Modules have been used by individual hams and manufacturers to make repeaters. Now, in the Hamtronics tradition of top quality and superb value, we are proud to offer a complete repeater package.

JUST LOOK AT THESE PRICES!

Band	Kit	Wired/Tested
6M,2M,220	$595	$745
440	$645	$795

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

CALL OR WRITE FOR COMPLETE DETAILS.

Also available for remote site linking/crossband & 10M.

FEATURES:

- SENSITIVITY SECOND TO NONE; TYPICALLY 0.15 uV ON VHF, 0.2 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY-TUNE TRANSMITTER; UP TO 20 WATTS OUT.

HIGH QUALITY MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.

INTRODUCING — NEW 1983 RECEIVERS

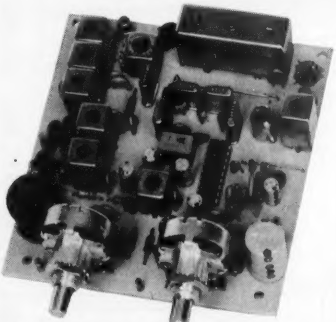

R144 Shown

- **R144/R220 FM RCVRS** for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity (curves at left). AFC incl., xtal oven avail. Kit only $119.95
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.2 uV sens. Kit only $119.95.
- **R76 FM RCVR** for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only $109.95. Also avail w/4 pole filter, only $94.95/ kit.
- **R110 VHF AM RECEIVER** kit for VHF aircraft band or ham bands. Only $84.95.
- **R110 UHF AM RECEIVER** for UHF uses, including special 296 MHz model to hear SPACE SHUTTLE. Kit $94.95.

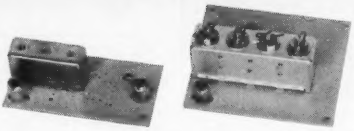

- **HELICAL RESONATOR FILTERS** available separately on pcb w/connectors.

HRF-144 for 143-150 MHz	$34.95
HRF-220 for 213-233 MHz	$34.95
HRF-432 for 420-450 MHz	$44.95

(See selectivity curves at left.)

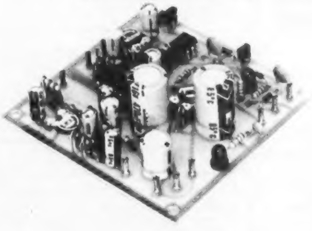

- **COR KITS** With audio mixer and speaker amplifier. Only $29.95.
- **CWID KITS** 158 bits, field programmable, clean audio. Only $59.95.

- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Only $18.00.

TRANSMITTERS AND ACCESSORIES

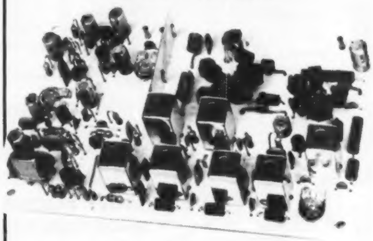

- **T51 VHF FM EXCITER** for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts continuous. Kits only $54.95

- **T451 UHF FM EXCITER** 2 to 3 Watts on 450 ham band or adjacent. Kits only $64.95.
- **VHF & UHF LINEAR AMPLIFIERS.** Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Kits from $69.95.

33

hamtronics ®

ANTENNA SPECIALISTS · AVANTI · ARRL PUBS · AMECO · BASH · BEARCAT · BENCHER · B&W · BIRD · CALLBOOK · COMMUNICATIONS SPECIALISTS · CUSHCRAFT · DRAKE · HAM KEY · HUSTLER · HY-GAIN · ICOM · KANTRONICS · LARSEN · MFJ · MORGAIN · PANASONIC · RAMSEY · SHURE · SONY · TELEX · TEN TEC · TRAC · TRANSCOM · VAN GORDON · VOCOM

HOLIDAY GIFT VALUES FROM SPECTRONICS!

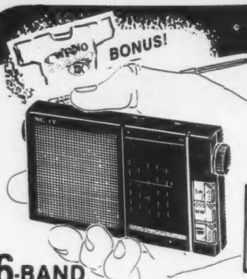

$89.95
plus $3.00 shipping (Cont'l U.S.)

6-BAND POCKET WORLD RECEIVER

- 6-band pocket world receiver—SW 1-5, plus MW
- Extremely compact and lightweight—palm sized!
- SW band spread dial-easy tuning • Tuning indicator

$8.50 VALUE!

FREE WRNO T-SHIRT with purchase of ICF-4800 Above. From WRNO — World's first commercial (3 Million Watts!) SW Radio station. Offer good thru December 31st, 1982.
SPECIFY SIZE (S,M,L, and XL)

"easy-talk'r" VOX PORTABLE TRANSCEIVER

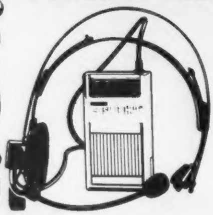

$49.95 ea.
plus $3.00 shipping

- Up to ½ mile FM Transmitting
- "Hands free" VOX operation
- Light weight—less than 9 Oz.

Valuable aid for Amateur use in antenna installation, tuning/pruning, field day, etc., plus hundreds of applications in home business, sports and recreation. Uses 9 volt battery (not supplied.)

BEARCAT BC-100 HAND-HELD PROGRAMMABLE SCANNER

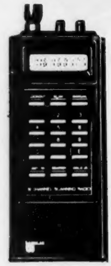

Reg. ~~$349.95~~

SALE **$299.95**
plus $3.00 shipping

- 8 Band, 16 Channel
- Auto Scan • Channel Lockout • "Now Take it With You Anywhere!"

ALEXANDER BP 4-W 500 MAH NICAD

$24.95 plus $2.00 shipping

Fits Wilson Mark II, and Mark IV plus Yaesu FT-207. 500 MAH, 11.7 V. Nickel-Cadmium.

AMECO PREAMPS

add $3.00 shipping (Cont'l USA only)

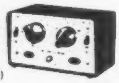

Model PLF-2	$52.95
Model PLF-2E (240V)	$57.95
Model PT-2	$79.95
Model PT-2E (240V)	$84.95

POPULAR HAMFEST SPECIALS!

VoCom POWER POCKET

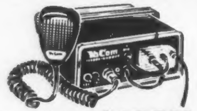

$199.95
plus $8.00 shipping (Cont'l USA)

Accepts any version of the IC-2A, applies its output to a wide-band rf amplifier, and delivers 25 watts to your mobile antenna. Mobile talk-out power!

SUB-AUDIBLE TONE HEADQUARTERS

ENCODERS **$29.95** EACH
plus $2.00 shipping (Cont'l USA only)

We stock **Communications Specialists** SS-32 and SS-32M encoders for most any mobile or hand-held applications including the very popular **Icom Handhelds.**

ICOM IC25A

NEW! IC3AT (220 MHz)
IC4AT (440 MHz)

ICOM IC2A, IC2AT

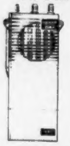

- Compact
- Quality Construction
- Versatile
- Affordable
- Wide Range of Accessories Available

CALL FOR PRICE & AVAILABILITY

SPECIAL PURCHASE FOR BIG HOLIDAY SAVINGS!

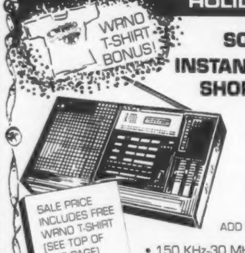

SALE PRICE INCLUDES FREE WRNO T-SHIRT (SEE TOP OF THIS PAGE) STATE SIZE WHEN ORDERING

SONY ICF-2001 INSTANT-ACCESS DIGITAL SHORTWAVE SCANNER

List ~~$349.95~~
Reg. ~~$289.95~~
Now Only **$259.95**

ADD $5.00 SHIPPING (CONT'L U.S.)

- 150 KHz-30 MHz + FM BROADCAST
- PLL SYNTHESIZED WITH SCANNING AND MEMORY • AC ADAPTOR • 1 YEAR FACTORY LIMITED WARRANTY • AM-CW-SSB

SPECIAL PURCHASE-LIMITED QUANTITIES

ANTENNA VALUE FAVORITES!

B&W PORTABLE APARTMENT ANTENNA

$39.50
plus $2.00 shipping

Quick, easy mounting. Tunes 2, 6, 10, 15, 20 and 40 meter Amateur bands, plus SW BC bands in some ranges. 360 watts SSB/CW. 22½" whip extends to 57". 14" mount. Includes 5 base-loading coils. Weighs less than 2 lbs.

AVANTI THRU-GLASS ANTENNA

$32.95 plus $3.00 shipping

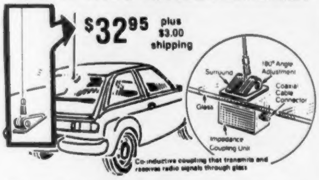

The Avanti On-Glass is the first two-way communications antenna that mounts on glass and transmits and receives through the glass. Extremely low VSWR is acheived by adjusting special tuning slug on matching network inside the vehicle. Can be easily removed for car washes without special tools.

TO ORDER: CALL OR WRITE. MASTER CARD, VISA, MONEY ORDERS, PERSONAL CHECKS TAKE 3 WEEKS TO CLEAR, ACCEPTED. **INTERNATIONAL ORDERS WELCOME,** PLEASE REQUEST PRO FORMA INVOICE. ILLINOIS RESIDENTS ADD 6% SALES TAX.

HOURS: MON. THRU WED. 9:30-6:00, THURS-FRI. 9:30-8:00, SAT. 9:30-3:00

STOP BY AND VISIT WHEN IN THE CHICAGOLAND AREA!!

SPECTRONICS, INC.
1009 GARFIELD ST. OAK PARK, IL. 60304

PHONE
(312)848-6777

2708,2716,2732 & 2764 EPROM Programmer

JE664 EPROM PROGRAMMER

8K TO 64K EPROMS — 24 AND 28 PIN PACKAGES

Self-Contained — Requires No Additional Systems for Operation

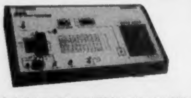

• Programs, validates, and checks for properly erased EPROMs • Emulates PROMs or EPROMs • RS232C Computer Interface for editing/program loading • Loads data into RAM by keyboard • Changes data in RAM by keyboard • Loads RAM from an EPROM • Compares EPROMs for content differences • Copies EPROMs • Power Input: 115VAC, 60Hz, ◄ 10W power consumption • Enclosure: Color-coordinated, light tan panels w/molded mocha brown end pieces • Size: 15-5/8"L x 8¾"D x 3½"H • Wt.: 5¾ lbs.

JE664-A EPROM Programmer **$995.00**
Assembled & Tested (Includes JM16A Module)

JE665 — RS232C INTERFACE OPTION — The JE665 RS232C Interface Option implements computer access to the JE664's RAM. Sample software written in BASIC provided for TRS-80® Model I, Level II Computer. Baud rate: 9600. Word Lgth: 8 bits - odd parity. Stop bits: 2. Option may be adapted to other computers.

JE664-ARS EPROM Prog. w/JE665 Option **$1195.00**
Assembled and Tested (Includes JM16A Module)

EPROM JUMPER MODULES — The JE664's JUMPER MODULE (Personality Module) is a plug-in Module that pre-sets JE664 for proper programming pulses to the EPROM & configures EPROM socket connections for that particular EPROM.

Part No.	EPROM	EPROM MANUFACTURER	PRICE
JM08A	2708	AMD, Motorola, National, Intel, TI	$14.95
JM16A	2716, TMS2516	Intel, Motorola, National, NEC, TI	$14.95
JM16B	TMS2716	Motorola, TI (+5,-12, +12)	$14.95
JM32A	TMS2532	Motorola, TI	$14.95
JM32B	2732	AMD, Fujitsu, NEC, Hitachi, Intel	$14.95
JM64A	MCM68764, MCM68L764	Motorola	$14.95
JM64B	2764	Intel	$14.95
JM64C	TMS2564	TI	$14.95

CONSUMER PRODUCTS

SECURITY ALARM SYSTEMS

Home Alarm System

• Self-Installation • Presettable w/individual 3-digit code — no key nec. • Instant or 10-sec. delayed warning system • Alarm system incl. window & door contacts • One 9V battery required (not incl.) Low power consumption (0.01mA) • Loud audible alarm (90db) • Delayed exit feature • System complete w/one control station with built-in siren and test button; 4 magnetic contact sets & connecting wires for entire system

ST-05 Home Alarm System **$59.95**

Door Security System

• Coded door alarm. • Instant or 7-second delay system. • Alarm activated as door is opened. • Can be de-activated by pressing personal code. • Power: One 9V battery (not incl.). • System includes one personal coded keyboard and one magnetic sensor.

ES-07 Door Alarm **$29.95**

Anti-Theft Auto Alarm System

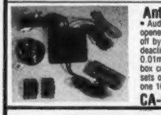

• Audible horn is activated when door or trunk is opened • Alarm sounds for 3 min. — unless turned off by secret 3-digit code. • Wire cutting will not deactivate alarm. • Code set by owner. • Uses only 0.01mA power. • System complete w/one black-box control unit; one personal coded keyboard; 2 sets of sensors; one audible horn; & wiring (incl. one 10A fuse).

CA-06 Auto Alarm **$59.95**

DIGITAL QUARTZ TIME PEN

• 5-Function: Hours, Minutes, Seconds, Month, Day • Liquid Crystal Display • 1/8" digits • Battery Included • Uses standard Parker ink refills • Ultra-slim design (5½" x ½")

77ILK	Black/Gold Trim	$9.95 each
77ISG	Stainless Steel/Gold Trim	$9.95 each
77ILR	Red/Gold Trim	$9.95 each

STICK-ON CLOCK

5-Function LCD Quartz Digital

• Hours • Minutes • Seconds • Month • Day • Flashing Colon • Ideal for car, kitchen, bathroom, office, etc. • 1/4" digits • Runs 2 years on 1 battery (incl.) • Size: 1-3/8" Round. Specify color: Red/ST-001R; White/ST-001W; Black/ST-001B

#ST-001____ (Specify letter) .... **$4.95 each or 2/$8.95**

Stereo Cassette Player

with FM Stereo Tuner Pack

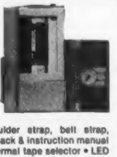

- **Lightweight Headphones**
- **Cr02/Metal/Normal Tape Selector**
- **Anti-Rolling Mechanism**

FEATURES: • Blue carrying case, shoulder strap, belt strap, lightweight headphones, FM stereo tuner pack & instruction manual • Talkline • Tone selector • Cr02/Metal/Normal tape selector • LED operation indicator • Built-in microphone • Stop/eject, play, rewind/review, fast forward/cue, tape/radio selector functions • Vol. control • Ext. power input jack • Headphone jack • Auto-stop mechanism (shuts off player when tape ends) • Anti-rolling mechanism (prevents sound from quivering when walking, jogging, etc.) • Weight: 13 oz. • Requires 4 AA batteries (not included) • Size: 6"L x 4"W x 1-1/8"H

Model TWF-802 .... **$69.95**
AM3-4 AA Alkaline Batteries .... **4/$3.95**

UTIC

Mini Stereo AM/FM Receiver

WITH HEADPHONES
For Joggers, Cyclists, Skaters & Sports Events

FEATURES: Lightweight headphones. Left/right balance control. Full fidelity stereo sound. Additional black soft carrying case and shoulder strap. Belt clip (hands free). Operates on 3 AA cell batteries (not incl. - see below). Compact size: 3-1/8"H x 4-7/8"L x 1"D. Wt. 6 oz.

Model 2830 .... **$29.95**
AM3-3 AA Alkaline Batteries .... **3/$2.95**

KEYBOARDS — POWER SUPPLIES

16⅞"L x 5¼"W x 1⅞"H

MICRO SWITCH 69-KEY KEYBOARD
Data Entry Keyboard, Encoded Output: 8-bit Parallel EBC DIC. Switching: Hall Effect, 24-pin Edge Card Connection. Complete w/Pin Connection. Can easily be modified to ASCII code.
Part No. KB69SD12-2 (Fits into DTE-20 Enclosure) .... **$19.95 each**

23"Lx5¾"Wx1-3/8"H

MICRO SWITCH 85-KEY KEYBOARD
Word Processing Keyboard, 26 Pin Edge Card Connection. Supply Voltage +5VDC. Main Keyboard is QWERTY. Additional Key Pads for Cursor and word processing functions.
Part No. 85SD18-1 .... **$29.95 each**

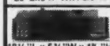

18¼"L x 5¾"W x 1⁹⁄₁₆"H

MICRO SWITCH 88-KEY KEYBOARD (PARALLEL)
Data Entry Keyboard used in a Diablo 1640 Terminal. Supply Voltage: +5V, -12V. Switching: Hall Effect — 10-pin Edge Card Connection. Schematic included. Uses 8048 Encoder Chip.
Part No. 88SD22 (Fits into DTE-20 Enclosure) .... **$69.95 each**

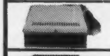

POWER SUPPLY +5VDC @ 1 AMP REGULATED *Transaction Tech*
Output +5VDC @ 1A (also +30VDC) reg. Input 115VAC 60Hz. 2-tone (black/beige) self-enclosed case. 6 ft., 3 cond. black power cord. 6½"W x 7"D x 2¾"H. Wt. 3 lbs. Data sheet incl.
Part No. PS51194 .... **$19.95 each**

POWER SUPPLY +5VDC @ 1 AMP REGULATED *B Industries*
Output +5VDC @ 1 amp, +36-42VDC adj. 400mA or less, 30VAC (isol.) @ 1.5 amp. Input 115VAC 60Hz. Circ. brkr. re-set button. Blk. self-encl. case w/4 rubber feet. 6 ft., 3 cond. blk. pow. cord. On/off switch. 6¾"W x 7¾"D x 3-7/8"H - wt. 7 lbs. Data sheet included.
Part No. PS407D .... **$24.95 each**

POWER SUPPLY +5VDC @ 3 AMP REGULATED *Deltron*
Input: 115VAC, 47-440Hz. Output: 5VDC Adjustable @ 3 amp, 6VDC @ 2.5 amp. Adjustable current limit, Ripple & Noise: 1MV rms, 5MV p-p — 2 mounting surfaces. UL recognized. Size: 4"W x 4½"L x 2-7/16"H - wt. 2 lbs. Data sheet included.
Part No. QPS-1 .... **$29.95 each**

MULTI-VOLTAGE POWER SUPPLY +5, +12, —12VDC REGULATED
Input: 105-125VAC, 47-63Hz / 205-250VAC, 47-63Hz. Output: +5VDC @ 2 amps Adj., 5VDC @ 50mA Fixed, +12VDC @ 1 amp Adj., —12V @ 2 amp adj. Overvoltage protection. Size: 12½"L x 4-7/8"W x 3¾"D. Data sheet included.
Part No. RA0250 .... **$39.95 each**

POWER SUPPLY +5VDC @ 7.5 AMP, 12VDC @ 1.5 AMP SWITCHING
Input: 115VAC, 50-60Hz @ 3 amp/230VAC, 50Hz @ 1.6 amp. Fan volt./power supply select switches (115/230VAC). Output: 5VDC @ 7.5 amp, 12VDC @ 1.5 amp. 8 ft. blk. pow. cord. 11⅛"W x 13¾"D x 3¾"H. Wt. 6 lbs.
Part No. PS94V0 .... **$49.95 each**

POWER SUPPLY 4-Channel Switching Power Supply
Microprocessor, mini-computer, terminal, medical equipment and process control applications. Input: 90-130VAC 47-440Hz. Output: +5VDC @ 5A, -5VDC @ 1A; +12VDC @ 1A, -12VDC @ 1A. Line reg.: ±0.2%. Ripple: 30mV p-p. Load reg.: ±1%. Overcurrent protection. Adj: 5V main output ±10%. 6-3/8"L x 1-7/8"W x 4-15/16"H. Wt. 1⅛ lbs.
Part No. FCS-604A .... **$69.95 each**

POWER SUPPLY Adjustable Switching 4-24VDC to 5 Amps
Adj. 4-24VDC; 5VDC @ 5A, 6VDC @ 4.8A, 9VDC @ 4.1A, 12VDC @ 3.3A, 18VDC @ 1.8A, 24VDC @ .5A. Overvoltage Protection. Input: 115VAC 50/60Hz. Output variations within 20mV. 8.25"L x 4.25"W x 2.25"H. Wt. 3.25 lbs.
JE224 Kit .... **$79.95 each**
JE224A Assembled & Tested .... **$99.95 each**

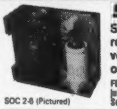

SOC 2-6 (Pictured)

SORENSEN Regulated Power Supplies

Sorensen's open construction (SOC) power supplies are series-regulated solid-state systems, designed to provide reg. DC voltages at 6 levels (2-28 v/range). These units are open-framed on sturdy black anodized aluminum for excellent mounting.

FEATURES: 115/208/230VAC Input @ 50-63Hz. Low Ripple: 1.5mVrms, 5mV P-P maximum. Adjustable current limit. Voltage adjustment control. All schematics and specifications supplied with unit. Series A,B,C,E have three mounting surfaces (Series F, bottom mounting only).

Part No.	Series	Output Voltage Adjustment Range		Output Current amps (Adc)			Size (Inches)	Weight	Price
		min.	max.	@40°C	@50°C	@60°C			
SOC 2-6	B	1.9	2.1	6.0	4.9	3.8	5.62 x 4.88 x 2.60	4.3 lbs.	$19.95
SOC 2-25	F	1.9	2.1	25.0	21.5	17.5	16.00 x 4.88 x 4.88	16 lbs.	29.95
SOC 5-18	E	4.25	5.25	18.0	15.0	12.0	14.00 x 4.88 x 2.75	12 lbs.	39.95
SOC 5-25	F	4.25	5.25	25.0	21.5	17.5	16.00 x 4.88 x 4.88	16 lbs.	49.95
SOC 12-11	E	11.4	12.6	11.0	9.2	6.8	14.00 x 4.88 x 1.62	12 lbs.	44.95
SOC15-5	C	14.25	15.75	5.0	4.2	3.5	7.00 x 4.88 x 3.37	6.6 lbs.	39.95
SOC 15-9.5	E	14.25	15.75	9.5	7.6	5.6	14.00 x 4.88 x 1.62	12 lbs.	44.95
SOC 15-13	F	14.25	15.75	13.0	10.5	8.5	16.00 x 4.88 x 4.88	16 lbs.	49.95
SOC 28-0.8	A	26.6	29.4	0.8	.64	.45	4.00 x 4.88 x 1.62	2 lbs.	34.95

BUG BOX™ — 30 individual compartments • Stores 60 8-pin or 30 14- or 16-pin DIPs • Heavy duty injection molded plastic • Clear plastic cover slides & locks • Cover marked w/numbers 1-30 • Compartment size: 1" x 3.75" x .5" deep • Box size: 4.9" x 3.3" x .6" • Weight: 1.75 oz.

BUG BOX™
Please specify color code: (B) Blue, (R) Red, (W) White, (Y) Yellow

Part No./Color Code	QTY	PRICE
BGX-001-( )	1	$ 2.29
BGX-010-( )	10	19.99
ANTI-STATIC		
BGX-001-( )AS	1	$ 3.29
BGX-010-( )AS	10	28.89

BUG CAGE™ — 12 locations store Bug Boxes, Big Bug Boxes or Bug Trays • Modular and interlocking • Heavy duty injection molded plastic • Each cage has 6 slip-on locations • 2 cages per pkg. • Cage size: 5-1/8" x 5" x 3-7/8" • 4 colors available — please specify color code: (B) Blue, (R) Red, (W) White, (Y) Yellow

Part No./Color Code	Price
BGC-001-( ) 2 Cages (6 loc. ea.)	$11.95/pkg.

BUG TRAY™ — Stores in Bug Cage • Molded plastic • Three styles: Open (1 compartment 3.05" x 4.6" x .6"); Vertical (5 compartments .5" x 4.6" x .6"); and Horizontal (8 compartments .4" x 3.95" x .6") • Ideal for tools, hardware, components, etc. • Tray size: 3.55" x 5.05" x .6" • Black color only

PART NO.	DESCRIPTION	PRICE
BTH-001	Horizontal Bug Tray	$1.95
BTV-001	Vertical Bug Tray	1.95
BTO-001	Open Bug Tray	1.95
BTX-003	1 of each Bug Tray (3)	4.95

BUG BOX™ STORAGE SYSTEMS

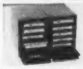

BUG CAGE™ (BGC-001-____) with Bug Boxes

LSI BIG BUG BOX™ — Designed to store large IC's, Resistors, Capacitors and Diodes • Divided into three compartments measuring 1" x 4.15" x .5" deep • Three vertical and three horizontal dividers included • Heavy duty injection molded plastic • Box size: 4.9" x 3.3" x .6" • Weight: 1.75 oz.

LSI BIG BUG BOX™
Please specify color code: (B) Blue, (R) Red, (W) White, (Y) Yellow

PART NO./COLOR CODE	QTY	PRICE
BLX-001-( )	1	$ 3.29
BLX-010-( )	10	26.79
ANTI-STATIC		
BLX-001-( )AS	1	$ 4.29
BLX-010-( )AS	10	37.89

BACK PACK™ — Self-adhesive labels for the back of ICs • Shows exact internal logic in relation to IC pins • 532 labels in each package (including several blank labels) • Each package for 8, 14, 16, 24, 28 and 40-pin ICs • Combo package includes 1,068 labels for TTL and CMOS ICs • Microprocessor package contains 744 labels

Part No.	Description	Price
BPT-012	TTL	$7.95
BPC-012	CMOS	8.95
BPM-012	Combo	14.95
BPU-012	Microprocessor	9.95

Custom Jumpers!

JUMPER AND CABLE ASSEMBLIES

Custom Cables!

STANDARD DIP JUMPERS

All jumpers use low profile dip plugs with heavy duty pins for repeated disconnect applications.

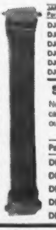

JAMECO Part No.	AP Cross-Reference	No. Pins	Description	Wire Length	Price
DJ14-1	924102-12	14	single end	12"	$1.79
DJ14-2	924102-24	14	single end	24"	2.05
DJ14-3	924102-36	14	single end	36"	2.35
DJ14-1-14	924106-12	14	double end	12"	2.95
DJ14-2-14	924106-24	14	double end	24"	3.19
DJ14-3-14	924106-36	14	double end	36"	3.49
DJ16-1	924112-12	16	single end	12"	1.89
DJ16-2	924112-24	16	single end	24"	2.19
DJ16-3	924112-36	16	single end	36"	2.59
DJ16-1-16	924116-12	16	double end	12"	2.95
DJ16-2-16	924116-24	16	double end	24"	3.29
DJ16-3-16	924116-36	16	double end	36"	3.59
DJ24-1	924122-12	24	single end	12"	2.69
DJ24-2	924122-24	24	single end	24"	3.19
DJ24-3	924122-36	24	single end	36"	3.59
DJ24-1-24	924126-12	24	double end	12"	4.49
DJ24-2-24	924126-24	24	double end	24"	4.95
DJ24-3-24	924126-36	24	double end	36"	5.39

JAMECO Part No.	AP Cross-Reference	No. Pins	Description	Wire Length	Price
DJ40-1	924132-12	40	single end	12"	5.39
DJ40-2	924132-24	40	single end	24"	6.19
DJ40-3	924132-36	40	single end	36"	6.89
DJ40-1-40	924136-12	40	double end	12"	9.49
DJ40-2-40	924136-24	40	double end	24"	10.29
DJ40-3-40	924136-36	40	double end	36"	10.95

STANDARD DB25 SERIES CABLES

Now you can order DB25 P or S connectors with the cable necessary to fit your application. Choose from our standard flat cable in 4-foot lengths. **Call today.**

STANDARD CABLES

Part No.	Cable Length	Connectors	Price
DB25P-4	4 feet	1-DB25P	$7.95
DB25S-4	4 feet	1-DB25S	8.49
DB25P-4-P	4 feet	2-DB25P	13.49
DB25P-4-S	4 feet	1-DB25P/1-DB25S	13.75
DB25S-4-S	4 feet	2-DB25S	13.95

$10.00 Minimum Order — U.S. Funds Only
California Residents Add 6½% Sales Tax
Postage — Add 5% plus $1.50 Insurance
Send S.A.S.E. for Monthly Sales Flyer!

Spec Sheets — 30¢ each
Send $1.00 Postage for your
FREE 1983 JAMECO CATALOG
Prices Subject to Change

Call for Quantity Discounts

Mail Order Electronics · Worldwide

Jameco® ELECTRONICS

NEW! Telex Number Telex 176043

1355 SHOREWAY ROAD, BELMONT, CA 94002
PHONE ORDERS WELCOME — (415) 592-8097

12/82 ✓38

5¼" Mini-Floppy Disc Drive

FOR TRS-80 MODEL I (Industry Standard)

Pertec Computer Corp.

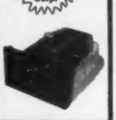

Features single or double density. Recording mode: FM single, MFM double density. Power: +12VDC (±0.6V) 1.6 amps max., +5VDC (±0.25V) 0.8 amps max. Unit as pictured at left (does not incl. case, power supply or cables). 30-page data book included. Weighs 3½ pounds. Size: 5¾"W x 8"D x 3¼"H

Limited Quantity!

Part No.	Price
FD200	**$179.95**
Single-sided, 40 tracks, 250K bytes capacity	
FD250	**$199.95**
Double-sided, 35 tracks, 438K bytes capacity	

EXPAND YOUR TRS-80

to 16K, 32K, or 48K

**Model 1 = From 4K to 16K Requires (1) One Kit
Model 3 = From 4K to 48K Requires (3) Three Kits
Color = From 4K to 16K Requires (1) One Kit

**Model 1 equipped with Expansion Board up to 48K Two Kits Required — One Kit Required for each 16K of Expansion —

TRS-80 16K Conversion Kit

Kit comes complete with 8 each MM5290 (UPD416/4116) 16K Dynamic RAM (*ns) and documentation for conversion.

TRS-16K2 *150ns	**$14.95**
TRS-16K3 *200ns	**$12.95**
TRS-16K4 *250ns	**$10.95**

TRS-80 Color 32K or 64K Conversion Kit

Kit comes complete with 8 ea. 4164-2 (200ns). 64K Dyn. RAMs & conversion documentation. Converts TRS-80 color computers from 4K-32K Memory or 16K-64K Memory.

TRS-64K2 (200ns) **$54.95**

Universal Computer Keyboard Enclosure

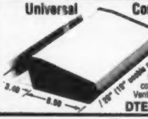

"DTE" Blank Desk-Top Enclosures are designed for easy modification. High strength epoxy molded end pieces in mocha brown finish. Sliding rear/bottom panel for service/component access. Top/bott. panels .080" thick alum. alodine type 1200 finish (gold tint color) for best paint adhesion after modification. Vented top & bottom panels for cooling efficiency.

DTE-20 Panel width 20" **$34.95**

Sprite-style Fan

- 36cfm free air delivery
- 3.125" sq. x 1.665" depth
- 10 yrs. cont. duty at 20°C
- 115V 50/60Hz
- For Apple users

*Metal Frame

PWS2107U Cleaned & tested (used) .... **$ 9.95 ea.**
***PWS2107F** New .... **$14.95 ea.**

Muffin-style Fan

- 105cfm free air delivery
- 4.68" sq. x 1.50" depth.
- 10 yrs. cont. duty at 20°C
- Impedance protected, ambients to 70°C
- 115V 50/60Hz 14W Wt. 17 oz.

*Metal Frame

MU2A1-U Cleaned & tested (used) .... **$9.95 ea.**
***MU2A-1N** New .... **$14.95 ea.**

JOYSTICKS

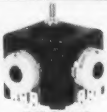

JS-5K (Pictured)

JS-5K	5K Linear Taper Pots	$5.25
JS-100K	100K Linear Taper Pots	$4.95
JS-150K	150K Linear Taper Pots	$4.75
JVC-40	40K (2) Video Controller in Case	$4.95

UV-EPROM Eraser

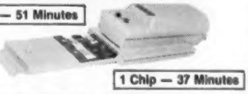

Erases 2708, 2716, 2732, 2764, 2516, 2532, 2564. Erases up to 8 chips within 51 minutes (1 chip in 37 minutes). Maintains constant exposure distance of one inch. Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact — only 9.00" x 3.70" x 2.80". Complete with holding tray for 8 chips.

UVS-11EL Replacement Bulb **$16.95**

DE-4 UV-EPROM Eraser **$79.95**

Wall Transformers AC and DC Types

AC250 (Pictured)

Part No.	Input	Output	Price
AC 250 (above)	117V/60Hz	12VAC 250mA	$3.95
AC 500	117V/60Hz	12VAC 500mA	$4.95
AC1000	117V/60Hz	12VAC 1 amp	$5.95
AC9004	117V/60Hz	9.2VAC 2.5 amp	$3.95
DC 800	120V/60Hz	8VDC 400mA	$1.95
DC6912	120V/60Hz	6,9,12VDC 300mA	$6.95
DC5490	117V/60Hz	9.5VDC 275mA	$2.95
DC900	120V/60Hz	9VDC 500mA	$3.95
DC1200	120V/60Hz	12VDC 300mA	$2.95
DV9200	117V/60Hz	9VAC 200mA	$3.25

Siemens 8" Floppy Disk Drive

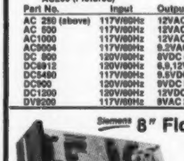

- Single-Sided
- 77 Tracks
- 400/800K Bytes Capacity
- Industry Standard

The **FDD100-8 8" Floppy Disk Drive** (Industry Standard) features single or double density. Recording mode: FM single, MFM double density. Transfer rate: 250K bits/sec. single density; 500K bits/sec. double density. The FDD100-8 is designed to work with the single-sided soft sectored IBM Diskette I, or eq. disk cartridge. Hard-sectored option available. Power: 115/230VAC @ 50-60Hz, +24VDC @ 1.7 amps max., +5VDC @ 1.2 amps max. Unit as pictured above (does not include case, power supply, or cables). Size: 8.55"W x 14"L x 4.5"H. Weighs 12 lbs. incl. 90-pg. manual.

Part No.		Price
FDD100-8	Buy 1 for	$269.95 each
FDD100-8	Buy 2 for	$259.95 each
FDD100-8	*Buy 10 for*	*$249.95 each*

RAMSEY ELECTRONIC'S Inc.

62

PARTS WAREHOUSE

We now have available a bunch of goodies too good to bypass. Items are limited so order today

2575 Baird Rd.
Penfield, NY 14526
716-586-3950

Call Your Phone Order in Today

TERMS: Satisfaction guaranteed or money refunded. C.O.D. add $2.00. Minimum order $6.00. Orders under $10.00 add $1.50. Add 5% for postage, insurance, handling. Overseas add 15%. N.Y. residents add 7% tax.

your BANKAMERICARD welcome

MINI KITS - YOU HAVE SEEN THESE BEFORE NOW HERE ARE OLD FAVORITE AND NEW ONES TOO. GREAT FOR THAT AFTERNOON HOBBY.

FM MINI MIKE

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.

FM-3 Kit	$14.95
FM-3 Wired and Tested	19.95

Color Organ

See music come alive! 3 different lights flicker with music. One light each for, high, mid-range and lows. Each individually adjustable and drives up to 300 W. runs on 110 VAC.

Complete kit, ML-1
$8.95

Video Modulator Kit

Converts any TV to video monitor. Super stable, tunable over ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market! Complete kit, VD-1 **$7.95**

Led Blinky Kit

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts.
Complete kit, BL-1
$2.95

Super Sleuth

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker.
Complete kit, BN-9 **$5.95**

CPO-1

Runs on 3-12 Vdc 1 wall out, 1 KHZ good for CPO, Alarm, Audio Oscillator. Complete kit **$2.95**

FM Wireless Mike Kit

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage.

FM-1 kit **$3.95** FM-2 kit **$4.95**

Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC.
Complete kit, WL-1
$6.95

Tone Decoder

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts.
Complete kit, TD-1 **$5.95**

Universal Timer Kit

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs.

UT-5 Kit **$5.95**

Mad Blaster Kit

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio. Runs on 6-15 VDC

MB-1 Kit **$4.95**

Siren Kit

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker.
Complete kit, SM-3 **$2.95**

60 Hz Time Base

Runs on 5-15 VDC. Low current (2.5ma) 1 min/month accuracy TB-7 Kit **$5.50**
TB-7 Assy **$9.95**

CLOCK KITS

Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!

Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify).

Clock kit, 12/24 hour, DC-5	**$24.95**
Clock with 10 min. ID timer, 12/24 hour, DC-10	**$29.95**
Alarm clock, 12 hour only, DC-8	**$29.95**
12V DC car clock, DC-7	**$29.95**

For wired and tested clocks add $10.00 to kit price.
SPECIFY 12 OR 24 HOUR FORMAT

Car Clock

The UN-KIT, only 5 solder connections

Here's a super looking, rugged and accurate auto clock, which is a snap to build and install. Clock movement is completely assembled — you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell — assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify).

DC-3 kit, 12 hour format	**$22.95**
DC-3 wired and tested	**$29.95**

Calendar Alarm Clock

The clock that's got it all: 6-.5" LEDs, 12/24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size: 5x4x2 inches. Complete kit, less case (not available)
DC-9 **$34.95**

Under Dash Car Clock

12/24 hour clock in a beautiful plastic case features 6 jumbo RED LEDS, high accuracy (.001%), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer atuomatically adjusts display to ambient light level.

DC-11 clock with mtg. bracket	**$27.95 kit**
DM-1 dimmer adapter	**$2.50**

Add $10.00 Assy. and Test

Video Terminal

A completely self-contained, stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Features are: single 5V supply, XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor. Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 6416 is 64 char. by 16 lines with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.

RE 6416, terminal card kit (add $60.00 for wired unit)	**$189.95**
Lower Case option	**$13.95**
Power Supply	**$14.95**
RF Modulator kit	**$7.95**

PARTS PARADE

IC SPECIALS

LINEAR

301	$ .35
324	$1.50
380	$1.50
555	$ .45
556	$1.00
565	$1.00
566	$1.00
567	$1.25
741	10/$2.00
1458	$ .50
3900	$ .50
3914	$2.95
8038	$2.95

TTL

74S00	$ .40
7447	$ .65
7475	$ .50
7490	$ .50
74196	$1.35

SPECIAL

11C90	$15.00
10116	$ 1.25
7208	$17.50
7207A	$ 5.50
7216D	$21.00
7107C	$12.50
5314	$ 2.95
5375AB/G	$ 2.95
7001	$ 6.50

CMOS

4011	.50
4013	.50
4046	$1.85
4049	.50
4059	$9.00
4511	$2.00
4518	$1.35
5639	$1.75

FERRITE BEADS

With info and specs	15/$1.00
6 Hole Balun Beads	5/$1.00

READOUTS

FND 359 .4" C.C.	$1.00
FND 507/510 .5" C.A.	1.00
MAN 72/HP7730 .33" C.A.	1.00
HP 7651 .43" C.A.	2.00

Sockets

8 Pin	10/$2.00
14 Pin	10/$2.00
16 Pin	10/$2.00
24 Pin	4/$2.00
28 Pin	4/$2.00
40 Pin	3/$2.00

TRANSISTORS

2N3904 NPN C+F	15/$1.00
2N3906 PNP C+F	15/$1.00
2N4403 PNP C+F	15/$1.00
2N4410 NPN C+F	15/$1.00
2N4916 FET C+F	4/$1.00
2N5401 PNP C+F	5/$1.00
2N6028 C+F	4/$1.00
2N3771 NPN Silicon	$1.50
2N5179 UHF NPN	3/$2.00
Power Tab NPN 40W	3/$1.00
Power Tab PNP 40W	3/1.00
MPF 102/2N5484	$.50
NPN 3904 Type T+R	50/$2.50
PNP 3906 Type T+R	50/$2.50
2N3055	$.60
2N2646 UJT	3/$2.00

Diodes

5.1 V Zener	20/$1.00
1N914 Type	50/$1.00
1KV 2Amp	8/$1.00
100V 1Amp	15/$1.00

25 AMP
100V Bridge
$1.50 each

Mini-Bridge 50V
1 AMP
2 for $1.00

Resistor Ass't

Assortment of Popular values - ¼ watt. Cut lead for PC mounting, ½" center, ½" leads, bag of 300 or more. **$1.50**

Crystals

3.579545 MHZ	$1.50
10.00000 MHZ	$5.00
5.248800 MHZ	$5.00

Switches

Mini toggle SPDT	$1.00
Red Pushbuttons N.O.	3/$1.00

AC Adapters

Good for clocks, nicad chargers, all 110 VAC plug one end

8.5 vdc @ 20 mA	$1.00
16. vac @ 160mA	$2.50
12. vac @ 250mA	$3.00

Earphones

3" leads, 8 ohm, good for small tone speakers, alarm clocks, etc.
5 for $1.00

Mini 8 ohm Speaker

Approx. 2¼" diam. Round type for radios, mike etc.
3 for $2.00

Solid State Buzzers

small buzzer 450 Hz, 86 dB, sound output on 5-12 vdc at 10-30 mA, TTL compatible. **$1.50**

Slug Tuned Coils

Small 3/16" Hex Slugs turned coil, 3 turns. 10 for $1.00

AC Outlet

Panel Mount with Leads
4/$1.00

CAPACITORS

TANTALUM Dipped Epoxy		ALUMINUM Electrolytic		DISK CERAMIC	
1.5 uF 25V	3/$1.00	1000 uF 16V Radial	$.50	.01 16V disk	20/$1.00
1.8 uF 25V	3/$1.00	500 uF 20V Axial	$.50	.1 16V	15/$1.00
.22 uF 25V	3/$1.00	150 uF 16V Axial	5/$1.00	.001 16V	20/$1.00
		10 uF 15V Radial	10/$1.00	100 pF	20/$1.00
				.047 16V	20/$1.00

DC-DC Converter

+5 vdc input prod. -9 vdc @ 30ma
+9 vdc produces -15 vdc @ 35ma **$1.25**

Ceramic IF Filters

Mini ceramic filters 7 kHz B.W. 455 kHz $1.50 ea.

25K 20 Turn Trim Pot	$1.00
1K 20 Turn Trim Pot	$ .50

Trimmer Caps

Sprague - 3-40 pf
Stable Polypropylene
.50 ea.

Crystal Microphone

Small 1" diameter ¼" thick crystal mike cartridge **$.75**

Mini RG-174 Coax
10 ft. for $1.00

Coax Connector

Chassis mount
BNC type **$1.00**

9 Volt Battery Clips

Nice quality clips	5 for $1.00
⅜" Rubber Grommets	10 for $1.00

Parts Bag

Asst. of chokes, disc. caps, tant., resistors, transistors, diodes, MICA caps etc.
sm. bag (100 pc) **$1.00** lg. bag (300 pc) **$2.50**

Connectors

6 pin type gold contacts for mA-1003 car clock module price **.75 ea.**

Leds - your choice, please specify

Mini Red, Jumbo Red, High Intensity Red, Illuminator Red	**8/$1**
Mini Yellow, Jumbo Yellow, Jumbo Green	**6/$1**

Varactors

Motorola MV 2209 30 PF Nominal cap 20-80 PF - Tunable range - **.50 each or 3/$1.00**

Audio Prescaler

Make high resolution audio measurments, great for musical instrument tuning, PL tones, etc. Multiplies audio UP in frequency, selectable x10 or x100, gives .01 HZ resolution with 1 sec. gate time! High sensitivity of 25 mv, 1 meg input z and built-in filtering gives great performance. Runs on 9V battery, all CMOS.

PS-2 kit	**$29.95**
PS-2 wired	**$39.95**

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. specify -10 or -100

Wired, tested, PS-1B	**$59.95**
Kit, PS-1B	**$44.95**

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 W in for 15 out, 4W in for 30 out. Max output of 35 W, incredible value, complete with all parts, less case and T-R relay.

PA-1, 30 W pwr amp kit	**$22.95**
TR-1, RF sensed T-R relay kit	**6.95**

MRF-238 transistor as used in PA-1
8-10db gain 150 mhz **$11.95**

RF actuated relay senses RF (1W) and closes DPDT relay.
For RF sensed T-R relay
TR-1 Kit **$6.95**

Power Supply Kit

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and +5 at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3 V @ 1 A and 24 VCT.
Complete kit, PS-3LT **$6.95**

OP-AMP Special

BI-FET LF 13741 - Direct pin for pin 741 compatible, but 500,000 MEG input z, super low 50 pa input current, low power drain.

50 for only $9.00 **10 for $2.00**

Regulators

78MG	$1.25	7812	$1.00
79MG	$1.25	7815	$1.00
723	$.50	7905	$1.25
309K	$1.15	7912	$1.25
7805	$1.00	7915	$1.25

Shrink Tubing Nubs

Nice precut pces of shrink size: 1" x ⅛" shrink to ⅛". Great for splices. **50/$1.00**

Mini TO-92 Heat Sinks

Thermalloy Brand	5 for $1.00
To-220 Heat Sinks	3 for $1.00

Opto Isolators - 4N28 type	**$.50 ea.**
Opto Reflectors - Photo diode + LED	**$1.00 ea.**

Molex Pins

Molex already precut in length of 7. Perfect for 14 pin sockets. **20 strips for $1.00**

CDS Photocells

Resistance varies with light, 250 ohms to over 3 meg **3 for $1.00**

PROPAGATION

J. H. Nelson
4 Plymouth Dr.
Whiting NJ 08759

EASTERN UNITED STATES TO:

GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	7A	7	3A	3A	3A	7	7	14	14	21	21A
ARGENTINA	14	7	7B	7B	7B	7	14	14	21A	21A	21	21
AUSTRALIA	21	14	7B	7B	7B	7B	7B	14B	14A	21	21	21A
CANAL ZONE	7	7	7	7	7	7	7A	14	21	21A	21	14
ENGLAND	7	7	7	3A	7	7B	14	14A	21A	14A	7A	7
HAWAII	21	7A	7B	7	7	7	7	7B	14	14A	21	21A
INDIA	7B	7B	7B	7B	7B	7B	14	14A	14	7B	7B	7B
JAPAN	14A	14B	7B	7B	7	7	7	7B	7B	7B	14B	14
MEXICO	14	7	7	7	7	7	7	14	14A	21A	21A	21
PHILIPPINES	14A	7B	7B	7B	7B	7B	7B	7B	14B	14B	14B	14
PUERTO RICO	7A	7	7	7	7	7	7A	14A	21A	21A	21	14
SOUTH AFRICA	7A	7B	7B	7B	7B	7A	14	21	21A	21A	21	14A
U. S. S. R.	7	7	3A	3A	7B	7B	14	21A	14A	14	7B	7
WEST COAST	14A	7A	7	7	7	7	7	14	21	21A	21A	21

CENTRAL UNITED STATES TO:

GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14A	7	7	3A	3A	3A	7	7	7A	14	21	21A
ARGENTINA	14	14	7	7B	7B	7	7A	14	21	21A	21A	21
AUSTRALIA	21	14	7B	7B	7B	7B	7B	7B	14	14	21A	21A
CANAL ZONE	14	7	7	7	7	7	7	14	21	21A	21A	14
ENGLAND	7	7	7	3A	7	7	7B	14	21A	14	7B	7B
HAWAII	21A	7	7	7	7	7	7	7	14	21	21A	21A
INDIA	7B	7B	7B	7B	7B	7B	7B	14B	14B	7B	7B	7B
JAPAN	21A	14	7B	7B	7B	7	7	7	7B	7B	14	21
MEXICO	14	7	7	7	7	7	7	14	14A	21A	21A	21
PHILIPPINES	21	14	7B	7B	7B	7B	7B	7	7B	7B	14B	14
PUERTO RICO	14	7	7	7	7	7	7	14	14A	21A	21A	14A
SOUTH AFRICA	7	7B	7B	7B	7B	7B	7	14	21A	21A	21	14
U. S. S. R.	7B	7	3A	3A	7	7B	7B	14A	14A	14B	7B	7B

WESTERN UNITED STATES TO:

GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	21A	7A	7	3A	3A	3A	3A	3A	7	14	21	21
ARGENTINA	21A	14	7	7B	7B	7B	7B	14	21	21	21A	21A
AUSTRALIA	21A	14	7A	7	7B	7B	7B	7B	14	14	21	21A
CANAL ZONE	21	14	7	7	7	7	7	14	14	21A	21A	21
ENGLAND	7B	7	7	3A	7	7	7B	14B	21	14A	14B	7B
HAWAII	21A	14	14	7	7	7	7	7	14	21	21A	21A
INDIA	7B	14	7B	7B	7B	7B	7B	7B	7A	7B	7B	7B
JAPAN	21A	14	7B	7B	7	7	7	7	7	7B	14	21
MEXICO	21	14	7	7	7	7	7	7A	14	21A	21A	21
PHILIPPINES	21A	14	7B	7B	7B	7B	7B	7B	7B	14	14	14
PUERTO RICO	21	7	7	7	7	7	7	14	21	21A	21A	21
SOUTH AFRICA	7	7B	7B	7B	7B	7B	7B	14	21	21A	21	14
U. S. S. R.	7B	7B	3B	3B	7B	7B	7B	7B	14	14B	7B	7B
EAST COAST	14A	7A	7	7	7	7	7	14	21	21A	21A	21

A = Next higher frequency may also be useful.
B = Difficult circuit this period.

First letter = night waves. Second = day waves.
G = Good, F = Fair, P = Poor. * = Chance of solar flares.
# = Chance of aurora.

NOTE THAT NIGHT WAVE LETTER NOW COMES FIRST.

DECEMBER

SUN	MON	TUE	WED	THU	FRI	SAT
			1 F/F*	2 F/F	3 F/G	4 F/G
5 G/G	6 G/G	7 G/G	8 G/G	9 G/G	10 G/G	11 F/G
12 G/G	13 G/G	14 G/G	15 G/G	16 G/G	17 F/F	18 F/F*
19 P/P*	20 P/F*	21 P/F	22 P/F	23 F/G	24 F/G	25 F/G
26 F/F	27 F/F	28 F/F	29 F/F	30 F/G	31 F/G	

DEALER DIRECTORY

Culver City CA

Jun's Electronics, 3919 Sepulveda Blvd., Culver City CA 90230, 390-8003. Trades 463-1886 San Diego. 827-5732 (Reno NV).

Fontana CA

Complete lines ICOM, DenTron, Ten-Tec, Mirage, Cubic, Lunar, over 4000 electronic products for hobbyist, technician, experimenter. Also CB radio, landmobile. **Fontana Electronics, 8628 Sierra Ave., Fontana CA 92335, 822-7710.**

San Diego CA

We buy and sell Surplus Army Navy Electronics, also Terminated Material. What do you want to sell? Write for catalogue. **Electronictown, Inc., 440-7th Avenue, PO Box 2048, San Diego CA 92112, 232-9379.**

New Castle DE

Factory Authorized Dealer! Yaesu, ICOM, Ten-Tec, KDK, Azden, AEA, Kantronics, Santec. Full Line of Accessories. No Sales Tax in Delaware. One mile off I-95. **Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 328-7728.**

San Jose CA

Bay area's newest Amateur Radio store. New & used Amateur Radio sales & service. We feature Kenwood, ICOM, Azden, Yaesu, Ten-Tec, Santee & many more. **Shaver Radio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.**

Smyrna GA

For your Kenwood, Yaesu, ICOM, Drake and other amateur needs, come to see us. **Britt's Two-Way Radio, 2506 N. Atlanta Rd., Smyrna GA 30080, 432-8006.**

Preston ID

Ross WB7BYZ has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham needs. **Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.**

Terre Haute IN

Your ham headquarters located in the heart of the midwest. **Hoosier Electronics, Inc., #9 Meadows Center, P.O. Box 3300, Terre Haute IN 478003, 238-1456.**

Baltimore MD

Always buying lab grade test equipment HP, Tek, Gr, L&N, Etc. Also buy microwave coaxial & waveguide HP, fxr, waveline, etc. Prefer "K", "P", "R" but will consider larger wg too. **Cadisco 514 Ensor St., Balto, MD 21202, 685-1893.**

Littleton MA

The Reliable Ham Store Serving N.E. Full line of ICOM & Kenwood. Yaesu HTs, Drake, Daiwa, B&W accessories. Curtis & Trac keyers. Larsen, Hustler, Telex/Hy-Gain products. Mirage amps., Astron P.S., Alpha Delta protectors, ARRL & Kantronics instruction aids. Whistler radar detectors. Full line of coax fittings. **TEL-COM Electronic Communications 675 Great Rd. (Rt. 119), Littleton MA 01460, 617-486-3400/3040.**

Ann Arbor MI

See us for products like Ten-Tec, R. L. Drake, DenTron and many more. Open Monday through Saturday, 0830 to 1730. WB8VGR, WB8UXO, WD8OKN and W8RP behind the counter. **Purchase Radio Supply, 327 E. Hoover Ave., Ann Arbor MI 48104, 668-8696.**

Hudson NH

New England's Distributor and Authorized Service Center for all Major Amateur Lines. **Tufts Radio Electronics, Inc., 61 Lowell Road, Hudson NH 03051, 883-5005.**

Somerset NJ

New Jersey's only factory-authorized ICOM and Yaesu distributor. Large inventory of new and used specials. Most major brands in stock. Complete service and facilities. **Radios Unlimited, 1760 Easton Avenue, P.O. Box 347, Somerset NJ 08873, 469-4599.**

Buffalo NY
WESTERN NEW YORK

Niagara Frontier's only full stocking Amateur dealer. Also Shortwave, CB, Scanners, Marine, Commercial. Operating displays featuring Kenwood and others. Towers, Antennas, Sales and Service. **DX Communications, 3214 Transit Road, West Seneca NY, 668-8873.**

Amsterdam NY
UPSTATE NEW YORK

Kenwood, ICOM, Drake, plus many other lines, Amateur Dealer for over 35 years. **Adirondack Radio Supply, Inc., 185 West Main Street, Amsterdam NY 12010, 842-8350.**

Syracuse-Rome-Utica NY

Featuring: Kenwood, Yaesu, ICOM, Drake, Ten-Tec, Swan, DenTron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy-Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products. You won't be disappointed with equipment/service. **Radio World, Oneida County Airport-Terminal Building, Oriskany NY 13424, 736-0184.**

Columbus OH

The biggest and best Ham Store in the midwest featuring quality Kenwood products with working displays. We sell only the best. Authorized Kenwood Service. **Universal Amateur Radio Inc., 1280 Aida Dr., Reynoldsburg (Columbus) OH 43068, 866-4267.**

Bend OR

Satellite TV. Known brands. Call today for more information and inquire about our dealer program. **WESPERCOM, P.O. Box 7226, Bend OR 97708, 389-0996.**

Philadelphia PA/ Camden NJ

Waveguide & Coaxial Microwave Components & Equipment. Laboratory Grade Test Instruments, Power Supplies, Buy, Sell & Trade all popular makes—HP, GR, FXR, ESI, Sorensen, Singer, etc. **Lectronic Research Labs, 1423 Ferry Ave., Camden NJ 08104, 541-4200.**

Scranton PA

ICOM, Bird, Cushcraft, Beckman, Fluke, Larsen, Hustler, Antenna Specialists, Astron, Avanti, Belden, W2AU/W2VS, CDE, AEA, Vibroplex, Ham-Key, CES, Amphenol, Sony, Fanon/Courier, B&W, Ameco, Shure. **LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.**

San Antonio TX

Amateur, Commercial 2-way. Selling Antenna Specialists, Avanti, Azden, Bird, Hy-Gain, Standard, Vibroplex, Midland, Henry, Cushcraft, Dielectric, Hustler, ICOM, MFJ, Nye, Shure, Cubic, Tempo, Ten-Tec and others. **Appliance & Equipment Co., Inc. 2317 Vance Jackson Road, San Antonio TX 78213, 734-7793.**

DEALERS

Your company name and message can contain up to 25 words for as little as $150 yearly (prepaid), or $15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the Feb. '83 issue must be in our hands by Dec. 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

World Class Performance and Features

The FT-ONE is the culmination of an all-out design project by Yaesu's top engineering team. Working without the usual cost constraints, Yaesu's design group is proud to unveil the instrument they "always wanted to design," a revolutionary blend of computer and RF technology.

GENERAL COVERAGE, ALL SOLID STATE

The FT-ONE is a full-coverage all-mode transceiver, equipped for reception on any frequency between 150 kHz and 29.99 MHz, with transmit coverage on all nine present and proposed amateur bands. In countries where permitted, the FT-ONE may be programmed to transmit throughout the 1.8-29.99 MHz range.

KEYBOARD FREQUENCY ENTRY

Fully digitally synthesized, the FT-ONE uses a front panel keyboard for initial frequency entry. Frequency change is then accomplished via the main tuning dial or the pushbutton scanner, with tuning in either 10 Hz or 100 Hz steps possible. Truly the contester's dream, the FT-ONE permits extremely fine tuning and instantaneous band change with equal facility.

DUAL VFO SYSTEM

Ten digital VFO's with memory are provided, in conjunction with an A-B selection scheme that allows instant recall of any transmit, receive, or transceive frequency desired. For split-frequency operation, such as on 7 MHz SSB, the operator may select TX on VFO-A and RX on VFO-B, automatically storing the calling and listening frequencies for each pile-up. For net operations, a non-volatile memory board is available as an option, to eliminate the possibility of dumping memory.

FULL CW BREAK-IN

Recent advances in solid-state technology have finally made full CW break-in reliable enough to be incorporated into a Yaesu product. Now you can select traditional semi-break-in (for use with amplifiers not equipped for full break-in) or full high-speed break-in. When using amplifiers so equipped, the keyer output lead may be interrupted via a rear panel jack and routed to the break-in sequencing input on your amplifier.

SWITCHING REGULATOR POWER SUPPLY

Extremely compact and light in weight, the switching regulator power supply reduces substantially the space required to produce the operating voltages used in the FT-ONE. Highly efficient and uniquely stable, the switching regulator supply provides superb reliability in a field of design long neglected by amateur manufacturers.

ELITE CLASS PERFORMANCE FEATURES

In addition to the full break-in and superb receiver filters, Yaesu's design team packed the FT-ONE with subtle virtues that others might have overlooked. Rear panel jacks allow the use of both an external receiver and an independent receive antenna, such as a 160 meter Beverage. While scanning, automatic halting on a received signal may be programmed . . . perfect for watching a band for openings. If you're a DX-peditioner, an optional Curtis 8044 keyer board is available, so you won't need an external keyer that only wastes suitcase space. And if your amplifier fan is louder than it should be, there's even a microphone squelch (AMGC) to reduce background noise pickup between words and sentences!

ONE YEAR FACTORY WARRANTY

Because of the level of attention to design detail, parts selection, and factory quality control, your FT-ONE is backed by a one-year *factory* warranty for the original purchaser at retail. Prompt and meticulous attention to your warranty needs will be provided by our Ohio And California Service Centers. In addition, all units sold in the United States will be inspected and tested after clearing Customs, and will include a Service Manual in the puchase price.

GAIN/INTERCEPT OPTIMIZED RECEIVER FRONT END

Utilizing up-conversion with a first IF of 73 MHz, the FT-ONE RF amplifier stage uses push-pull power transistors configured to produce a typical output intercept of +40 dBm. The first mixer utilizes a diode ring module followed by a low noise post amp, for optimum noise figure consistent with modern day intercept requirements. The result is a receiver with a typical two-tone dynamic range well in excess of 95 dB (14 MHz, CW bandwidth). Additional gain tailoring is provided via a PIN diode attenuator controlled from the front panel.

FILTERS READY FOR COMPETITION

Three filter bandwidths are available for CW operation (two for FSK!), using optional 600 Hz or 300 Hz crystal filters. Filter insertion losses are equalized for constant IF gain. Both IF Shift and Variable Bandwidth are provided, and two CW filters may be cascaded, for competition-grade selectivity. For SSB work, the Variable Bandwidth feature eliminates the need for costly 1.5 kHz or 1.8 kHz filters, as any intermediate bandwidth may easily be programmed using the standard, cascaded SSB filters. To top it all off, a high-performance audio peak and notch filter is standard equipment.

EXPANDED OPERATING DISPLAYS

Digital displays for the VFO Frequency, memory channel, and RIT offset are provided for quick frequency identification. The large front panel meter provides easy viewing of transceiver operating parameters, including final transistor collector current, input DC voltage, FM discriminator center tuning, speech processor compression level, and forward/reflected relative power.

NOT AVAILABLE AS OPTIONS

It's hard to believe that other manufacturers still insist on making such essential items as a noise blanker or speech processor extra-cost options. We find that these are less expensive to incorporate and more reliable in operation when installed on our assembly line. No AC power supply is available as an option for the FT-ONE, either; it's equipped for operation from 100/110/117/200/220/234 volts AC or 13.5 volts DC. And it goes without saying that there will not be an external VFO offered for the FT-ONE — we're confident that ten VFO's are quite enough!

Experience the FT-ONE in your Authorized Yaesu Dealer's showroom today. This may be the last Amateur transceiver you will ever own.

Warranty policy available upon request. SASE, please.

Specifications subject to change without notice or obligation

FT-ONE

YAESU FT-ONE
General Coverage All Mode Solid State Transceiver

Bold Adventure In Engineering!

YAESU
The radio.

1081

YAESU ELECTRONICS CORPORATION, 6851 Walthall Way, Paramount, CA 90723 ● (213) 633-4007
Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246 ● (513) 874-3100

NEW

Watts to see...

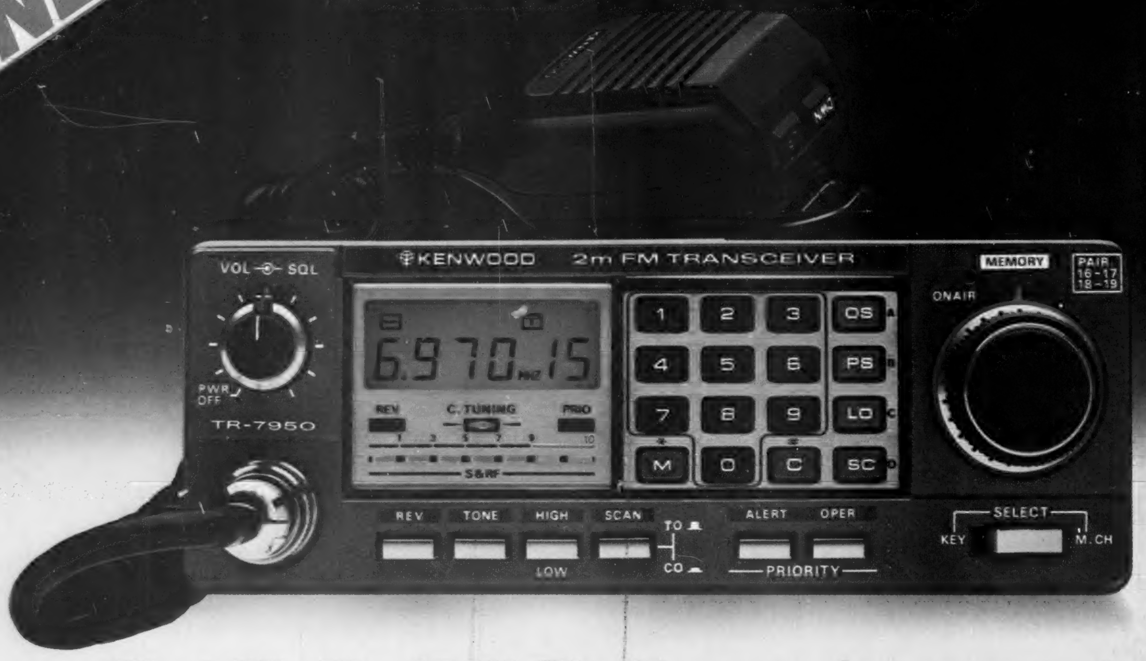

Big LCD, Big 45 W, Big 21 memories, compact.

TR-7950/7930

Outstanding features providing maximum ease of operation include a large, easy-to-read (direct sunlight or dark) LCD display, 21 multi-function memories, automatic offset, programmable priority channel, memory and band scans, built-in lithium battery memory back-up, built-in 16-key autopatch encoder, and a choice of a hefty 45 watts output (TR-7950), or 25 watts output (TR-7930).

TR-7950/TR-7930 FEATURES:

- **NEW, large, easy-to-read LCD digital display**
  Easy to read in direct sunlight or dark (back-lighted). Displays transmit/receive frequencies, memory channel, repeater offset, (+,S,−), sub-tone number (F-0, 1, 2, 3), tone, scan, and memory scan lock-out. Includes LED S/RF bar meter, and LED indicators for REVERSE, CENTER TUNING, PRIORITY, and ON AIR.
- **21 NEW, multi-function memory channels**
  Stores frequency, repeater offset, and optional sub-tone channels. Memories 1 through 15 for simplex or ± 600 kHz offset. Memory pairs 16/17, and 18/19 are paired for non-standard repeater offset. Memories "A" and "B" set upper and lower scan limits, or for simplex or ± 600 kHz offset. In MEMORY mode, a circle of light appears around the memory selector knob. When the memory selector knob is rotated in either direction to channel 1, an audible "beep" will sound.
- **Choice of 45 or 25 watts output**
  The TR-7950 provides a hefty 45 watts output, while the TR-7930 features a more modest 25 watts. A HI/LOW power switch allows power reduction to approx. 5 watts.
- **Long-life lithium battery memory back-up**
  Built-in lithium battery has an estimated 5 year life.
- **Automatic offset**
  The microprocessor is pre-programmed for simplex or ± 600 kHz offset, in accordance with the 2 meter band plan. "OS" key allows manual change in offset.
- **Programmable priority alert**
  The PRIORITY channel may be programmed in any of the 21 memories. With ALERT switch "ON," a dual "beep" sounds when a signal is present on the PRIORITY channel. An OPER switch allows an easy move to the PRIORITY channel.
- **Programmable memory scan lock-out**
  "LO" key for programming scan to skip selected memory channels, without erasing the memory.
- **Programmable band-scan width**
  The lower limit may be programmed into memory "A," and the upper limit into memory "B."
- **Center stop during band-scan, with indicator**
  Stops in center of channel during band-scan, with center tuning indicator.
- **Scan resume selectable**
  Scan stops on busy channel. Selectable automatic time resume-scan (approx. 5 sec., adjustable), or carrier operated resume-scan. A scan delay of approx. 1.5 seconds built-in.
- **Scan control using up/down microphone**
  Momentarily pressing UP or DOWN button on microphone tunes one step in the selected direction, on memory or on 5-kHz step tuning. Holding the button for about 2 seconds starts UP or DOWN automatic scan action. Scan start also possible using "SC" key on keyboard. Scan may be cancelled by momentarily pressing the PTT switch, or by pressing both UP/DOWN buttons simultaneously.
- **Programmable sub-tone channels**
  Optional TU-79 3 frequency sub-tone u provides keyboard selectable sub-tone channels, which may be stored in memory.
- **Built-in 16-key autopatch, with monit**
  The keyboard functions as a 16-key autopatch encoder during transmit. DTMF tones appear in the speaker outp when a key is pressed during transmit.
- **Front panel keyboard control**
  Used for selecting frequency, offset, pro gramming memories, controlling scan, and autopatch encode. Keyboard lighti is provided.
- **Extended frequency coverage**
  Covers 142.000-148.995 MHz, in 5-kHz steps.
- **Repeater reverse switch**
  Locking-type switch, with indicator.
- **"Beeper" amplified through speaker**
- **Compact, lightweight design**
- **Easy-to-install adjustable-angle mobi mounting bracket**

Optional accessories:

- TU-79 three frequency tone unit.
- KPS-12 fixed-station power supply for TR-7950.
- KPS-7A fixed-station power supply for TR-7930.
- SP-40 compact mobile speaker.

More information on the TR-7950 and TR-7930 is available from all authorize dealers of Trio-Kenwood Communicatio
1111 West Walnut Street,
Compton, California 90220.

KENWOO

...pacesetter in amateur radio

Specifications and prices are subject to change without notice or obligati

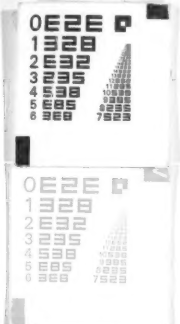C27